 


SOLID STATE PULSE CIRCUITS

DAVID A. BELL

DAYE / ANGUAY



EX LIBRIS

DAVE AND MARY TANGUAY
143 MICHELANGELO DRIVE
SIERRA VISTA, ARIZONA 85631
PHONE (602) 458-9379

"THE FUTURE IS NOW!"



Digitized by the Internet Archive
in 2010

SOLID STATE PULSE CIRCUITS

SOLID STATE
PULSE CIRCUITS

SOLID STATE PULSE CIRCUITS

David A. Bell

*Lambton College of
Applied Arts and Technology
Sarnia, Ontario, Canada*

RESTON PUBLISHING COMPANY, INC.

Reston, Virginia
A Prentice-Hall Company

Library of Congress Cataloging in Publication Data

Bell, David A

Solid state pulse circuits.

Includes index.

1. Pulse circuits. 2. Digital electronics. 3. Semiconductor devices. I. Title.

TK7868.P8B44

621.3815'34

75-37608

ISBN 0-87909-777-9

© 1976 by

Reston Publishing Company, Inc.

A Prentice-Hall Company

Reston, Virginia 22090

All rights reserved. No part of this book may be reproduced in any way, or by any means, without permission in writing from the publisher.

10 9 8 7 6

Printed in the United States of America.

CONTENTS

	PREFACE	xi
Chapter 1	WAVEFORMS	1
	<i>Introduction, 1</i>	
1-1	Types of Waveforms, 1	
1-2	Characteristics of Pulse Waveforms, 7	
1-3	Harmonic Content of Waveforms, 15	
	<i>Review Questions and Problems, 24</i>	
Chapter 2	CAPACITIVE RESISTIVE (CR) CIRCUITS	28
	<i>Introduction, 28</i>	
2-1	CR Circuit Operation, 28	
2-2	CR Circuit Response to Square Waves, 39	

- 2-3 Integrating Circuits, 43
- 2-4 Differentiating Circuits, 49
- Review Questions and Problems, 55*

Chapter 3 DIODE SWITCHING 57

Introduction, 57

- 3-1 The Diode as a Switch, 57
- 3-2 The Zener Diode, 61
- 3-3 Diode Clipper Circuits, 62
- 3-4 Diode Clamper Circuits, 72
- Review Questions and Problems, 80*

Chapter 4 TRANSISTOR SWITCHING 85

Introduction, 85

- 4-1 Ideal Transistor Switch, 85
- 4-2 Practical Transistor Switch, 88
- 4-3 Transistor Switching Times, 93
- 4-4 Improving the Switching Times, 97
- 4-5 Junction Field Effect Transistor (JFET) Switch, 101
- 4-6 MOSFET Switch, 105
- 4-7 CMOS Switch, 105
- Review Questions and Problems, 107*

Chapter 5 THE INVERTER CIRCUIT 110

Introduction, 110

- 5-1 Direct-Coupled Bipolar Transistor Inverter, 110
- 5-2 Capacitor-Coupled Inverter Circuits, 117
- 5-3 JFET Inverter Circuits, 124
- 5-4 IC Operational Amplifier Inverter, 126
- Review Questions and Problems, 130*

Chapter 6 THE SCHMITT TRIGGER CIRCUIT 132

Introduction, 132

- 6-1 Operation of Schmitt Trigger Circuit, 132
- 6-2 Designing for a Given Upper Trigger Point, 135
- 6-3 Analyzing for UTP and LTP, 138
- 6-4 Designing for Given UTP and LTP, 141
- 6-5 Selection of the Speed-Up Capacitor, 142
- 6-6 Output/Input Characteristics, 143

- 6-7 The IC Operational Amplifier as a Schmitt
Trigger Circuit, 146
Review Questions and Problems, 151

Chapter 7 RAMP GENERATORS 153

Introduction, 153

- 7-1 CR Ramp Generator, 153
7-2 Constant Current Ramp Generator, 157
7-3 UJT Relaxation Oscillators, 162
7-4 Programmable UJT Relaxation Oscillators, 167
7-5 Transistor Bootstrap Ramp Generator, 170
7-6 IC Bootstrap Ramp Generator, 175
7-7 Free-Running Ramp Generator, 178
7-8 Miller Integrator Circuit, 180
7-9 Triangular Waveform Generator, 186
7-10 CRT Time Base, 188
Review Questions and Problems, 190

Chapter 8 MONOSTABLE AND ASTABLE MULTIVIBRATORS 192

Introduction, 192

- 8-1 Collector-Coupled Monostable Multivibrator, 193
8-2 Design of a Collector-Coupled Monostable
Multivibrator, 196
8-3 Triggering the Monostable Multivibrator, 202
8-4 Emitter-Coupled Monostable Multivibrator, 204
8-5 The IC Operational Amplifier as a
Monostable Multivibrator, 210
8-6 IC Monostable Multivibrator, 214
8-7 Astable Multivibrator, 214
Review Questions and Problems, 221

Chapter 9 BISTABLE MULTIVIBRATORS 223

Introduction, 223

- 9-1 The Collector-Coupled Bistable Multivibrator, 223
9-2 Design of a Collector-Coupled Bistable
Multivibrator, 225
9-3 Emitter-Coupled Bistable Multivibrator, 230
9-4 Collector Triggering, 237
9-5 Base Triggering, 243

- 9-6 Emitter Triggering, 247
- 9-7 IC Flip-Flops, 250
- Review Questions and Problems, 255*

Chapter 10 LOGIC GATES 257

Introduction, 257

- 10-1 Diode *AND* Gate, 258
- 10-2 Diode *OR* Gate, 260
- 10-3 Positive Logic and Negative Logic, 262
- 10-4 Diode Transistor Logic (DTL), 263
- 10-5 Fan-In and Fan-Out, 267
- 10-6 High Threshold Logic (HTL), 270
- 10-7 Resistor Transistor Logic (RTL), 272
- 10-8 Transistor Transistor Logic (TTL), 275
- 10-9 Emitter-Coupled Logic (ECL), 278
- 10-10 Complementary MOSFET Logic (CMOS), 282
- 10-11 Comparison of Major Types of IC Logic, 285
- Review Questions and Problems, 285*

Chapter 11 SAMPLING GATES 288

Introduction, 288

- 11-1 Diode Sampling Gate, 288
- 11-2 Bipolar Transistor Series Gate, 290
- 11-3 Bipolar Transistor Shunt Gate, 294
- 11-4 JFET Series Gate, 297
- 11-5 JFET Shunt Gate, 300
- 11-6 MOSFET Sampling Gates, 303
- Review Questions and Problems, 303*

Chapter 12 DIGITAL COUNTING 305

Introduction, 305

- 12-1 Flip-Flops in Cascade, 305
- 12-2 Decade Counter, 310
- 12-3 Integrated Circuit Counters, 314
- 12-4 Digital Displays or Readouts, 318
- 12-5 Binary to Decimal Conversion, 326
- 12-6 Seven-Segment LED Display Driver, 330
- 12-7 Scale-of-10,000 Counter, 333
- 12-8 Counter Controls, 335
- Review Questions and Problems, 336*

Chapter 13	DIGITAL FREQUENCY METERS AND DIGITAL VOLTMETERS	339
	<i>Introduction, 339</i>	
13-1	Timing System, 340	
13-2	Latch Circuits, 342	
13-3	Digital Frequency Meter, 344	
13-4	Dual Slope Integrator for Digital Voltmeter, 347	
13-5	Digital Voltmeter (DVM), 352	
	<i>Review Questions and Problems, 353</i>	
Chapter 14	PULSE MODULATION AND MULTIPLEXING	355
	<i>Introduction, 355</i>	
14-1	Types of Pulse Modulation, 356	
14-2	PAM Modulation and Demodulation, 358	
14-3	PDM Modulation and Demodulation, 360	
14-4	PPM Modulation and Demodulation, 363	
14-5	Time Division Multiplexing, 365	
14-6	PCM Modulation and Demodulation, 373	
	<i>Review Questions and Problems, 378</i>	
Appendix 1	DATA SHEETS	380
Appendix 2	RESISTOR AND CAPACITOR VALUES	418
	INDEX	421

Chapter 15	DIGITAL FREQUENCY METER AND DIGITAL VOLTAGE	239
Chapter 16	PULSE MODULATION AND MULTIPLEXING	322
Appendix 1	DATA SHEETS	350
Appendix 2	RESISTOR AND CAPACITOR VALUES	418
INDEX		421

PREFACE

This book attempts to explain the operation, design, and analysis of all the basic semiconductor pulse circuits. The design approach is a simple step-by-step procedure in which the designer knows exactly why each component value is selected. Many design examples are included in the text, device data sheets included in Appendix 1 are referred to when appropriate, and standard value component values are selected. The mathematics employed does not go beyond algebraic equations and logarithms.

As well as discrete component circuits, the design procedure for using IC operational amplifiers in the various pulse circuits is discussed. Digital integrated circuits, including CMOS logic, are also treated. However, this is a text on *pulse circuits*, not a book on computer logic.

The text progresses through pulse waveforms, RC circuits, diode switching, and transistor switching, to transistor, FET, and IC inverter circuits. Then it treats the Schmitt trigger circuit; monostable, astable, and bistable multivibrators; logic gates; and sampling gates. After the

individual circuits are fully explained, they are used as building blocks to describe digital counting, digital frequency meters, digital voltmeters, pulse modulation, and time division multiplexing. The various seven-segment numerical display devices are covered, as are IC flip-flops and counting circuits.

It is believed that this text shows that pulse circuits are easy to understand, and that their design is fairly simple.

David A. Bell

Chapter 1

Waveforms


INTRODUCTION

The term **PULSE WAVEFORM** normally is applied only to approximately rectangular waveshapes. However, many different types of waveforms are involved in the study of pulse circuits. Waveforms are defined in terms of amplitude and time interval measurements. Each of the various waveforms can be shown to contain many higher frequency sinusoidal components, known as **HARMONICS**. A study of the harmonics shows a definite relationship between the bandwidth of an amplifier and the distortion produced in a square wave output from the amplifier.


1-1 TYPES OF WAVEFORM

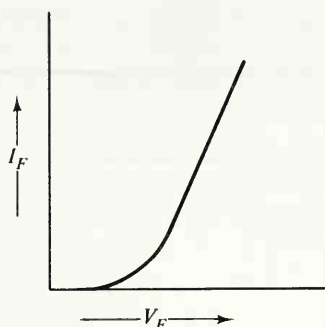1-1.1 Repetitive Waveforms and Transients


When one quantity varies in relation to another quantity, the relationship can be represented by plotting a graph. Thus, for a semiconductor diode,




(a) Graph of I_F versus V_F for diode

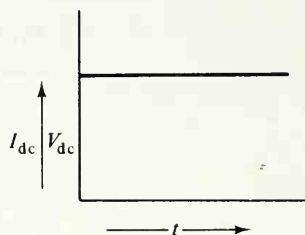

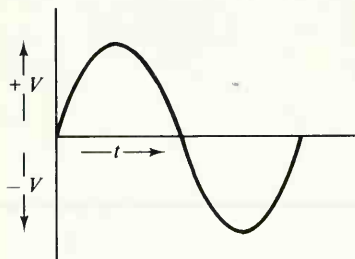(b) Graph of I_{dc} or V_{dc} versus time



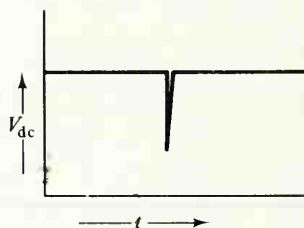(c) Graph of instantaneous value of ac voltage plotted versus time



(d) Transient on a dc voltage

FIGURE 1-1. Various graphs showing relationships between two quantities.

I_F plotted against V_F gives the forward characteristics of the device [see Figure 1-1 (a)]. Similarly, graphs may be plotted to show how certain quantities vary with respect to time. A plot of dc voltage or current *versus* time normally produces a straight line graph, as in Figure 1-1 (b). An alternating voltage, as its name implies, increases and decreases with respect to time. When the instantaneous voltage levels v are plotted against time t , the graph that results is called the waveform of the voltage. In Figure 1-1 (c) the instantaneous values of a sinusoidal alternating voltage are plotted to a base of time. It is seen that the voltage increases positively to a peak value, decreases through zero to a negative peak value, then returns to zero; then the cycle recommences. Thus the sine wave is a repeating cycle of voltage (or current) with a sinusoidal relationship to time. All waveforms which are composed of identical cycles that keep repeating are termed *repetitive waveforms* or *periodic waveforms*.

It is necessary to study only one cycle of such a waveform to gain an understanding of the behavior of the voltage or current involved. When successive cycles of an alternating voltage are not identical, the waveform is described as *aperiodic*.

Sometimes a direct voltage suddenly decreases (or increases) for a brief instant and then returns to its normal level [Figure 1-1(d)]. This may happen, for example, when a load is suddenly switched onto a power supply. Such brief nonrepetitive waveforms are termed *transients*.

1-1.2 Display Methods

Since electrical waveforms (repetitive and nonrepetitive) usually occur during a period of milliseconds or microseconds, manual measurements cannot be taken of such instantaneous levels for plotting on a graph. Instead, instruments are employed to do the actual plotting of voltage or current to a base of time. One such instrument is the *strip chart recorder* (Figure 1-2) in which a pen or another marking device traces the waveform on a moving strip of paper. The vertical movement of the pen is directly proportional to the instantaneous value of the applied voltage and, since the paper moves at a constant speed, the horizontal trace is directly proportional to time. Similar instruments replace the moving arm and pen with a beam of light, reflected from a moving mirror, onto photographically treated paper.

Although the chart recorder provides a permanent record of the waveform under study, its major drawback is that it is essentially a low-frequency instrument. The *cathode-ray oscilloscope*, which has a much

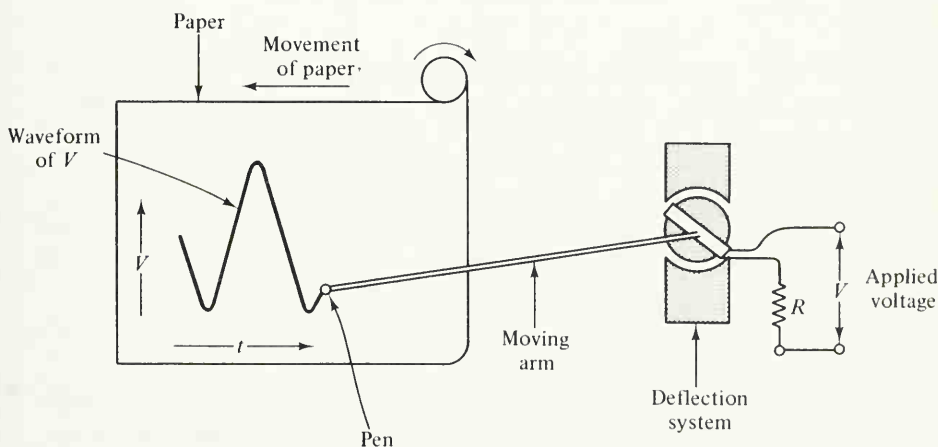


FIGURE 1-2. Waveform display by strip chart recorder.

higher frequency response, is widely used in the study of electrical waveforms. In the oscilloscope, an electron beam striking a fluorescent screen produces a tiny spot of light. The light spot becomes a line when the electron beam is deflected vertically by the voltage to be displayed and horizontally in proportion to time (see Figure 1-3). The light spot starts at the left-hand side of the screen and moves to the right. At the end of one (or more) cycles of the waveform, the light spot returns almost instantaneously to the left-hand side of the screen. Thus, a repetitive waveform is traced on the screen again and again. When a permanent record of the waveform is required, a camera is used to photograph the display on the oscilloscope. A camera can be employed also to obtain

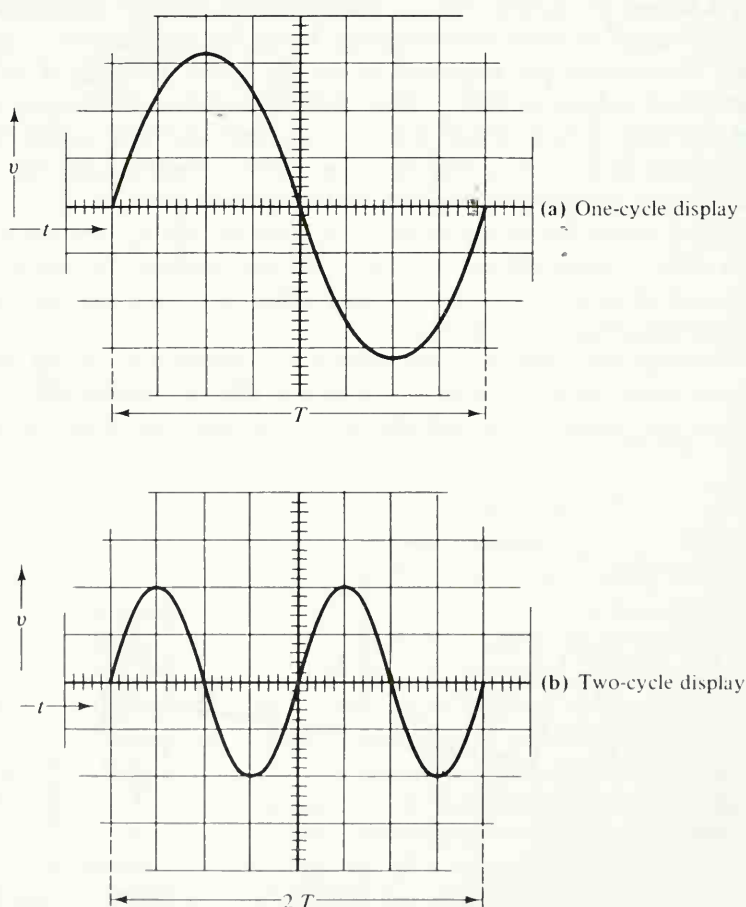


FIGURE 1-3. Waveform display by cathode ray oscilloscope.

photographs of any transient waveform that might appear briefly on the oscilloscope screen.

1-1.3 Miscellaneous Waveforms

Sinusoidal. The most common electrical waveform is the sine wave, shown in Figure 1-3. Half-wave rectification removes the negative (or positive) half-cycles of a sine wave [Figure 1-4 (a)], while full-wave rectification produces a train of unidirectional half-sine waves, as shown in Figure 1-4(b).

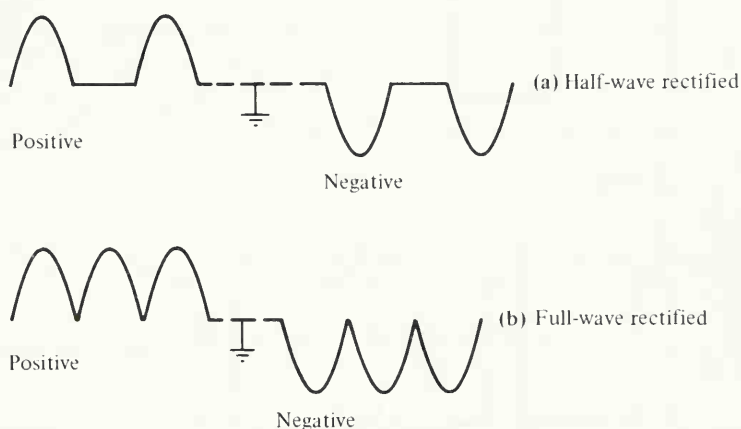


FIGURE 1-4. Rectified sine waves.

Rectangular. When a dc voltage suddenly changes from one level to another, the change is referred to as a *step change*. The change might be positive or negative, as shown in Figure 1-5(a). A *rectangular waveform* consists simply of successive cycles of positive step changes followed by negative step changes. Where the time duration t_1 for the upper dc level is equal to the time duration t_2 for the lower level, the waveform is termed a *square wave* [Figure 1-5(b)]. When t_1 and t_2 are unequal, as illustrated in Figure 1-5(c), the wave is usually referred to as a *pulse waveform*.

Ramp. When a voltage increases or decreases at a constant rate with respect to time, its graph is that of a positive or negative *ramp* [Figure 1-6(a)]. A repetitive cycle of positive ramp followed by negative ramp is known as a *triangular waveform* [Figure 1-6(b)]. When one ramp is much

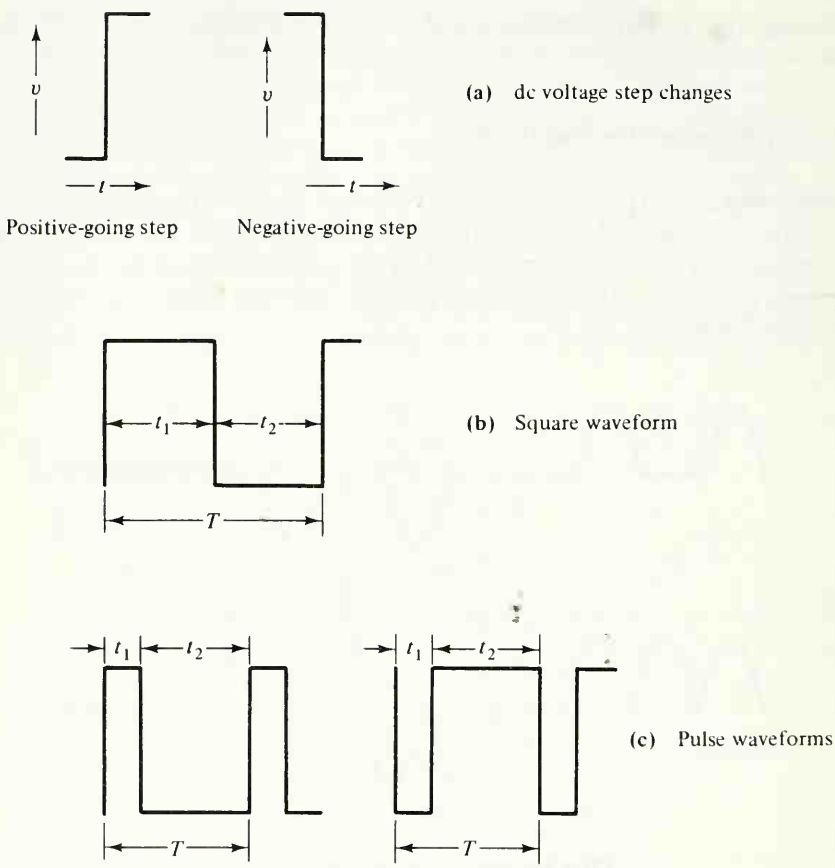


FIGURE 1-5. Rectangular waveforms.

steeper than the other, as illustrated in Figure 1-6(c), the waveform is usually termed a *sawtooth waveform*.

Exponential. In this case the voltage varies with respect to time according to the equation, $V = \epsilon^{kt}$ or $V = \epsilon^{-kt}$, where t is time, k is a constant, and ϵ is the *exponential constant* ($\epsilon = 2.718$). The resultant graphs of voltage *versus* time are of the form shown in Figure 1-7(a). Repetitive cycles of positive and negative exponentials produce an *exponential waveform*, as in Figure 1-7(b). An exponential change followed by a step change gives the waveforms shown in Figure 1-7(c). Introduction of a gap results in the *spike waveforms* of Figure 1-7(d). Obviously a great variety

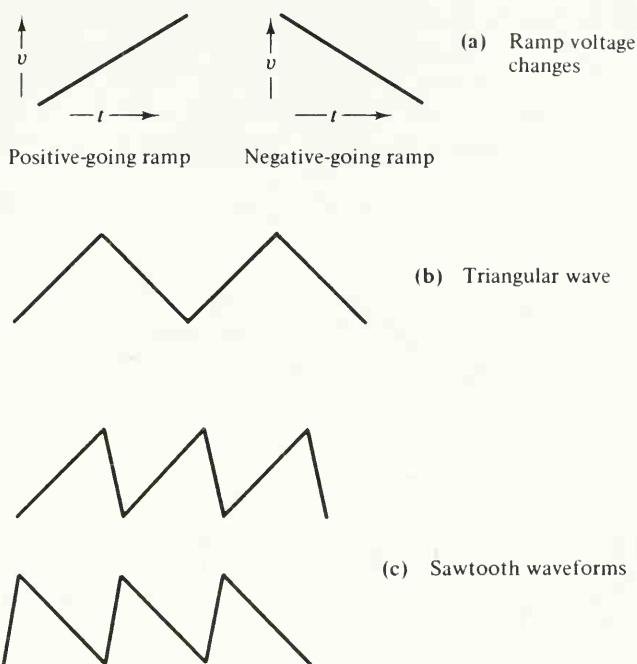


FIGURE 1-6. Ramp waveforms.

of waveforms can be produced by combining two or more of the various voltage changes discussed above.

1-2 CHARACTERISTICS OF PULSE WAVEFORMS

Consider the ideal pulse waveform shown in Figure 1-8. In this particular case the pulses are positive with respect to ground. The pulse amplitude is simply the voltage level of the top of the pulse measured from ground. The first edge of the pulse (at $t = 0$) is referred to as the *leading edge*, and the second edge is termed the *trailing edge* or *lagging edge*.

The *time period* T is the time measured from the leading edge of one pulse to the leading edge of the next pulse. If $T = 1$ sec, then the *pulse repetition frequency* (PRF) is 1 cycle/sec, or 1 pulse per sec (pps), or $\text{PRF} = 1/T$ pps. Instead of pulse repetition frequency, the term *pulse repetition rate* (PRR) is sometimes used.

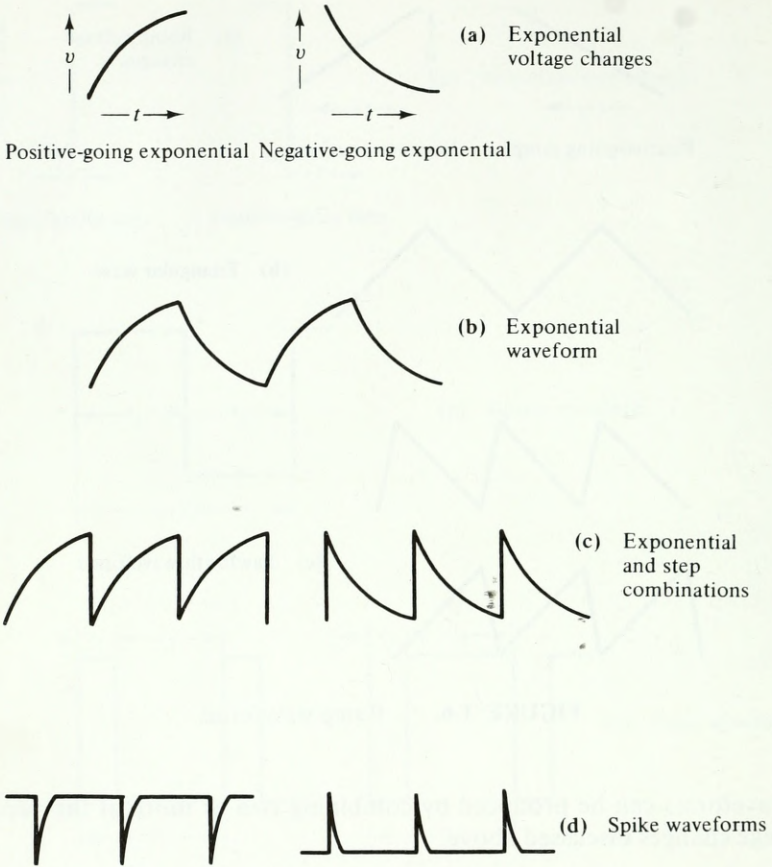


FIGURE 1-7. Exponential waveforms.

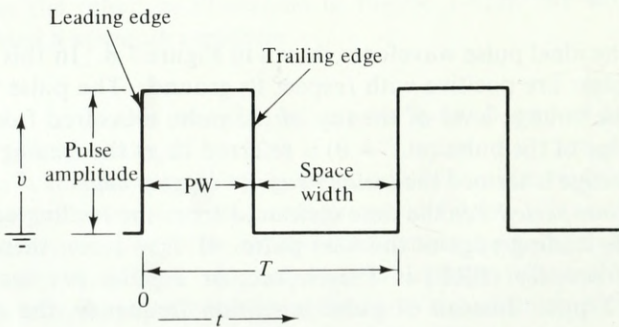


FIGURE 1-8. Ideal pulse waveform.

The time measured from the leading edge to the trailing edge of one pulse is known as the *pulse width* (PW), the *pulse duration* (PD), or sometimes as the *mark length*. The time between pulses is simply referred to as the *space width*. The proportion of the time period occupied by the pulse is defined as the *duty cycle*, or as the *mark-to-space* (*M/S*) *ratio*:

$$\text{Duty cycle} = (\text{PW}/T) \times 100\% \quad (1-1)$$

and

$$\text{M/S ratio} = \text{PW}/(\text{space width}) \quad (1-2)$$

The duty cycle usually is expressed as a percentage, while the mark-to-space ratio is expressed simply as a ratio.

EXAMPLE 1-1

For the pulse waveform displayed in Figure 1-9, determine the pulse amplitude, PRF, PW, duty cycle, and M/S ratio. The vertical scale is 1 V per division, and the horizontal scale is 0.1 ms per division.

solution

$$\begin{aligned} \text{Pulse amplitude} &= (3.5 \text{ divisions}) \times (1 \text{ V/division}) \\ &= 3.5 \text{ V} \end{aligned}$$

$$\begin{aligned} T &= (6 \text{ divisions}) \times (0.1 \text{ ms/division}) \\ &= 0.6 \text{ ms} \end{aligned}$$

$$\text{PRF} = 1/T = 1/0.6 \text{ ms} = 1666 \text{ pps}$$

$$\begin{aligned} \text{PW} &= (2.5 \text{ divisions}) \times (0.1 \text{ ms/division}) \\ &= 0.25 \text{ ms} \end{aligned}$$

$$\text{Space width} = 3.5 \times 0.1 \text{ ms} = 0.35 \text{ ms}$$

$$\begin{aligned} \text{Duty cycle} &= \frac{\text{PW}}{T} \times 100\% \\ &= \frac{0.25 \text{ ms}}{0.6 \text{ ms}} \times 100\% = 41.6\% \end{aligned}$$

$$\begin{aligned} \text{M/S ratio} &= \frac{\text{PW}}{\text{Space width}} = \frac{0.25 \text{ ms}}{0.35 \text{ ms}} \\ &= 0.71 \end{aligned}$$

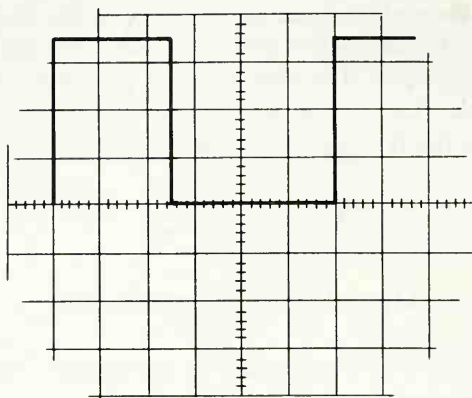


FIGURE 1-9. Pulse waveform on oscilloscope.

The pulse displayed in Figure 1-9 appears to have a perfectly flat top and perfectly vertical sides. When pulses are examined very carefully, however, it is found that the top is never perfectly flat. The amplitude of the lagging edge normally is less than that of the leading edge. In many cases the slope at the top of the pulse may be so small that it cannot be easily measured. In other cases, as in Figure 1-10, the slope may be very obvious. The pulse voltage does not go from zero to its maximum level instantaneously, and from maximum to zero instantaneously. In fact, there is a definite *rise time* t_r and *fall time* t_f at the leading and lagging edges of the pulse. This is also illustrated in Figure 1-10.

In Figure 1-10(a), E_1 is the maximum pulse amplitude, E_2 is the minimum amplitude, and E is the average pulse amplitude:

$$E = \frac{E_1 + E_2}{2}$$

The rise time is defined as the time required for the voltage to go from 10% to 90% of the average amplitude. Similarly, the fall time is the time required for the pulse to fall from 90% to 10% of the average amplitude. The *slope* or *tilt* at the top of the waveform is defined in terms of the average amplitude:

$$\begin{aligned} \text{Tilt} &= \frac{E_3}{E} \times 100\% \\ &= \frac{E_1 - E_2}{E} \times 100\% \end{aligned} \quad (1-3)$$

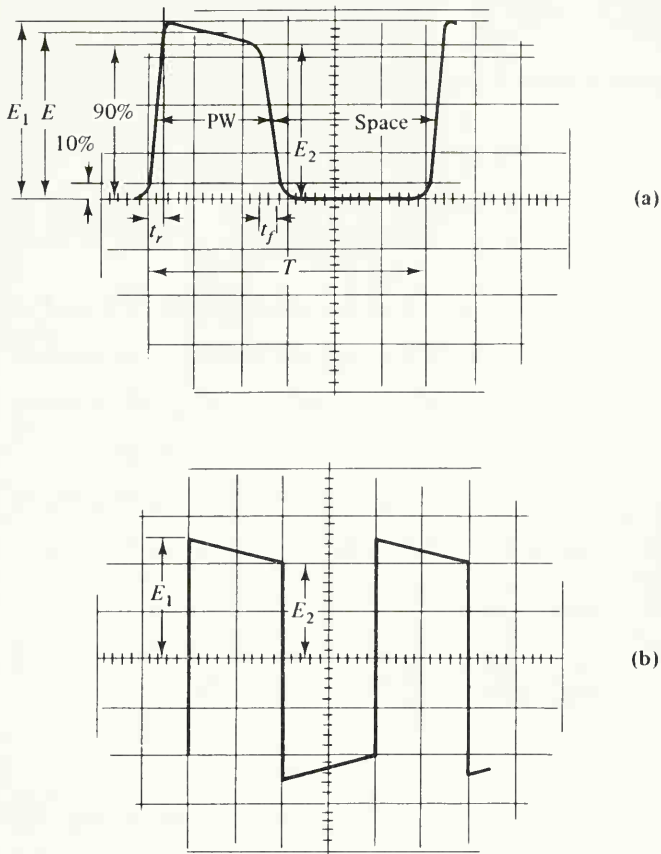


FIGURE 1-10. Waveforms with rise and fall times and tilt.

In Figure 1-10(b) is a square wave which is symmetrical above and below ground level. Although there is obvious tilt, the leading and trailing edges are equal in amplitude. Thus if E_1 was measured as leading edge and E_2 as trailing edge, Equation (1-3) would give zero tilt. Instead, E_1 and E_2 are each measured with respect to ground, as shown.

EXAMPLE 1-2 _____

For the waveform displayed in Figure 1-10(a), determine pulse amplitude, tilt, t_r , t_f , PW , PRF , mark-to-space ratio, and duty cycle. For the square wave in Figure 1-10(b), determine tilt. The vertical scale is 100 mV/division, and the horizontal scale is 100 μs /division in each case.

solution (a)

$$\text{Pulse amplitude, } E = \frac{E_1 + E_2}{2} = \frac{380 \text{ mV} + 330 \text{ mV}}{2} = 355 \text{ mV}$$

$$\begin{aligned} \text{Tilt} &= \frac{E_1 - E_2}{E} \times 100\% \\ &= \frac{380 \text{ mV} - 330 \text{ mV}}{355 \text{ mV}} \times 100\% = 14.1\% \end{aligned}$$

$$t_r = (0.3 \text{ divisions}) \times (100 \mu\text{s}/\text{division}) = 30 \mu\text{s}$$

$$t_f = (0.4 \text{ divisions}) \times (100 \mu\text{s}/\text{division}) = 40 \mu\text{s}$$

$$T = (6.1 \text{ divisions}) \times (100 \mu\text{s}/\text{division}) = 610 \mu\text{s}$$

$$\text{PRF} = 1/T = 1/610 \mu\text{s} = 1639 \text{ pps}$$

$$\text{PW} = (2.2 \text{ divisions}) \times (100 \mu\text{s}/\text{division}) = 220 \mu\text{s}$$

$$\text{Space width} = (3.9 \text{ divisions}) \times (100 \mu\text{s}/\text{division}) = 390 \mu\text{s}$$

$$\text{M/S ratio} = \frac{220 \mu\text{s}}{390 \mu\text{s}} = 0.564$$

$$\text{duty cycle} = \frac{220 \mu\text{s}}{610 \mu\text{s}} \times 100\% = 36.1\%$$

solution (b)


$$E_1 = (2.5 \text{ divisions}) \times (100 \text{ mV}/\text{division}) = 250 \text{ mV}$$

$$E_2 = (2 \text{ divisions}) \times (100 \text{ mV}/\text{division}) = 200 \text{ mV}$$


$$\begin{aligned} \text{Average voltage} = E &= \frac{E_1 + E_2}{2} = \frac{250 \text{ mV} + 200 \text{ mV}}{2} \\ &= 225 \text{ mV} \end{aligned}$$

$$\text{Tilt} = \frac{250 \text{ mV} - 200 \text{ mV}}{225 \text{ mV}} \times 100\% = 22.2\%$$

The square waveform shown in Figure 1-11(a) is symmetrical above and below ground level. The positive and negative peaks are of equal amplitudes and equal widths (*i.e.*, $t_1 = t_2$). This means that the average value of the waveform is zero. If this waveform were applied to a dc voltmeter, the instrument would indicate zero. The average value of the waveform is found simply by summing the positive and negative areas enclosed by one cycle and dividing by the time period.

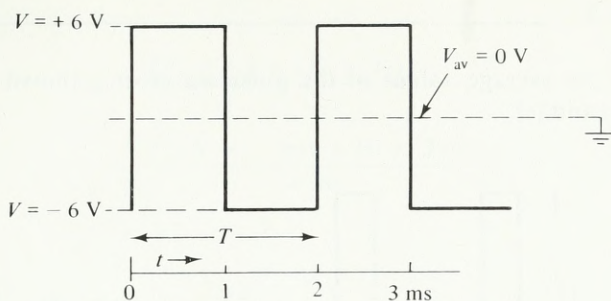

(a)

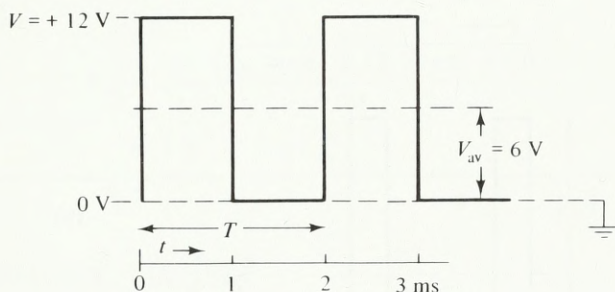

(b)

FIGURE 1-11. Waveforms with the same peak-to-peak amplitude but different average values.

$$\text{Average voltage} = V_{av} = \frac{(V_+ \times t_1) + (V_- \times t_2)}{T} \quad (1-4)$$

For Figure 1-11(a):

$$\text{Average voltage} = \frac{(6 \text{ V} \times 1 \text{ ms}) + (-6 \text{ V} \times 1 \text{ ms})}{2 \text{ ms}} = 0 \text{ V}$$

The waveform of Figure 1-11(b), has no negative portion, and the average value is:

$$V_{av} = \frac{(12 \text{ V} \times 1 \text{ ms}) - (0)}{2 \text{ ms}} = 6 \text{ V}$$

EXAMPLE 1-3

Determine the average values of the pulse waveforms shown in Figures 1-12(a), (b) and (c).

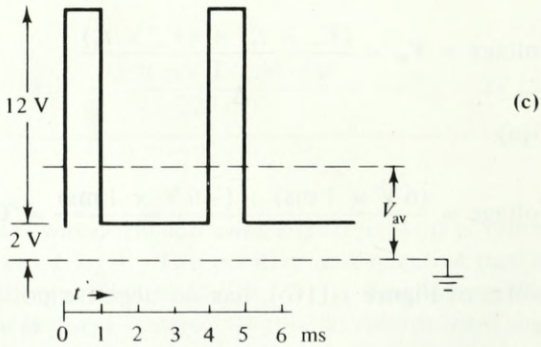
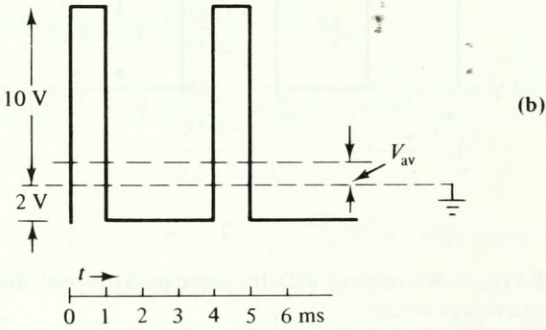
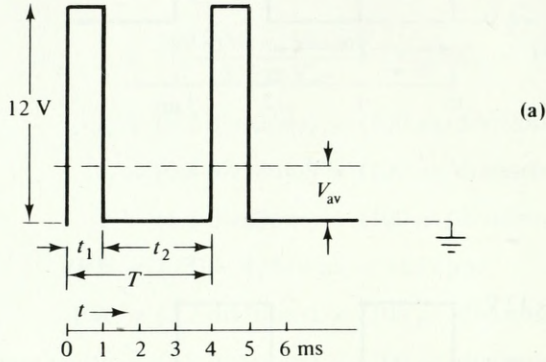


FIGURE 1-12. Pulse waveforms with different average values.

solution (a)

$$\begin{aligned}
 V_{av} &= \frac{(V_1 \times t_1) + (V_2 \times t_2)}{T} \\
 &= \frac{(12 \text{ V} \times 1 \text{ ms}) + (0 \times 3 \text{ ms})}{4 \text{ ms}} \\
 &= 3 \text{ V}
 \end{aligned}$$

solution (b)

$$\begin{aligned}
 V_{av} &= \frac{(10 \text{ V} \times 1 \text{ ms}) + (-2 \text{ V} \times 3 \text{ ms})}{4 \text{ ms}} \\
 &= 1 \text{ V}
 \end{aligned}$$


solution (c)

$$\begin{aligned}
 V_{av} &= \frac{(14 \text{ V} \times 1 \text{ ms}) + (2 \text{ V} \times 3 \text{ ms})}{4 \text{ ms}} \\
 &= 5 \text{ V}
 \end{aligned}$$

1-3 HARMONIC CONTENT OF WAVEFORMS

In Figure 1-13(a) two signal generators are shown connected in series. Generator A is producing a sinusoidal output waveform as shown. The output of generator B is also a sine wave, but its frequency is three times the frequency from signal generator A. The amplitude of the output from B is also less than that from A. The waveform produced by the two generators in series shown in the figure, is the larger amplitude (and lower frequency) signal, with the smaller amplitude signal superimposed. It is seen that the combination approximately resembles a square wave with its peaks dented. Figure 1-13(b) shows a third generator connected in series with A and B. The output from generator C is smaller in amplitude than that from B, and the frequency of this third signal is five times the frequency of the output of generator A. The waveform produced by the three generators in series now more closely resembles a square wave. It is important to note that the resultant waveforms shown in Figures 1-13(a) and (b) are produced only when *the generators are synchronized*, i.e. all component waves must commence exactly at the same instant.

(a) Fundamental and third harmonic

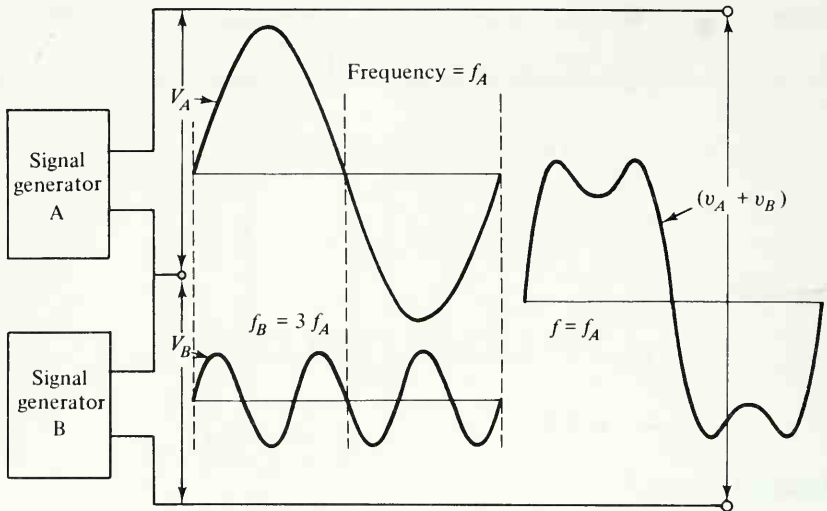

(b) Fundamental, third and fifth harmonic

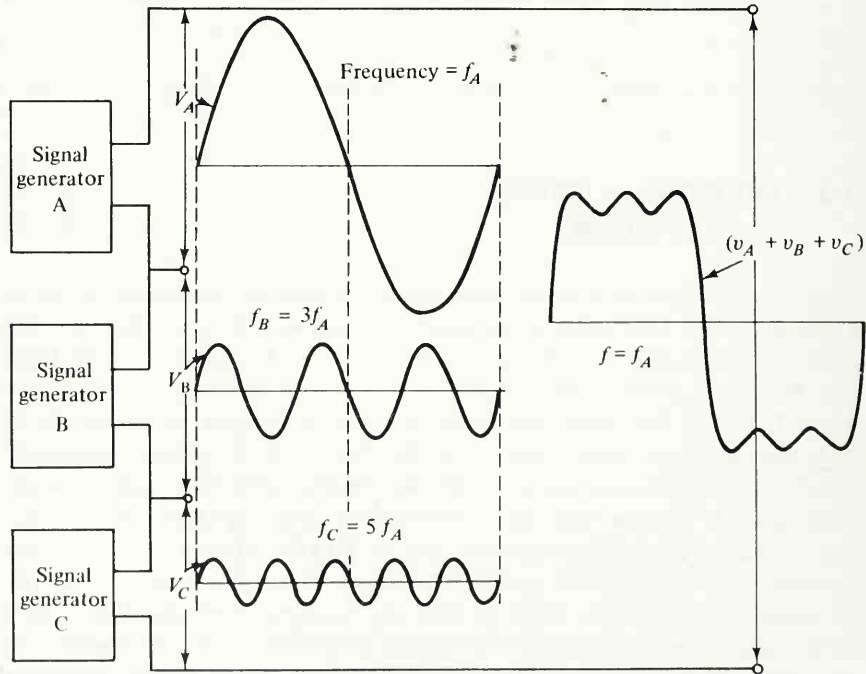


FIGURE 1-13. Combination of fundamental and harmonics to form approximate square wave. (Note that the signal generators must be synchronized.)

The building up of the approximate square waveform is easily seen by referring to Figure 1-14. In part (a) of the figure, the instantaneous amplitudes of waveforms A and B are added at a given time. At time t_1 , for example, the amplitude of waveform A is 6.5 V, and that of B is approximately 2.5 V. Therefore the amplitude of the resultant waveform at time t_1 is 9 V (point 1). At time t_2 , the amplitude of B is zero, so the resultant amplitude is 8.5 V, that is, the amplitude of A at t_2 (point 2). At t_3 , the amplitudes of B, -3 V, and of A, 10 V, are added together to produce an amplitude of 7 V. When this process is continued, it can be seen how the final waveform is constructed.

The process of building up a particular waveform by combining several sine waves of different frequencies and amplitudes is referred to

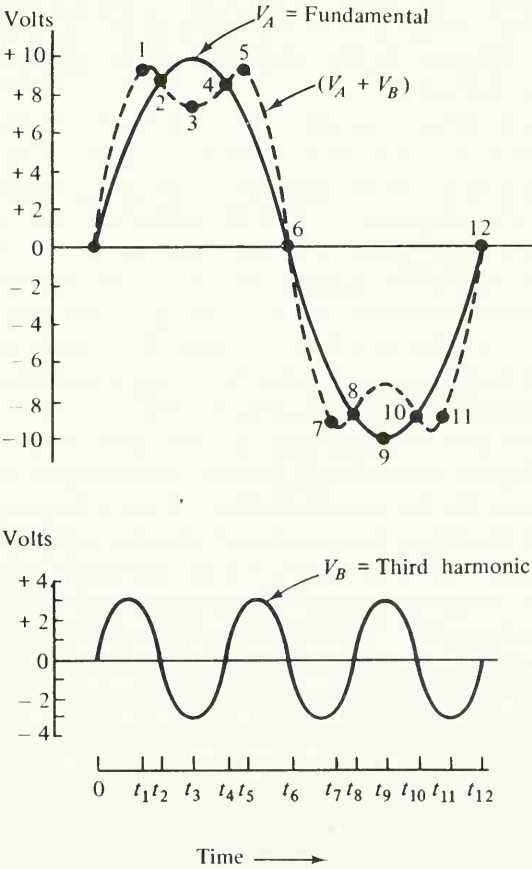


FIGURE 1-14. Addition of the instantaneous levels of a fundamental and third harmonic.

as *frequency synthesis*. If the process were continued and more and higher frequency waveforms were added, the resultant each time would more closely resemble a square wave.

The converse of frequency synthesis is *harmonic analysis*. In this process a waveform is analyzed to discover the sine wave frequencies it contains. By harmonic analysis, it can be shown that periodic non-sinusoidal waveforms are composed of combinations of pure sine waves. Some waveforms can also have dc components. One major component, a large amplitude sine wave of the same frequency as the periodic wave under consideration, is termed the *fundamental*. The other components of a periodic waveform are sine waves with frequencies which are exact multiples of the frequency of the fundamental. These waves, referred to as *harmonics*, are numbered according to the ratio between their frequencies and that of the fundamental. For example, a harmonic with a frequency exactly double that of the fundamental is called the *second harmonic*. The frequency of the *third harmonic*, obviously, is three times the fundamental frequency.

By the mathematical operation known as *Fourier analysis* waveforms can be analyzed to determine their harmonic content. The amplitude of each harmonic and its phase relationship to the fundamental can be found. Also, the amplitude of any dc component can be calculated. A perfect square wave which is symmetrical above and below ground has been shown, by Fourier analysis, to have a fundamental component and odd-numbered harmonics, but no even-numbered harmonics and no dc component. A pulse waveform is found to contain both odd- and even-numbered harmonics and (usually) a dc component. Sawtooth waveforms, triangular waveforms, and rectified sine waves are made up of more complicated combinations of odd- and even-numbered harmonics. In all cases, the harmonic content actually goes to infinity, but the amplitudes of the harmonics decrease as their frequencies increase. Thus the higher frequency components are the least important.

Information which can be derived by harmonic analysis becomes very important when considering the circuitry through which various waveforms are processed. Suppose a square wave with a frequency of 1 kHz is applied to an amplifier with an upper frequency limit of 15 kHz. In this case, the amplifier will not reproduce waveforms with frequencies greater than 15 kHz. Thus the amplifier will not pass harmonics of 1 kHz greater than the fifteenth. If the square wave applied to the same amplifier had a frequency of 5 kHz, only the first, second, and third harmonics would be passed. If a 5 kHz square wave were to be amplified, and if all harmonics up to the thirty-third were to be reproduced, then the amplifier must have an upper frequency limit greater than 33×5 kHz. Fifteen to twenty harmonics are usually required to reproduce a wave-

form in its original shape. For accurate reproduction, however, many more harmonics may be required.

The number of harmonics required to accurately reproduce a pulse waveform with a small duty cycle is approximately inversely proportional to the duty cycle.

$$\text{Highest harmonic frequency} = \frac{1}{\text{Duty cycle}} \times \text{PRF} \quad (1-5)$$

EXAMPLE 1-4

A pulse waveform has a PRF of 15 kHz and a duty cycle of 3%. (a) Determine the frequency of the highest harmonic required for accurate reconstruction of the waveform. (b) If the 15 kHz pulse is to be amplified by equipment with a high frequency limit of 1.5 MHz, calculate the minimum pulse width that can be reproduced accurately.

solution (a)

$$\begin{aligned} \text{Highest harmonic frequency} &= \frac{1}{0.03} \times 15 \text{ kHz} \\ &= 500 \text{ kHz} \end{aligned}$$

solution (b)

$$\begin{aligned} 1.5 \text{ MHz} &= \frac{1}{\text{Duty cycle}} \times 15 \text{ kHz} \\ \therefore \text{Duty cycle} &= \frac{15 \text{ kHz}}{1.5 \text{ MHz}} = 0.01 \end{aligned}$$

and

$$\begin{aligned} \text{PW} &= \text{Duty cycle} \times T \\ \text{PW} &= 0.01 \times \frac{1}{15 \text{ kHz}} = 0.66 \mu\text{s} \end{aligned}$$

If a square wave is applied to circuitry that does not pass all the necessary frequency components, the resultant output is a distorted square wave. The type of distortion depends upon whether the circuitry has poor low-frequency response or poor high-frequency response. In Figure

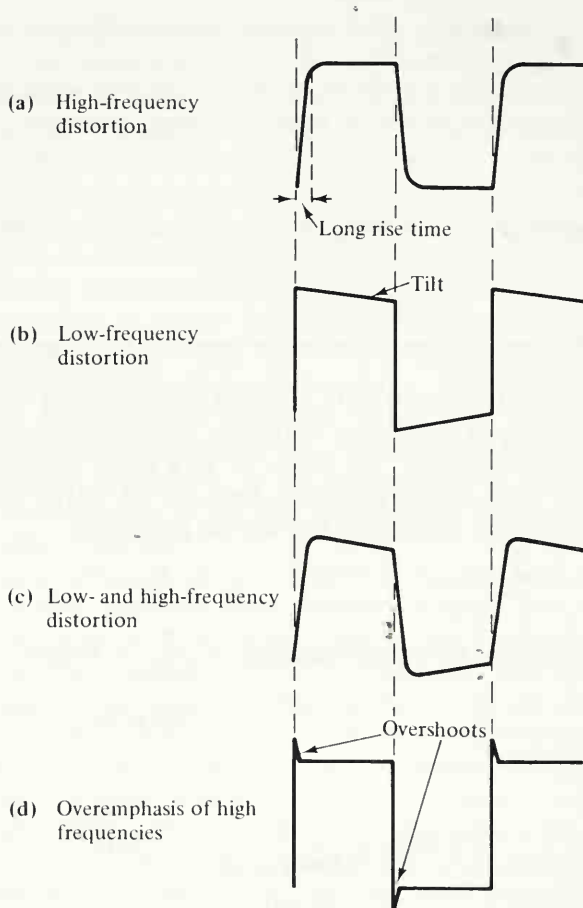


FIGURE 1-15. Distortion on square waves due to poor frequency response of circuitry.

1-15(a) the long rise and fall times of the square wave show that the high-frequency harmonics are attenuated and thus the circuit has poor high-frequency response. Figure 1-15(b) shows the output from a circuit which has good high-frequency response but poor low-frequency response. The *tilt* on the top and bottom of the square wave results because the low-frequency components were not passed by the circuit. The waveform in 1-15(c) shows both long rise times and tilt. This result is obtained when the involved circuitry has neither a low enough nor a high enough frequency response for the applied square wave. When circuits overemphasize some of the high-frequency harmonics, *overshoots* are produced, as shown in Figure 1-15(d).

When a square wave is applied to an amplifier the rise time of the

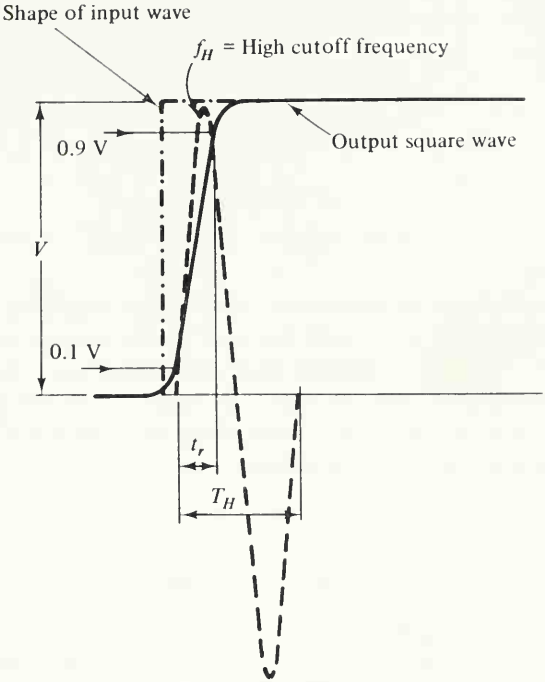


FIGURE 1-16. Origin of rise time on square wave output from an amplifier.

output waveform is limited by the time taken for the highest harmonic frequency to go from zero to its peak value (see Figure 1-16). Of course, the highest harmonic frequency that can be reproduced is the upper cutoff frequency f_H . It is found that:

$$t_r = 0.35 \times (\text{Time period of } f_H)$$

$$t_r = \frac{0.35}{f_H} \tag{1-6}$$

By Equation (1-6) the output rise time can be predicted when the upper cutoff frequency of the circuitry is known. Equation (1-6) also affords a fast means of pulse testing to determine the cutoff frequency of any circuit or device.

EXAMPLE 1-5 _____

The output waveform from an amplifier under pulse test has a rise time of $1 \mu\text{s}$. Determine the upper 3 dB frequency of the amplifier.

solution

From Equation (1-6):

$$\begin{aligned} f_H &= \frac{0.35}{t_r} = \frac{0.35}{1 \mu s} \\ &= 350 \text{ kHz} \end{aligned}$$

If a square wave is applied as input to an amplifier with a lower cutoff frequency of $f_L = 0$, then the top of the output square wave is perfectly flat. When f_L is greater than zero, however, tilt is present on the output waveform. As illustrated in Figure 1-17, the tilt is proportional to the ratio between the square wave time period T and the time period T_L of the lower cutoff frequency.

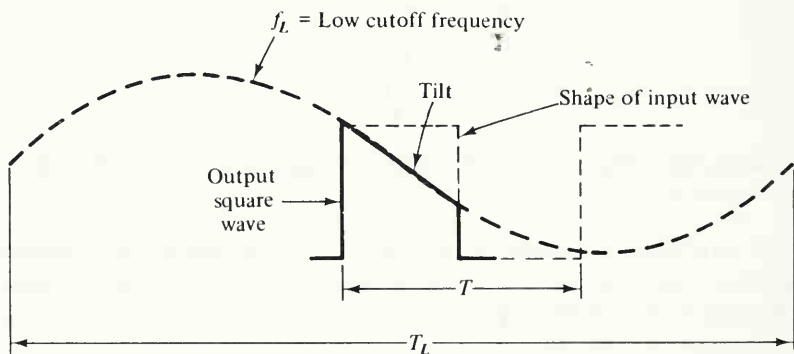


FIGURE 1-17. Origin of tilt on square wave output from an amplifier.

It is found that:

$$\text{Fractional tilt} = \pi \times \frac{T}{T_L}$$

or

$$\text{Fractional tilt} = \pi \frac{f_L}{f} \quad (1-7)$$

EXAMPLE 1-6

An amplifier with a low cutoff frequency of 10 Hz is to be employed for amplification of square waves. For the tilt on the output waveform to not exceed 2%, calculate the lowest input frequency that can be amplified.

solution

From Equation (1-7):

$$\begin{aligned} f &= \frac{\pi f_L}{\text{Fractional tilt}} \\ &= \frac{\pi \times 10 \text{ Hz}}{0.02} \\ &= 1.57 \text{ kHz} \end{aligned}$$

EXAMPLE 1-7

Determine the bandwidth required to amplify a 1-kHz square wave, if the rise time of the output is not to exceed 200 ns and 3% tilt is acceptable.

solution

From Equation (1-6):

$$f_H = \frac{0.35}{t_r} = \frac{0.35}{200 \text{ ns}} = 1.75 \text{ MHz}$$

From Equation (1-7):

$$\begin{aligned} f_L &= \frac{f \times \text{Fractional tilt}}{\pi} = \frac{1 \text{ kHz} \times 0.03}{\pi} \\ &= 9.5 \text{ Hz} \end{aligned}$$

EXAMPLE 1-8

Determine the upper and lower 3 dB frequencies of the circuitry which produced the output waveform shown in Figure 1-10.

solution

From Example 1-2:

$$t_r = 30 \mu s \quad \text{PRF} = 1639 \text{ pps} \quad \text{Tilt} = 14.1\%$$

From Equation (1-6):

$$f_H = \frac{0.35}{t_r} = \frac{0.35}{30 \mu s} = 116 \text{ kHz}$$

From Equation (1-7):

$$f_L = \frac{f \times (\text{Fractional tilt})}{\pi} = \frac{1639 \times 0.141}{\pi} = 73.6 \text{ Hz}$$

REVIEW QUESTIONS AND PROBLEMS

- 1-1 Define: repetitive waveforms, periodic waveforms, aperiodic waveforms, transients.
- 1-2 Draw sketches to show the shapes of the following waveforms: square, pulse, triangular, sawtooth, exponential.
- 1-3 For a pulse waveform, define: leading edge, lagging edge, trailing edge, T , PRF, PRR, PW, PD, M/S ratio, duty cycle.
- 1-4 For the pulse waveform illustrated in Figure 1-18, determine: pulse amplitude, PRF, PW, duty cycle, and M/S ratio. The vertical

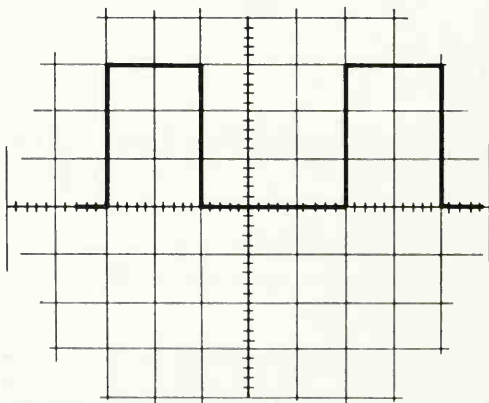


FIGURE 1-18. Problem 1-4.

scale is 0.1 V per division, and the horizontal scale is 1 ms per division.

- 1-5 (a) Define rise time, fall time, and tilt. (b) Determine the percentage tilt on the square wave shown in Figure 1-19.

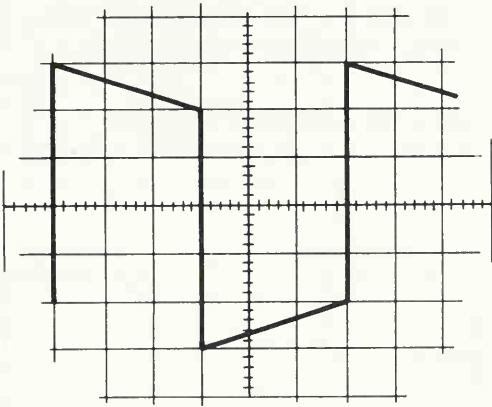


FIGURE 1-19. Problem 1-5.

- 1-6 For the waveform displayed in Figure 1-20, determine: pulse amplitude, tilt, t_r , t_f , PW, PRF, M/S ratio, and duty cycle. The vertical scale is 1 V/division, and the horizontal scale is 10 μ s/division.

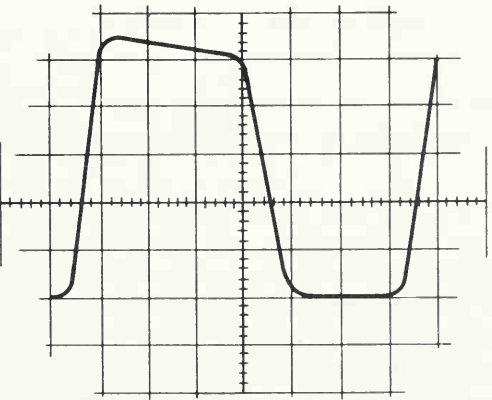


FIGURE 1-20. Problem 1-6.

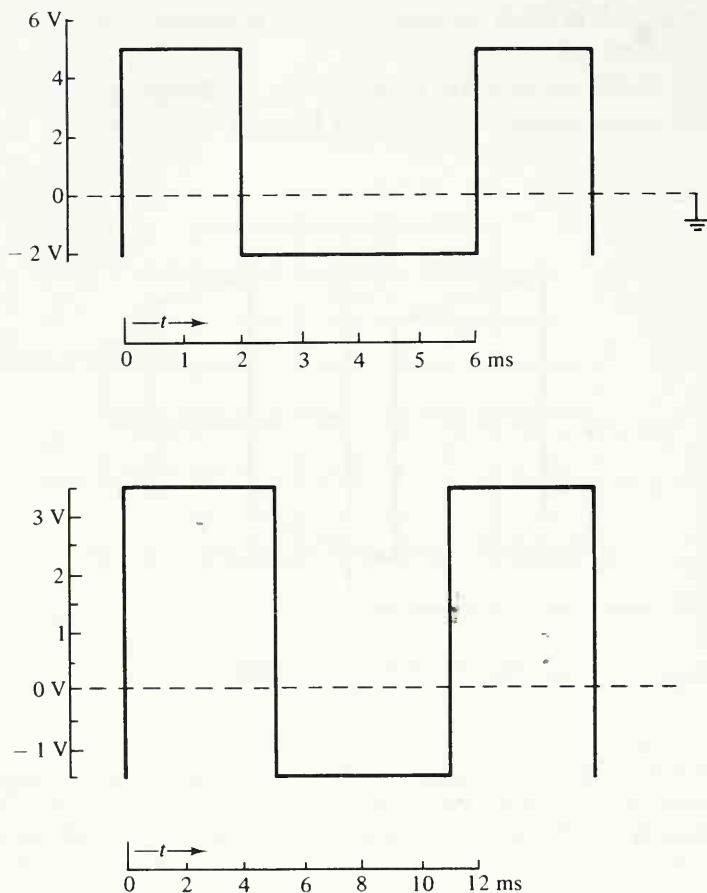


FIGURE 1-21. Problem 1-7.

- 1-7** If the pulse waveforms shown in Figure 1-21 were applied to a dc voltmeter, determine the voltages that would be indicated in each case.
- 1-8** (a) Define the following terms: fundamental, harmonic, frequency synthesis, harmonic analysis. (b) What harmonics will be passed by an amplifier which has an upper cutoff frequency of 1 MHz: (i) when a 10 kHz square wave is applied to it? and (ii) when the input is a 150 kHz square wave?
- 1-9** (a) A 12 kHz pulse waveform is amplified by a circuit having a high-frequency limit of 1 MHz. Determine the minimum pulse width that can be reproduced accurately. (b) If the duty cycle of the 12 kHz pulse waveform becomes 0.5%, determine the approximate

upper cutoff frequency of a circuit that will reproduce the waveform accurately.

- 1-10** Sketch a square wave which is amplified by equipment which: (a) has poor low-frequency response; (b) has poor high-frequency response; (c) over emphasizes high frequencies; (d) has a combination of poor low-frequency and poor high-frequency responses.
- 1-11** A 1 kHz square wave output from an amplifier has $t_r = 350$ ns and tilt = 5%. Determine the upper and lower 3 dB frequencies of the amplifier.
- 1-12** Calculate the rise time and tilt that may be expected on the square wave output of an amplifier with a bandwidth extending from 10 Hz to 500 kHz. The applied square wave has a frequency of 5 kHz.
- 1-13** Determine the bandwidth of the circuitry which produced the output waveform shown in Figure 1-20 (Problem 1-6).
- 1-14** Construct the waveform which results when the fundamental and harmonics shown in Figure 1-22 are added together.

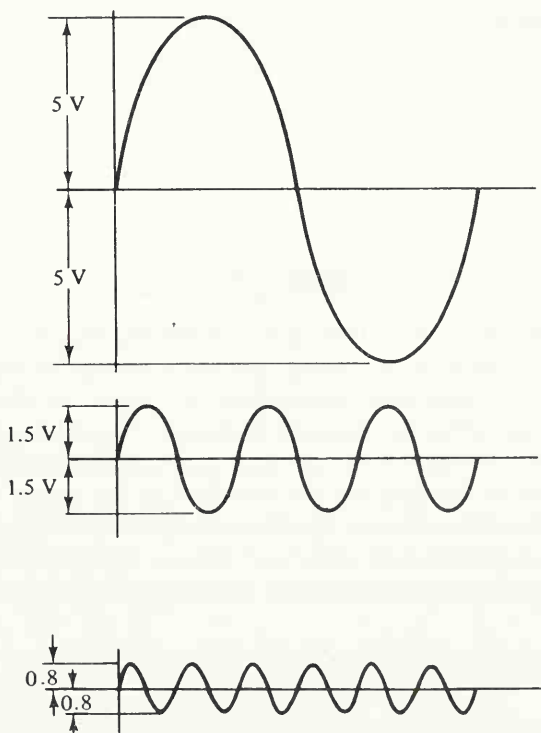


FIGURE 1-22. Problem 1-14.

Chapter 2

Capacitive Resistive (CR) Circuits

INTRODUCTION

When a capacitor is charged from a dc voltage source, via a resistor, the instantaneous level of capacitor voltage may be calculated at any given time. There is a definite relationship between the *TIME CONSTANT* of a CR circuit, and the times required for the capacitor to charge to approximately 63% and 99% of the input voltage. Also, an important relationship exists between the time constant of a circuit and the rise time of the output voltage from the circuit. Depending upon the arrangement of the CR circuit, it may be employed as an *INTEGRATOR* or a *DIFFERENTIATOR*. In each case, the circuit time constant must be related to the time period of the input waveform.

2-1 CR CIRCUIT OPERATION

Consider the circuit and graph shown in Figure 2-1. If the charge on capacitor *C* is zero at the instant that switch *S* is closed, then the voltage

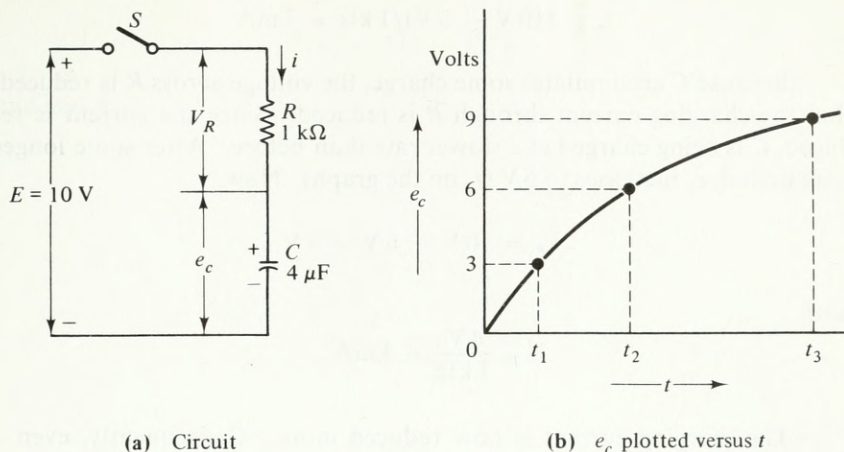


FIGURE 2-1. Circuit for charging capacitor via resistor, and graph of capacitor voltage variation with respect to time.

across R at $t = 0$ is

$$V_R = E - e_c$$

where E is the supply voltage and e_c is the capacitor voltage. The current through R at $t = 0$ is

$$\begin{aligned}
 i_c &= \frac{V_R}{R} \\
 &= \frac{E - e_c}{R} \\
 &= \frac{10 \text{ V} - 0}{1 \text{ k}\Omega} \\
 &= 10 \text{ mA}
 \end{aligned} \tag{2-1}$$

This current causes capacitor C to charge with the polarity shown, so that at some time t_1 the capacitor voltage e_c might be 3 V [see Figure 2-1(b)]. This alters V_R :

$$\begin{aligned}
 V_R &= E - e_c \\
 &= 10 \text{ V} - 3 \text{ V} = 7 \text{ V}
 \end{aligned}$$

Now,

$$i_c = (10 \text{ V} - 3 \text{ V}) / 1 \text{ k}\Omega = 7 \text{ mA}$$

Because C accumulates some charge, the voltage across R is reduced; thus the charging current through R is reduced. Since the current is reduced, C is being charged at a slower rate than before. After some longer time period, e_c increases to 6 V (t_2 on the graph). Now,

$$V_R = 10 \text{ V} - 6 \text{ V} = 4 \text{ V}$$

and

$$i_c = \frac{4 \text{ V}}{1 \text{ k}\Omega} = 4 \text{ mA}$$

The charging current is now reduced more. Consequently, even a longer time period is required to charge C by another 3 V.

The capacitor does not receive its charge at a constant rate. Instead, e_c is continuously increasing, so the voltage across R is continuously decreasing, and the charging current is decreasing. This means that C is charged at a rapid rate initially, and then the rate decreases as the capacitor voltage grows.

It can be shown that the capacitor voltage follows an exponential law:

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}} \quad (2-2)$$

where

e_c = capacitor voltage at instant t

E = charging voltage

E_o = initial charge on the capacitor

ϵ = exponential constant = 2.718

t = time from commencement of charge

C = capacitance being charged

R = charging resistance

When there is no initial charge on the capacitor,

$$E_o = 0$$

$$e_c = E - [E - 0]\epsilon^{\frac{-t}{CR}}$$

or

$$e_c = E(1 - e^{\frac{-t}{CR}}) \quad (2-3)$$

and, since

$$\begin{aligned} i_c &= \frac{E - e_c}{R} \\ &= \frac{E - E(1 - e^{\frac{-t}{CR}})}{R} \\ &= \frac{E}{R} e^{\frac{-t}{CR}} \end{aligned}$$

or

$$i_c = I e^{\frac{-t}{CR}} \quad (2-4)$$

where $I = E/R$ is the initial level of charging current when $t = 0$.

EXAMPLE 2-1

Calculate the levels of e_c , the capacitor voltage across C in the circuit of Figure 2-1(a), at 2 ms intervals from the instant when switch S is closed. Plot a graph of e_c versus time.

solution

Since $E_o = 0$, Equation (2-3) may be used to calculate e_c . At $t = 0$,

$$e_c = E(1 - e^0) = 0 \text{ V} \quad \text{point 1}$$

At $t = 2 \text{ ms}$,

$$e_c = 10 \text{ V}(1 - e^{\frac{-2\text{ms}}{4\mu\text{F} \times 1\text{k}\Omega}}) = 3.93 \text{ V} \quad \text{point 2}$$

At $t = 4 \text{ ms}$,

$$e_c = 10 \text{ V}(1 - e^{\frac{-4\text{ms}}{4\mu\text{F} \times 1\text{k}\Omega}}) = 6.32 \text{ V} \quad \text{point 3}$$

At $t = 6 \text{ ms}$,

$$e_c = 7.77 \text{ V} \quad \text{point 4}$$

At $t = 8$ ms,

$$e_c = 8.65 \text{ V} \quad \text{point 5}$$

At $t = 10$ ms,

$$e_c = 9.18 \text{ V} \quad \text{point 6}$$

At $t = 12$ ms,

$$e_c = 9.5 \text{ V} \quad \text{point 7}$$

At $t = 14$ ms,

$$e_c = 9.7 \text{ V} \quad \text{point 8}$$

At $t = 16$ ms,

$$e_c = 9.82 \text{ V} \quad \text{point 9}$$

The above points are plotted in Figure 2-2.

EXAMPLE 2-2

Determine the instantaneous levels of charging current, in the circuit of Figure 2-1(a) at 2 ms time intervals from the instant that switch S is closed. Plot a graph showing i_c versus time.

solution

By Equation (2-1);

$$i_c = \frac{E - e_c}{R}$$

At $t = 0$,

$$i_c = \frac{10 \text{ V} - 0}{1 \text{ k}\Omega} = 10 \text{ mA}, \quad \text{point 11}$$

$t = 2$ ms,

$$e_c = 3.93 \text{ V (from Example 2-1)}$$

$$i_c = \frac{10 \text{ V} - 3.93 \text{ V}}{1 \text{ k}\Omega} = 6.07 \text{ mA} \quad \text{point 12}$$

$t = 4$ ms,

$$i_c = \frac{10 \text{ V} - 6.32 \text{ V}}{1 \text{ k}\Omega} = 3.68 \text{ mA} \quad \text{point 13}$$

$t = 6 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 7.77 \text{ V}}{1 \text{ k}\Omega} = 2.23 \text{ mA} \qquad \text{point 14}$$

$t = 8 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 8.65 \text{ V}}{1 \text{ k}\Omega} = 1.35 \text{ mA} \qquad \text{point 15}$$

$t = 10 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 9.18 \text{ V}}{1 \text{ k}\Omega} = 0.82 \text{ mA} \qquad \text{point 16}$$

$t = 12 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 9.5 \text{ V}}{1 \text{ k}\Omega} = 0.5 \text{ mA} \qquad \text{point 17}$$

$t = 14 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 9.7 \text{ V}}{1 \text{ k}\Omega} = 0.3 \text{ mA} \qquad \text{point 18}$$

$t = 16 \text{ ms},$

$$i_c = \frac{10 \text{ V} - 9.82 \text{ V}}{1 \text{ k}\Omega} = 0.18 \text{ mA} \qquad \text{point 19}$$

These points are plotted on Figure 2-2.



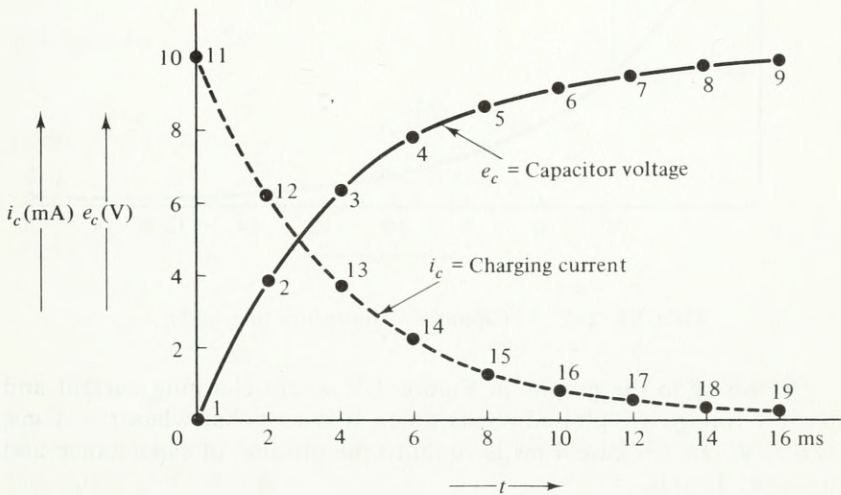


FIGURE 2-2. Capacitor current and voltage plotted versus time.

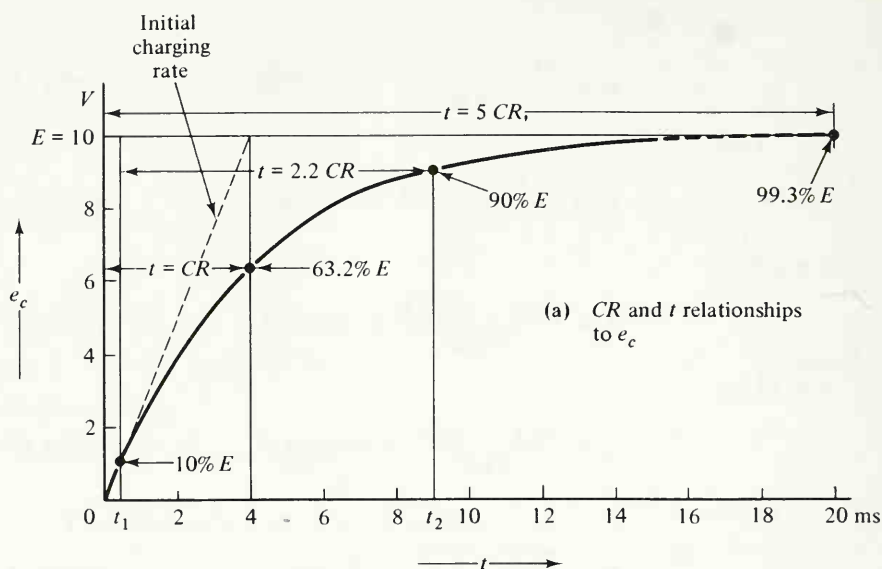

(a) CR and t relationships to e_c

 

(b) CR and t relationships to i_c

FIGURE 2-3. CR and t relationships to e_c and i_c .

Referring to the graphs in Figure 2-3, where charging current and capacitor voltage are plotted *versus* time. It is seen that when $t = 4$ ms, e_c is 6.32 V. In this case 4 ms is equal to the product of capacitance and resistance. That is,

$$t = C \times R = 4 \mu\text{F} \times 1 \text{ k}\Omega = 4 \times 10^{-3}$$

Therefore, when $t = CR$, e_c is 6.32 V or 63.2% of E . Consider Equation (2-3) once again:

$$e_c = E(1 - e^{-\frac{t}{CR}})$$

When $t = CR$,

$$\begin{aligned} e_c &= E(1 - e^{-\frac{CR}{CR}}) \\ &= E(1 - e^{-1}) \\ &= E \times 0.632 \end{aligned} \quad (2-5)$$

Thus, when $t = CR$, $e_c = 63.2\%$ of E , no matter what the value of E , C , or R .

The product CR is termed the *time constant* of a circuit. As will be seen, the time constant is a very important quantity. It can be used to classify a circuit, and it can be related to the rise time of an output pulse. The Greek letter τ is frequently employed as the symbol for the time constant. For a resistive capacitive circuit, $\tau = CR$.

Now consider the equation for instantaneous charging current [Equation (2-4)]:

$$i_c = I e^{-\frac{t}{CR}}$$

and again let $t = CR$.

$$\begin{aligned} i_c &= I e^{-\frac{CR}{CR}} = I e^{-1} \\ &= I \times 0.368 \end{aligned}$$

or, when $t = CR$,

$$i_c = I(1 - 0.632) \quad (2-6)$$

Thus, after time $t = CR$, the charging current is reduced by 63.2% of its initial value [see Figure 2-3(b)]. If the charging current were to remain constant at its initial level, the quantity of charge contained in the capacitor would be:

$$Q = I \times t \text{ coulombs}$$

also,

$$Q = C \times V \text{ coulombs}$$

where C is the capacitance (in farads), and V is the capacitor voltage (in volts).

Therefore,

$$It = CV$$

or

$$V = \frac{It}{C} \quad (2-7)$$

It is important to note that Equation (2-7) applies only to circuits in which the charging current is held at a constant level. It does not apply to the circuit of Figure 2-1(a). However, this equation can be employed to learn a little more about the time constant CR .

The initial level of charging current in an ordinary resistive capacitive circuit [as in Figure 2-1(a)] is $I = E/R$. If this were to remain constant then the time for the capacitor to become completely charged could be calculated from Equation (2-7).

$$t = \frac{CV}{I}$$

for $V = E$, and $I = E/R$,

$$t = \frac{C \times E}{E/R} = CR$$

As illustrated by the broken line in Figure 2-3(a), with the initial charging current constant, the capacitor would be completely charged in a time period of $t = CR$. Again, note that the time constant is involved.

Once again refer to Figure 2-3(a). It is seen that even after 16 ms, the capacitor is not completely charged to the level of the supply voltage. Theoretically, because the charging current continuously decreases, the capacitor cannot become completely charged to the supply voltage level. However, after a period of five time constants, that is, $t = 5 \times CR$, the capacitor is more than 99% charged and, for all practical purposes, can be regarded as completely charged. For the circuit of Figure 2-1(a), after $t = 5 \times CR$ the capacitor voltage is

$$e_c = 10 \text{ V} (1 - e^{\frac{-5CR}{CR}}) = 9.93 \text{ V}$$

Similarly, it can be shown that i_c reduces to less than 1% of its initial level (I) after a time period of $5 CR$ [see Figure 2-3(b)].

It was pointed out in Chapter 1 that the rise time of a pulse output from a circuit is determined as the time it takes for the output to go from 10% to 90% of maximum output level. The CR circuit shown in Figure 2-1(a) has a step input of 10 V applied to it when switch S is closed. It has been shown that the output eventually approaches the maximum level of the step input. The rise time of the output can then be calculated as

$$(t \text{ at } e_c = 90\% E) - (t \text{ at } e_c = 10\% E)$$

An expression for t at a given level of e_c can be derived from Equation (2-2):

$$\begin{aligned} e_c &= E - (E - E_o) e^{\frac{-t}{CR}} \\ (E - E_o) e^{\frac{-t}{CR}} &= E - e_c \\ e^{\frac{-t}{CR}} &= \left(\frac{E - e_c}{E - E_o} \right) \\ e^{\frac{t}{CR}} &= \left(\frac{E - E_o}{E - e_c} \right) \\ \frac{t}{CR} &= \ln \left(\frac{E - E_o}{E - e_c} \right) \\ t &= CR \ln \left(\frac{E - E_o}{E - e_c} \right) \end{aligned} \quad (2-8)$$

For $e_c = 90\%$ of E (t_2 on Figure 2-3):

$$\begin{aligned} t_2 &= CR \ln \left(\frac{E - E_o}{E - 0.9E} \right) = CR (\ln 10) \\ &= 2.3 CR \end{aligned} \quad (2-9)$$

For $e_c = 10\%$ of E (t_1 on Figure 2-3):

$$(\ln 10 = 2.3)$$

$$\begin{aligned}
 t_1 &= CR \ln \left(\frac{E - 0}{E - 0.1 E} \right) \\
 &= 0.1 CR
 \end{aligned}
 \tag{2-10}$$

Therefore the rise time of the output is

$$\begin{aligned}
 t_r &= (t_2 - t_1) = CR(2.3 - 0.1) \\
 &= 2.2 CR
 \end{aligned}
 \tag{2-11}$$

Equation (2-11) can be applied to any resistive capacitive circuit when the time constant CR is known. Sometimes a time constant is calculated for an amplifier or for a single transistor. Then Equation (2-11) can be used to determine the rise time of an output pulse. It can also be shown that the upper cutoff frequency (f_H) of a circuit is related to CR by the equation:

$$f_H = \frac{1}{2\pi CR} \tag{2-12}$$

To summarize the relationships between CR and e_c and time; when $t = CR$,

$$\begin{aligned}
 e_c &= 0.632 E \\
 i_c &= I(1 - 0.632)
 \end{aligned}$$

when $t = 5 CR$,

$$\begin{aligned}
 e_c &= 0.993 E \\
 i_c &= I(1 - 0.993)
 \end{aligned}$$

The output rise time, t_r is equal to $2.2 CR$ and the upper cutoff frequency,

$$f_H = \frac{1}{2\pi CR}$$

EXAMPLE 2-3

A $1 \mu\text{F}$ capacitor is charged from a 6 V source through a $10 \text{ k}\Omega$ resistor. If the capacitor has an initial charge of -3 V , calculate its charge after 8 ms .

solution

By Equation (2-2),

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}}$$

At $t = 8 \text{ ms}$,

$$\begin{aligned} e_c &= 6 \text{ V} - [6 \text{ V} - (-3 \text{ V})]\epsilon^{\frac{-8 \text{ ms}}{1 \mu\text{F} \times 10 \text{ k}\Omega}} \\ &= 6 \text{ V} - [9 \text{ V}]\epsilon^{-0.8} = 1.96 \text{ V} \end{aligned}$$

EXAMPLE 2-4

A 5 V step is switched *on* to a 39 k Ω resistor in series with a 500 pF capacitor. Calculate the rise time of the capacitor voltage, the time for the capacitor to charge to 63.2% of its maximum voltage, and the time for the capacitor to become completely charged.

solution

Rise time:

$$\begin{aligned} t_r &= 2.2 CR \\ &= 2.2 \times 500 \text{ pF} \times 39 \text{ k}\Omega \\ &= 42.9 \mu\text{s} \end{aligned}$$

$e_c = 0.632 E$, at $t = CR$:


$$\begin{aligned} t &= 500 \text{ pF} \times 39 \text{ k}\Omega \\ &= 19.5 \mu\text{s} \end{aligned}$$

Capacitor is 99.3% charged at $t = 5 CR$:


$$t = 97.5 \mu\text{s}$$

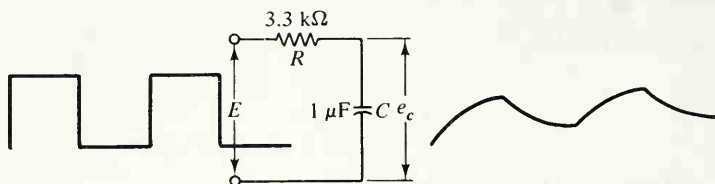2-2 CR CIRCUIT RESPONSE TO SQUARE WAVES


A resistive capacitive circuit with an input square wave is shown in Figure 2-4(a). The capacitor voltage first increases from zero to a level e_1 at



(a) Circuit

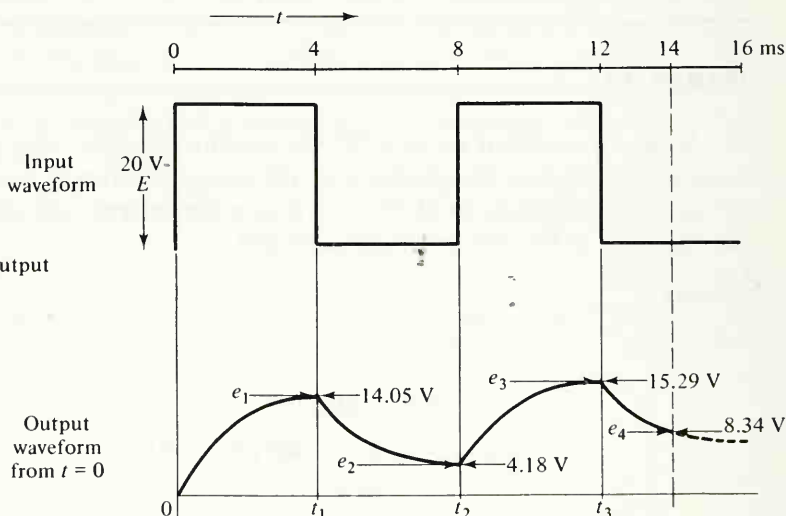

(b) Input and output waveforms

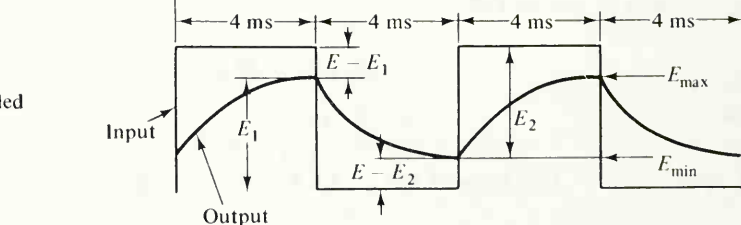

(c) Output settled waveform

FIGURE 2-4. CR circuit response to a square wave input.

time t_1 [see Figure 2-4(b)]. Between t_1 and t_2 the applied voltage is zero, so the capacitor discharges to e_2 volts. Then the capacitor charges to a new level e_3 at time t_3 . To determine the level of e_c at any time greater than t_2 it is necessary first to calculate e_1 at time t_1 . Then e_2 must be calculated using the initial charge on the capacitor as e_1 , and noting that

the input voltage is zero from t_1 to t_2 . Between t_2 and t_3 , the initial charge is e_2 volts, and the input voltage is again greater than zero.

EXAMPLE 2-5

Calculate the capacitor voltage in the circuit of Figure 2-4(a) at 14 ms from $t = 0$.

solution

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}}$$

At $t = 4$ ms,

$$\begin{aligned} e_c &= 20 \text{ V} - (20 \text{ V} - 0)\epsilon^{\frac{-4\text{ms}}{1\mu\text{F} \times 3.3\text{k}\Omega}} \\ &= 14.05 \text{ V} \quad [e_1 \text{ in Figure 2-4(b)}] \end{aligned}$$

From $t = 4$ ms to $t = 8$ ms; $E = 0$ V and $E_o = 14.05$ V. At $t = 8$ ms,

$$\begin{aligned} e_c &= 0 - (0 - 14.05 \text{ V})\epsilon^{\frac{-4\text{ms}}{1\mu\text{F} \times 3.3\text{k}\Omega}} \\ &= 4.18 \text{ V} \quad [e_2 \text{ in Figure 2-4(b)}] \end{aligned}$$

From $t = 8$ ms to $t = 12$ ms; $E = 20$ V and $E_o = 4.18$ V. At $t = 12$ ms,

$$\begin{aligned} e_c &= 20 \text{ V} - (20 \text{ V} - 4.18 \text{ V})\epsilon^{\frac{-4\text{ms}}{1\mu\text{F} \times 3.3\text{k}\Omega}} \\ &= 15.29 \text{ V} \quad [e_3 \text{ in Figure 2-4(b)}] \end{aligned}$$

From $t = 12$ ms to $t = 16$ ms; $E = 0$ and $E_o = 15.29$ V. At $t = 14$ ms,

$$\begin{aligned} e_c &= 0 - (0 - 15.29 \text{ V})\epsilon^{\frac{-2\text{ms}}{1\mu\text{F} \times 3.3\text{k}\Omega}} \\ &= 8.34 \text{ V} \quad [e_4 \text{ in Figure 2-4(b)}] \end{aligned}$$

After several intervals of charging, partially discharging, and recharging, the capacitor voltage will eventually arrive at a settled condition. When this occurs, the capacitor always charges to a maximum level, E_{\max} , and discharges to a minimum level, E_{\min} , as shown in Figure 2-4(c). These final levels occur when the charging and discharging

voltages are equal. Thus, in Figure 2-4(c) $E_1 = E_2$. Also $E_{\max} = E_1$, and $E_{\min} = (E - E_{\max})$.

Calculating E_{\min} , starting from $E_o = E_{\max}$ and $E = 0$ V,

$$\begin{aligned} E_{\min} &= e_c = 0 - (0 - E_{\max})\epsilon^{\frac{-t}{CR}} \\ &= E_{\max}\epsilon^{\frac{-t}{CR}} \end{aligned}$$

and since $E_{\min} = (E - E_{\max})$

$$\begin{aligned} E - E_{\max} &= E_{\max}\epsilon^{\frac{-t}{CR}} \\ E &= E_{\max}\epsilon^{\frac{-t}{CR}} + E_{\max} \\ &= E_{\max}(\epsilon^{\frac{-t}{CR}} + 1) \end{aligned}$$

and

$$E_{\max} = \frac{E}{1 + \epsilon^{\frac{-t}{CR}}} \quad (2-13)$$

EXAMPLE 2-6

For the circuit of Figure 2-4(a) determine the maximum and minimum levels at which the capacitor voltage will settle.

solution

Refer to Equation (2-13):

$$\begin{aligned} E_{\max} &= \frac{E}{1 + \epsilon^{\frac{-t}{CR}}} \\ &= \frac{20 \text{ V}}{1 + \epsilon^{\frac{-4 \text{ ms}}{1 \mu\text{F} \times 3.3 \text{ k}\Omega}}} \\ &= 15.41 \text{ V} \\ E_{\min} &= E - E_{\max} \\ &= 20 - 15.41 = 4.59 \text{ V} \end{aligned}$$

The charging current for the circuit of Figure 2-4(a) may be most easily calculated at any time as:

$$i_c = \frac{E - e_c}{R}$$

Note that during the time intervals when $E = 0$, i_c is a negative quantity. Because the capacitor is discharging, the current through R is reversed. The charging current is also discussed in Section 2-4.

2-3 INTEGRATING CIRCUITS

Figure 2-5 shows a CR circuit with a square wave input and the output voltage taken across the capacitor. The shape of the output (capacitor) voltage waveform is dependent upon the relationship between the time constant (CR) and the pulse width (PW).

Consider the case where CR is much smaller than PW [waveform (a) in Figure 2-5]. In Sec. 2-1, it was demonstrated that the capacitor is charged to 99.3% of the input voltage after time $t = 5 CR$: Let

$$CR = \frac{1}{10} \text{ PW}$$

Then,

$$e_c = 99.3\% \text{ of } E \text{ at } t = 5 \left(\frac{1}{10} \text{ PW} \right)$$

That is,

$$e_c \simeq E \text{ at } t = \frac{1}{2} \text{ PW}$$

In this case the output roughly approximates the square wave input. If CR is made smaller than $\frac{1}{10} \text{ PW}$, then the output even more closely resembles the square wave input.

For the waveform (b) in Figure 2-5, CR is equal to the pulse width. In Sec. 2-1 it was shown that the capacitor is charged to 63.2% of the input voltage after time $t = CR$. However, the settled waveform has an amplitude which is less than 63.2% of E . Under these conditions the waveform of capacitor voltage begins to approach a triangular shape.

When CR is made equal to ten times the pulse width, waveform of Figure 2-5 (c) results. In this case the CR circuit, as arranged, is referred to as an *integrator*. To understand how the circuit integrates, it is neces-

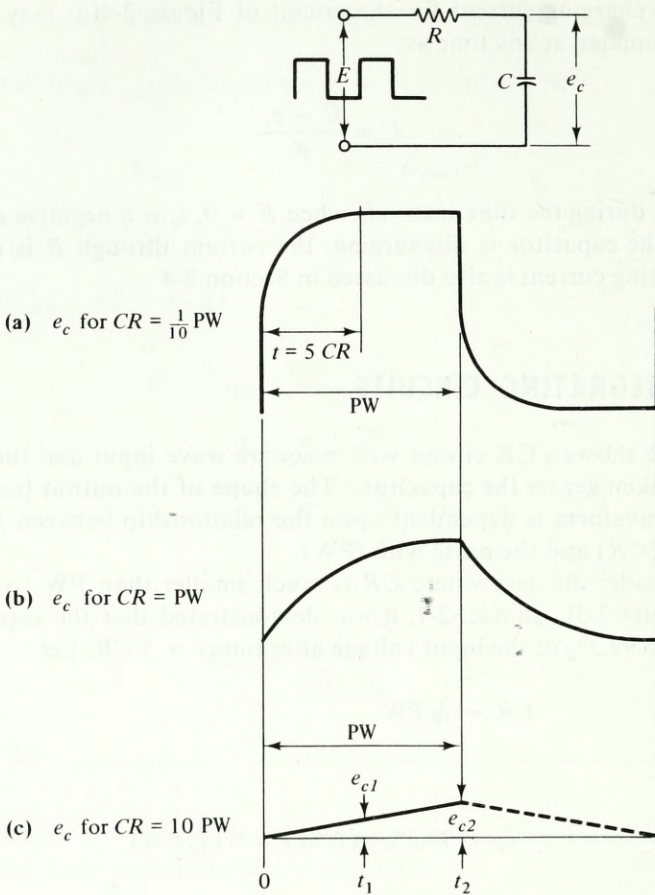


FIGURE 2-5. Integrating circuit and output waveforms.

sary to calculate the output voltage levels in relation to time. At $CR = 10 \times PW$, use Equation (2-2) to obtain:

$$\begin{aligned} e_{c2} &= E - (E - E_o)\epsilon^{\frac{-PW}{10PW}} \\ &\simeq E - E\epsilon^{-1/10} \quad \text{for } E_o = 0 \\ &\simeq E(1 - 0.9) \\ &\simeq 0.1 E \end{aligned}$$

To calculate e_{c1} at $\frac{1}{2} PW$:

$$\begin{aligned}
 e_{c1} &= E - E\epsilon^{\frac{-1/2 \text{ PW}}{10 \text{ PW}}} \\
 &= E - E\epsilon^{-1/20} \\
 &\simeq E(1 - 0.95) \\
 &\simeq 0.05 E
 \end{aligned}$$

This result shows that after time t_1 , $e_{c1} = 0.05 E$ and after $t_2 = 2t_1$, $e_{c2} = 0.1 E$. That is, $e_{c2} \simeq 2e_{c1}$ when $t_2 = 2t_1$ (see Figure 2-5). Thus the capacitor voltage is growing almost linearly. To further examine the output waveform when CR is 10 (or more) times the pulse width, consider Example 2-7.

EXAMPLE 2-7

The circuit shown in Figure 2-6 has the following pulse inputs applied: (a) $E = 10 \text{ V}$, $\text{PW} = 1 \text{ ms}$; (b) $E = 10 \text{ V}$, $\text{PW} = 2 \text{ ms}$; (c) $E = 20 \text{ V}$, $\text{PW} = 1 \text{ ms}$. Calculate the level of e_c at the end of each pulse. The initial charge on C is assumed to be zero.

solution

From Equation (2-2),

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}}$$

For input (a):

$$\begin{aligned}
 e_{c(a)} &= 10 \text{ V} - (10 \text{ V} - 0 \text{ V})\epsilon^{\frac{-1 \text{ ms}}{20 \mu\text{F} \times 10 \text{ k}\Omega}} \\
 &\simeq 50 \text{ mV}
 \end{aligned}$$

For input (b):

$$\begin{aligned}
 e_{c(b)} &= 10 \text{ V} - (10 \text{ V} - 0 \text{ V})\epsilon^{\frac{-2 \text{ ms}}{20 \mu\text{F} \times 10 \text{ k}\Omega}} \\
 &\simeq 100 \text{ mV}
 \end{aligned}$$

For input (c):

$$\begin{aligned}
 e_{c(c)} &= 20 \text{ V} - (20 \text{ V} - 0 \text{ V})\epsilon^{\frac{-1 \text{ ms}}{20 \mu\text{F} \times 10 \text{ k}\Omega}} \\
 &\simeq 100 \text{ mV}
 \end{aligned}$$

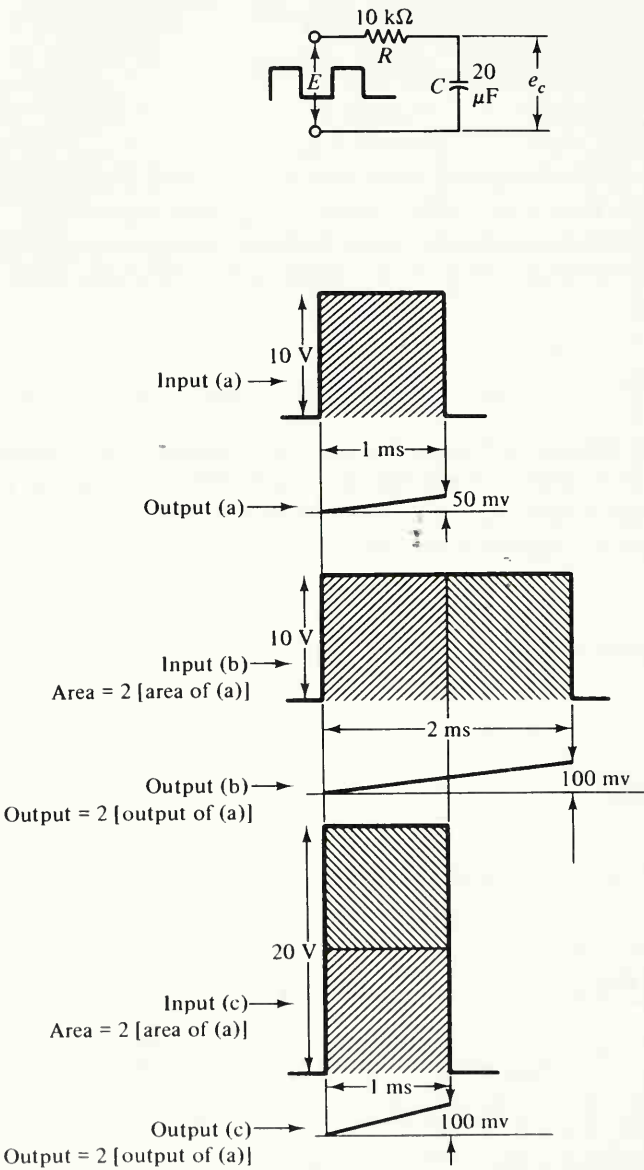


FIGURE 2-6. Integration of pulses having different widths and amplitudes.

Since the charging current remains substantially constant during the input PW, this problem can also be solved by using Equation (2-7):

$$\begin{aligned} V &= \frac{It}{C} \\ &= \frac{E}{R} \times \frac{t}{C} \end{aligned}$$

For input (a):

$$e_{c(a)} = \frac{10 \text{ V} \times 1 \text{ ms}}{10 \text{ k}\Omega \times 20 \text{ }\mu\text{F}} = 50 \text{ mV}$$

For input (b):

$$e_{c(b)} = \frac{10 \text{ V} \times 2 \text{ ms}}{10 \text{ k}\Omega \times 20 \text{ }\mu\text{F}} = 100 \text{ mV}$$

For input (c):

$$e_{c(c)} = \frac{20 \text{ V} \times 1 \text{ ms}}{10 \text{ k}\Omega \times 20 \text{ }\mu\text{F}} = 100 \text{ mV}$$

Example 2-7 shows that when the pulse width is doubled, the output voltage is doubled. Because the charging rate is (almost) linear, the output amplitude is proportional to the pulse width. Also, when the pulse amplitude is doubled, the output voltage is doubled. In this case, the charging rate is increased in proportion to the input voltage. Thus, the output voltage is proportional to the product of the pulse width (PW) and the pulse amplitude (PA). That is,

$$e_c \propto \text{PA} \times \text{PW}$$

Figure 2-6 and Example 2-7 show that the output voltage from an integrating circuit is proportional to the area of the pulse expressed as (volts \times time). An *integrating circuit* is a CR circuit with the output taken across the capacitor, and $CR \geq (10 \times \text{PW})$. In other integrator circuits to be discussed in Chapter 7, the capacitor charging current is held constant by the use of additional components.

Figure 2-7 illustrates the integration of a sine wave. From time zero at the peak of the sine wave, the wave is divided into sections of equal

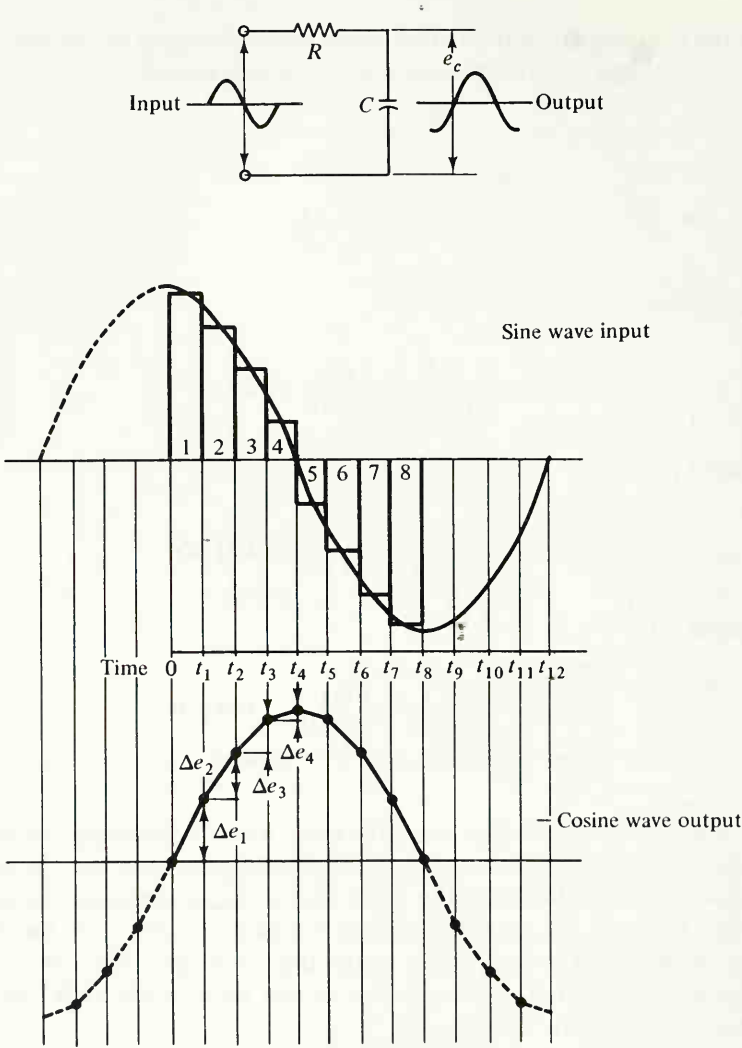


FIGURE 2-7. Integration of a sine wave.

widths. The height of each section corresponds approximately to the instantaneous sine wave amplitude. Thus the sine wave is represented by a series of pulses of varying amplitudes. The first pulse causes a linear increase in capacitor voltage from time 0 to t_1 . This produces output voltage Δe_1 . The second pulse, from t_1 to t_2 , also produces a linear increase in the capacitor voltage. However, the pulse amplitude is now smaller, so that the rate of increase in capacitor voltage is reduced. Thus Δe_2 is less than Δe_1 . Similarly, the third and fourth pulses produce linear vol-

tage increases, at decreasing rates. Since pulse 5 is negative, it causes the capacitor voltage to decrease by a small amount equal to the increase (Δe_4) produced by pulse 4. Also, negative pulses 6, 7, and 8 linearly decrease the output (capacitor) voltage. Extending the waveforms (broken lines), it is seen that integration of the sine wave input produces a negative cosine wave output.

2-4 DIFFERENTIATING CIRCUITS

When the output from a CR circuit is taken across R , the output voltage is the differential of the input. As in the case of the integrating circuit, the relationship between CR and the pulse width is important. Figure 2-8 shows the various output waveforms that can occur, depending upon PW and CR.

The voltage across R is the product of the charging current and the resistance, that is, $e_R = i_c \times R$. When the time constant CR is 10 times the pulse width (or greater), the capacitor charges very little during the pulse time. The charging current falls only a small amount from its initial level [see waveform (a) in Figure 2-8]. Thus, e_R remains almost constant during the PW. During the space width the capacitor is discharged, and i_c is a negative quantity. The resistor voltage is now negative and, again, remains nearly constant for the discharge time.

If CR is made equal to the pulse width, the capacitor is charged to approximately 60% of the input voltage during the pulse time. Consequently the charging current falls by about 60% of its initial value, giving an output waveform with a very pronounced tilt [see the waveform in Figure 2-8(b)].

When CR is less than one-tenth of the pulse width, the capacitor is charged very rapidly. Only a brief pulse of current is necessary to charge and discharge the capacitor at the beginning and end of the pulse. The resultant waveform of resistor voltage is a series of positive and negative spikes at the pulse leading and lagging edges, respectively [see Figure 2-8(c)]. The *differential* of a quantity is a measure of the rate of change of the quantity. At the leading edge of the pulse (for $CR = \frac{1}{10}$ PW), the input voltage is changing rapidly in a positive direction. At the lagging edge of the pulse, the input voltage is changing rapidly in a negative direction. During both the pulse width and the space width, the input voltage does not change at all. Thus, it is seen that the positive and negative spikes with intervening spaces do indeed represent a differentiated square wave.

When a ramp voltage is applied to the input of a differentiating circuit, the resultant output is a constant dc voltage level (Figure 2-9).

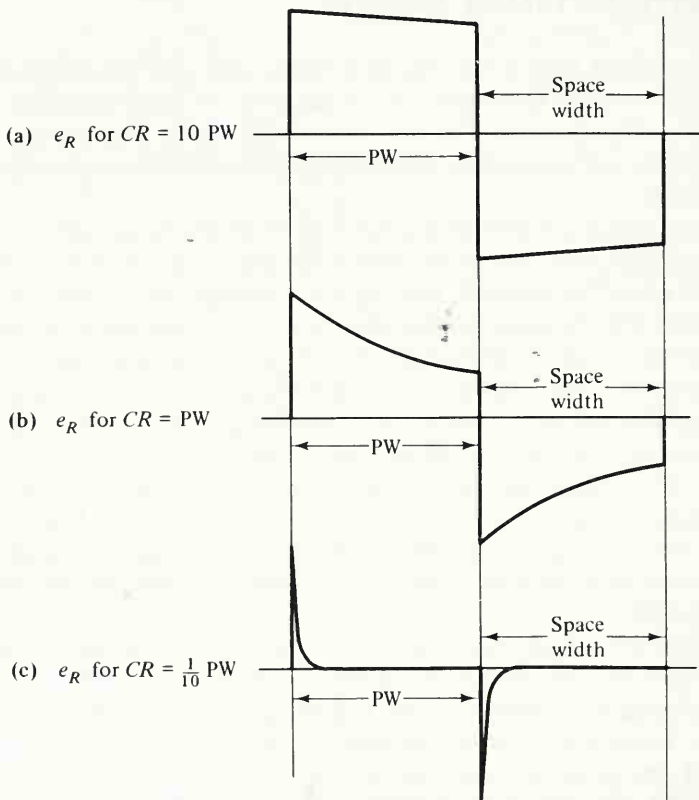
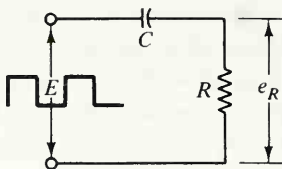


FIGURE 2-8. Differentiating circuit and output waveform.

While the input voltage continuously increases, the capacitor cannot become completely charged. Hence, the instantaneous capacitor voltage is always slightly less than the instantaneous input voltage. This small difference in E and e_c is developed across R , giving a constant level of charging current, and thus a constant level of e_R . While the ramp increases positively, the capacitor is charged with the polarity shown and i_c pro-

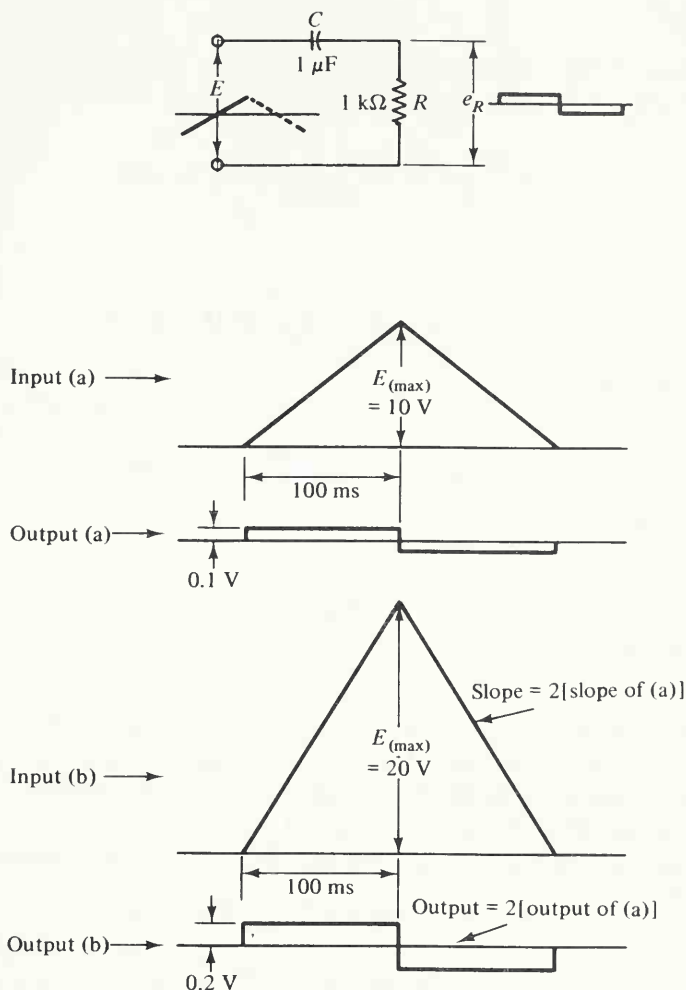


FIGURE 2-9. Differentiation of ramp voltage changes.

duces a positive level of e_R . When the ramp goes negative, i_C is reversed and, consequently, e_R is negative.

EXAMPLE 2-8

For inputs (a) and (b), calculate the level of the outputs from the differentiating circuit shown in Figure 2-9.

solution

At the end of the input ramp $e_c \simeq E_{\max}$. Since the charging current is constant, Equation (2-7), $V = It/C$, may be applied. For the 10 V ramp:

$$I = \frac{CE_{\max}}{t} = \frac{1 \mu\text{F} \times 10 \text{ V}}{100 \text{ ms}} = 0.1 \text{ mA}$$

and

$$e_R = I \times R = 0.1 \text{ mA} \times 1 \text{ k}\Omega = 0.1 \text{ V}$$

For the 20 V ramp:

$$I = \frac{CE_{\max}}{t} = \frac{1 \mu\text{F} \times 20 \text{ V}}{100 \text{ ms}} = 0.2 \text{ mA}$$

and

$$e_R = I \times R = 0.2 \text{ mA} \times 1 \text{ k}\Omega = 0.2 \text{ V}$$

In Example 2-8, the rate of change of the 10 V ramp is 10 V/100 ms, that is, 0.1 V/ms. For the 20 V ramp, the rate of change is 0.2 V/ms. Thus as shown in the example, the differential output doubles when the rate of change of input voltage is doubled.

From Example 2-8 an equation for the output from a differentiating circuit is

$$e_R = CR \times \frac{E_{\max}}{t} \quad (2-14)$$

That is, $e_R = CR \times (\text{rate of change of input})$. This equation may be applied in the case of pulse waveforms with known rise and fall times, as illustrated in Figure 2-10.

EXAMPLE 2-9

Calculate the amplitude of the differentiated output waveform for the circuit and input pulse shown in Figure 2-10.

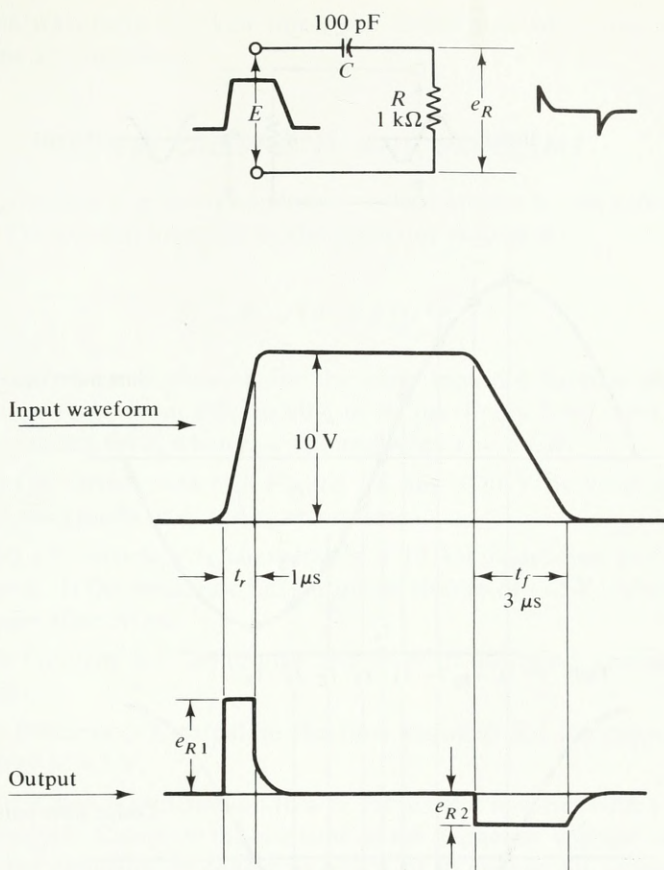


FIGURE 2-10. Differentiation of pulse wave.

solution

$$e_R = CR \times (\text{slope})$$

$$e_{R1} = CR \times \frac{E_{\max}}{t_r} = 100 \text{ pF} \times 1 \text{ k}\Omega \times 10 \text{ V}/\mu\text{s}$$

$$= 1 \text{ V}$$

$$e_{R2} = CR \times \frac{E_{\max}}{t_f} = 100 \text{ pF} \times 1 \text{ k}\Omega \times 10 \text{ V}/3 \mu\text{s}$$

$$= 0.3 \text{ V}$$

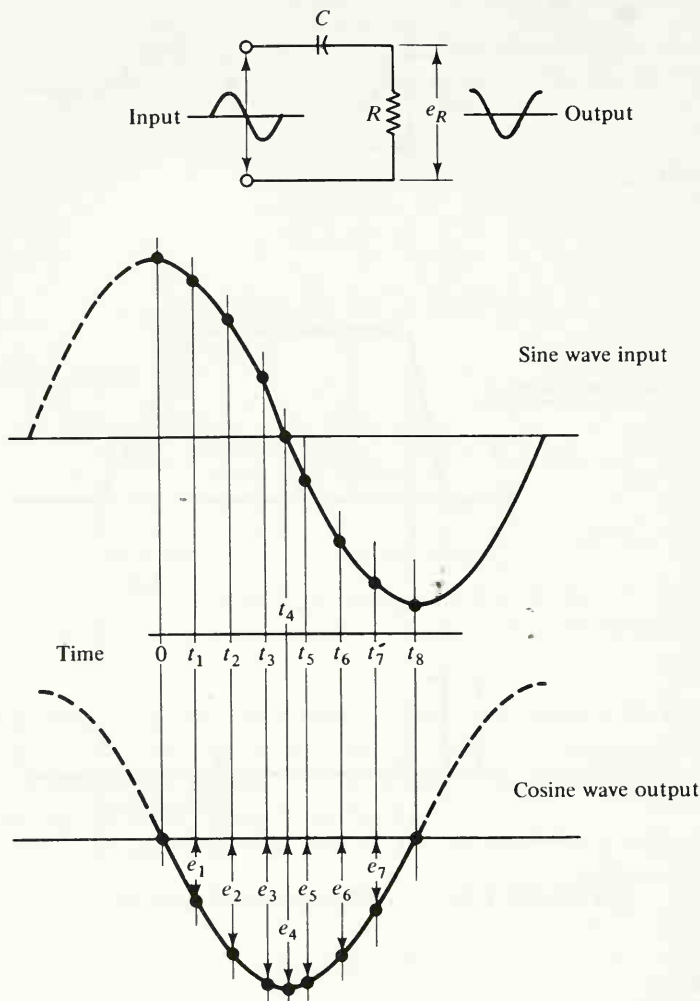


FIGURE 2-11. Differentiation of a sine wave.

The process by which a sine wave is differentiated is illustrated in Figure 2-11. At the peak of the sine wave ($t = 0$), the rate of change of the voltage is zero. Thus the differentiated output voltage is zero. At time t_1 the sine wave amplitude decreases, producing a negative rate of change. Consequently, the differentiated output voltage is $-e_1$. At t_2 and t_3 the negative rate of change increases and becomes maximum at t_4 . The differentiated output, therefore, increases negatively through $-e_2$ and $-e_3$ to $-e_4$. Beyond t_4 , the negative rate of change decreases to zero at t_8 . Ex-

tending the waveform (broken lines) the differential of a sine wave is shown to be a cosine wave.

REVIEW QUESTIONS AND PROBLEMS

- 2-1** A capacitor C is charged from a voltage source E , via a resistance R . The general formula for the capacitor voltage is

$$e_c = E - (E - E_o)e^{\frac{-t}{CR}}$$

- (a) Derive an expression for the time required for the capacitor voltage to go from 10% to 90% of its maximum level. (b) Derive expressions for e_c when $t = CR$ and when $t = 5 CR$.
- 2-2** The CR circuit shown in Figure 2-6 has a 20 V dc voltage input. Plot the graphs of e_c and e_R versus time.
- 2-3** A 10 μF capacitor is charged via a 10 k Ω resistance from a 5V source. If the capacitor has an initial charge of -2 V, calculate its charge after 50 ms.
- 2-4** For Problem 2-3, determine the level of charging current after 35 ms.
- 2-5** For Problem 2-3, calculate the time required for the capacitor to charge to 4.5 V.
- 2-6** A 10 V step is switched on to a 22 k Ω resistor in series with a 300 pF capacitor. Calculate the rise time of the capacitor voltage, the time for the capacitor to charge to 63.2% of its maximum voltage, and the time for the capacitor to become completely charged.
- 2-7** If the square wave input to the circuit shown in Figure 2-4 (a) has a frequency of 250 Hz, and an amplitude of 15 V, determine the capacitor voltage at $t = 7$ ms.
- 2-8** For Problem 2-7, determine the maximum and minimum levels of capacitor voltage when the waveform has settled. Sketch the waveform of e_c to show its relationship to the input square wave.
- 2-9** For Problem 2-7, determine the maximum and minimum levels of charging current when the waveform has settled. Sketch the waveform of i_c to show its relationship to the e_c waveform.
- 2-10** For the circuit and input shown in Figure 2-12; (a) determine the level of e_c and i_c at $t = 2.5$ ms. (b) Sketch the settled waveform of e_c .
- 2-11** Sketch an integrating circuit with a square wave input. Show the

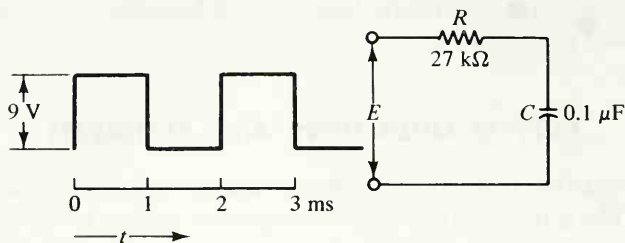


FIGURE 2-12. Circuit and input for Problem 2-10.

output waveforms for (a) $CR \simeq 10 \times PW$, (b) $CR \simeq \frac{1}{10} PW$, (c) $CR \simeq PW$.

- 2-12** Explain why the output of an integrating circuit represents the integration of the input waveform.
- 2-13** Sketch the shape of the output waveform from an integrator when the input is a cosine wave.
- 2-14** A pulse having an amplitude of 5 V and a PW of $100 \mu s$ is applied to the CR circuit shown in Figure 2-12. Determine the amplitude of e_c at the end of the pulse. If the input PW goes to $150 \mu s$ and the amplitude goes to 7.5 V, calculate the new level of e_c at the end of the pulse time.
- 2-15** Sketch a differentiating circuit with a square wave input. Show the waveforms for (a) $CR \simeq \frac{1}{10} PW$, (b) $CR \simeq 10 \times PW$, (c) $CR \simeq PW$.
- 2-16** Explain why the output of a differentiating circuit represents the differential of the input waveform.
- 2-17** Sketch the shape of the output waveform from a differentiator when the input is a cosine wave.
- 2-18** A 100 Hz triangular wave with a peak-to-peak amplitude of 9 V is applied to a differentiating circuit. $R = 1 M\Omega$ and $C = 100 pF$. Calculate the output amplitude and sketch the waveform of the output.
- 2-19** A pulse with a rise time of $t_r = 500 ns$, a fall time of $t_f = 1 \mu s$, $PA = 12 V$, and $PW = 10 \mu s$ is applied to a differentiating circuit with $C = 200 pF$ and $R = 470 \Omega$. Determine the amplitude of the differentiated outputs, and sketch the output waveform.

Chapter 3

Diode Switching

INTRODUCTION

Because it passes a large current when forward-biased and an extremely small current when reverse-biased, a semiconductor diode can be employed as a switch. The speed with which a diode can be switched is determined by the **REVERSE RECOVERY TIME** of the device. Diodes are widely applied to **CLIP** unwanted portions from a waveform, or to **CLAMP** the peak of a waveform to a desired dc level. Zener diodes may be used as reference voltage sources in clipping and clamping circuits.

3-1 THE DIODE AS A SWITCH

Typical characteristics for a low-current silicon diode are shown in Figure 3-1. It is seen that when the *forward bias voltage* V_F exceeds approxi-

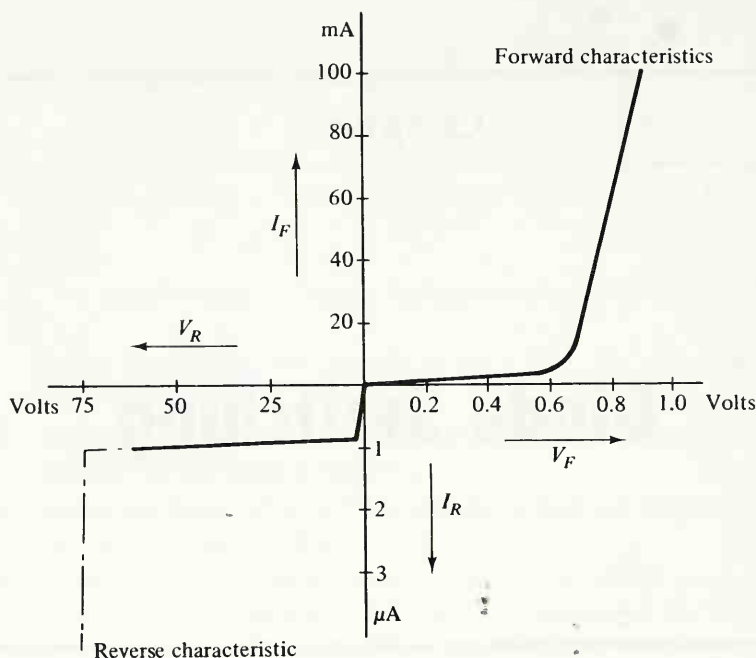



FIGURE 3-1. Forward and reverse characteristics for a typical low current silicon diode.

mately 0.7 V the forward current I_F is approximately 20 mA. Above the 20 mA level, I_F increases substantially with very small increases in V_F . The reverse characteristics show an approximately constant reverse saturation current I_S of 1 μA for reverse voltages ranging up to reverse breakdown at 75 V. (Some diodes can survive reverse biases much greater than 75 V.) Since the typical reverse current is on the order of 1/20,000 of the forward current, the reverse current can be neglected for many purposes. The diode is then thought of as a *one-way device*. It simulates a switch, which is closed when the device is forward-biased and open when it is reverse-biased.


A switch is characterized by zero voltage drop when closed and zero current when open. This is true, as well, of an ideal diode. Figure 3-2(a) illustrates these characteristics of a switch, and Figures 3-2(b) and (c) show similar approximate diode characteristics. The silicon device has a typical forward voltage drop of 0.7 V, while V_F for the germanium diode is approximately 0.3 V. For both silicon and germanium, the reverse current is normally very small.

In a great many applications, diode characteristics can be ignored.

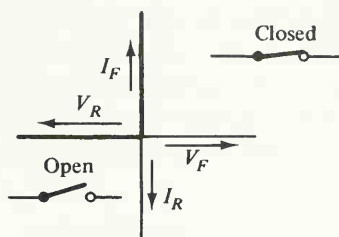(a) Switch and ideal diode characteristic



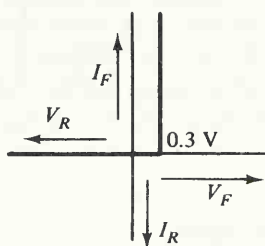(b) Approximate characteristics for a germanium diode



(c) Approximate characteristics for a silicon diode

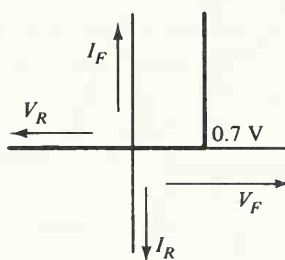


FIGURE 3-2. Switch characteristics and approximate diode characteristics.

The device is assumed to have a constant forward voltage drop V_F when forward-biased and a constant (temperature dependent) *reverse leakage current* I_S when reverse-biased. To select a diode for a particular application, it is necessary to determine the forward current that must be passed, the power dissipation, the reverse voltage, and the maximum leakage current that can be tolerated. Another item that must be considered is the required operating frequency of the diode.

The effect of a sudden change of a diode from forward bias to reverse bias is illustrated in Figure 3-3(a). Instead of switching *off* sharply

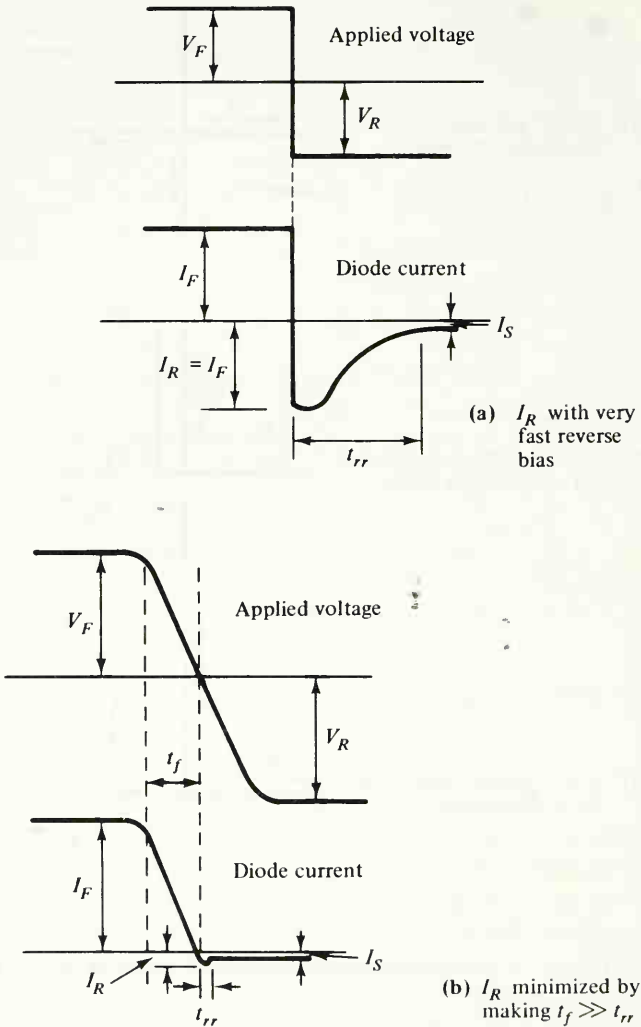


FIGURE 3-3. Effect of diode reverse recovery time.

when the input becomes negative, the diode initially conducts in reverse. The reverse current I_R is at first equal to I_F ; then it gradually falls off to the reverse saturation level I_S . At the instant of reverse bias there are charge carriers crossing the junction depletion region, and these must be removed. This removal of charge carriers constitutes the reverse current I_R . The *reverse recovery time* t_{rr} is the time required for the reverse current to go to I_S . Typical values of t_{rr} range from 4 ns to 50 ns.

If the diode forward current is reduced to a very small value before

the device is reverse-biased, then the reverse current will also be very small. Even when a large forward current is flowing, the reverse current can be kept small if the forward current is reduced slowly. This means that for minimum reverse current, the fall time of forward current should be much longer than the diode reverse recovery time [see Figure 3-3(b)].

3-2 THE ZENER DIODE

The symbol for and characteristics of a *Zener diode* are shown in Figure 3-4. This device is a semiconductor diode designed to operate in the *reverse breakdown region* of its characteristics. If the reverse current is maintained within certain limits, the voltage drop across the diode is maintained at a reliable constant level. Thus the Zener diode (also known as an *avalanche diode* or *breakdown diode*) is useful as a voltage reference source.

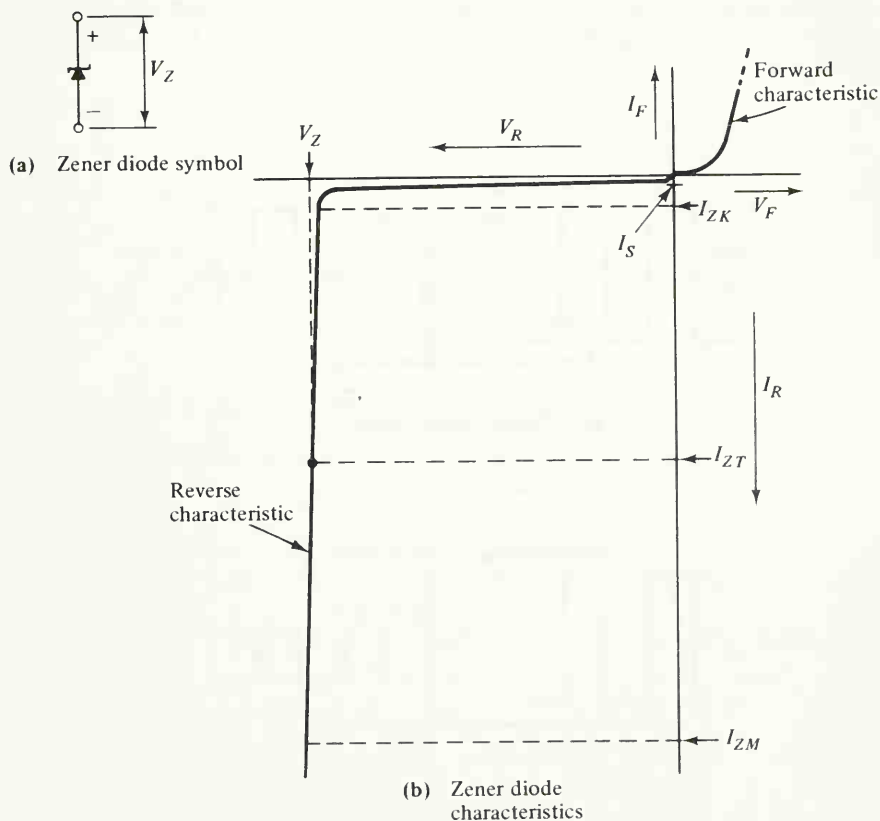


FIGURE 3-4. Zener diode characteristic.

From Figure 3-4(b), V_Z is the Zener voltage measured at test current I_{ZT} . The knee current, I_{ZK} , is the minimum current that should pass through the device to maintain a constant V_Z . The maximum Zener current that may be passed for the device not to exceed maximum permissible power dissipation is designated as I_{ZM} .

For correct operation a Zener diode must be positively biased on the cathode and negatively biased on the anode; that is, it must be reverse-biased. When the reverse voltage is smaller than V_Z only the normal diode reverse saturation current I_S flows. When the Zener diode is forward-biased it behaves as an ordinary diode. Thus a large forward current flows, and the diode voltage is typically $V_F = 0.7\text{ V}$.

3-3 DIODE CLIPPER CIRCUITS

3-3.1 Series Clipper

A clipper (or limiter) circuit is one that clips off a portion of an input waveform. Two clipping circuits are shown in Figure 3-5. In the *nega-*

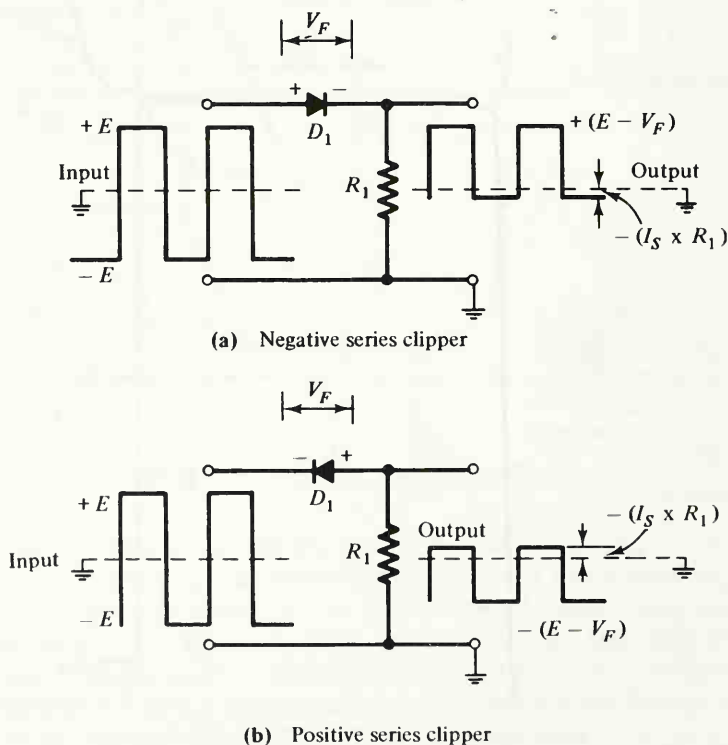


FIGURE 3-5. Negative and positive series clipping circuits.

tive series clipper, the diode is forward-biased when the input becomes positive. Thus, the output voltage at this time is the peak input voltage minus the diode voltage drop. When the input becomes negative, the diode is reverse-biased and the reverse saturation current I_S flows through resistor R_1 . The output then is a very small negative voltage $-(I_S \times R_1)$. The resultant output waveform from the circuit is essentially the input, with the negative portion clipped off.

The *positive series clipper* operates in the same way as the *negative clipper* except that, in this case, the diode is turned around, and the positive portion of the input waveform is clipped off.

EXAMPLE 3-1

The negative series clipping circuit in Figure 3-5(a) is to have an input of $E = \pm 50 \text{ V}$. The output current from the circuit is to be $I_L = 20 \text{ mA}$, and the negative output voltage $-V_o$ is not to exceed 0.5 V . Calculate the value of R_1 . Specify the diode in terms of forward current, power dissipation, and peak reverse voltage.

solution

For a negative input:

$$\begin{aligned} I_S &= 5 \mu\text{A} \text{ (typical)} \\ -V_o &= I_S \times R_1 \\ R_1 &= \frac{V_o}{I_S} = \frac{0.5 \text{ V}}{5 \mu\text{A}} = 100 \text{ k}\Omega \end{aligned}$$

Use a $100 \text{ k}\Omega$ standard value (see Appendix 2).

Diode peak reverse voltage:

$$-E = -50 \text{ V}$$

For a positive input:

$$\begin{aligned} I_{R1} &= \frac{E}{R_1} \\ &= \frac{50 \text{ V}}{100 \text{ k}\Omega} \\ &\simeq 0.5 \text{ mA} \end{aligned}$$

Power dissipation in R_1 :

$$\begin{aligned}
 P_{R1} &= \frac{E^2}{R} = \frac{(50 \text{ V})^2}{100 \text{ k}\Omega} \\
 &= 25 \text{ mW}
 \end{aligned}$$

Diode forward current:

$$\begin{aligned}
 I_F &= I_L + I_{R1} \\
 &= 20 \text{ mA} + 0.5 \text{ mA} \\
 &= 20.5 \text{ mA}
 \end{aligned}$$

Diode power dissipation:

$$\begin{aligned}
 P_{D1} &= V_F \times I_F \\
 &= 0.7 \text{ V} \times 20.5 \text{ mA} \quad (\text{for a silicon diode}) \\
 &= 14.35 \text{ mW}
 \end{aligned}$$

EXAMPLE 3-2

From the diode data sheets in Appendix 1 select a suitable device for the circuit designed in Example 3-1.

solution

From Example 3-1:

Reverse saturation current $I_S = 5 \mu\text{A}$

Peak reverse voltage $E = 50 \text{ V}$


Forward current $I_F = 20.5 \text{ mA}$

Therefore, the diode selected must have a reverse current I_R *not greater than* $5 \mu\text{A}$, a maximum reverse voltage V_R *not less than* 50 V , and a maximum forward current *not less than* 20.5 mA . The 1N914, 1N915, and 1N916 diodes fulfill all of the required conditions. The 1N917 can take a maximum reverse voltage of only 30 V ; therefore it is not suitable.

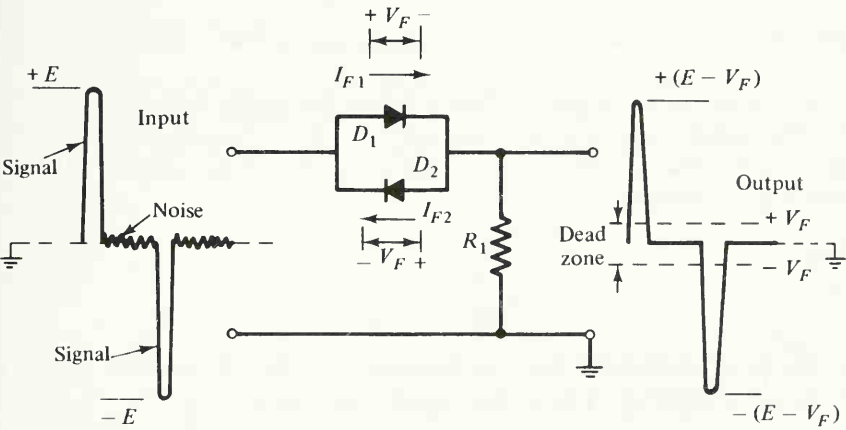
3-3.2 Series Noise Clipper

Frequently a signal has unwanted voltage fluctuation (called *noise*) which can trigger sensitive circuits. To eliminate noise, a *series noise clipping*

circuit may be employed. If the noise is considerably smaller than the normal forward voltage drop of a diode and the signal voltages are larger than V_F , then the diode noise clipper shown in Figure 3-6(a) may be employed. Since the peaks of noise voltage are not large enough to forward bias either D_1 or D_2 , the output during the time between signals is zero. The wanted signals readily forward bias the diodes, and the output peak voltage is $(E - V_F)$. A dead zone of $\pm V_F$ exists around ground level at the output. This simply indicates that for signals to be passed to the output, they must exceed $\pm V_F$.



(a) Diode noise clipper

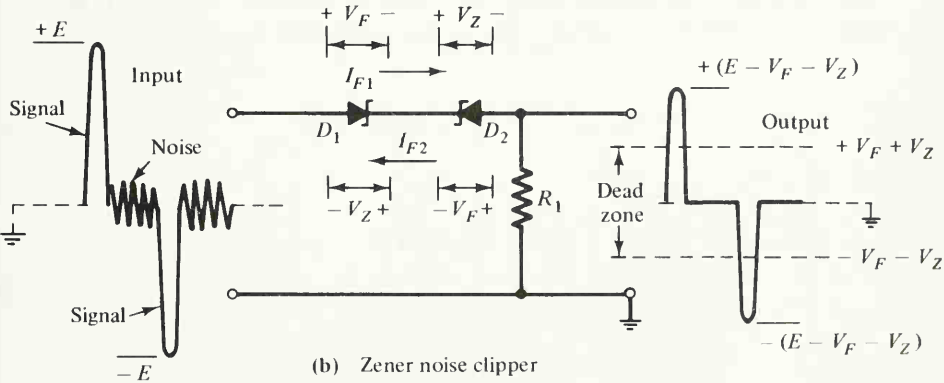

(b) Zener noise clipper

FIGURE 3-6. Series noise clipping circuits.

When noise is too large for ordinary diodes, Zener diodes can be used, as shown in Figure 3-6(b). In this case, when the signal input goes positive, D_1 behaves as an ordinary forward-biased diode, while D_2 goes into breakdown. Similarly, when the signal is negative, D_2 is forward-biased and D_1 is in breakdown. The *dead zone* is now $\pm(V_F + V_Z)$, and only signals greater than this will be passed to the output. That is, the signals must be large enough to drive one diode into breakdown and to forward bias the other diode. The voltage drop across the two diodes is subtracted from the input signal, so the output peak is $(E - V_F - V_Z)$.

EXAMPLE 3-3

The Zener diode noise clipper in Figure 3-6(b) has input signals of $E = \pm 6\text{ V}$. The input noise has an amplitude of $\pm 2\text{ V}$. Specify the Zener diodes required and calculate the resistance of R_1 . Also calculate the amplitude of the output signals.

solution

$$V_Z > 2\text{ V}$$

From the Zener diode data sheet in Appendix 1-3, the IN746 with $V_Z = 3.3\text{ V}$ is a suitable device. The output signal amplitude is

$$\begin{aligned} V_o &= \pm(E - V_F - V_Z) \\ &= \pm(6\text{ V} - 0.7\text{ V} - 3.3\text{ V}) \\ &= \pm 2\text{ V} \end{aligned}$$

In the absence of a load current, R_1 must pass enough current to keep the diode conducting when the signal is present. From the data sheet, $I_{ZT} = 20\text{ mA}$. To ensure that I_{R1} is greater than I_{ZK} , make

$$I_{R1} \simeq \frac{1}{4}I_{ZT} = 5\text{ mA}$$

and

$$\begin{aligned} V_{R1} &= V_o = \pm 2\text{ V} \\ R_1 &= \frac{V_{R1}}{I_{R1}} = \frac{2\text{ V}}{5\text{ mA}} \\ &= 400\ \Omega \end{aligned}$$

Use a standard value resistor ($R_1 = 390\ \Omega$). See Appendix 2.

Power dissipation in R_1 is

$$\begin{aligned} P_{R1} &= \frac{V_o^2}{R_1} \\ &= \frac{(2\text{ V})^2}{390\ \Omega} \\ &= 10.3\text{ mW} \end{aligned}$$

3-3.3 Shunt Clipper

Negative and positive shunt clipping circuits are shown in Figure 3-7. In each case the clipping circuit is applied to protect the base-emitter junction of a transistor from excessive reverse bias. Most transistors will not

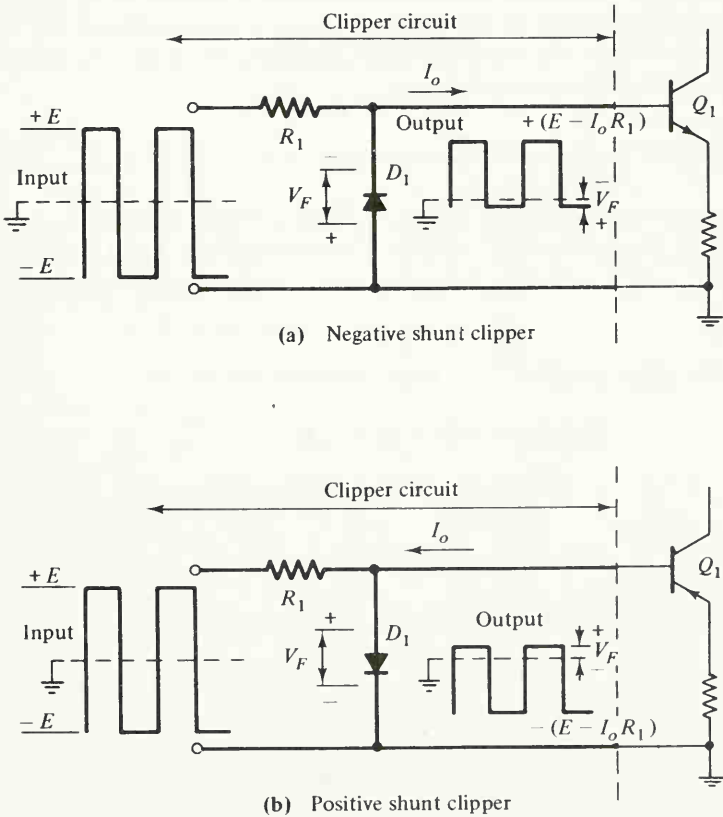


FIGURE 3-7. Negative and positive shunt clipping circuits.

survive more than 5 V applied in reverse across the base-emitter junction. Consequently, when input signals are greater than 5 V, some sort of protective circuitry is needed.

In the circuit of Figure 3-7(a), the negative portion of the input signal is clipped off to protect the *npn* transistor. When the signal becomes positive, D_1 is reverse-biased and all of the current I_o flows through the transistor base. The voltage at the transistor base, *i.e.*, the clipper output, is

$$(\text{Input voltage}) - (\text{Voltage drop across } R_1) = E - I_o R_1$$

When the input becomes negative, the transistor base-emitter junction is reverse-biased, and the diode is forward-biased. Since the diode is in parallel with the transistor input, the maximum reverse base-emitter voltage is limited to the diode forward voltage drop V_F .

Diode D_1 in Figure 3-7(b) is forward-biased when the input is positive. Thus, the transistor base-emitter voltage is limited to V_F , positive on the base and negative on the emitter, which is reverse-biased for the *pnp* transistor. When the input becomes negative, D_1 is reverse-biased and I_o flows through the transistor base.

EXAMPLE 3-4

The negative shunt clipper circuit in Figure 3-7(a) is to have an output voltage of 9 V, and output current of approximately 1 mA. If the input voltage is ± 10 V, calculate the value of R_1 and the diode forward current.

solution

When the input is +10 V:

$$\begin{aligned}\text{Output} &= 9 \text{ V} = E - I_o R_1 \\ I_o R_1 &= E - 9 \text{ V} = 10 \text{ V} - 9 \text{ V} = 1 \text{ V} \\ R_1 &= \frac{1 \text{ V}}{I_o} = \frac{1 \text{ V}}{1 \text{ mA}} = 1 \text{ k}\Omega\end{aligned}$$

When the input is -10 V, D_1 is forward-biased and

$$\begin{aligned}V_F &\simeq 0.7 \text{ V} \\ V_F &= E - I_F R_1 \\ I_F &= \frac{E - V_F}{R_1} = \frac{10 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} \\ &= 9.3 \text{ mA}\end{aligned}$$

3-3.4 Biased Shunt Clipper

All the shunt clipping circuits discussed clip off either the positive or the negative portion of an input waveform. The unwanted output is limited to a maximum of V_F above or below ground. In the circuit of Figure 3-8(a), diode D_1 has its cathode connected to a bias of 2 V. In this case the diode will not be forward-biased while the output of the clipping circuit is below 2 V. The presence of D_1 then limits the positive output to a maximum of $(2\text{ V} + V_F)$. Similarly, D_2 will be reverse-biased until the output is more negative than -2 V . This limits the negative output to a maximum of $-(2\text{ V} + V_F)$.

The biased shunt clipper normally is used to protect a device or cir-

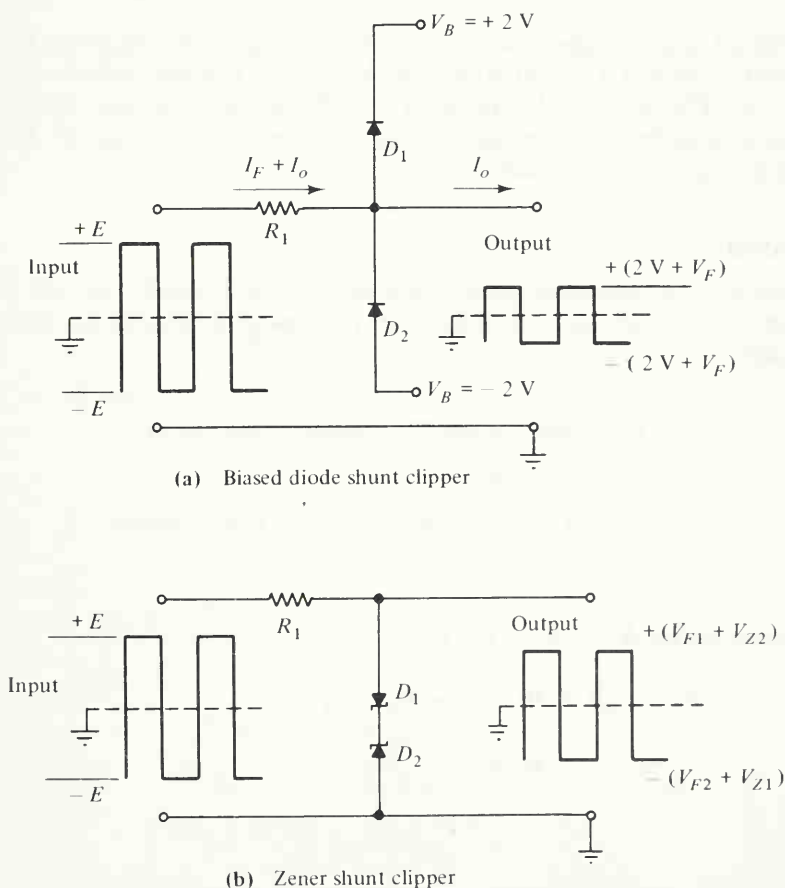


FIGURE 3-8. Biased diode shunt clipper circuit and Zener shunt clipper circuit.

cuit which has both positive and negative input signals. The bias voltage is selected to prevent the input (either positive or negative) from exceeding a maximum safe level.

The Zener clipper shown in Figure 3-8(b) performs a function similar to that of the circuit of Figure 3-8(a). In this case, however, no separate bias voltage supplies are necessary. When the input signal becomes positive, D_1 operates like an ordinary forward-biased diode while D_2 goes into Zener breakdown. The output voltage at this time is $(V_{F1} + V_{Z2})$. When the input is negative, D_1 is in Zener breakdown and D_2 is forward-biased. The output voltage now is $-(V_{F2} + V_{Z1})$.

EXAMPLE 3-5

A biased shunt clipper circuit [as shown in Figure 3-8(a)] is to be designed to protect a circuit which cannot accept voltages exceeding $V_o = \pm 2.7$ V. The input to the clipper is a ± 8 V square wave, and the output current is to be a maximum of 1 mA. Calculate the value of R_1 and specify the diodes to be used.

solution

To ensure that the diodes become properly forward-biased, take the minimum forward current I_F as 10 mA (see the typical diode characteristics in Figure 3-1).

$$V_o = \text{bias voltage } V_B + \text{diode voltage drop } V_F$$

$$V_B = V_o - V_F$$

$$= 2.7 \text{ V} - 0.7 \text{ V} \quad (\text{using a silicon diode})$$

$$= 2 \text{ V}$$

$$\text{Voltage across } R_1 = (I_F + I_o) \times R_1$$

$$(I_F + I_o) \times R_1 = E - V_B - V_F$$

$$R_1 = \frac{E - V_B - V_F}{I_F + I_o}$$

$$= \frac{8 \text{ V} - 2 \text{ V} - 0.7 \text{ V}}{10 \text{ mA} + 1 \text{ mA}}$$

$$= 482 \, \Omega \quad [\text{use } 470 \, \Omega \text{ standard value resistor (see Appendix 2)}]$$

The diodes selected should be low current devices with $V_F \simeq 0.7 \text{ V}$ at $I_F = 10 \text{ mA}$, and should have a peak reverse voltage greater than 10 V .

EXAMPLE 3-6

Design a Zener diode shunt clipper circuit [as shown in Figure 3-8(b)] to be connected between a $\pm 25 \text{ V}$ square wave signal and a circuit which cannot accept inputs greater than $\pm 11 \text{ V}$. The output current is to be a maximum of 1 mA .

solution

Clipper circuit output is $V_O = \pm 11 \text{ V}$

$$\begin{aligned} V_O &= V_F + V_Z \\ V_Z &= V_O - V_F \\ &= 11 \text{ V} - 0.7 \text{ V} = 10.3 \text{ V} \end{aligned}$$

Refer to the breakdown diode data sheet in Appendix 1-3;

$$V_Z = 10 \text{ V for the 1N758 device}$$

Use 1N758 breakdown diodes.

$$\begin{aligned} V_{R1} &= E - V_O \\ &= E - (V_F + V_Z) \\ &= 25 \text{ V} - 10 \text{ V} - 0.7 \text{ V} = 14.3 \text{ V} \end{aligned}$$

To ensure that $I_Z > I_{ZK}$ make

$$\begin{aligned} I_Z &\simeq \frac{1}{4} I_{ZT} \\ &= \frac{1}{4} \times 20 \text{ mA} = 5 \text{ mA} \\ I_{R1} &= I_Z + I_O \\ &= 5 \text{ mA} + 1 \text{ mA} = 6 \text{ mA} \end{aligned}$$

$$R_1 = \frac{V_{R1}}{I_{R1}} = \frac{14.3 \text{ V}}{6 \text{ mA}} = 2.38 \text{ k}\Omega \quad [\text{use a } 2.2 \text{ k}\Omega \text{ standard value resistor (see Appendix 2)}]$$

3-4 DIODE CLAMPER CIRCUITS

3-4.1 Negative and Positive Clamping Circuits

The *clamper circuit* (also known as a *dc restorer circuit*) changes the dc level but does not affect the shape of a waveform. When the input is positive, in the *negative voltage clamper* circuit of Figure 3-9(a), diode D_1 is forward-biased, and capacitor C_1 charges with the polarity shown. During the positive input peak, the output cannot exceed the diode forward bias voltage V_F . At this time, therefore, the voltage on the right-hand side (RHS) of the capacitor is $+V_F$, while on the left-hand side (LHS) of the capacitor the voltage is $+E$. Thus, the capacitor is charged to $E - V_F$, positive on the LHS, negative on the RHS, as shown.

When the input becomes negative the diode is reverse-biased and it has no further effect on the capacitor voltage. Also, resistor R_1 has a very large value and cannot discharge the capacitor significantly during the

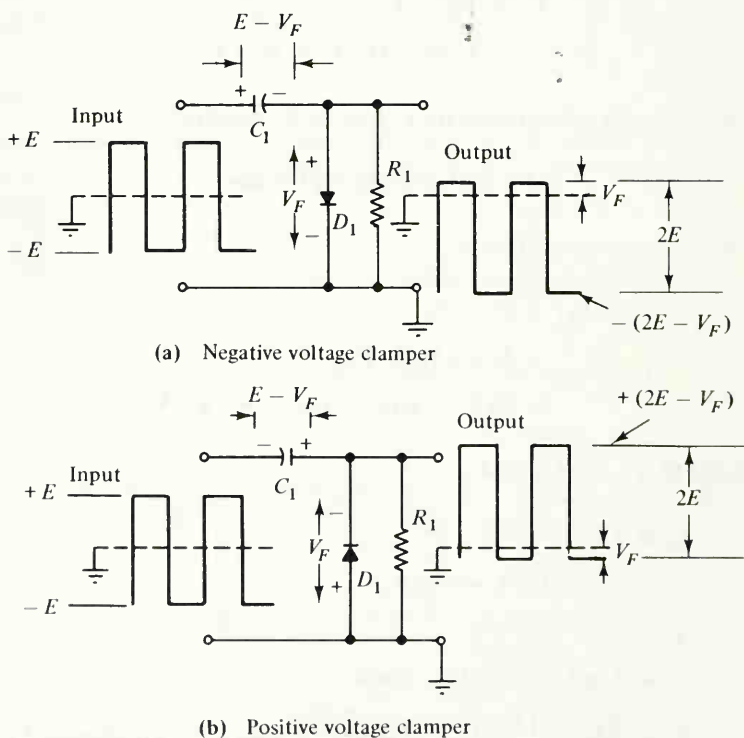


FIGURE 3-9. Negative and positive clamping circuits.

negative (or positive) portion of the waveform. While the input is negative, the output voltage is the sum of the input voltage and the capacitor voltage. Since the polarity of the capacitor voltage is the same as the (negative) input, the result is a negative output larger than the input voltage.

Thus

$$\begin{aligned}\text{Negative output} &= -E - (E - V_F) \\ &= -(2E - V_F)\end{aligned}$$

The peak-to-peak (*p-to-p*) output is the difference between the negative and positive peak voltages.

$$\begin{aligned}\text{p-to-p output} &= (\text{positive peak}) - (\text{negative peak}) \\ &= V_F - [-(2E - V_F)] \\ &= 2E\end{aligned}$$

It is seen that the output waveform from the *negative voltage clamper* is exactly the same as the input waveform. Instead of being symmetrical above and below ground, however, the output positive peak is clamped to a level of V_F above ground. The difference between *clipping* and *clamping* circuits, is that while the clipper *clips off* an unwanted portion of the input waveform, the clamper simply *clamps* the maximum positive or negative peak to a desired dc level.

The function of R_1 is to discharge C_1 over several cycles of the input waveform. This would not be necessary if the input signal never changed. However if the input is made smaller, C_1 must be partially discharged for the positive output peak to rise to V_F once again.

The *positive voltage clamping circuit* [Figure 3-9(b)] functions in exactly the same way as the negative voltage clamper. The diode, connected as shown, clamps the negative output peak at $-V_F$. Capacitor C_1 charges to $E - V_F$ positive on the RHS, negative on the LHS. The positive output then becomes $2E - V_F$.

To design a clamping circuit, C_1 should be selected so that it becomes completely charged during about five cycles of the input waveform. Since a capacitor takes approximately five time constants to become fully charged,

$$5CR = 5 \times PW,$$

where PW is the width of the pulse which forward-biases the diode.

$$CR = PW$$


In this case, R is the total resistance in series with the capacitor when it is being charged. This is the sum of the source resistance R_S and the diode forward resistance R_F [see Figure 3-10 (a)].

$$C(R_S + R_F) = PW$$


Since usually $R_S \gg R_F$,

$$CR_S = PW \quad (3-1)$$

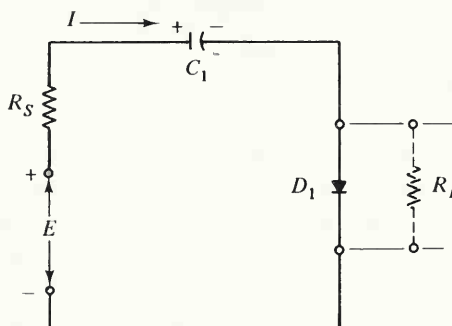When the capacitor partially discharges during the negative input



(a) Charge of C_1 via R_S and R_F

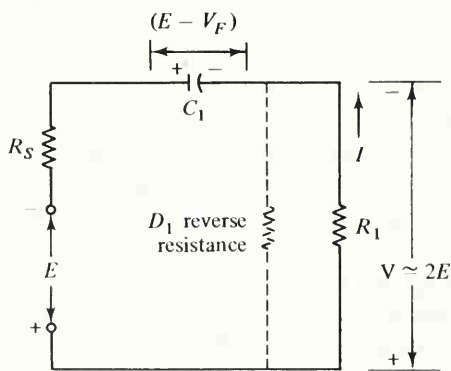

(b) Discharge of C_1

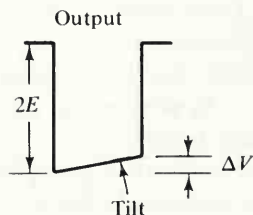


FIGURE 3-10. Capacitor charge and discharge circuits for clamping circuit.

peak (for a *negative* voltage clamper), some tilt will appear on the output, as shown in Figure 3-10 (b). The acceptable amount of tilt determines the value of the discharge resistor R_1 . The voltage across R_1 during this time is approximately $2E$. Therefore, the discharge current is

$$I \simeq \frac{2E}{R_1}$$

The diode reverse resistance is also involved but, since it is in parallel with R_1 and is very much larger than R_1 , it may be neglected. The current I remains approximately constant during the discharge time so Equation (2-7), $V = It/C$, may be applied. In this case, a change in capacitor voltage ΔV is involved. Replacing I with $(2E)/R_1$ in the equation gives:

$$\Delta V = \frac{2E}{R_1} \times \frac{t}{C}$$

or

$$R_1 = \frac{2Et}{\Delta VC} \quad (3-2)$$

EXAMPLE 3-7

A negative voltage clamper has a 1 kHz square wave input with an amplitude of ± 10 V. The signal source resistance R_s is 500 Ω , and the tilt on the output waveform is not to exceed 1%. Design a suitable circuit.

solution

For the input,

$$T = \frac{1}{f} = \frac{1}{1 \text{ kHz}} = 1 \text{ ms}$$

and $PW = \frac{1}{2}T = 500 \mu s$. From Equation (3-1),

$$\begin{aligned} C &= \frac{PW}{R_s} \\ &= \frac{500 \mu s}{500 \Omega} = 1 \mu F \end{aligned}$$

For 1% tilt on the output,

$$\Delta V = 0.01 (2E)$$

From Equation (3-2),

$$\begin{aligned} R_1 &= \frac{2Et}{0.01(2E) \times C} \\ &= \frac{t}{0.01C} \end{aligned}$$

and $t = PW = 500 \mu s$,

$$R_1 = \frac{500 \mu s}{0.01 \times 1 \mu F} = 50 \text{ k}\Omega \quad (\text{use } 47 \text{ k}\Omega \text{ standard value})$$

3-4.2 Biased Clamping Circuits


In the biased clamping circuit shown in Figure 3-11 (a), the cathode of diode D_1 is connected to a 2 V bias level. When the input becomes positive, the output level is clamped to the bias level plus the diode voltage drop, that is, $2 \text{ V} + V_F$. At this time the voltage on the RHS of C_1 is $2 \text{ V} + V_F$, and on the LHS is E . Therefore, C_1 charges to $E - (2 \text{ V} + V_F)$, positive on the LHS and negative on the RHS. When the input goes to $-E$, the output becomes $-E$ plus the capacitor voltage. That is,

$$\begin{aligned} \text{Negative output} &= -[E + (E - 2 \text{ V} - V_F)] \\ &= -(2E - 2 \text{ V} - V_F) \end{aligned}$$


and the peak-to-peak output is equal to (positive peak) - (negative peak), or

$$\begin{aligned} \text{p-to-p output} &= (2 \text{ V} + V_F) - [-(2E - 2 \text{ V} - V_F)] \\ &= 2E \end{aligned}$$

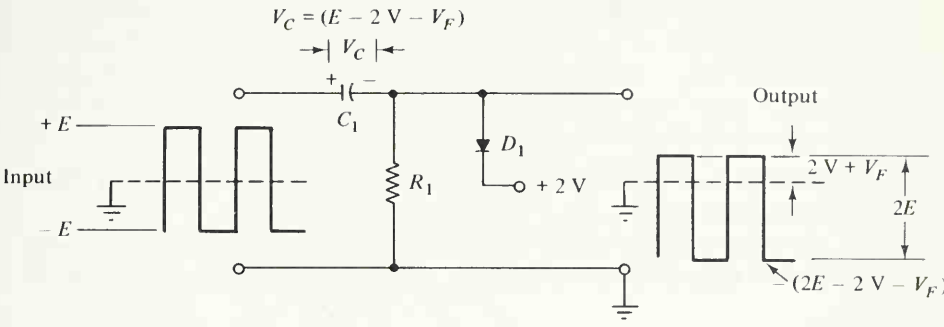It is seen that, although the output is clamped to a maximum dc level of $2 \text{ V} + V_F$, the waveform shape is unchanged. As before, the function of R_1 is to partially discharge C_1 over several cycles of the input. The clamper circuit in Figure 3-11 (b) is similar to that in Figure 3-11 (a) except that the diode is inverted. Since the capacitor charges with a different



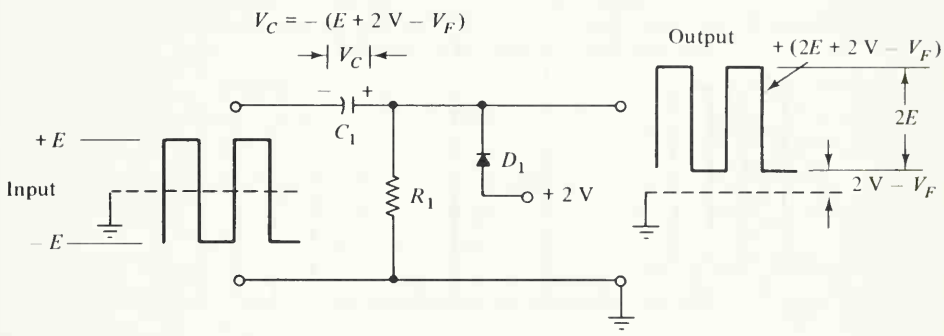(a) Circuit to clamp output at approximately $+2\text{ V}$ maximum



(b) Circuit to clamp output at approximately $+2\text{ V}$ minimum

FIGURE 3-11. Biased clamping circuits.

polarity, C_1 also is inverted from its condition in Figure 3-11 (a). The anode of the diode is always at the bias voltage level, which is 2 V in this case. When the diode is forward-biased, its cathode voltage is $2\text{ V} - V_F$, and the cathode cannot go below this level. Therefore, the lowest level of output voltage is $2\text{ V} - V_F$.

The diode is forward-biased during the time that the input voltage is $-E$. Capacitor C_1 charges, during this time, to $-E$ on the LHS, and to $2\text{ V} - V_F$ on the RHS.

$$\therefore V_C = \text{Capacitor voltage} = (-E) - (2\text{ V} - V_F) \\ = -(E + 2\text{ V} - V_F)$$


This is positive on the RHS and negative on the LHS. When the input becomes $+E$, the capacitor voltage and the input have the same polarities

and add together to give:


$$\begin{aligned}\text{Output} &= E + E + 2V - V_F \\ &= 2E + 2V - V_F\end{aligned}$$

The peak-to-peak value of the output waveform is again $2E$, and its lower level is clamped to $2V - V_F$.

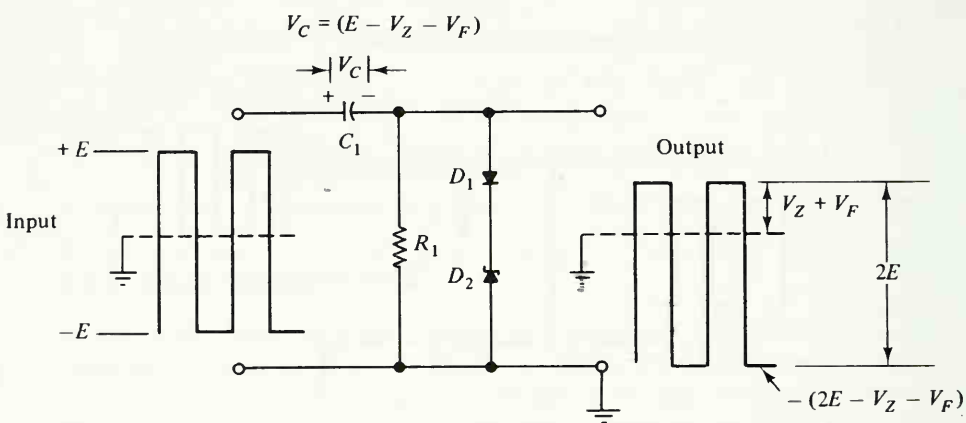The Zener diode clamping circuits in Figure 3-12 perform the same function as biased clamping circuits. In Figure 3-12(a), the Zener diode



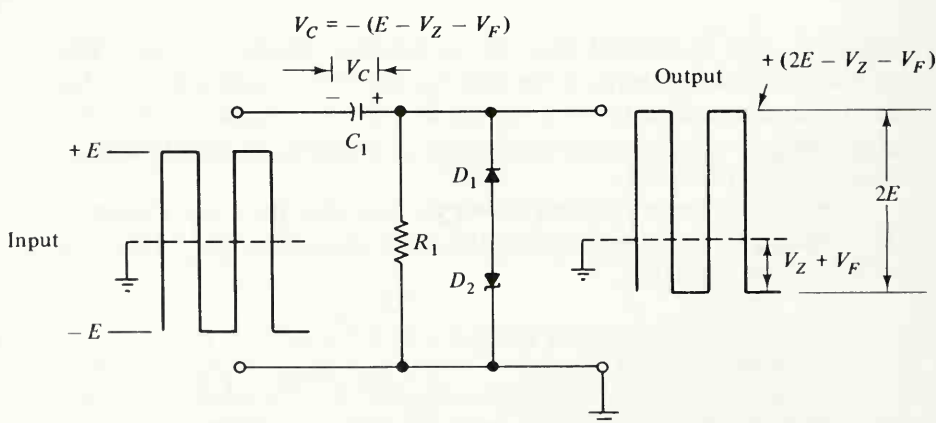(a) Circuit to clamp output at approximately $+V_Z$ maximum



(b) Circuit to clamp output at approximately $-V_Z$ minimum

FIGURE 3-12. Zener diode clamping circuits.

behaves like a bias source with a voltage of V_Z . When it is thought of in this way, its operation is seen to be exactly the same as the biased clamper in Figure 3-11(a). The Zener diode circuit in Figure 3-12(b) clamps the negative output at $-(V_Z + V_F)$. The capacitor charge then causes the positive output to be $2E - V_Z - V_F$. As always, the peak-to-peak output voltage is $2E$.

EXAMPLE 3-8

Design the biased positive voltage clamper circuit shown in Figure 3-11(b). The input waveform is ± 20 V with a frequency of 2 kHz, and the tilt on the output is not to exceed 2%. The signal source resistance is $600\ \Omega$.

solution

For the input waveform, $T = 1/f = 1/2\text{ kHz} = 0.5\text{ ms}$.

$$PW = \frac{1}{2}T = 250\ \mu s$$

From Equation (3-1),

$$C = \frac{PW}{R_s} = \frac{250\ \mu s}{600\ \Omega} \simeq 0.42\ \mu F \quad \text{[use a } 0.5\ \mu F \text{ standard value capacitor (see Appendix 2)]}$$

For 2% tilt, $\Delta V = 0.02 \times 2E$.

From Equation (3-2),

$$\begin{aligned} R_1 &= \frac{2E \times PW}{0.02 \times 2E \times C} \\ &= \frac{2E \times 250\ \mu s}{0.02 \times 2E \times 0.5\ \mu F} \\ &= 25\text{ k}\Omega \quad (\text{use } 22\text{ k}\Omega \text{ standard value}) \end{aligned}$$

The bias voltage should be +2 V as shown in the figure, or any other desired level. The capacitor voltage should be rated at $V_i + V_B$, i.e., for the circuit designed the capacitor selected should survive at least 22 V.

EXAMPLE 3-9

A square wave having an amplitude of ± 15 V and a source resistance R_s of $1\text{ k}\Omega$ is to be clamped to a maximum positive level of approximately 9 V. The square wave frequency ranges from 500 Hz to 5 kHz, and the output tilt is not to exceed 1%. Design a suitable Zener diode clamping circuit.

solution

Maximum tilt occurs when the PW is longest, i.e., when f is a minimum.

$$\text{Maximum } T = \frac{1}{f_{\min}} = \frac{1}{500\text{ Hz}} = 2\text{ ms}$$

$$\text{PW} = \frac{1}{2} T = 1\text{ ms}$$

From Equation (3-1),

$$C = \frac{\text{PW}}{R_s} = \frac{1\text{ ms}}{1\text{ k}\Omega} = 1\text{ }\mu\text{F} \quad [\text{standard value (see Appendix 2)}]$$

For 1% tilt, $V = 0.01 \times 2E$.

From Equation (3-2),

$$\begin{aligned} R_1 &= \frac{2E \times \text{PW}}{0.01 \times 2E \times C} \\ &= \frac{2E \times 1\text{ ms}}{0.01 \times 2E \times 1\text{ }\mu\text{F}} = 100\text{ k}\Omega \quad [\text{standard value (see Appendix 2)}] \end{aligned}$$

$$V_O = V_Z + V_F = 9\text{ V}$$

$$V_Z = V_O - V_F$$

$$= 9\text{ V} - 0.7\text{ V} = 8.3\text{ V}$$

From the regulator diode data sheet (Appendix 1-3), the 1N756 has $V_Z = 8.2$ V; therefore use 1N756 diodes. The capacitor voltage should be at least $V_i + V_Z$, i.e., minimum capacitor voltage is 23.2 V for this circuit.

REVIEW QUESTIONS AND PROBLEMS

- 3-1** Sketch typical characteristics for a low-current silicon diode. Briefly explain why the diode can be thought of as a one-way device.

- 3-2 Sketch ideal diode characteristics, and approximate characteristics for silicon and germanium diodes. Briefly discuss the parameters that should be considered when selecting a diode.
- 3-3 Explain the origin of *reverse recovery time* for a semiconductor diode. By means of sketches, explain why a large reverse current flows when a very fast reverse bias is applied to a diode. Also show how the reverse current can be minimized.
- 3-4 Sketch typical characteristics for a Zener diode. Indicate all important quantities related to the characteristics, and define each quantity.
- 3-5 Sketch the circuit of a positive series clipper, showing the input and output waveforms. Briefly explain its operation.
- 3-6 Repeat Problem 3-5 for a negative series clipper.
- 3-7 A negative series clipping circuit employs a diode with $V_F = 0.3 \text{ V}$ and $I_S = 10 \mu\text{A}$. The input voltage is $\pm 9 \text{ V}$, and the output current is to be a maximum of 10 mA . Calculate the value of the resistance R_1 . Specify the diode in terms of forward current, power dissipation, and peak reverse voltage. The negative output voltage is to be maximum at 0.2 V .
- 3-8 Design a circuit to clip the positive peaks off a $\pm 20 \text{ V}$ square wave. A silicon diode is available with a maximum reverse leakage current of $10 \mu\text{A}$. The positive output voltage is not to exceed 0.5 V . Calculate the amplitude of the negative output peak.
- 3-9 From the diode data sheets in Appendix 1 select a suitable device for the circuit designed in Problem 3-8.
- 3-10 Sketch the circuit of a diode noise clipper, showing typical input and output waveforms. Briefly explain how the circuit operates.
- 3-11 Repeat Problem 3-10 for a Zener diode noise clipper.
- 3-12 A Zener diode noise clipper has an input pulse signal with an amplitude of $\pm 7 \text{ V}$ and with noise amplitude of $\pm 3 \text{ V}$. Design a circuit and select suitable Zener diodes and resistance value. Also calculate the amplitude of the output signal.
- 3-13 A *pnp* transistor which can take a maximum of 5 V in reverse at its base-emitter junction is to be protected from excessive input signal amplitude. Identify the required circuit and sketch the input and output waveforms. Briefly explain the operation of the circuit.
- 3-14 Repeat Problem 3-13 for an *nnp* transistor.
- 3-15 A negative shunt clipper circuit has a square wave input of $\pm 15 \text{ V}$. The output voltage is to be 13 V and -0.7 V , and the output current is to be $250 \mu\text{A}$. Calculate the required resistance value, and the diode forward current.

- 3-16** Sketch the circuit of a biased diode shunt clipper that has an output limited to a maximum of approximately ± 4 V. Explain the operation of the circuit.
- 3-17** The input to the circuit of Problem 3-16 is ± 16 V, and the output current is to be $500 \mu\text{A}$. Determine the required resistance value, allowing the diode forward currents to be 10 mA.
- 3-18** Sketch a Zener diode shunt clipper circuit, and select suitable

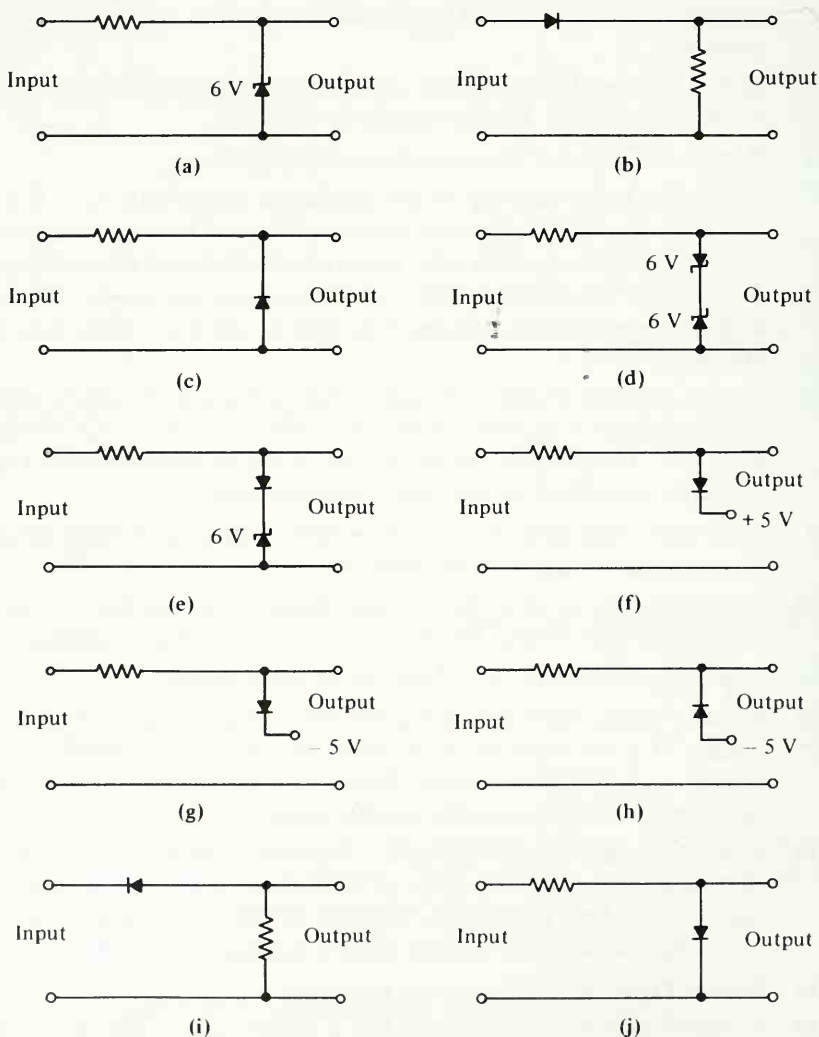


FIGURE 3-13. Circuits for Problem 3-24.

diodes which will clip off input peaks greater than approximately 6 V. Explain the operation of the circuit.

- 3-19** A ± 14 V square wave is applied to the circuit of Problem 3-18. The output current is to be 2 mA maximum. Design a suitable current.
- 3-20** Define the difference between clipping and clamping circuits. A ± 10 V square wave is applied to the input terminals of a negative voltage clamping circuit, and to the input of a negative shunt clipper. Sketch the output waveform that will result in each case.
- 3-21** Sketch a negative voltage clamping circuit, showing input and output waveforms. Briefly explain the operation of the circuit.
- 3-22** Repeat Problem 3-21 for a positive voltage clamper.
- 3-23** A negative voltage clamper has a 5 kHz square wave input with an amplitude of ± 6 V. The signal source resistance is 1 k Ω , and the tilt on the output waveform is not to exceed 1%. Design a suitable circuit.
- 3-24** Sketch the output waveforms you would expect from each of the circuits shown in Figure 3-13. Assume the input to each circuit is a ± 12 V square wave.
- 3-25** Sketch the output waveforms you would expect from each of the circuits shown in Figure 3-14. Assume the input to each circuit is a ± 9 V square wave.
- 3-26** Design a biased clamper circuit to clamp a ± 12 V square wave to a minimum level of +3 V. The input waveform has a frequency which ranges from 1 kHz to 10 kHz, and the signal source resistance is 500 Ω . The tilt on the output is not to exceed 1%.

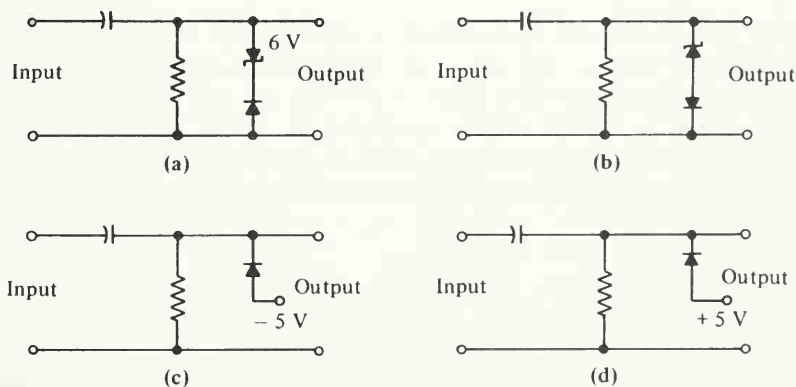


FIGURE 3-14. Circuits for Problem 3-25.

- 3-27** A square wave having an amplitude of $\pm 18\text{ V}$ and a source resistance of 700Ω is to be clamped to a maximum positive level of approximately 10 V . The square wave frequency is 800 Hz , and the output tilt is not to exceed 0.5% . Design a suitable Zener diode clamping circuit.

Chapter 4


Transistor Switching

INTRODUCTION


A bipolar transistor can be made to approximate an ideal switch. When the transistor is off, a small collector-base LEAKAGE CURRENT flows through the load. When it is on, there is a small collector-emitter SATURATION VOLTAGE across the device. A transistor will not switch ON or OFF instantaneously. TURN-ON and TURN-OFF times depend upon the device and the circuit conditions. Field effect transistors have several advantages over bipolar transistor switches.

4-1 IDEAL TRANSISTOR SWITCH


Figure 4-1(a) shows a common emitter transistor circuit arranged to function as a switch. A load resistance R_L is connected from the transistor

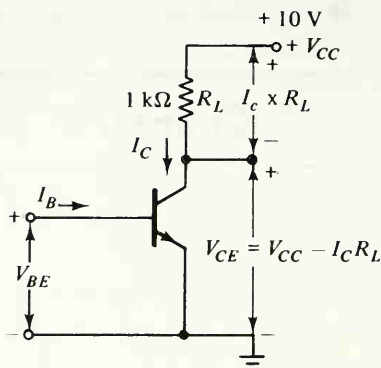

(a) Common emitter circuit

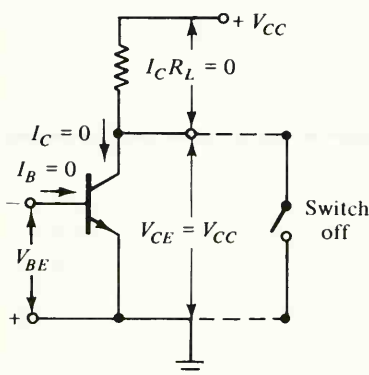

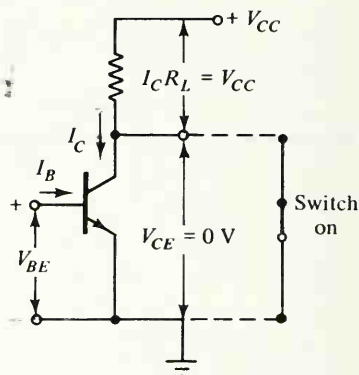(b) Ideal transistor switch in off condition



(c) Ideal transistor switch in on condition

FIGURE 4-1. Ideal transistor switch.

collector to the supply voltage V_{CC} . The emitter terminal of the device is grounded. For the transistor to simulate a switch, the terminals of the switch are the transistor collector and emitter. The input voltage, or controlling voltage, for the transistor switch is the base-emitter voltage V_{BE} . The collector-emitter voltage V_{CE} is equal to the supply voltage minus the voltage drop across R_L :

$$V_{CE} = V_{CC} - I_C R_L \quad (4-1)$$

When the transistor base-emitter voltage is zero, or reverse-biased,

as in Figure 4-1(b), the base current I_B is zero and the collector current I_C is also zero. The transistor switch is now in its *off* condition. Since there is no collector current, there can be no voltage drop across the load resistor. When $I_C = 0$, Equation (4-1) gives:

$$\begin{aligned} V_{CE} &= V_{CC} - (0 \times R_L) \\ &= V_{CC} \end{aligned}$$

Thus, when the ideal transistor is *off*, its collector-emitter voltage equals the supply voltage.

When the transistor base is made positive with respect to the emitter, [Figure 4-1(c)], a base current I_B flows. The collector current I_C is equal to I_B multiplied by the transistor *common emitter dc current gain* h_{FE} , that is, $I_C = h_{FE} \times I_B$. If I_B is made large enough, $I_C \times R_L$ can become equal to the supply voltage V_{CC} . Then by Equation (4-1),

$$\begin{aligned} V_{CE} &= V_{CC} - V_{CC} \\ V_{CE} &= 0 \end{aligned}$$

When the ideal transistor is *on*, its collector-emitter voltage equals zero.

The transistor can also simulate a switch in that, *ideally*, it dissipates zero power both when *on* and *off*. The only time power is dissipated in the device is when it is switching between *on* and *off*. Transistor power dissipation is given by:

$$P_D = I_C \times V_{CE}$$

When *off*,

$$I_C = 0, \quad P_D = 0 \times V_{CE} = 0$$

When *on*,

$$V_{CE} = 0, \quad P_D = I_C \times 0 = 0$$

As described above, the transistor can be operated as a switch which is *off* when V_{BE} is zero or negative, and which is *on* when V_{BE} is positive. Ideally, $V_{CE} = V_{CC}$ when the transistor is *off*, and $V_{CE} = 0$ V when the device is *on*. With a practical transistor these conditions are not achieved; however, they can be approximated.

4-2 PRACTICAL TRANSISTOR SWITCH

To understand how a practical transistor switch differs from the ideal case, it is necessary to consider the common emitter characteristics. In Figure 4-2, the dc load line for the circuit of Figure 4-1(a) is drawn on the transistor common emitter characteristics. Using Equation (4-1), the procedure for drawing the load line is as follows: When $I_C = 0$, $V_{CE} = V_{CC} - 0$. For the circuit shown, $V_{CE} = 10\text{ V}$. Plot point A on the characteristics at $I_C = 0$, and $V_{CE} = 10\text{ V}$. When $V_{CE} = 0$,

$$\begin{aligned} 0 &= V_{CC} - I_C R_L \\ I_C &= \frac{V_{CC}}{R_L} \\ &= \frac{10\text{ V}}{1\text{ k}\Omega} = 10\text{ mA} \end{aligned}$$

[for the circuit of Figure 4-1(a)]

Plot point B on the characteristics at $V_{CE} = 0$, $I_C = 10\text{ mA}$. Draw the dc load line for $R_L = 1\text{ k}\Omega$ by joining points A and B together.

The dc load line defines all corresponding current and voltage conditions that can exist in the circuit. For any given level of I_C , a particular V_{CE} is dictated by Equation (4-1) and is illustrated by the load line. The common emitter characteristics are divided into three regions, as shown in Figure 4-2. The active region of the characteristics usually is employed only in amplifier circuits. Here a linear change in base current produces a nearly linear collector-emitter voltage change. When the collector current is so large that V_{CE} is less than approximately 0.7 V , the device is said to be operating in the *saturation region* of the characteristics. The *cutoff region* exists below the level of $I_B = 0$.

Again, with reference to the load line, it is seen that when $I_B = 0$, I_C is not zero. Instead, a small current I_{CO} flows. This is the collector-base *reverse saturation current*, or *collector cutoff current*, sometimes designated I_{CBO} . This current is the sum of the minority charge carriers which are crossing the reverse-biased collector-base junction, and leaking along the junction surface. I_{CO} is a very temperature sensitive quantity. Typical values are on the order of $1\text{ }\mu\text{A}$ for silicon transistors. For the most recent transistors, I_{CO} at 25°C can be in the nA range. Refer to the data sheet for 2N3903 and 2N3904 transistors in Appendix 1. The collector cutoff current is designated by I_{CEX} . This is the collector-base leakage current measured under particular conditions specified by the manufac-

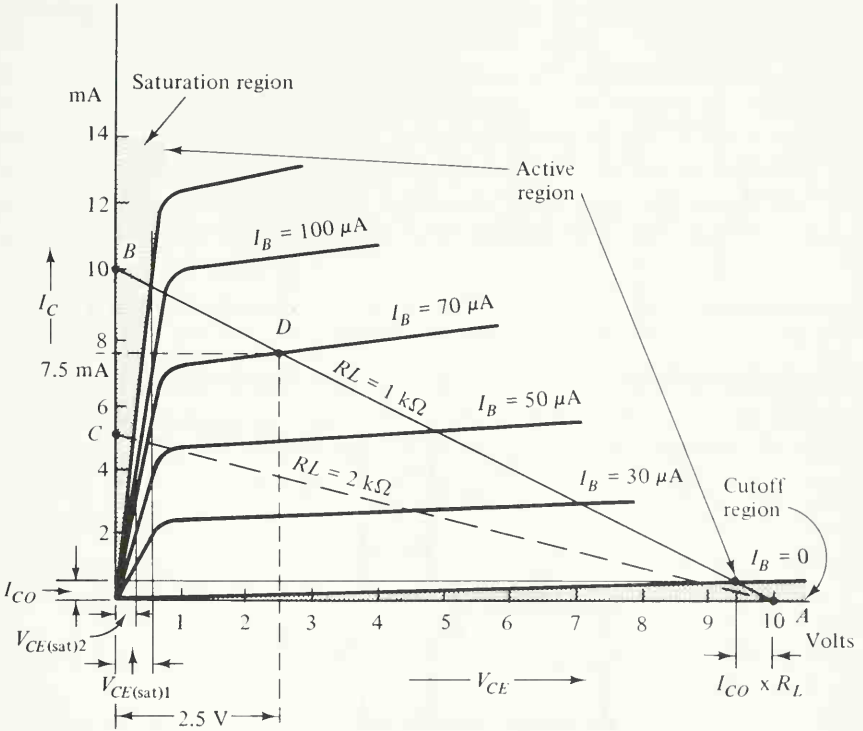


FIGURE 4-2. Characteristics and dc load line for transistor switch.


turer, and I_{CEX} can be regarded as essentially equal to I_{CO} . From the data sheet, the collector cutoff current for 2N3903 and 2N3904 transistors is 50 nA. The presence of I_{CO} makes V_{CE} slightly less than V_{CC} when the transistor is cutoff [see Figure 4-3(a)].

$$V_{CE} = V_{CC} - I_{CO} R_L \tag{4-2}$$


For $V_{CC} = 10\text{ V}$, $R_L = 1\text{ k}\Omega$, and $I_{CO} = 1\text{ }\mu\text{A}$:

$$\begin{aligned} V_{CE} &= 10\text{ V} - (1\text{ }\mu\text{A} \times 1\text{ k}\Omega) \\ &= 9.999\text{ V} \\ &\simeq V_{CC} \end{aligned}$$

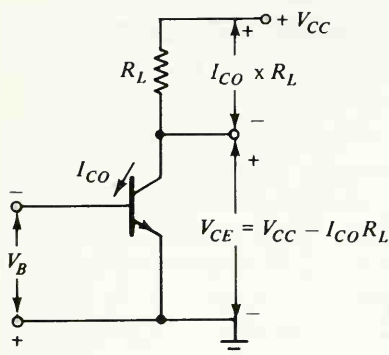
When the transistor is in saturation, a small collector-emitter satura-



(a) Transistor in cutoff

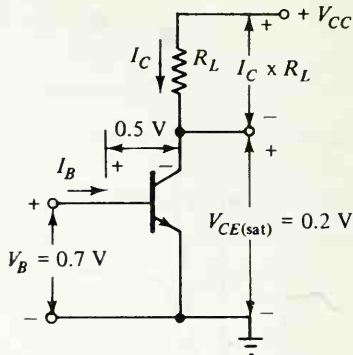

(b) Transistor in saturation

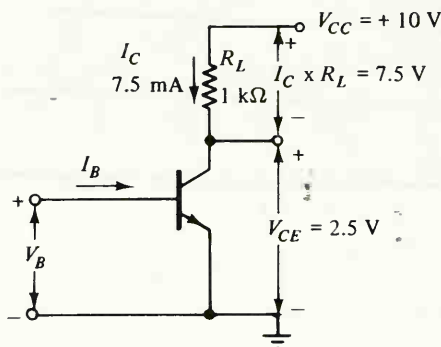

(c) Transistor in active region of characteristics

FIGURE 4-3. Transistors operated in cutoff, saturation, and active region of their characteristics.

tion voltage, $V_{CE(sat)}$, exists. Typically about 0.2 V , $V_{CE(sat)}$ largely depends upon I_C and the resistance of the semiconductor material that forms the transistor collector. The load line for $R_L = 2\text{ k}\Omega$ (broken line in Figure 4-2), reveals that when saturation occurs with smaller levels of I_C , then $V_{CE(sat)}$ is reduced. The 2N3903 and 2N3904 data sheet in Appendix 1 specifies $V_{CE(sat)}$ as 0.3 V at $I_C = 50\text{ mA}$ and 0.2 V at $I_C = 10\text{ mA}$.

The saturated transistor circuit in Figure 4-3(b) has typical voltages of $V_{BE} = 0.7\text{ V}$ and $V_{CE} = 0.2\text{ V}$. Thus the base terminal is 0.5 V positive with respect to the collector terminal, and the normally reverse-biased collector-base junction is actually forward-biased. As will be seen later, this forward bias at the collector-base junction limits the switching speed of the transistor.

The forward bias at the collector-base junction when a transistor is saturated reduces the dc current gain (h_{FE}). This happens because, to

draw the maximum number of charge carriers from emitter to collector, the collector-base junction must be reverse-biased. For saturation to occur, the transistor current gain must have a minimum value, $h_{FE(\min)}$, depending upon the circuit conditions. Suppose a transistor has a base current of $I_B = 50 \mu\text{A}$ and requires a collector current I_C of 1 mA for saturation. Then, $h_{FE(\min)} = I_C/I_B = 1 \text{ mA}/50 \mu\text{A} = 20$. If h_{FE} is less than 20 in this case, I_C will be less than 1 mA and saturation will *not* occur. If h_{FE} is greater than 20, I_C will tend to be greater than the required 1 mA, and saturation will occur.

EXAMPLE 4-1

For the circuit of Figure 4-1(a), $I_B = 0.2 \text{ mA}$. (a) Determine the value of $h_{FE(\min)}$ for saturation to occur. (b) If R_L in Figure 4-1(a) is changed to 220Ω and a 2N3904 transistor is employed, will the transistor be saturated?

solution (a)

For saturation:

$$\begin{aligned} I_C &\simeq \frac{V_{CC}}{R_L} \\ &= \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA} \\ h_{FE(\min)} &= \frac{I_C}{I_B} \\ &= \frac{10 \text{ mA}}{0.2 \text{ mA}} = 50 \end{aligned}$$

solution (b)

For saturation:

$$\begin{aligned} I_C &\simeq \frac{V_{CC}}{R_L} \\ &= \frac{10 \text{ V}}{220 \Omega} \simeq 45 \text{ mA} \\ h_{FE(\min)} &= \frac{I_C}{I_B} \\ &= \frac{45 \text{ mA}}{0.2 \text{ mA}} \\ &= 275 \end{aligned}$$

From the 2N3904 data sheet in Appendix 1, at $I_C = 50 \text{ mA}$, $h_{FE(\min)} = 60$. Therefore, the transistor will *not* be saturated.

Suppose a 2N3904 transistor is employed in the case of Example 4-1(a). From the 2N3904 data sheet in Appendix 1, at $I_C = 10 \text{ mA}$, $h_{FE(\min)} = 100$ and $h_{FE(\max)} = 300$. This suggests that for $I_B = 0.2 \text{ mA}$, I_C could be any value between $100 \times 0.2 \text{ mA}$ and $300 \times 0.2 \text{ mA}$, that is, from 20 mA to 60 mA . In fact, the maximum collector current that can flow is $I_C = V_{CC}/R_L = 10 \text{ mA}$, as calculated in the example. Thus, with an h_{FE} value greater than 50, more base current flows than is needed to drive the transistor into saturation. The extra base current flows out through the emitter terminal. In this situation the transistor is said to be *overdriven*.

Although transistors in switching circuits usually are switched from cutoff to saturation, and *vice versa*, they can also be switched between cutoff and the active region. For example, if the base current is limited to $70 \mu\text{A}$ for the load line shown in Figure 4-2 (point *D*), then V_{CE} is 2.5 V . In this case the transistor is referred to as a *nonsaturated switch* [Figure 4-3(c)].

The power dissipation is very small with a practical transistor in saturation or cutoff. For a nonsaturated transistor switch, the power dissipation is much larger than for either the cutoff or saturated cases.

EXAMPLE 4-2

If the circuit of Figure 4-1(a) employs a 2N3904 transistor, calculate the transistor power dissipation (a) at cut-off, (b) at saturation cutoff, and (c) when $V_{CE} = 2 \text{ V}$.

solution (a)

For cutoff:

From the 2N3904 data sheet, $I_C \simeq I_{CEX} = 50 \text{ nA}$,

$$\begin{aligned} P_D &\simeq I_C \times V_{CC} \\ &= 50 \text{ nA} \times 10 \text{ V} \\ &= 0.5 \mu\text{W} \end{aligned}$$

solution (b)

For saturation,

$$\begin{aligned}
 I_C &\simeq \frac{V_{CC}}{R_L} \\
 &= \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA}
 \end{aligned}$$

from the 2N3904 data sheet; at $I_C = 10 \text{ mA}$, $V_{CE(\text{sat})} = 0.2 \text{ V}$

$$\begin{aligned}
 P_D &= I_C \times V_{CE(\text{sat})} \\
 &= 10 \text{ mA} \times 0.2 \text{ V} \\
 &= 2 \text{ mW}
 \end{aligned}$$

solution (c)

At $V_{CE} = 2 \text{ V}$:

From Equation (4-1),

$$V_{CE} = V_{CC} - I_C R_L$$

$$\begin{aligned}
 I_C &= \frac{V_{CC} - V_{CE}}{R_L} \\
 &= \frac{10 \text{ V} - 2 \text{ V}}{1 \text{ k}\Omega} \\
 &= 8 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 P_D &= I_C \times V_{CE} \\
 &= 8 \text{ mA} \times 2 \text{ V} \\
 &= 16 \text{ mW}
 \end{aligned}$$

4-3 TRANSISTOR SWITCHING TIMES

One most important characteristic of a switching transistor is the speed with which it can be switched *on* and *off*. Consider Figure 4-4, where the time relationship between collector current and base current is shown. When the input current I_B is applied, the transistor does not switch *on* immediately. The time between application of base current and commencement of collector current is termed the *delay time* t_d (see Figure 4-4). The delay time is defined as the time required for I_C to reach 10% of its final level, after I_B has commenced. Even when the transistor begins to switch *on*, a finite time elapses before I_C reaches its maximum level. The

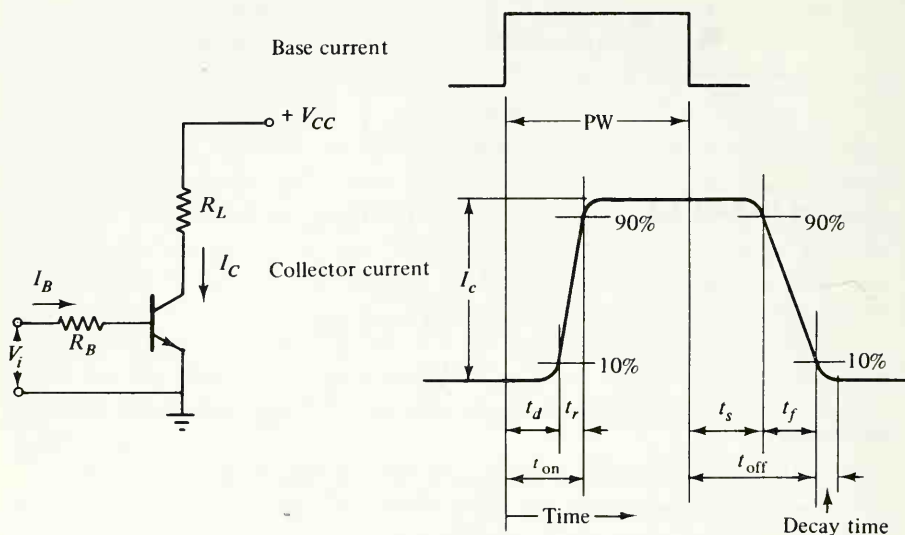


FIGURE 4-4. Time relationships between base current and collector current in a transistor switching circuit.

rise time t_r , is defined as the time it takes for I_C to go from 10% to 90% of its maximum level. The turn-on time (t_{on}) for the transistor is the sum of t_d and t_r (see Figure 4-4).

Similarly, a transistor cannot be switched off instantaneously. The turn-off time t_{off} is composed of a storage time t_s and a fall time t_f (Figure 4-4). The storage time results from the fact that the collector-base junction is forward-biased when the transistor is in saturation. Charge carriers crossing a forward-biased junction are trapped (or stored) in the depletion region when the junction is reversed. These charge carriers must be withdrawn or made to recombine with charge carriers of an opposite type before the collector current begins to fall. The storage time t_s is defined as the time between I_B switch off and I_C falling to 90% of its maximum level. The fall time t_f is the time required for I_C to fall from 90% to 10% of its maximum. A further quantity, the decay time is sometimes included in the turn-off time. This is the time required for I_C to go from its 10% level to I_{CO} . Usually, this is not an important quantity, since the transistor is regarded as being off when I_C falls to the 10% level.

Refer to the data sheet for the 2N3904 transistor in Appendix 1. The turn-on and turn-off times given are:

$$\text{Turn-on time} = t_d + t_r = 35 \text{ ns} + 35 \text{ ns} = 70 \text{ ns}$$

$$\text{Turn-off time} = t_s + t_f = 200 \text{ ns} + 50 \text{ ns} = 250 \text{ ns}$$

In the case of a nonsaturated transistor switch, the collector-base voltage is reverse-biased when the transistor is *on*. Therefore, no storage time is involved, and the turn-off time is not much larger than the fall time. This faster turn-off time is the major advantage of the nonsaturated switch.

Figure 4-5 shows the time relationship of the input and output voltages as well as the I_B and I_C waveforms for the circuit in Figure 4-4. I_B commences almost immediately when V_B is applied. The approximate level of I_B is input voltage V_i divided by base resistor R_B , that is, V_i/R_B (assuming V_{BE} is initially zero). The output voltage at any instant depends

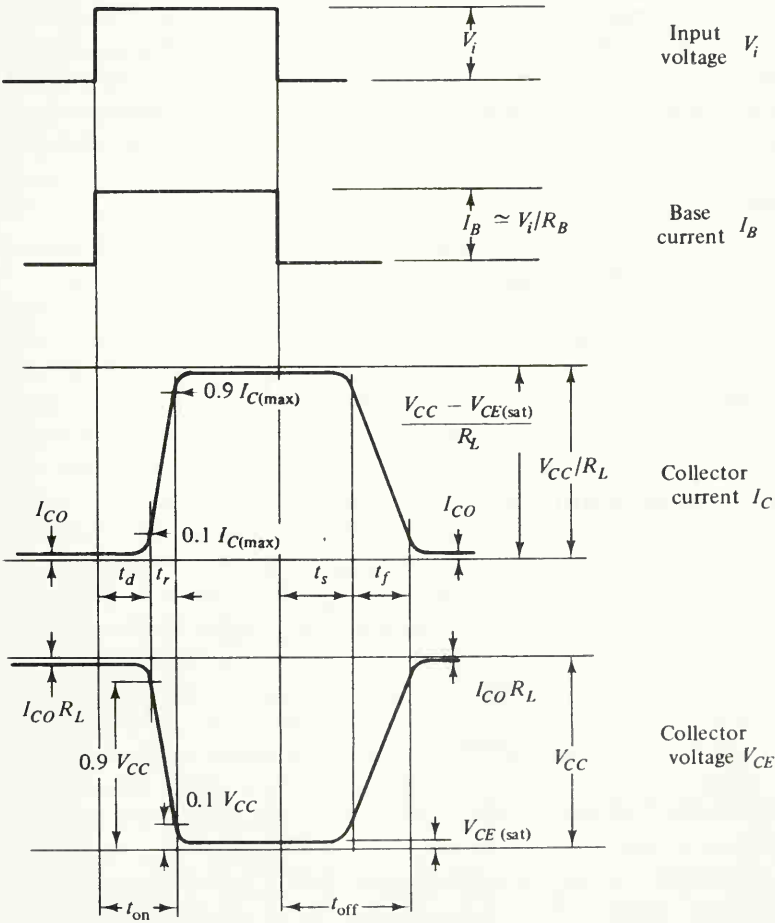


FIGURE 4-5. Time relationships between voltages and currents in a transistor switching circuit.

upon the instantaneous level of I_C . Thus, V_{CE} is initially $(V_{CC} - I_{CO}R_L)$ and falls to 90% of V_{CC} when I_C becomes 10% of $I_{C(\max)}$ after t_d . When I_C is 90% of $I_{C(\max)}$, V_{CE} is 10% of V_{CC} and finally falls to $V_{CE(\text{sat})}$ when I_C reaches its maximum level. When I_B goes to zero, the storage time elapses before I_C commences to fall. Then V_{CE} again becomes approximately 0.1 V_{CC} when I_C is 90% of its maximum level, and V_{CE} becomes 0.9 V_{CC} when I_C is 10% of maximum. Finally, V_{CE} returns to $V_{CC} - I_{CO}R_L$ when I_C falls to the level of the reverse saturation current.

EXAMPLE 4-3

The circuit in Figure 4-4 has $V_{CC} = 12\text{ V}$ and $R_L = 3.3\text{ k}\Omega$. The transistor employed is a 2N3904, and the input voltage has a PW of $5\text{ }\mu\text{s}$. Calculate the level of V_{CE} , (a) before the input pulse is applied, (b) at the end of the delay time, (c) at the end of the turn-on time. Also determine the time from commencement of the input pulse until the transistor switches off.

solution

In the 2N3904 data sheet (Appendix 1-4) the collector cutoff current is defined as $I_{CEX} = 50\text{ nA}$. Before the transistor switches on,

$$\begin{aligned} V_{CE} &= V_{CC} - I_{CEX}R_L \\ &= 12\text{ V} - (50\text{ nA} \times 3.3\text{ k}\Omega) \\ &= 11.9998\text{ V} \end{aligned}$$

At the end of the delay time,

$$\begin{aligned} V_{CE} &= V_{CC} - (0.1 I_{C(\max)} R_L) \\ &= V_{CC} - \left(0.1 \times \frac{V_{CC}}{R_L} \times R_L\right) \\ &= 12\text{ V} - (0.1 \times 12\text{ V}) \\ &= 10.8\text{ V} \end{aligned}$$

At the end of the turn-on time,

$$\begin{aligned} V_{CE} &= V_{CC} - \left(0.9 \times \frac{V_{CC}}{R_L} \times R_L\right) \\ &= 12\text{ V} - (0.9 \times 12\text{ V}) \\ &= 1.2\text{ V} \end{aligned}$$

For the 2N3904, $t_{\text{off}} = 250 \text{ ns}$. Time from commencement of input to transistor switching off is $PW + t_{\text{off}}$.

$$\begin{aligned} PW + t_{\text{off}} &= 5 \mu\text{s} + 250 \text{ ns} \\ &= 5.25 \mu\text{s} \end{aligned}$$

4-4 IMPROVING THE SWITCHING TIMES

If the base-emitter of the transistor is reverse-biased before switch-on, the delay time is longer than in the case when V_{BE} is initially zero. This is because the transistor input capacitance is charged to the reverse bias voltage, and must be discharged before V_{BE} can become positive. Therefore, to minimize the turn-on time, V_{BE} should be zero or have a very small reverse bias before switch-on. Both the delay time and the rise time can be reduced if the transistor is *overdriven*, i.e., if I_B is made larger than the minimum required for saturation. With a larger I_B , the junction capacitances are charged faster, thus reducing the turn-on time.

A major disadvantage of overdriving is that the storage time is extended, by the larger current flow across the forward-biased collector-base junction, when the transistor is in saturation. Therefore, although an overdriven transistor will turn on faster it has a longer turn-off time than a transistor which has just enough base current for saturation. One way to shorten the turn-off time is to provide a large negative input voltage at switch-off. This produces a reverse base current flow which causes the junction capacitance to discharge rapidly. Again, this has a disadvantage in that the turn-on time is increased because of the initial large reverse bias of the base-emitter junction.

Ideally, for fast switching V_{BE} should start at zero volts, and I_B should initially be large at switch-on but should rapidly settle down to the minimum required for saturation. Also, switch-off should be accomplished by a large reverse bias voltage which quickly returns to zero. Exactly these conditions are achieved when a capacitor is connected in parallel with R_B , as shown in Figure 4-6. This capacitor, termed a *speed-up capacitor*, is initially uncharged before the input voltage pulse is applied. When the input voltage rises, the capacitor commences to charge to $(V_i - V_{BE})$ [Figure 4-6(a)]. The capacitor charging current flows into the transistor base terminal. Thus I_B is initially large, but quickly settles down to its minimum dc level as the capacitor becomes charged. At switch-off [Figure 4-6(b)], the capacitor discharge produces a reverse base current which rapidly returns to zero.

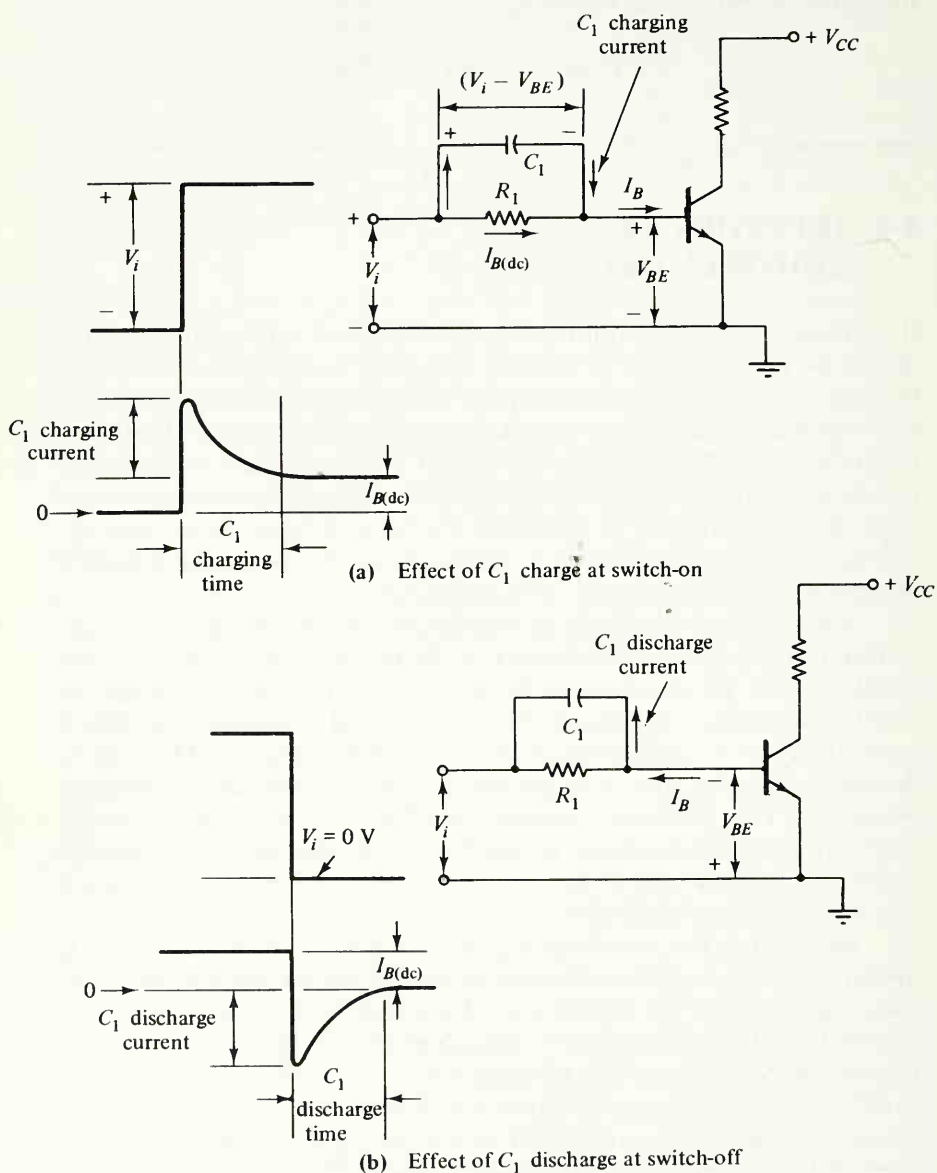


FIGURE 4-6. Effect of C_1 charge and discharge when the transistor is switched *on* and *off*.

The speed-up capacitor tends to reduce t_d and t_s as well as t_r and t_f . However, if C_1 is so small that it becomes completely charged within the delay time, then it will not have a significant effect upon the rise time. Similarly, if C_1 is completely discharged during the storage time, it will not produce a marked improvement in the fall time.

Consider the circuit of Figure 4-7. The settled base current level (*i.e.*, after the capacitor is completely charged) can be calculated using V_i , R_B , and R_S .

$$\begin{aligned} I_B &= \frac{V_i - V_{BE}}{R_S + R_B} \\ &= \frac{5 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega + 8.2 \text{ k}\Omega} \approx 0.5 \text{ mA} \end{aligned}$$

The initial level of capacitor charging current is approximately the signal voltage divided by the signal source resistance.

$$\begin{aligned} I_1 &\approx \frac{V_i - V_{BE}}{R_S} \\ &= \frac{5 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = 4.3 \text{ mA} \end{aligned}$$

This is considerably greater than the dc level of I_B . Therefore, an

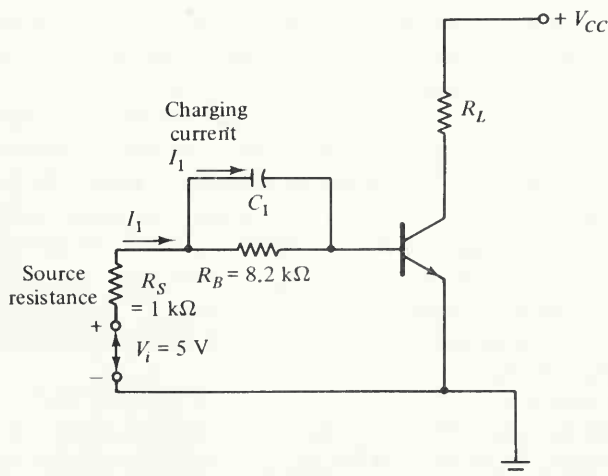


FIGURE 4-7. Circuit for calculation of initial charging current level.

improvement in switching speed may be expected. For the best possible improvement in switching speed, a speed-up capacitor should be selected that is large enough to maintain the charging current (*i.e.*, base current) nearly constant at its maximum level during the transistor turn-on time. The charging current will drop by only 10% from its maximum level, if the capacitor is allowed to charge by 10% during the turn-on time. C_1 charges by 10% during a time of $0.1 C_1 R_s$ (Chapter 2). Therefore,

$$t_{\text{on}} = 0.1 C_1 R_s$$

and

$$C_1 = \frac{t_{\text{on}}}{0.1 R_s} \quad (4-3)$$

For $t_{\text{on}} = 300 \text{ ns}$, and $R_s = 1 \text{ k}\Omega$:

$$C_1 = \frac{300 \text{ ns}}{0.1 \times 1 \text{ k}\Omega} = 3000 \text{ pF}$$

A larger capacitor than this is not likely to offer any greater improvement in switching time. Also, if a ten times improvement in switching time is achieved, then a capacitor of 300 pF might be almost as effective as one with a value of 3000 pF. This is because t_{on} in the above calculation would be reduced from 300 ns to 30 ns and, consequently, C_1 is calculated as 300 pF. To achieve such an improvement in switching time, however, the transistor must initially operate well below its maximum switching speed. Also, the input pulse must have a rise time very much less than the minimum switching time sought.

The upper limit to the value of C_1 that may be used depends upon the maximum signal frequency. When the transistor is switched *off*, C_1 discharges through R_B . For correct switching, C_1 should be at least 90% discharged during the time interval between transistor *switch-off* and *switch-on*. The time required for the capacitor to return to its discharged condition is variously referred to as the *settling time*, the *resolving time*, or the *recovery time* t_{re} of the circuit. In this case, the transistor is *off* and the capacitor is discharged through R_B . C_1 will discharge by 90% in a time $t = 2.3 C_1 R_B$ (Chapter 2).

$$t_{re} = 2.3 C_1 R_B$$

or

$$\text{maximum } C_1 = \frac{t_{re}}{2.3 R_B} \quad (4-4)$$

EXAMPLE 4-4

The circuit of Figure 4-7 is to have a 50 kHz input square wave. Calculate the maximum value of the speed-up capacitor that may be used.

solution

$$T = \frac{1}{f} = \frac{1}{50 \text{ kHz}} = 20 \mu\text{s}$$

$$t_{re} \text{ between switch-off and switch-on} = \frac{T}{2} = 10 \mu\text{s}$$

$$\begin{aligned} C_{1(\text{max})} &= \frac{t_{re}}{2.3 R_1} = \frac{10 \mu\text{s}}{2.3 \times 8.2 \text{ k}\Omega} \\ &= 530 \text{ pF} \end{aligned}$$

EXAMPLE 4-5

Determine the maximum input frequency for the circuit of Figure 4-7 when $C_1 = 200 \text{ pF}$.

solution

$$\begin{aligned} t_{re} &= 2.3 C_1 R_1 \\ &= 2.3 \times 200 \text{ pF} \times 8.2 \text{ k}\Omega \\ &= 3.772 \mu\text{s} \end{aligned}$$

$$T = 2t_{re} = 7.544 \mu\text{s}$$


$$f = \frac{1}{T} = \frac{1}{7.544 \mu\text{s}} \simeq 133 \text{ kHz}$$

4-5 JUNCTION FIELD EFFECT TRANSISTOR (JFET) SWITCH


An *n*-channel *junction field effect transistor* (JFET), connected in common source configuration, is shown in Figure 4-8(a). The output voltage from the circuit equals the supply voltage minus the voltage drop across R_L .

$$V_O = V_{DD} - I_D R_L \quad (4-5)$$

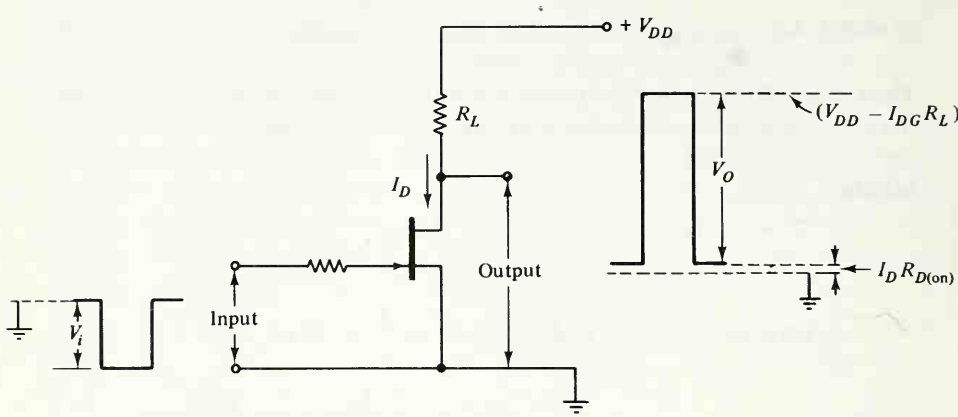Ideally, $V_O = V_{DD}$ when the device is *off*, and $V_O = 0$ when the




(a) Common source circuit as switch

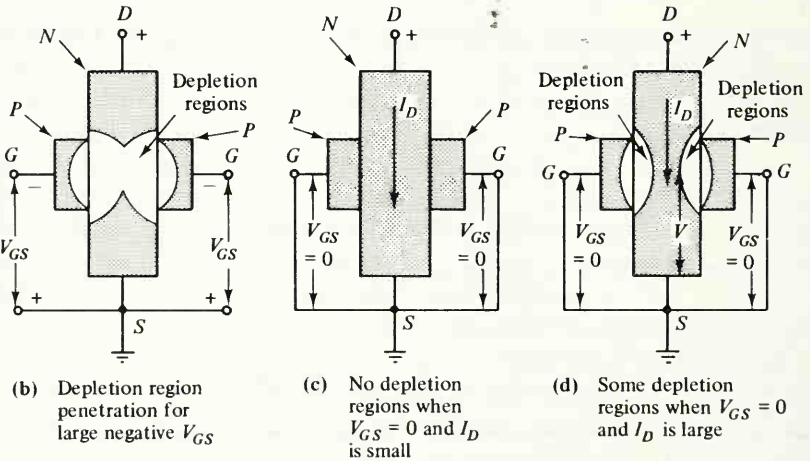**FIGURE 4-8.** JFET switching circuit and effects of V_{GS} and I_D .


transistor is *on*. The input signal biases the transistor *off* when V_i is negative. The effect is illustrated in Figure 4-8(b) where the *depletion regions* resulting from the negative bias on the gate are shown to penetrate so deeply into the *n*-type channel that they meet at the center. The channel is interrupted by the depletion regions, so that the *drain current* I_D cannot flow. When the input signal is at ground level, the *gate* potential equals that at the source terminal. In this case there are no depletion regions

so the drain current easily flows through the channels [Figure 4-8(c)]. If the drain current is small, there will be only a small voltage drop along the channel, due to the small *drain-source on resistance* $R_{D(\text{on})}$.

Actually there could be depletion regions even when the gate is at source potential, if a substantial drain current flows. Figure 4-8(d) illustrates the situation. The drain current I_D causes sufficient voltage drop along the channel so that the source (and, consequently, the gate) becomes negative with respect to part of the channel. This produces depletion regions which again penetrate into the channel. The narrowed channel

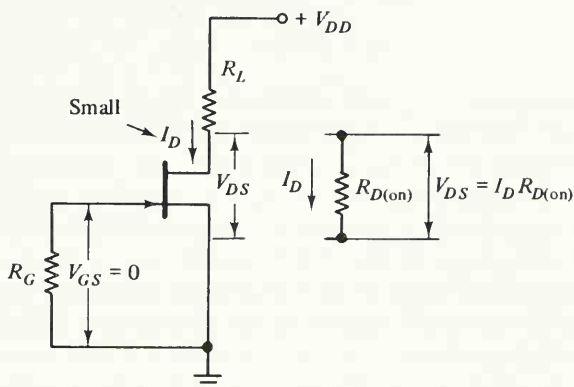

(a) On-biased JFET with small I_D

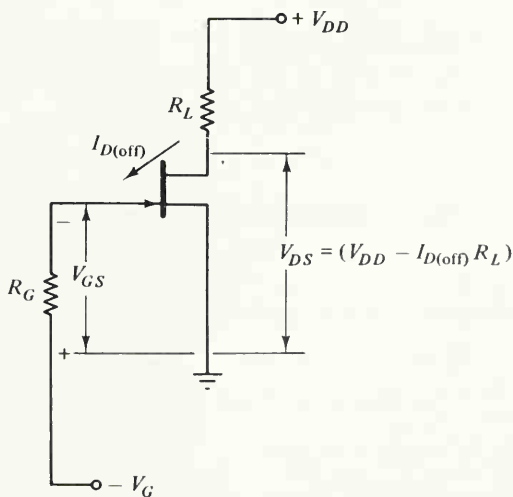

(b) Off-biased JFET

FIGURE 4-9. Drain-source voltage for on- and off-biased JFETs.

has an increased drain-source resistance, and thus a relatively large drain-source *on* voltage.

When the JFET is biased *on*, [Figure 4-9(a)], the output voltage is

$$V_{D(\text{on})} = I_D \times R_{D(\text{on})} \quad (4-6)$$

Typically, $R_{D(\text{on})}$ is 30Ω or less. With a drain current of $100\mu\text{A}$, the typical level of $V_{D(\text{on})}$ can be quite small:

$$\begin{aligned} V_{D(\text{on})} &= 100\mu\text{A} \times 30\Omega \\ &= 3\text{mV} \end{aligned}$$

A comparison of $V_{D(\text{on})}$ with the typical $V_{CE(\text{sat})}$ of 0.2V for a bipolar transistor shows that this is a major advantage of the JFET switch.

The *off*-biased JFET has a small *drain gate leakage-current* $I_{D(\text{off})}$ flowing across the reverse-biased gate-channel junctions. As illustrated in Figure 4-9(b), $I_{D(\text{off})}$ causes a very small voltage drop across R_L .

Another advantage of the JFET switch over a bipolar transistor switch, is that the JFET has a much higher input resistance than a bipolar transistor. Thus, the JFET can be easily switched by signals that have large source resistances.

EXAMPLE 4-6

The circuit in Figure 4-8(a) uses a 2N4857 JFET and has $V_{DD} = 15\text{V}$ and $R_L = 3.9\text{k}\Omega$. Determine the level of the output voltage (a) when the device is cut off, and (b) when the transistor is switched *on*.

solution

From the 2N4857 data sheet in Appendix 1-8, the maximum drain current at cutoff is

$$\begin{aligned} I_{D(\text{off})} &= 0.25\text{nA} \quad (\text{i.e., at } 25^\circ\text{C}) \\ V_o &= V_{DD} - I_{D(\text{off})}R_L \\ &= 15\text{V} - (0.25\text{nA} \times 3.9\text{k}\Omega) \\ &= 15\text{V} - 1\mu\text{V} \\ &\simeq 15\text{V} \end{aligned}$$

In the data sheet, $R_{D(\text{on})}$ is identified as

$$r_{ds(on)} = 40\Omega$$

and when the FET is *on*:

$$\begin{aligned} I_D &\simeq \frac{V_{DD}}{R_L} \\ &= \frac{15\text{ V}}{3.9\text{ k}\Omega} = 3.85\text{ mA} \\ V_O &= I_D r_{ds(on)} \\ &= 3.85\text{ mA} \times 40\Omega \\ &= 154\text{ mV} \end{aligned}$$

4-6 MOSFET SWITCH

N-channel and *p*-channel *metal oxide semiconductor field effect transistor* (MOSFET) switching circuits are shown in Figures 4-10(a) and (b) together with input and output waveforms. In the *enhancement* devices shown no channel exists while the gate is at the same potential as the source. Therefore, these transistors require no external bias voltage to switch them *off*; that is, they can be operated from a single polarity supply. For the *n*-channel MOSFET a positive input pulse is necessary for switch-on. When the input signal becomes positive, I_D flows, and the output voltage drops from V_{DD} to $I_D R_{D(on)}$. In the case of the *p*-channel device, the output is $-V_{DD}$ while no drain current is flowing. A negative signal on the gate terminal switches the transistor *on*, causing the output level to change to $-I_D R_{D(on)}$.

Since the gate terminal in a MOSFET is insulated from the channel, there is no drain gate leakage-current. This results in an input resistance even higher than that of a JFET circuit. There is a small drain source leakage current, which causes some voltage drop along R_L when the MOSFET is *off*.

4-7 CMOS SWITCH

When two devices are identical in every way except for their supply voltage polarities, they are termed *complementary devices*. For example, if two bipolar transistors have identical parameters, but one is an *npn* device

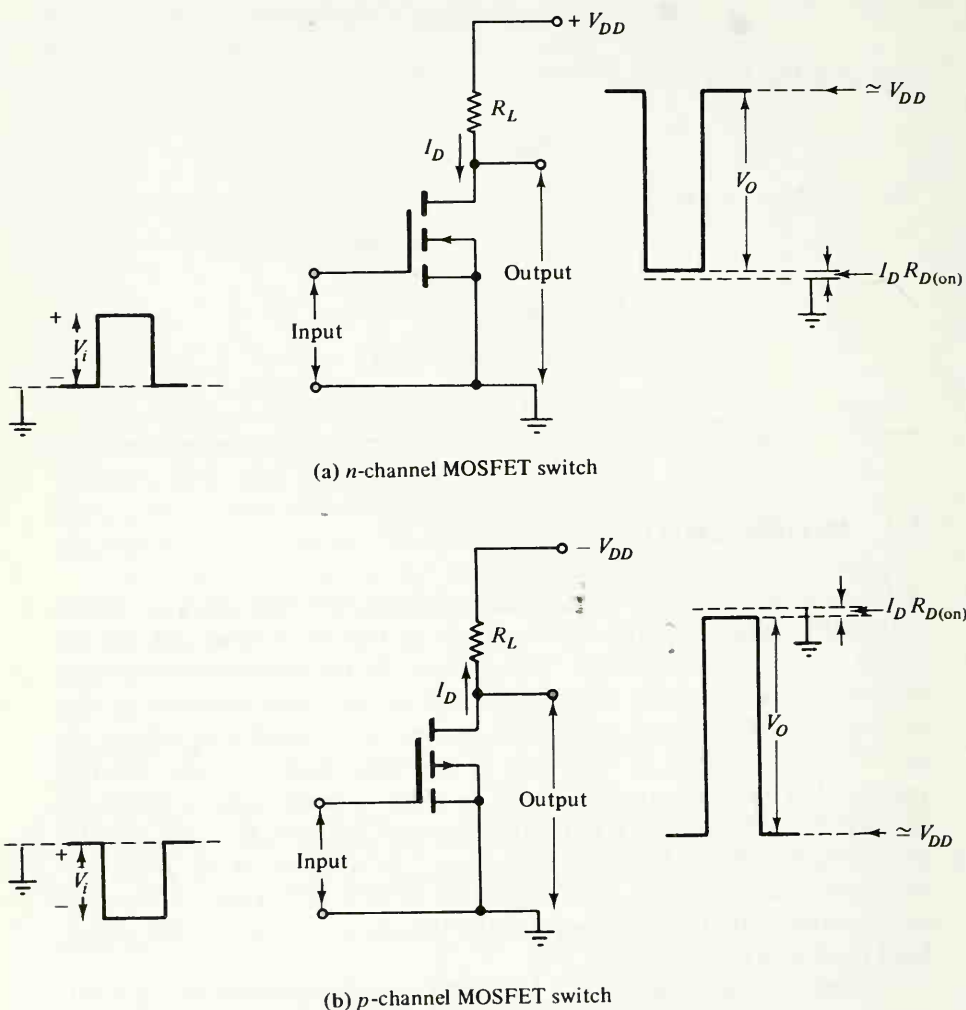


FIGURE 4-10. *n*-channel and *p*-channel MOSFET switches.

and the other is *pnp*, they are complementary. Similarly, two MOSFETs, one which is *p*-channel and the other *n*-channel, can be complementary. When *p*-channel and *n*-channel MOSFETs are combined, the resulting circuitry is termed *complementary MOS*, or *CMOS*.

Figure 4-11 shows the circuit of a CMOS switch. Both devices are enhancement MOSFETs, so that no channel exists until one of them is switched *on*. When the input voltage is zero at the common gate terminal, the *p*-channel device is biased *on* and the *n*-channel device is *off*. In this condition there is only a very small voltage drop from drain to source for

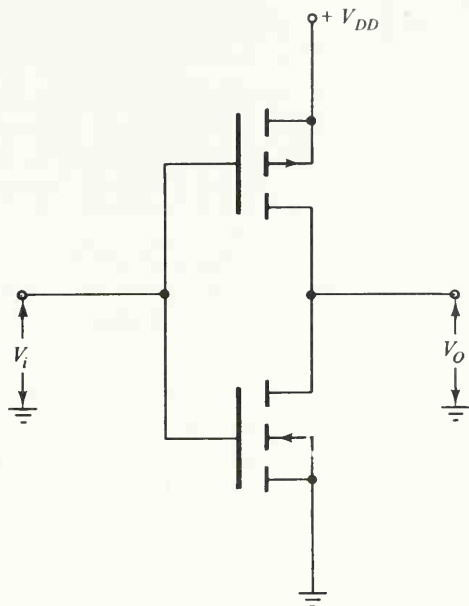


FIGURE 4-11. CMOS switch.

the p -channel device, and the output voltage is very close to V_{DD} . At this time the n -channel transistor is biased *off*. When the input voltage becomes positive, the n -channel transistor is biased *on* and the p -channel device is *off*. There is now only a very small voltage drop along the n -channel device and, consequently, the output voltage is very close to ground.

The major advantage of CMOS circuits is that their power dissipation is extremely small compared to other circuits. The small power dissipation, together with the small volt drop across the *on* transistor and the high input impedance, makes the CMOS inverter approach the ideal switch. CMOS is discussed further in Chapter 10.

REVIEW QUESTIONS AND PROBLEMS

- 4-1 Sketch a circuit to show a bipolar transistor employed as a switch. Compare the transistor to an ideal switch.
- 4-2 Define the following terms: saturated switch, nonsaturated switch, saturation voltage, collector-base leakage current, and $h_{FE(\min)}$. Discuss the importance of the latter three items in relation to a transistor switch.
- 4-3 Sketch typical transistor common emitter characteristics. Identify

the various regions of the characteristics and show how $V_{CE(sat)}$ differs with different transistor load resistances.

- 4-4** (a) A common emitter transistor circuit has $V_{CC} = 20\text{ V}$, $R_L = 2.2\text{ k}\Omega$ and $I_B = 0.3\text{ mA}$. Determine $h_{FE(min)}$ if the transistor is to be saturated. (b) If a 2N3903 transistor is used in the above circuit, calculate the minimum I_B level at which the transistor will become saturated.
- 4-5** A common emitter circuit, using a 2N3904 transistor, has $V_{CC} = 25\text{ V}$. The load resistance can be $22\text{ k}\Omega$ or $2.2\text{ k}\Omega$. Calculate the minimum level of base current needed to achieve saturation in each case.
- 4-6** For the circuit described in Problem 4-5, calculate the transistor power dissipation for each load resistance, at both saturation and cutoff. Also calculate the transistor power dissipation for each load resistance, when the collector-emitter voltage is 3 V .
- 4-7** For a transistor switch, sketch the waveforms of the input voltage, base current, collector current, and collector voltage. Show the various components of transistor turn-on time and turn-off time, and discuss their origins.
- 4-8** A switching circuit using a 2N4418 transistor (data sheet in Appendix 1-7) has $V_{CC} = 15\text{ V}$ and $R_L = 2.7\text{ k}\Omega$. The input pulse width is $2\text{ }\mu\text{s}$. Calculate the level of V_{CE} (a) before the pulse is applied, (b) at the end of the delay time, (c) at the end of the storage time. Also determine the times from commencement of the input pulse until the transistor switches *on* and until the transistor switches *off*.
- 4-9** Show how a *speed-up capacitor* may be employed to improve the turn-on and turn-off time of a transistor. Sketch the waveforms of base current with and without the speed-up capacitor. Explain how the capacitor improves switching speed.
- 4-10** The circuit described in Problem 4-5 has a base resistance of $27\text{ k}\Omega$. (a) If the circuit is to be switched at a maximum frequency of 100 kHz , calculate the maximum size of the speed-up capacitor that should be used. (b) Determine the maximum switching signal frequency when a 100 pF speed-up capacitor is employed.
- 4-11** Explain how a junction field effect transistor can be employed as a switch. Sketch a circuit which uses a JFET switch. Sketch the input and output waveforms and show how the JFET operates when *on* and when *off*. Compare the JFET switch to a bipolar transistor switch.
- 4-12** A 2N4856 JFET (data sheet in Appendix 1-8) is connected as a

switch, with $V_{DD} = 20\text{ V}$ and $R_L = 4.7\text{ k}\Omega$. Determine the level of the output (drain-source) voltage (a) when the device is cut off and (b) when switched *on*.

- 4-13** Sketch *p*-channel and *n*-channel MOSFET switching circuits. Show input and output waveforms in each case, and discuss the advantages of MOSFET switches.
- 4-14** Define CMOS. Sketch the basic CMOS inverter circuit and explain how it operates. Describe the advantages and disadvantages of CMOS.

Chapter 5

The Inverter Circuit

INTRODUCTION

An INVERTER CIRCUIT, as the name suggests, performs the function of inverting an input signal. When the input goes positive, the output goes negative, and vice versa. Usually, a small input signal can drive the inverter output from one extreme voltage level to the other extreme, but large input signals may also be employed. Bipolar transistor inverters may have the input signal direct-coupled or capacitor-coupled. JFET inverters can also be constructed for direct- or capacitor-coupled signals. An IC operational amplifier without any additional components can be employed as an inverter.

5-1 DIRECT-COUPLED BIPOLAR TRANSISTOR INVERTER

A transistor *inverter circuit* is essentially an overdriven common emitter circuit. The input may be a square wave, a pulse waveform, or even a sine

wave, provided that the input amplitude is sufficient to drive the transistor into saturation and cutoff. Figure 5-1(a) shows an inverter circuit with a pulse wave input. When the input is zero, there is no collector current and the output is approximately V_{CC} . When the input becomes positive, the transistor switches into saturation, and the output becomes $V_{CE(sat)}$. Thus, a positive going input produces a negative going output, and *vice versa*. The output waveform is then the inverse of the input, hence the name *inverter*.

Figure 5-1(b) illustrates the effect of a sine wave input to an inverter. If the amplitude is large enough to switch the transistor rapidly to saturation and cutoff, then an inverted square wave output will result.

When the input waveform to an inverter has a large amplitude, the base-emitter junction of the transistor may be destroyed by an excessive

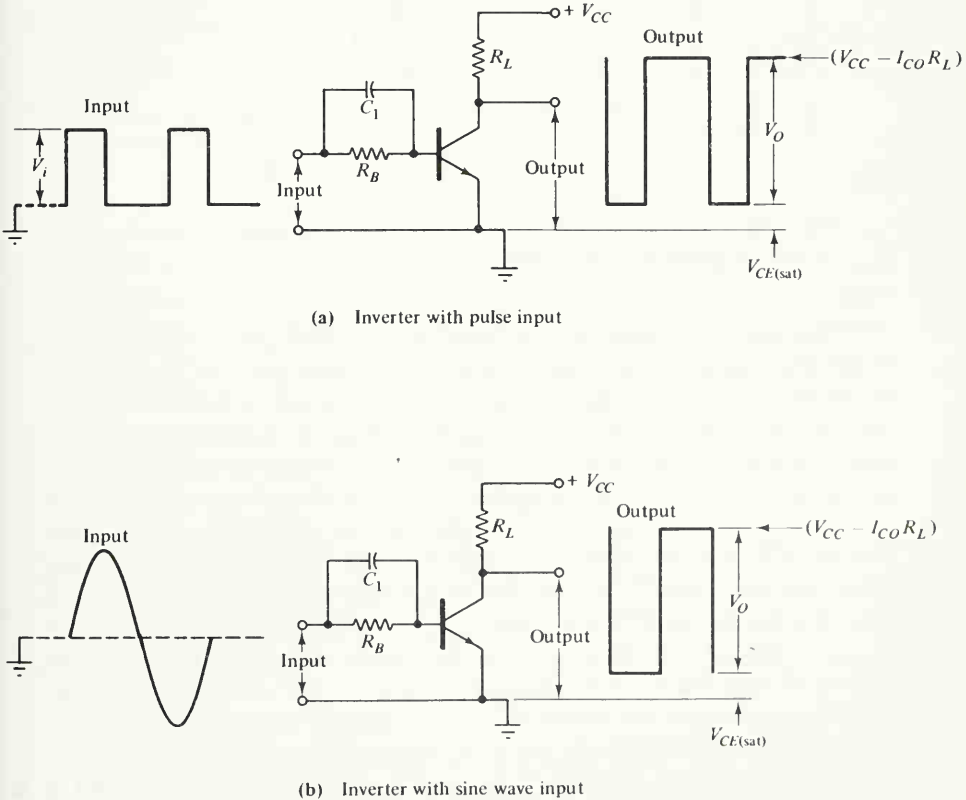


FIGURE 5-1. Transistor inverter circuits with pulse and sine wave inputs.

reverse voltage. Most transistors can take only about 5 V in reverse at the base-emitter junction. To protect the transistor, a diode connected as a negative clipper may be employed (see Figure 3-7). Alternatively, a diode may be connected in series with the transistor emitter terminal, as shown in Figure 5-2. Since the diode normally can survive reverse bias voltages on the order of at least 50 V, the combined base-emitter junction and diode will withstand a large reverse bias.

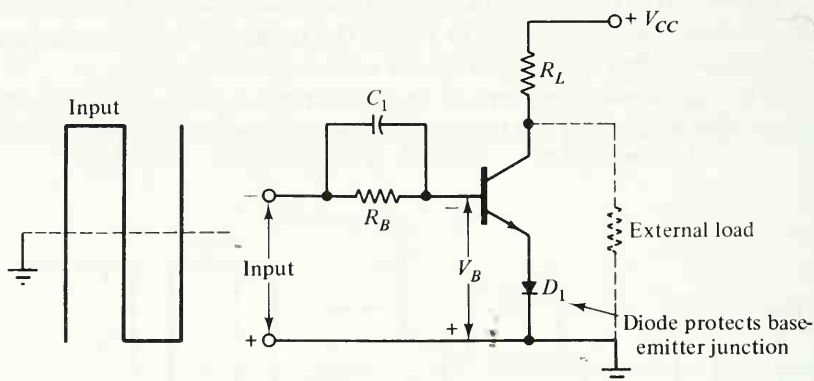


FIGURE 5-2. Use of diode to protect base-emitter junction against excessive reverse voltage.

The design of a transistor inverter circuit should begin with selection of the load resistance R_L , unless it is already specified. In general, R_L should be much smaller than the load to be connected to the inverter output. However, R_L should also be made as large as possible in order to keep I_C to a minimum. If this principle is followed in all circuit design, the current demand from power supplies is kept to a minimum. Also, with current maintained as small as possible, power dissipation in all components is minimized. The lower limit for I_C is dependent upon the particular transistor used. The data sheets in Appendix 1-4 and Appendix 1-6 show that for the 2N3904 transistor, $h_{FE(\min)}$ is only 40 at $I_C = 0.1$ mA, and $h_{FE(\min)} = 100$ at $I_C = 10$ mA. For the 2N930 transistor, $h_{FE(\min)} = 100$ at an I_C of only 10 μ A, and $h_{FE(\min)}$ is 150 at $I_C = 500$ μ A. Obviously, the 2N3904 should not be operated with a collector current much below 100 μ A, while the 2N930 can easily be operated with I_C as low as 10 μ A. One disadvantage of operating a transistor at very low current levels is that the resultant large resistance values make the circuit more susceptible to picking up unwanted signals.

If V_{CC} and I_C are known, R_L is calculated simply as (voltage across R_L) divided by (current through R_L).

$$R_L = \frac{V_{CC} - V_{CE(sat)}}{I_C} \quad (5-1)$$

Usually, the calculated value of R_L is not exactly equal to an available standard resistance value. In this case, the next higher standard value should be selected. With I_C flowing, the voltage drop across R_L must at least equal $V_{CC} - V_{CE(sat)}$ for transistor saturation. A value of R_L that is larger than calculated gives saturation with a lower I_C level. If a value of R_L that is smaller than calculated is used, I_C must be increased to ensure saturation.

Frequently an external load is to be connected to the circuit, as shown broken in Figure 5-2. In this case, R_L should be made much smaller than the external load, so that the load does not significantly affect the circuit performance. Then I_C is calculated from Equation (5-1).

The minimum base current for saturation is calculated as:

$$I_{B(min)} = \frac{I_C}{h_{FE(min)}} \quad (5-2)$$

Here, the use of $h_{FE(min)}$ is necessary for transistor saturation. If the particular transistor used has a larger than minimum value of h_{FE} , for a given I_B , I_C will tend to be larger than necessary, and saturation will be achieved.

The value of R_B is determined by dividing the voltage across R_B by the current through R_B :

$$R_B = \frac{V_i - V_{BE}}{I_{B(min)}}$$

Again, an available standard resistance must be selected, but this time the next *lower* standard value should be selected. This is because the voltage across R_B is a fixed quantity, ($V_i - V_{BE}$), and

$$I_B = \frac{V_i - V_{BE}}{R_B}$$

If R_B is selected larger than the calculated value, then I_B will be less than the value of $I_{B(min)}$ required to saturate the transistor. If R_B is smaller than calculated, I_B is greater than $I_{B(min)}$ and transistor saturation will occur.

Speed-up capacitor C_1 is calculated for maximum signal frequency, as explained in Sec. 4-4.

EXAMPLE 5-1

Design a transistor inverter circuit using a 2N3904 transistor. The value of V_{CC} is 12 V and the input is a ± 3 V square wave. Use $I_C = 1$ mA.

solution

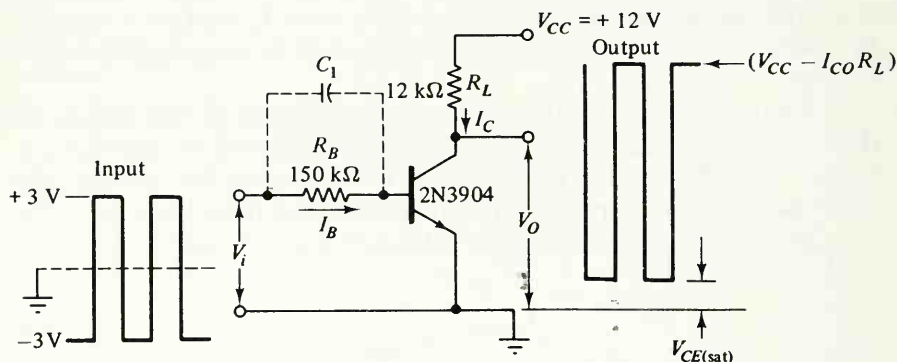


FIGURE 5-3. Inverter circuit for Example 5-1.

At saturation,

$$I_C R_L = V_{CC} - V_{CE(sat)}$$

$$R_L = \frac{V_{CC} - V_{CE(sat)}}{I_C} = \frac{12\text{ V} - 0.2\text{ V}}{1\text{ mA}} = 11.8\text{ k}\Omega \quad (\text{use } 12\text{ k}\Omega \text{ standard value})$$

$$I_{B(\min)} = \frac{I_C}{h_{FE(\min)}}$$

From the 2N3904 data sheet, $h_{FE(\min)} = 70$ at $I_C = 1$ mA.

$$I_B = \frac{1\text{ mA}}{70} \simeq 14.3\text{ }\mu\text{A}$$

$$R_B = \frac{V_i - V_{BE}}{I_B} + \frac{3\text{ V} - 0.7\text{ V}}{14.3\text{ }\mu\text{A}} \simeq 160\text{ k}\Omega \quad (\text{use } 150\text{ k}\Omega \text{ standard value})$$

EXAMPLE 5-2

The square wave input to the circuit designed in Example 5-1 has a maximum frequency of 45 kHz. Determine the maximum value of the speed-up capacitor C_1 .

solution

C_1 must discharge via R_B by about 90% during the negative (or *off*) portion of the square wave input.

$$\begin{aligned}\text{Resolving time } t_{re} &= \frac{T}{2} = \frac{1}{2f} \\ &= \frac{1}{2 \times 45 \text{ kHz}} \simeq 11 \mu\text{s}\end{aligned}$$

Recall Equation (4-4):

$$C_{(\text{max})} = \frac{t_{re}}{2.3 R}$$

Then, for 90% discharge:

$$\begin{aligned}C &= \frac{t_{re}}{2.3 R_B} = \frac{11 \mu\text{s}}{2.3 \times 150 \text{ k}\Omega} \\ &\simeq 32 \text{ pF} \quad (\text{use } 30 \text{ pF standard value})\end{aligned}$$

EXAMPLE 5-3

Design a transistor inverter circuit to handle a square wave input of ± 10 V. V_{CC} is 15 V, and the external load has a resistance of 100 k Ω . Use a 2N3903 transistor, and determine the amplitude of the output waveform.

solution

Since the input can be -10 V, diode D_1 (Figure 5-4) is necessary to protect the transistor.

$$R_L \ll R_1$$

Make

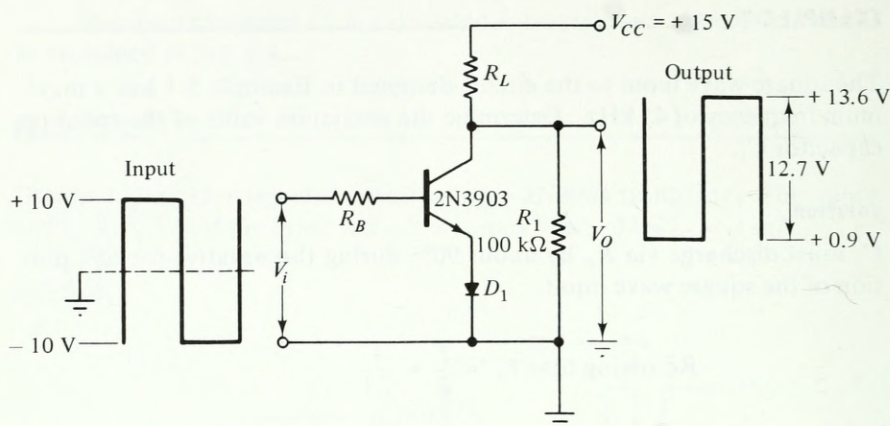


FIGURE 5-4. Inverter circuit for Example 5-3.

$$\begin{aligned}
 R_L &\simeq \frac{1}{10} R_1 \\
 &= \frac{1}{10} \times 100 \text{ k}\Omega = 10 \text{ k}\Omega \quad (\text{standard value})
 \end{aligned}$$

At saturation,

$$\begin{aligned}
 I_C &\simeq \frac{V_{CC} - V_{CE(\text{sat})} - V_{D1}}{R_L} \\
 &= \frac{15 \text{ V} - 0.2 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} \\
 &= 1.41 \text{ mA}
 \end{aligned}$$

From the 2N3903 data sheet in Appendix 1-4, $h_{FE(\text{min})} \simeq 35$:

$$\begin{aligned}
 I_{B(\text{min})} &= \frac{I_C}{h_{FE(\text{min})}} \\
 &= \frac{1.41 \text{ mA}}{35} \\
 &\simeq 40 \mu\text{A}
 \end{aligned}$$

and

$$\begin{aligned}
 R_B &= \frac{V_i - V_{BE} - V_{D1}}{I_{B(\min)}} \\
 &= \frac{10 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V}}{40 \mu\text{A}} = 215 \text{ k}\Omega \quad (\text{use } 180 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

D_1 should be a low-current diode with reverse breakdown voltage greater than 10 V. The 2N914 is a suitable device; see the 2N914 data sheet in Appendix 1.

When the transistor is saturated:

$$\begin{aligned}
 V_o &= V_{D1} + V_{CE(\text{sat})} \\
 &= 0.7 \text{ V} + 0.2 \text{ V} = 0.9 \text{ V}
 \end{aligned}$$

At cutoff, R_1 and R_L act as a potential divider, and

$$\begin{aligned}
 V_o &= \frac{V_{CC} \times R_1}{R_1 + R_L} = \frac{15 \text{ V} \times 100 \text{ k}\Omega}{100 \text{ k}\Omega + 10 \text{ k}\Omega} \\
 &= 13.6 \text{ V}
 \end{aligned}$$

Peak-to-peak output amplitude is equal to $13.6 \text{ V} - 0.9 \text{ V}$, or 12.7 V .

5-2 CAPACITOR-COUPLED INVERTER CIRCUITS

Sometimes a transistor is required to be biased in the *on* condition, until an input signal is applied to switch it *off*. In this case the signal may be capacitor-coupled. Such a circuit is shown in Figure 5-5. Bias resistor R_B provides base current from the supply to keep the device in saturation. Capacitor C_c couples the negative-going signal to the transistor base. When the signal pulls the base below the emitter voltage level, the transistor switches *off*. The value of C_c is calculated from a knowledge of the input voltage amplitude and pulse width. For reasons of economy, physical size, and shortest capacitor recharge time, it is best to choose the smallest possible coupling capacitor.

Consider the voltage waveforms shown in Figure 5-5. The circuit input terminal is normally at ground level (*i.e.*, before the signal pulse is applied). The other terminal of C_c (the transistor base terminal) is at V_{BE} . Therefore, the capacitor charge is normally V_{BE} , positive on the RHS, as

illustrated on the diagram. When the input pulse with an amplitude of $-V_i$ is applied, the transistor base is pulled down to $-(V_i - V_{BE})$. The capacitor immediately commences to charge via R_B , so that the negative pulse appearing at the base has tilt, as shown. The tilt must not be so great that V_B rises above ground; otherwise the transistor may switch *on* before the signal pulse has ended. The capacitor charging current is approximately constant, and can be calculated by dividing the voltage across R_B by R_B :

$$I \simeq \frac{V_{CC} - V_i}{R_B}$$

If V_B is allowed to rise to -0.5 V, then ΔV is $(V_i - V_{BE}) - 0.5$ V. When time t is equal to the pulse width, the simple constant current capacitor equation, Equation (2-7), may be employed. From that equation,

$$C = \frac{It}{\Delta V}$$

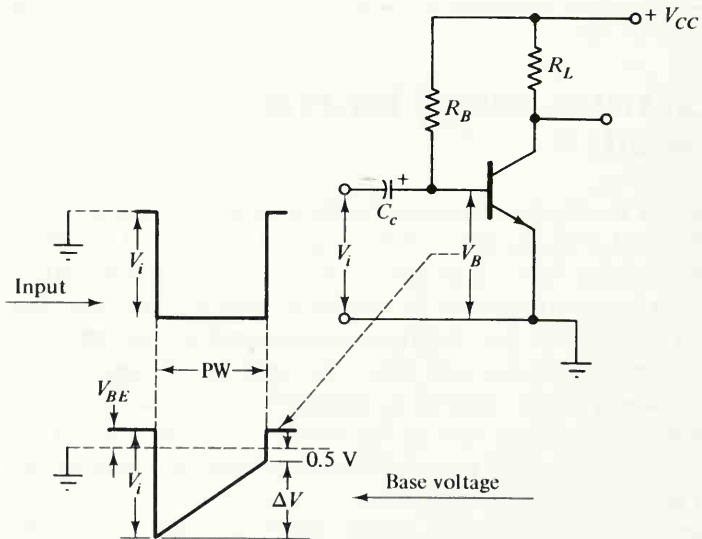


FIGURE 5-5. Normally-on capacitor-coupled inverter circuit using an *npn* transistor.

EXAMPLE 5-4

The capacitor-coupled inverter circuit of Figure 5-5 has a signal pulse input of -4 V amplitude and $PW = 1\text{ ms}$. V_{CC} is to equal 10 V and I_C is to be 10 mA . Using a 2N3904 transistor, design a suitable circuit.

solution

$$R_L = \frac{V_{CC} - V_{CE(\text{sat})}}{I_C} = \frac{10\text{ V} - 0.2\text{ V}}{10\text{ mA}}$$

$$= 980\Omega \quad (\text{use a } 1\text{ k}\Omega \text{ standard value})$$

From the 2N3904 data sheet, $h_{FE(\text{min})} = 100$ at $I_C = 10\text{ mA}$:

$$I_{B(\text{min})} = \frac{I_C}{h_{FE(\text{min})}}$$

$$= \frac{10\text{ mA}}{100}$$

$$= 100\mu\text{A}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_{B(\text{min})}} = \frac{10\text{ V} - 0.7\text{ V}}{100\mu\text{A}}$$

$$= 93\text{ k}\Omega \quad (\text{use } 82\text{ k}\Omega \text{ standard value})$$

$$\Delta V = V_i - V_{BE} - 0.5\text{ V}$$

$$= 4\text{ V} - 0.7\text{ V} - 0.5\text{ V}$$

$$= 2.8\text{ V}$$

Capacitor charging current,

$$I \approx \frac{V_{CC} - V_i}{R_B}$$

$$= \frac{10\text{ V} - (-4\text{ V})}{82\text{ k}\Omega}$$

$$= 0.17\text{ mA}$$

$$t = PW = 1\text{ ms}$$

$$C_c = \frac{I \times t}{V} = \frac{0.17 \text{ mA} \times 1 \text{ ms}}{2.8 \text{ V}} = 0.06 \mu\text{F}$$

(use a $0.06 \mu\text{F}$ standard value)

Although the calculation of C_c in Example 5-4 assumes that the input pulse is negative with respect to ground, actually the pulse could be negative with respect to any other initial level. For example, the pulse could go from $+8 \text{ V}$ to $+4 \text{ V}$, and have exactly the same effect on the inverter circuit as a completely negative pulse. The calculated value of C_c would be the same as in the example.

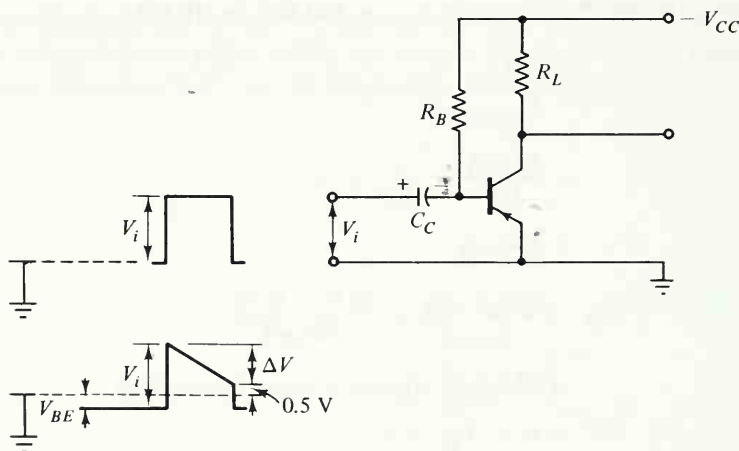


FIGURE 5-6. Normally-on capacitor-coupled inverter circuit using a *pnp* transistor.

The circuit in Figure 5-6 is similar to that in Figure 5-5. Since the transistor is now *pnp*, however, all voltage polarities are inverted. For the *pnp* transistor to switch *off*, a positive input pulse must be applied. Also, the voltage at the transistor base should be maintained positive until the end of the pulse width. Design procedure for this circuit is exactly the same as for the *npn* inverter.

The converse of the circuit in Figure 5-5 is the normally *off* transistor circuit shown in Figure 5-7. Here, R_B connects the base and emitter terminals, and thus keeps V_{BE} equal to zero until a positive-going input pulse is applied.

When no input pulse is present, the only current that flows through R_B is the reverse saturation current I_{CO} . The voltage drop across R_B must

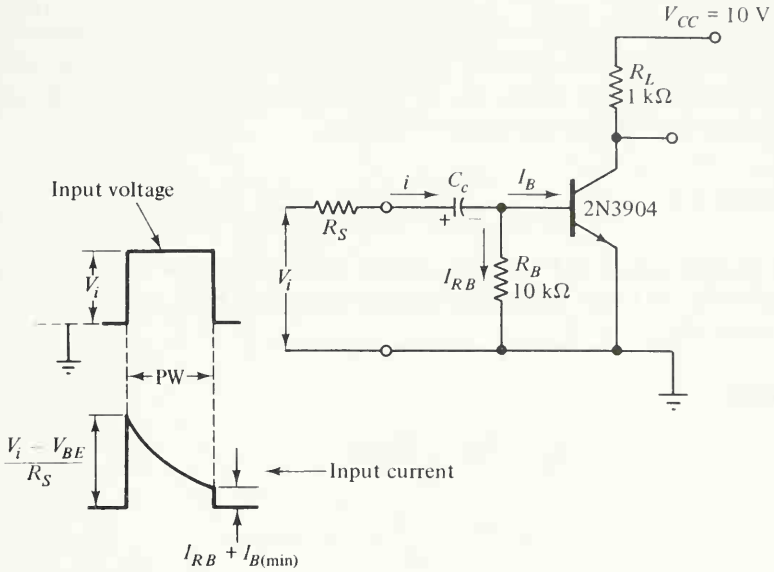


FIGURE 5-7. Normally-off capacitor-coupled inverter circuit.

not be so large as to partially forward bias the base-emitter junction; otherwise there may be a small collector current flow. With a maximum I_{CO} of $10\text{ }\mu\text{A}$ (at highest ambient temperature), and $V_{RB} = 0.1\text{ V}$, a typical value for R_B is $0.1\text{ V}/10\text{ }\mu\text{A} = 10\text{ k}\Omega$.

In the circuit of Figure 5-7, C_c starts at zero volts and charges via the signal source resistance while the input pulse is present. The charging current i_c flows through R_B and the transistor base terminal. This current begins at $i_c = (V_i - V_{BE})/R_S$, and then falls off as C_c becomes charged. At the end of the input pulse, i_c must still be large enough to provide current through R_B and sufficient base current to saturate the transistor. By use of the equation for capacitor charging current, Equation (2-4) (Chapter 2),

$$i_c = I e^{\frac{-t}{CR}}$$

an expression for the coupling capacitor can be determined:

$$\begin{aligned} \frac{I}{i_c} &= e^{\frac{t}{CR}} \\ \frac{t}{CR} &= \ln \frac{I}{i_c} \\ C_c &= \frac{t}{R \ln(I/i_c)} \end{aligned}$$

In this expression, R is the signal source resistance R_S , t is the input pulse width, I is the initial charging current, and i_c is the charging current at the end of the signal pulse. As in the circuit of Example 5-4, the input pulse does not have to start at ground level.

EXAMPLE 5-5

The inverter circuit in Figure 5-7 has an input pulse of 4 V amplitude and pulse width of 1 ms. The signal source resistance R_S is 1 k Ω . Determine the value of C_c .

solution

$$\begin{aligned} I_C &= \frac{V_{CC} - V_{CE(\text{sat})}}{R_L} \\ &= \frac{10 \text{ V} - 0.2 \text{ V}}{1 \text{ k}\Omega} = 9.8 \text{ mA} \\ I_{B(\text{min})} &= \frac{I_C}{h_{FE(\text{min})}} = \frac{9.8 \text{ mA}}{100} = 98 \mu\text{A} \\ I_{RB} &= \frac{V_{BE}}{R_B} = \frac{0.7 \text{ V}}{10 \text{ k}\Omega} = 70 \mu\text{A} \end{aligned}$$

At the end of the pulse,

$$\begin{aligned} i_c &= I_{B(\text{min})} + I_{RB} \\ &= 98 \mu\text{A} + 70 \mu\text{A} \\ &= 168 \mu\text{A} \end{aligned}$$

The initial charging current,

$$\begin{aligned} I &= \frac{V_i - V_{BE}}{R_S} \\ &= \frac{4 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = 3.3 \text{ mA} \\ t &= \text{PW} = 1 \text{ ms} \\ C_c &= \frac{t}{R_S \ln(I/i_c)} = \frac{1 \text{ ms}}{1 \text{ k}\Omega \ln(3.3 \text{ mA}/168 \mu\text{A})} \\ &= 0.33 \mu\text{F} = \text{standard value} \end{aligned}$$

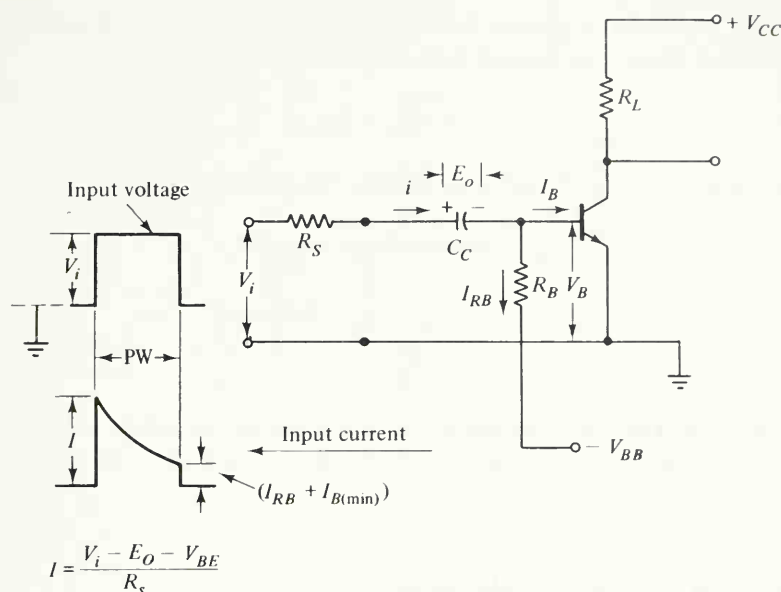


FIGURE 5-8. Normally-off capacitor-coupled inverter circuit with negative bias voltage.

Another normally-off capacitive coupled inverter circuit is shown in Figure 5-8. In this case the transistor base is biased to a negative voltage $-V_{BB}$, so that the base-emitter junction is reverse biased. The capacitor C_c now has an initial charge of $E_o = V_{BB}$, with the polarity shown. When a positive input voltage V_i is applied, the transistor base voltage is

$$V_B = V_i - iR_s - E_o$$

Thus, the transistor will not switch on unless V_i is greater than $(iR_s + E_o)$.

When the transistor switches on, its base voltage becomes $+V_{BE}$ above ground level. The current through R_B now is

$$I_{RB} = \frac{V_{BE} - V_{BB}}{R_B}$$

Also, the transistor minimum base current remains

$$I_{B(\min)} = \frac{I_C}{h_{FE(\min)}}$$

For the transistor to remain conducting during the input PW, the input (capacitor) current at the end of the PW must be at least

$$i_c = I_{RB} + I_{B(\min)}$$

The initial capacitor charging current for this circuit is

$$\begin{aligned} I &= \frac{\text{initial voltage across } R_s}{R_s} \\ &= \frac{V_i - E_O - V_{BE}}{R_s} \end{aligned}$$


When i_c and I are determined as explained above, the value of C_c for the circuit in Figure 5-8 can be determined in the same way as for Example 5-5.

5-3 JFET INVERTER CIRCUITS


The direct-coupled inverter circuit illustrated in Figure 5-9(a) has an output which goes approximately from ground to V_{DD} . When the input signal is at ground level, the device is *on*. Drain current I_D flows, causing a voltage drop of almost V_{DD} across R_L . When V_i is negative, the device is biased *off* and the output goes to V_{DD} . To ensure that the FET is switched *off*, the negative input pulse must exceed the device *pinchoff* voltage V_p . For a 2N5459 JFET (see data sheet in Appendix 1-9) the *pinchoff* voltage is designated *gate-source cutoff voltage* $V_{GS(\text{off})}$. For the 2N5459, $V_{GS(\text{off})}$ is a maximum of 8 V. Therefore, the input pulse to the circuit of Figure 5-9(a) must exceed -8 V, if a 2N5459 is employed. The only function served by R_G in Figure 5-9(a) is to limit the gate current in the event that the input voltage goes positive. Typically R_G is selected as $1\text{ M}\Omega$.

In Figure 5-9(b) a capacitor-coupled JFET inverter circuit is shown. Again, R_G is typically $1\text{ M}\Omega$, this time to present a high input impedance to signals. The circuit shown has the gate biased to the same potential as the source terminal; therefore the FET normally is *on*. To switch the device *off*, the input signal amplitude must exceed V_p . Since the input resistance of the FET circuit is very high, the charging current to the coupling capacitor is extremely small, so C_c can be quite a small capacitor.

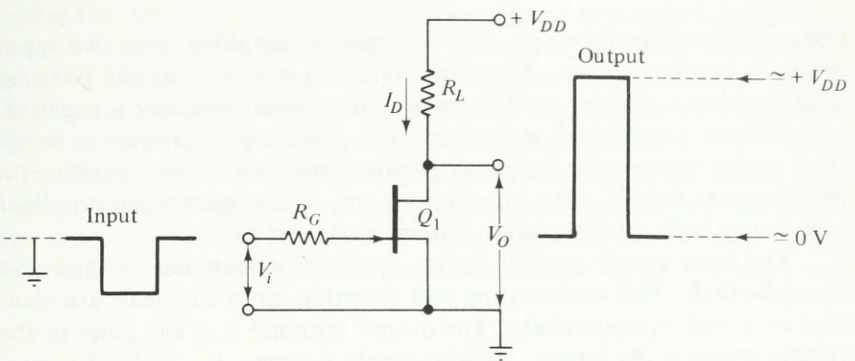
A normally *off* JFET inverter circuit is shown in Figure 5-9(c). Here, the gate is biased to a negative dc level to keep the FET *off* when no signal is present. The device *pinchoff* voltage must be exceeded by V_G . Again, C_c can be a very small capacitor.



(a) Direct-coupled inverter

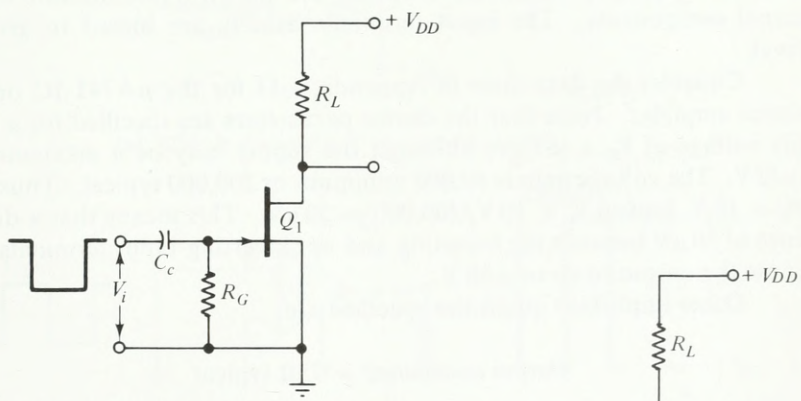

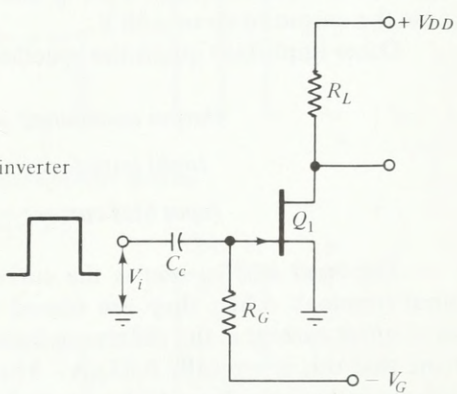(b) Normally on capacitive-coupled inverter



(c) Normally off capacitive-coupled circuit

FIGURE 5-9. JFET inverter circuits.

5-4 IC OPERATIONAL AMPLIFIER INVERTER

The *operational amplifier* is a very high gain dc amplifier with two input terminals and one output. One input terminal is known as the *inverting input*, because a positive-going signal at this input produces a negative-going output voltage, and *vice versa*. The other input terminal is designated as the *noninverting input*. A positive-going signal here produces a positive-going output. The input impedance of the operational amplifier is extremely high, and the output impedance is very low.

The basic circuit symbol for an operational amplifier is shown in Figure 5-10(a). The noninverting and inverting input terminals are identified as + and -, respectively. The output terminal is at the point of the triangle opposite the inputs. Power supply voltages V_{CC} and $-V_{EE}$ normally are symmetrical with respect to ground. A typical supply voltage is ± 15 V. Frequently, additional terminals are shown for connection of external components. The input terminals usually are biased to ground level.

Consider the data sheet in Appendix 1-11 for the $\mu A741$ IC operational amplifier. Note that the device parameters are specified for a supply voltage of $V_S = \pm 15$ V, although the supply may be a maximum of ± 22 V. The voltage gain is 50,000 minimum or 200,000 typical. Thus, for $V_o = 10$ V, typical $V_i = 10 \text{ V}/200,000 = 50 \mu\text{V}$. This means that a difference of $50 \mu\text{V}$ between the inverting and noninverting input terminals will cause the output to go to ± 10 V.

Other important quantities specified are:

$$\text{Output impedance} = 75 \Omega \text{ typical}$$

$$\text{Input impedance} = 1 \text{ M}\Omega \text{ typical}$$


$$\text{Input bias current} = 0.2 \mu\text{A typical}$$

The *input bias current* is the current flowing into each of the two input terminals when they are biased to the same voltage level. The *input offset current* is the difference between the two input bias currents. Note that this is typically $0.03 \mu\text{A}$. The *input offset voltage* is the voltage difference that may have to be applied between the two input terminals in order to adjust the output level to exactly zero. For the $\mu A741$, this quantity is typically 1 mV. Note that an illustration on the $\mu A741$ data sheet shows an arrangement by which the offset voltage can be adjusted to zero.


In switching applications it is important to note that the typical *output voltage swing* for the $\mu A741$ is ± 14 V when a ± 15 V supply is used.

Also, note that this output voltage swing may be a minimum of ± 10 V if a $2\text{ k}\Omega$ load is connected to the output terminals of the amplifier. An input voltage of approximately $V_i = V_o/(\text{voltage gain})$ is required to drive the output to its extreme levels. For a ± 15 V supply, $V_i \approx 15\text{ V}/200,000 = 75\text{ }\mu\text{V}$. This is the voltage difference between the two input terminals. The actual input voltage can be very much higher than this minimum. The data sheet specifies a typical input voltage range of ± 13 V.

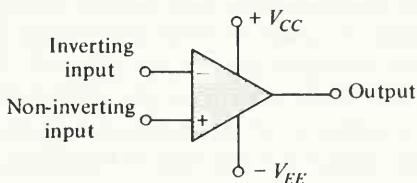
The *slew rate*, particularly important in switching applications, is the rate of change of output voltage, or the speed with which the output changes. For the $\mu\text{A}741$, the slew rate is specified as $0.5\text{ V}/\mu\text{s}$. Thus, a time of $1\text{ }\mu\text{s}$ is required for the output to change by 0.5 V when a step



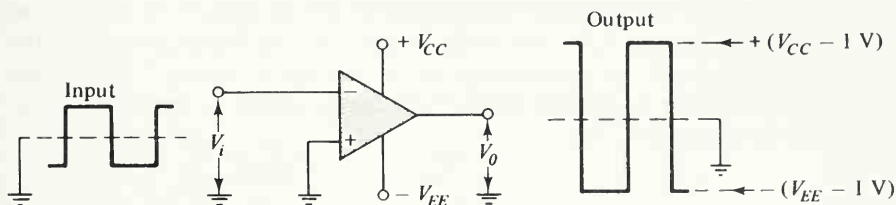(a) Circuit symbol for IC operational amplifier



(b) IC operational amplifier inverter

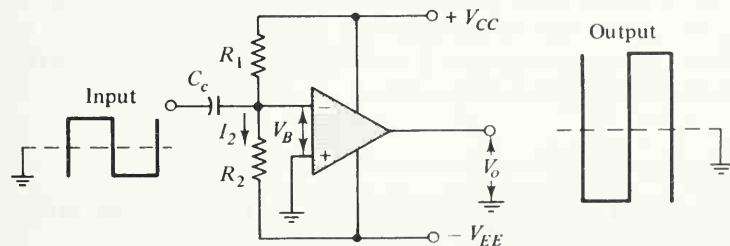

(c) Capacitive coupled IC inverter

FIGURE 5-10. IC operational amplifier circuit symbol and IC inverter circuits.

input is applied. The output moves from -10 V to $+10\text{ V}$ in a time of $20\text{ V}/0.5\text{ V} = 40\text{ }\mu\text{s}$. In an application for which the slew rate of the $\mu\text{A}741$ is too slow, another amplifier must be selected. The $\mu\text{A}715$, for example, has a slew rate of $100\text{ V}/\mu\text{s}$.

An IC operational amplifier employed as an inverter is shown in Figure 5-10(b). The noninverting terminal is connected directly to ground, and the input pulse is directly connected to the inverting input terminal. When V_i is more than about $75\text{ }\mu\text{V}$ below ground level, the output voltage is approximately $V_{CC} - 1\text{ V}$. At $V_i > 75\text{ }\mu\text{V}$ above ground, the output becomes approximately $-(V_{EE} - 1\text{ V})$. Thus an IC operational amplifier can be directly employed as an inverter without using additional components.

Sometimes an IC inverter must have a bias voltage provided at its inverting input terminal, in order to hold the output at its positive or negative extreme when no input signals are present. Such a circuit is shown in Figure 5-10(c). If V_B is positive, the output is negative; if V_B is negative, the output is positive. If the inverting terminal were grounded via a resistance, the dc output voltage cannot be predicted as either positive or negative. Normally, V_B should be about $\pm 0.5\text{ V}$, so that a small input signal can easily drive the inverter output from one maximum level to the other.

To design the capacitor-coupled inverter, R_2 should be selected so that the bias current I_2 is very much larger than the input current of the device. Then, R_1 is determined as $R_1 \simeq (V_{CC} - V_B)/I_2$. C_c should be selected for an acceptable level of tilt on the signal at the inverting input terminal (see Sec. 5-2).

EXAMPLE 5-6

Using a $\mu\text{A}741$ IC operational amplifier, design an inverter to provide an output of $V_o \simeq \pm 11\text{ V}$. The output normally should be negative when no input is present. The input voltage is a $\pm 6\text{ V}$ square wave with $f = 1\text{ kHz}$. Calculate the rise time of the output voltage.

solution

The circuit is shown in Figure 5-10(c). For $V_o \simeq \pm 11\text{ V}$, the supply should be $\pm 12\text{ V}$.

$$V_{CC} = +12\text{ V}$$

$$V_{EE} = -12\text{ V}$$

To maintain a negative dc output, V_B must be positive. Take $V_B \simeq +0.5 \text{ V}$.

$$\begin{aligned} V_{R2} &= V_B - V_{EE} \\ &= 0.5 \text{ V} - (-12 \text{ V}) \\ &= 12.5 \text{ V} \end{aligned}$$

The maximum input bias current is 500 nA, as taken from $\mu\text{A}741$ data sheet in Appendix 1-11.

$$I_2 \gg 500 \text{ nA}$$

Make

$$\begin{aligned} I_2 &= 100 \times 500 \text{ nA} \\ &= 50 \mu\text{A} \\ R_2 &= \frac{V_{R2}}{I_2} = \frac{12.5 \text{ V}}{50 \mu\text{A}} \\ &= 250 \text{ k}\Omega \quad (\text{use } 220 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

I_2 becomes

$$\begin{aligned} \frac{V_{R2}}{R_2} &= \frac{12.5 \text{ V}}{220 \text{ k}\Omega} = 54.5 \mu\text{A} \\ R_1 &= \frac{V_{CC} - V_B}{I_2} \\ &= \frac{12 \text{ V} - 0.5 \text{ V}}{54.5 \mu\text{A}} \\ &= 211 \text{ k}\Omega \quad (\text{use } 180 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

Note that use of a *smaller-than-calculated* value of R_1 ensures that V_B is larger than is required for the output to be negative.

During the pulse time, C_C charges via R_1 and R_2 , so that the input waveform has *tilt* as it appears at the inverting input terminal. For a $\pm 6 \text{ V}$ input, a tilt of two or three volts will have no effect on the inverter operation.

Let $\Delta V_C = 2 \text{ V}$.

$$\begin{aligned}
 \text{Input resistance} &= R_1 \parallel R_2 \\
 &= 180 \text{ k}\Omega \parallel 220 \text{ k}\Omega \\
 &= 99 \text{ k}\Omega
 \end{aligned}$$

For a $\pm 6 \text{ V}$ input, the initial input current I is calculated as

$$\begin{aligned}
 I &= \frac{6 \text{ V}}{99 \text{ k}\Omega} \\
 &\simeq 60.6 \mu\text{A}
 \end{aligned}$$

For I assumed constant;

$$\begin{aligned}
 C &= \frac{It}{\Delta V} \\
 I &= 60.6 \mu\text{A}, \quad \Delta V = 2 \text{ V}, \quad t = \frac{1}{2f} \\
 t &= \frac{1}{2 \times 1 \text{ kHz}} = 500 \mu\text{s}
 \end{aligned}$$

Thus,

$$\begin{aligned}
 C &= \frac{60.6 \mu\text{A} \times 500 \mu\text{s}}{2 \text{ V}} \\
 &= 1.515 \times 10^{-8} \\
 &\simeq 0.015 \mu\text{F} \quad (\text{standard capacitance value})
 \end{aligned}$$

The time taken for the output to go from $+11 \text{ V}$ to -11 V is expressed as:

$$\begin{aligned}
 t &= \frac{22 \text{ V}}{\text{Slew rate}} \\
 &= \frac{22 \text{ V}}{0.5 \text{ V}/\mu\text{s}} = 44 \mu\text{s}
 \end{aligned}$$

REVIEW QUESTIONS AND PROBLEMS

- 5-1 Sketch the complete circuit of a direct-coupled bipolar transistor inverter and explain the function of each component. Show the

output waveform when the following inputs are applied: (a) pulse wave, (b) square wave, (c) sine wave.

- 5-2 Show two methods of protecting a transistor base-emitter voltage against excessive reverse input voltages.
- 5-3 Design a direct-coupled transistor inverter circuit using a 2N3903 transistor. For this circuit, V_{CC} is 9 V, the input is a ± 5 V square wave, and $I_C = 10$ mA.
- 5-4 If, in the circuit of Problem 5-3, a 200 pF speed-up capacitor is used, determine the maximum input signal frequency that may be employed.
- 5-5 A direct-coupled transistor inverter using a 2N3904 transistor has an input square wave of ± 9 V, and $V_{CC} = 20$ V. An external load of 220 k Ω is connected to the inverter output terminals. Design a suitable circuit and determine the amplitude of the output voltage.
- 5-6 Sketch the circuit of a normally-on capacitor-coupled inverter using (a) an *npn* transistor and (b) a *pnp* transistor. In each case show the input voltage and current waveforms, and explain the operation of the circuit.
- 5-7 Repeat Problem 5-6 for a normally-off capacitor-coupled inverter.
- 5-8 A normally-on transistor inverter has a capacitor-coupled pulse input signal with PA = -3 V and PW = 600 μ s; $V_{CC} = 12$ V and I_C is to be 1 mA. Design a suitable circuit.
- 5-9 The conditions specified in Problem 5-6 can be applied to a normally-off inverter if the pulse amplitude is +3 V. Design the circuit, taking the signal source resistance as 1 k Ω .
- 5-10 A normally-off inverter circuit using a 2N4418 transistor has $V_{CC} = 9$ V, and $V_{BB} = -3$ V. I_C is to be approximately 10 mA, and the input pulse has PA = 6 V, PW = 500 μ s, and $R_s = 600 \Omega$. Design the circuit.
- 5-11 Sketch the circuits of direct-coupled and capacitor-coupled JFET inverter circuits. Explain the operation of the circuits and discuss their advantages and disadvantages compared to bipolar inverters.
- 5-12 Using a μ A741 IC operational amplifier, design an inverter that will provide an output of $V_o \simeq \pm 14$ V. The output normally should be positive when no input is applied. The input voltage is a ± 4 V square wave with $f = 500$ Hz. Calculate the approximate rise time of the output voltage.

Chapter 6

The Schmitt Trigger Circuit

INTRODUCTION

Essentially, a SCHMITT TRIGGER CIRCUIT is a fast-operating voltage level detector. When the input voltage arrives at the upper or lower triggering levels, the output voltage rapidly changes level. The circuit operates from almost any input waveform and always gives a pulse-type output. Transistor Schmitt trigger circuits can be designed to trigger at specified upper and lower levels of input voltage. An IC operational amplifier circuit can also be employed as a Schmitt trigger circuit.

6-1 OPERATION OF SCHMITT TRIGGER CIRCUIT

A transistor Schmitt trigger circuit is shown in Figure 6-1(a). The figure shows that transistors Q_1 and Q_2 have a common emitter resistor R_E .

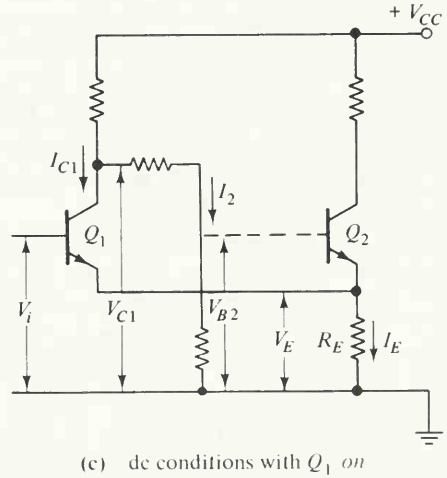
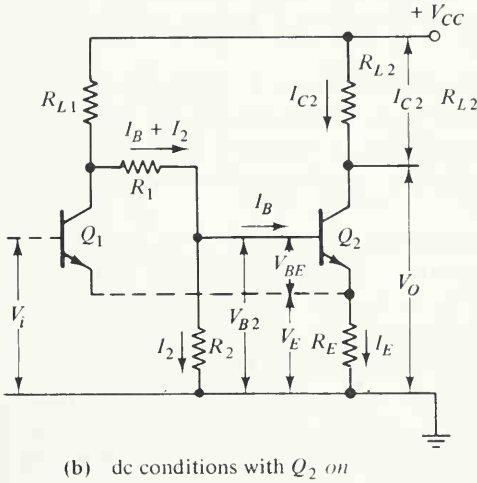
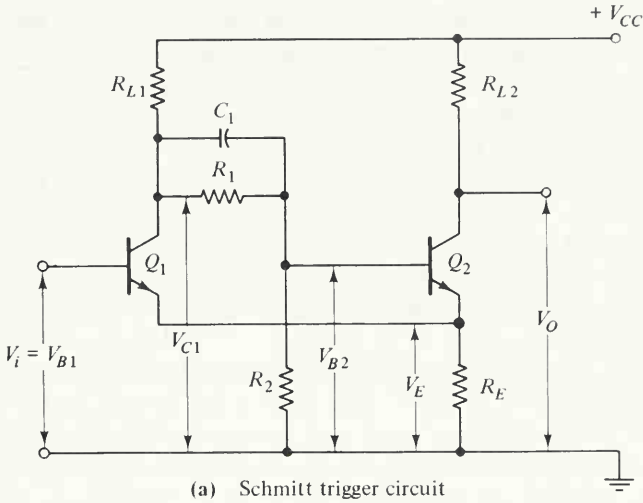


FIGURE 6-1. Schmitt trigger circuit and dc conditions with Q_2 on and with Q_1 on.

The Q_2 base voltage, V_{B2} , is derived via the potential divider (R_1 and R_2) from the collector of Q_1 . Transistors Q_1 and Q_2 have load resistances R_{L1} and R_{L2} , respectively. The arrangement is such that when transistor Q_1 is on, transistor Q_2 is off, and for Q_2 to switch on, Q_1 must switch off.

To understand the operation of this type of circuit, first consider the dc conditions when Q_1 is off. When it is off, Q_1 can be regarded as

an open circuit; therefore, it can be left out of the circuit as is shown in Figure 6-1(b). The Q_2 base voltage now is derived from V_{CC} via a potential divider consisting of R_1 , R_2 , and R_{L1} . Thus, Q_2 is *on* and a collector current I_{C2} flows, producing a voltage drop across R_{L2} . Thus the output voltage is $(V_{CC} - I_{C2}R_{L2})$.

If, as in Figure 6-1(c), Q_1 is now triggered *on*, the emitter voltage becomes $V_E = V_i - V_{BE}$. Also, the collector current I_{C1} causes a voltage drop across R_{L1} , in turn causing V_{B2} to fall below the level of V_E . Thus, when Q_1 is *on*, Q_2 is biased *off* and I_{C2} becomes zero. At this point there is no longer any significant drop across R_{L2} , and the output voltage is approximately V_{CC} .

Now, reconsider the conditions illustrated in Figure 6-1(b). It is seen that with Q_2 *on*, $V_E = V_{B2} - V_{BE}$. This is the voltage at the emitter terminal of both transistors since they are connected together. Transistor Q_1 will not switch *on* until its base voltage becomes greater than V_E . In fact, Q_1 switches *on* approximately at $V_i = V_E + V_{BE}$. Obviously, if V_i is suddenly made greater than this level, Q_1 would switch *on* rapidly. The lowest level of V_i that causes Q_1 to switch *on* is known as the *upper trigger point* (UTP) for the circuit.

At the moment that Q_1 begins to switch *on* it starts to pull the common emitter voltage up, the flow of I_C causes V_{C1} to fall and, consequently, V_{B2} falls. Thus, as Q_1 switches *on*, it causes a rapid reduction in V_{BE2} . This effect, known as *regeneration*, produces a very rapid switch-over from Q_2 *on* to Q_1 *on*.

Now consider the process of switching from Q_1 *on* to Q_2 *on*. Refer to Figure 6-1(c). With Q_1 *on*, $I_E = (V_i - V_{BE})/R_E$. Thus, a reduction in V_i also reduces I_E , and since $I_C \simeq I_E$, I_{C1} also becomes smaller. The voltage drop across R_{L1} is approximately $(I_{C1}R_{L1})$, and the collector voltage of Q_1 is approximately $(V_{CC} - I_{C1}R_{L1})$. Therefore, when V_i is reduced, I_{C1} becomes smaller causing V_{C1} to rise. In turn, the base voltage V_{B2} of Q_2 rises. If V_i is reduced by a very small amount, the resultant small increase in V_{B2} may leave Q_2 base still below the level of its emitter voltage. In fact, Q_2 switches *on* again only when V_{B2} and V_i become equal. The input voltage at which this occurs is known as the *lower trigger point* (LTP).

In the changeover from Q_1 *on* to Q_2 *on*, regeneration again occurs. When Q_2 starts to switch *on*, it causes Q_1 to begin to switch *off* because of the rise in the common emitter voltage. Q_1 switching *off* helps Q_2 to turn *on*. Again, the changeover occurs very rapidly.

Speed-up capacitor C_1 [Figure 6-1(a)] is provided solely to improve the circuit switching speed. The effect is exactly as explained in Sec. 4-4.

Figure 6-2 shows the effects of various input waveforms on the Schmitt trigger circuit. In each case the output is $(V_{CC} - I_{C2}R_{L2})$ until

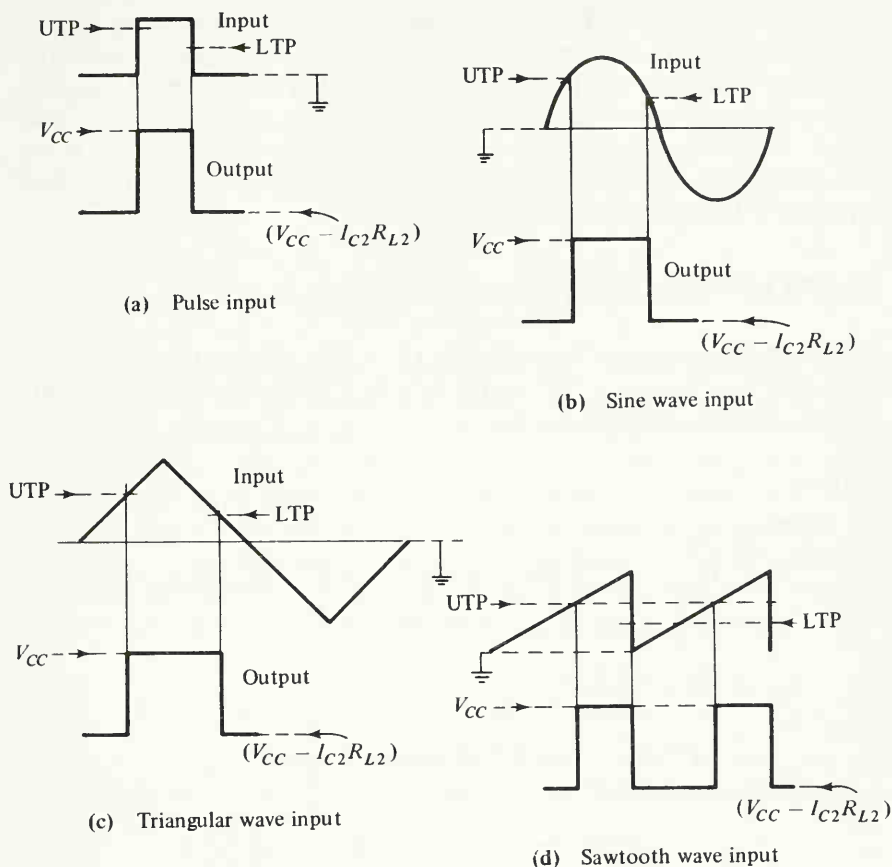


FIGURE 6-2. Schmitt trigger circuit outputs for various input waveforms.

the upper trigger point is reached. Then with Q_2 switched *off*, the output becomes approximately V_{CC} . When the signal input falls to the LTP, the output again drops to $(V_{CC} - I_{C2}R_{L2})$ as Q_2 switches *on*. The Schmitt trigger circuit is seen to be essentially a voltage level detector, capable of producing a fast-moving output when either a slow- or fast-moving input arrives at the trigger points.

6-2 DESIGNING FOR A GIVEN UPPER TRIGGER POINT

Design of any circuit starts from a specification. For the Schmitt trigger circuit the most important parameters are the upper and lower trigger

Taking Q_2 as saturated, $V_{CE(\text{sat})} = 0.2 \text{ V}$ typically. The voltage drop across $R_{L2} = I_C R_{L2}$ and

$$\begin{aligned} I_C R_{L2} &= V_{CC} - V_E - V_{CE(\text{sat})} \\ &= 12 \text{ V} - 4.3 \text{ V} - 0.2 \text{ V} \\ &= 7.5 \text{ V} \end{aligned}$$

$$R_{L2} = \frac{7.5 \text{ V}}{I_C} = \frac{7.5 \text{ V}}{2 \text{ mA}} = 3.75 \text{ k}\Omega \quad (\text{use } 3.9 \text{ k}\Omega \text{ standard value})$$

Potential divider (R_1 and R_2), together with R_{L1} , must provide a stable bias voltage V_{B2} for Q_2 (Figure 6-3). However, R_1 and R_2 must be large enough to avoid overloading R_{L1} . For example, if R_1 and R_2 were made smaller than R_{L1} , then Q_1 collector current would have very little effect on V_{B2} when Q_1 is switched *on*. If R_1 and R_2 are made very large, I_{B2} will cause a large voltage drop across R_1 when Q_2 is switched *on*. Therefore, R_1 and R_2 must be kept as small as possible, but they must be several times larger than R_{L1} . A good rule-of-thumb here is to take the value of $I_2 \cong \frac{1}{10} I_{E2}$. Then calculate R_2 as V_{B2}/I_2 .

$$I_2 \cong \frac{1}{10} I_E = \frac{1}{10} \times 2 \text{ mA} = 0.2 \text{ mA}$$

$$R_2 = \frac{V_{B2}}{I_2} = \frac{5 \text{ V}}{0.2 \text{ mA}} = 25 \text{ k}\Omega \quad (\text{use } 22 \text{ k}\Omega \text{ standard value})$$

$$I_2 \text{ now becomes } \frac{5 \text{ V}}{22 \text{ k}\Omega} = 0.227 \text{ mA}.$$

$$I_{B2} = \frac{I_{C2}}{h_{FE(\text{min})}} = \frac{2 \text{ mA}}{100} = 20 \mu\text{A}$$

$$I_{B2} + I_2 = 20 \mu\text{A} + 0.227 \text{ mA} = 0.247 \text{ mA}$$

$$\begin{aligned} R_{L1} + R_1 &= \frac{V_{CC} - V_{B2}}{I_2 + I_{B2}} \\ &= \frac{12 \text{ V} - 5 \text{ V}}{0.247 \text{ mA}} \\ &= 28.3 \text{ k}\Omega \end{aligned}$$

When the LTP is not specified, R_{L1} may be made equal to R_{L2} . *This cannot be done when the circuit is to be designed for a given LTP level.*

$$R_{L1} = R_{L2} = 3.9 \text{ k}\Omega$$

$$\begin{aligned} R_1 &= (R_{L1} + R_1) - R_{L1} \\ &= 28.3 \text{ k}\Omega - 3.9 \text{ k}\Omega \\ &= 24.4 \text{ k}\Omega \quad (\text{use } 22 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

6-3 ANALYZING FOR UTP AND LTP

When standard resistor values are substituted for the actual calculated values, the performance of the circuit will be affected. The UTP will not be exactly as specified. To find the new UTP level and to determine the LTP, the circuit must be analyzed.

EXAMPLE 6-2

Using the selected standard component values, analyze the circuit designed in Example 6-1. Determine the actual UTP.

solution

With Q_1 off and Q_2 on, the potential divider (R_{L1} , R_1 , and R_2) is replaced by its open circuit voltage V and its internal resistance (R_B) (see Figure 6-4).

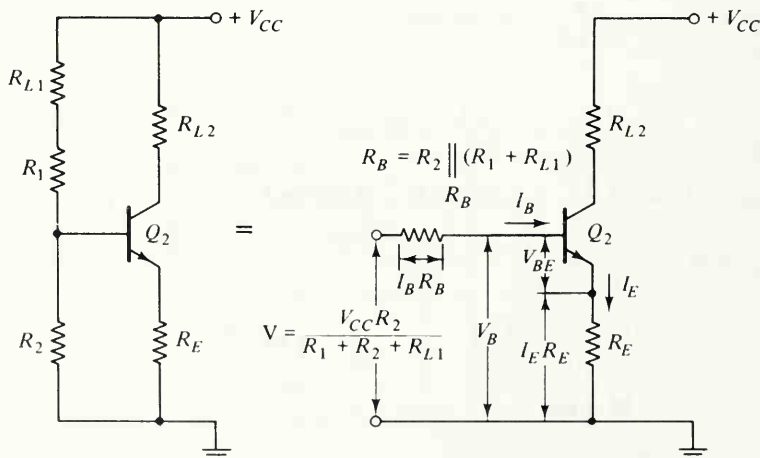


FIGURE 6-4. Circuit analysis to determine UTP.

$$V = \frac{V_{CC} \times R_2}{R_{L1} + R_1 + R_2} = \frac{12 \text{ V} \times 22 \text{ k}\Omega}{3.9 \text{ k}\Omega + 22 \text{ k}\Omega + 22 \text{ k}\Omega} = 5.51 \text{ V}$$

$$R_B = R_2 \parallel (R_1 + R_{L1}) = 22 \text{ k}\Omega \parallel (22 \text{ k}\Omega + 3.9 \text{ k}\Omega) = 11.9 \text{ k}\Omega$$

$$V = I_B R_B + V_{BE} + I_E R_E$$

$$I_E = I_B(1 + h_{FE})$$

$$\therefore V = I_B R_B + V_{BE} + I_B R_E(1 + h_{FE})$$

and

$$\begin{aligned} I_B &= \frac{V - V_{BE}}{R_B + R_E(1 + h_{FE})} \\ &= \frac{5.51 \text{ V} - 0.7 \text{ V}}{11.9 \text{ k}\Omega + 2.2 \text{ k}\Omega(1 + 100)} \\ &= 20.5 \mu\text{A} \end{aligned}$$

$$\begin{aligned} \text{UTP} = V_B &= V - I_B R_B \\ &= 5.51 - (20.5 \mu\text{A} \times 11.9 \text{ k}\Omega) \\ &= 5.27 \text{ V} \end{aligned}$$

EXAMPLE 6-3

Using the selected standard value components, determine the LTP for the circuit designed in Example 6-1.

solution

At the LTP, Q_1 is *on* and Q_2 is *off*. Such a circuit is shown in Figure 6-5. The LTP occurs when V_{B2} becomes equal to V_i (that is, at $V_{B1} = V_{B2}$).

$$V_{B1} = V_{B2} = V_i$$

$$I_E = \frac{V_i - V_{BE}}{R_E} \simeq I_{C1}$$

$$I_1 = \frac{V_{B2}}{R_2} = \frac{V_i}{R_2}$$

$$V_{C1} = I_2(R_1 + R_2) = \frac{V_i}{R_2} (R_1 + R_2)$$

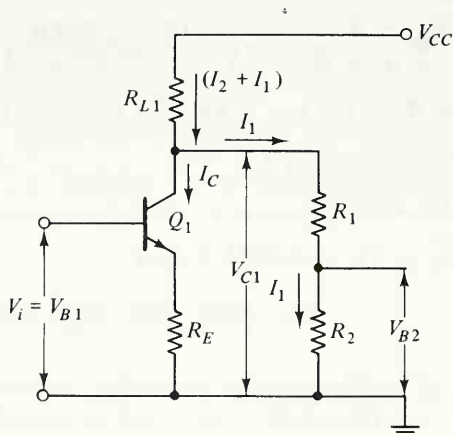


FIGURE 6-5. Circuit analysis to determine LTP.

$$\begin{aligned}
 V_{CC} &= V_C + R_{L1}(I_{C1} + I_1) \\
 &= \overbrace{I_1(R_1 + R_2)} + R_{L1}(I_{C1} + I_1) \\
 &= \frac{V_i}{R_2}(R_1 + R_2) + R_{L1} \left[\frac{V_i - V_{BE}}{R_E} + \frac{V_i}{R_2} \right] \\
 &= \frac{V_i}{R_2}(R_1 + R_2) + \frac{R_{L1}V_i}{R_E} - \frac{R_{L1}V_{BE}}{R_E} + \frac{R_{L1}V_i}{R_2} \\
 &= V_i \left[\frac{R_1 + R_2}{R_2} + \frac{R_{L1}}{R_E} + \frac{R_{L1}}{R_2} \right] - \frac{R_{L1}V_{BE}}{R_E} \\
 12 \text{ V} &= V_i \left[\frac{22 \text{ k}\Omega + 22 \text{ k}\Omega}{22 \text{ k}\Omega} + \frac{3.9 \text{ k}\Omega}{2.2 \text{ k}\Omega} + \frac{3.9 \text{ k}\Omega}{22 \text{ k}\Omega} \right] - \frac{3.9 \text{ k}\Omega \times 0.7 \text{ V}}{2.2 \text{ k}\Omega} \\
 &= V_i[3.95] - 1.24 \\
 V_i &= 3.35 \text{ V} = \text{LTP}
 \end{aligned}$$

Expressions for upper and lower trigger points can be usefully applied when analyzing a Schmitt trigger circuit. From Example 6-2,

$$\begin{aligned}
 \text{UTP} &= V - I_B R_B \\
 &= V - \frac{(V - V_{BE})R_B}{R_B + R_E(1 + h_{FE})} \\
 &= \frac{V_{CC}R_2}{R_{L1} + R_1 + R_2} - \left[\frac{V_{CC}R_2}{R_{L1} + R_1 + R_L} - V_{BE} \right] \frac{R_B}{R_B + R_E(1 + h_{FE})} \quad (6-1)
 \end{aligned}$$

If the base current is neglected, Equation (6-1) becomes approximately:

$$UTP \simeq \frac{V_{CC}R_2}{R_{L1} + R_1 + R_2}$$

From Example 6-3,

$$\begin{aligned} V_{CC} &= LTP \left[\frac{R_1 + R_2}{R_2} + \frac{R_{L1}}{R_E} + \frac{R_{L1}}{R_2} \right] - \frac{R_{L1} V_{BE}}{R_E} \\ LTP &= \frac{V_{CC} + \frac{R_{L1} V_{BE}}{R_E}}{\frac{R_1 + R_2}{R_2} + \frac{R_{L1}}{R_E} + \frac{R_{L1}}{R_2}} \end{aligned} \quad (6-2)$$

6-4 DESIGNING FOR GIVEN UTP AND LTP

The design procedure, when both UTP and LTP are specified, is exactly the same as in Example 6-1, up to the point at which R_{L1} is chosen.

EXAMPLE 6-4

A Schmitt trigger circuit is to be designed with a UTP of 5 V, and an LTP of 3 V. The silicon transistors employed have $h_{FE(\min)} = 100$, and I_C is to be 2 mA. The available supply is 12 V. Design a suitable circuit.

solution

With the exception of the LTP, the circuit is exactly as specified for Example 6-1. Therefore, from Example 6-1,

$$\begin{aligned} R_{L2} &= 3.9 \text{ k}\Omega & R_E &= 2.2 \text{ k}\Omega & R_2 &= 22 \text{ k}\Omega \\ (R_1 + R_{L1}) &= 28.3 \text{ k}\Omega \end{aligned}$$

Figure 6-5 shows the circuit conditions when Q_1 is *on* and V_i is exactly at the LTP. For $V_i = LTP = 3 \text{ V}$, $V_{B2} = LTP = 3 \text{ V}$.

$$\begin{aligned} I_1 &= \frac{V_{B2}}{R_2} = \frac{3 \text{ V}}{22 \text{ k}\Omega} = 0.136 \text{ mA} \\ I_{C1} \simeq I_E &= \frac{V_{B1} - V_{BE}}{R_E} = \frac{3 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega} = 1.045 \text{ mA} \end{aligned}$$

$$V_{CC} = R_{L1}(I_{C1} + I_1) + I_1(R_1 + R_2)$$

$$12 \text{ V} = R_{L1}(1.045 \text{ mA} + 0.136 \text{ mA}) + 0.136 \text{ mA}(R_1 + 22 \text{ k}\Omega)$$

$$R_1 + R_{L1} = 28.3 \text{ k}\Omega$$

$$R_1 = 28.3 \text{ k}\Omega - R_{L1}$$

$$12 \text{ V} = R_{L1}(1.045 \text{ mA} + 0.136 \text{ mA}) \\ + 0.136 \text{ mA}(28.3 \text{ k}\Omega - R_{L1} + 22 \text{ k}\Omega)$$

$$= R_{L1}(1.181 \text{ mA}) + 3.85 \text{ V} - R_{L1}(0.136 \text{ mA}) + 2.99 \text{ V}$$

$$12 \text{ V} - 3.85 \text{ V} - 2.99 \text{ V} = R_{L1}(1.181 \text{ mA} - 0.136 \text{ mA})$$

$$R_{L1} = 4.94 \text{ k}\Omega \quad (\text{use } 4.7 \text{ k}\Omega \text{ standard value})$$

$$R_1 = 28.3 \text{ k}\Omega - R_{L1}$$

$$= 28.3 \text{ k}\Omega - 4.7 \text{ k}\Omega$$

$$= 23.6 \text{ k}\Omega \quad (\text{use } 22 \text{ k}\Omega \text{ standard value})$$

EXAMPLE 6-5

Using the selected standard resistance values, determine the actual LTP of the circuit designed in Example 6-4.

solution

Refer to Equation (6-2). The actual LTP is determined as:

$$\text{LTP} = \frac{12 \text{ V} + \frac{4.7 \text{ k}\Omega \times 0.7 \text{ V}}{2.2 \text{ k}\Omega}}{\frac{22 \text{ k}\Omega + 22 \text{ k}\Omega}{22 \text{ k}\Omega} + \frac{4.7 \text{ k}\Omega}{2.2 \text{ k}\Omega} + \frac{4.7 \text{ k}\Omega}{22 \text{ k}\Omega}} \\ = 3.1 \text{ V}$$

6-5 SELECTION OF THE SPEED-UP CAPACITOR

The effects of a speed-up capacitor on transistor switching times were discussed in Sec. 4-4. As already explained, the capacitor should be as large as possible, but must be small enough to allow its voltage to return

to normal dc levels between switching. For a Schmitt circuit to trigger at the UTP and LTP levels as designed, the capacitor C_1 voltage must settle to the dc level across R_1 in the time interval between triggering.

EXAMPLE 6-6

The Schmitt trigger circuit designed in Example 6-4 is to be triggered at a maximum frequency of 1 MHz. Determine the largest speed-up capacitor that may be used.

solution

Resistance in parallel with the capacitor terminals when Q_1 is off:

$$\begin{aligned} R &= R_1 \parallel (R_{L1} + R_2) \\ &= 22 \text{ k}\Omega \parallel (4.7 \text{ k}\Omega + 22 \text{ k}\Omega) \\ &\simeq 12 \text{ k}\Omega \end{aligned}$$

Actually, the input resistance of Q_2 is in parallel with R_2 but is very large compared to R_2 .

$$\begin{aligned} \text{Resolving time} &= t_{re} = \frac{1}{\text{Triggering frequency}} \\ &= \frac{1}{1 \text{ MHz}} = 1 \mu\text{s} \end{aligned}$$

For C to charge through 90% of its total voltage change:

$$C_{\max} = \frac{t_{re}}{2.3R} \quad [\text{Equation (4-4)}]$$

$$C = \frac{1 \mu\text{s}}{2.3 \times 12 \text{ k}\Omega} = 36 \text{ pF} \quad (\text{use } 35 \text{ pF standard value})$$

6-6 OUTPUT/INPUT CHARACTERISTICS

Consider the Schmitt trigger circuit design as finalized in Example 6-4. When Q_2 is on, the output voltage is:

$$V_o = V_{CC} - I_C R_{L2}$$

$$\begin{aligned}
 &= 12 \text{ V} - (2 \text{ mA} \times 3.9 \text{ k}\Omega) \\
 &= 4.2 \text{ V}
 \end{aligned}$$

When Q_2 is *off*, the output voltage is:

$$\begin{aligned}
 V_o &= V_{CC} - I_{CO}R_{L2} \\
 &\simeq V_{CC} = 12 \text{ V}
 \end{aligned}$$

The UTP and LTP are approximately, as designed, 5 V and 3 V, respectively. With the triggering levels and the output voltage levels known, a graph showing output voltage *versus* input voltage may be plotted.

When the input voltage is zero, Q_1 is *off* and Q_2 is *on*. Therefore, $V_o = 4.2 \text{ V}$. This may be plotted as point *A* on the output/input characteristics in Figure 6-6(a). As V_i is increased above zero volts, Q_1 remains *off* and Q_2 remains *on* until V_i becomes equal to the UTP, which for this particular circuit, is at 5 V. Hence V_o remains at 4.2 V from $V_i = 0$ to $V_i = 5 \text{ V}$. Point *B* is plotted at $V_o = 4.2 \text{ V}$ and $V_i = 5 \text{ V}$.

When the UTP is reached, Q_1 switches *on* and Q_2 switches *off*. Thus, V_o changes from 4.2 V to 12 V. Point *C* is plotted at $V_o = V_{CC}$ and $V_i = \text{UTP}$. Now, any further increase in V_i has no effect on V_o . The horizontal line from point *C* to point *D* Figure 6-6(a) shows that V_o remains equal to V_{CC} as V_i increases above the UTP.

Now, consider the effect of reducing V_i from a level greater than the UTP. The output voltage V_o remains equal to 12 V until V_i becomes equal to the LTP, at point *E* on Figure 6-6(b). At the LTP, Q_1 switches *off* and Q_2 switches *on*, returning V_o to 4.2 V. Point *F* is plotted at $V_o = 4.2 \text{ V}$ and $V_i = \text{LTP} = 3 \text{ V}$. As V_i is reduced below the LTP, V_o remains at 4.2 V, shown by the line from point *F* to point *A* in Figure 6-6(b). The two graphs, taken together as in Figure 6-6(c), give the complete output/input characteristics for the circuit.

The difference between the UTP and LTP levels is termed the *hysteresis* of the circuit. For many circuit applications, the hysteresis is not very important. In some circumstances, however, circuits with the least possible hysteresis are desirable. Zero hysteresis occurs when the upper and lower trigger points are equal.

The hysteresis can be adjusted by altering the ratio of R_1 and R_2 or by adjusting the value of R_{L1} . The *loop gain* or stage gain of Q_1 (when Q_1 is *on*) determines the amount of hysteresis in the circuit. With a large loop gain, a very small value of input voltage is sufficient to produce a large (phase inverted) output to Q_2 base which keeps Q_2 biased *off*. Consequently, the lower trigger point is found at a very low level of input voltage. Thus, it is seen that the largest loop gain produces greatest hysteresis.

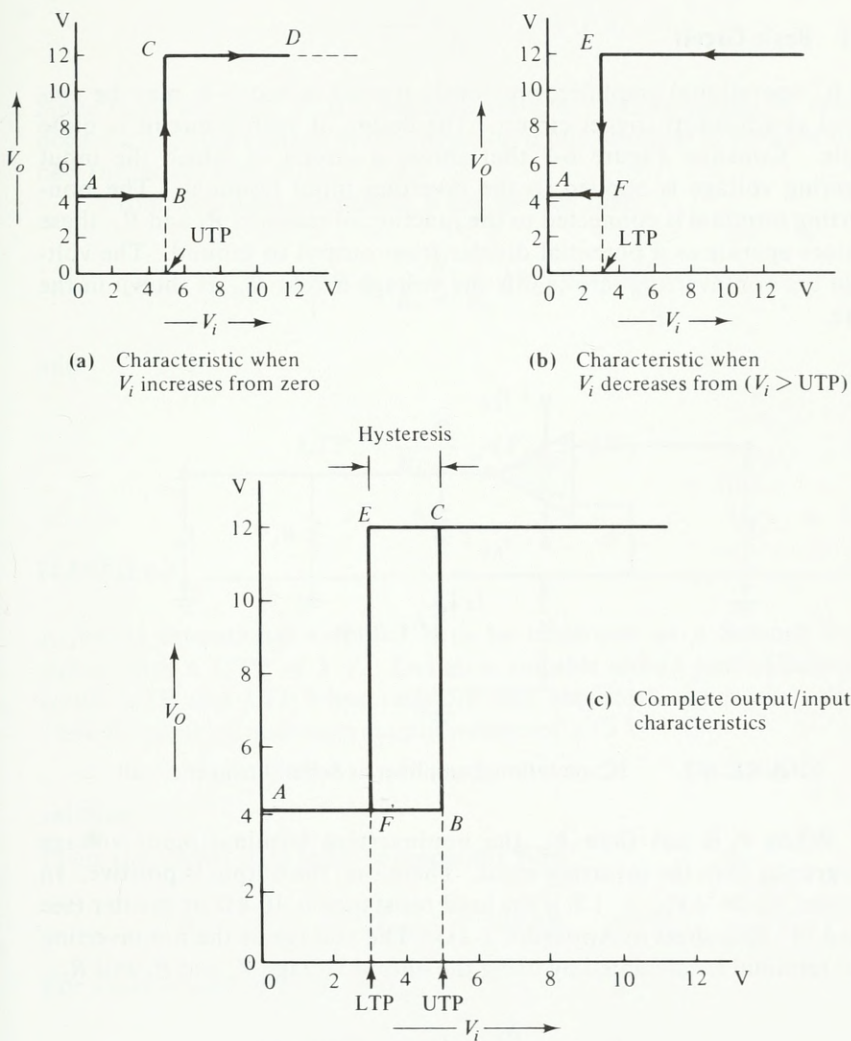


FIGURE 6-6. Output/input characteristics for Schmitt trigger circuit.

6-7 THE IC OPERATIONAL AMPLIFIER AS A SCHMITT TRIGGER CIRCUIT

6-7.1 Basic Circuit

The IC operational amplifier, previously treated in Sec. 5-4, may be employed as a Schmitt trigger circuit. The design of such a circuit is quite simple. Consider Figure 6-7 that shows a circuit in which the input triggering voltage is applied to the inverting input terminal. The non-inverting terminal is connected to the junction of resistors R_1 and R_2 ; these resistors operate as a potential divider from output to ground. The voltage at the noninverting terminal is the voltage across R_2 , as shown in the figure.

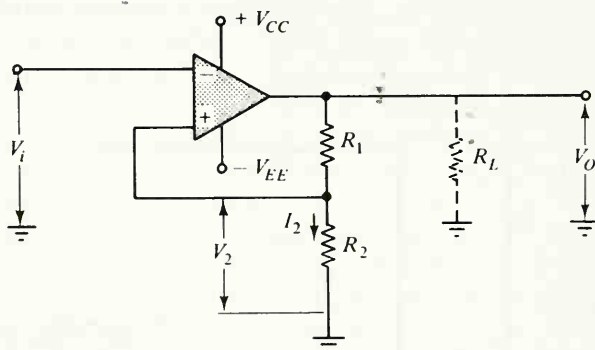


FIGURE 6-7. IC operational amplifier as Schmitt trigger circuit.

When V_i is less than V_2 , the noninverting terminal input voltage V_2 is greater than the inverting input. Therefore, the output is positive. In this case, $V_o \simeq +V_{CC} - 1\text{ V}$ if the load resistance is $10\text{ k}\Omega$ or greater (see the $\mu\text{A}741$ data sheet in Appendix I-11). The voltage at the noninverting input terminal is calculated by using the output voltage V_o and R_1 and R_2 :

$$V_2 = \frac{R_2}{R_1 + R_2} (V_{CC} - 1\text{ V})$$

When the input voltage is raised to the level of V_2 , the output begins to go negative. This causes V_2 to fall, thus the noninverting input terminal rapidly becomes negative with respect to the inverting input terminal. When this occurs the output changes over very rapidly from approxi-

mately ($V_{CC} - 1$ V) to approximately ($V_{EE} + 1$ V). It is seen that the upper trigger point is equal to V_2 when the output is positive.

When the output is ($V_{EE} + 1$ V), V_2 becomes:

$$V_2 = \frac{R_2}{R_1 + R_2} (V_{EE} + 1 \text{ V})$$

Since V_{EE} is negative, V_2 is a negative voltage, and the output V_o remains negative until the voltage at the inverting input terminal is reduced to the new (negative) level of V_2 .

From the above discussion, it can be seen that:

$$\text{UTP} \simeq \frac{R_2}{R_1 + R_2} (V_{CC} - 1 \text{ V}) \quad (6-3)$$

and

$$\text{LTP} \simeq \frac{R_2}{R_1 + R_2} (V_{EE} + 1 \text{ V}) \quad (6-4)$$

EXAMPLE 6-7

A $\mu\text{A}741$ operational amplifier is to be employed as a Schmitt trigger circuit with a UTP of 3 V. Design a suitable circuit and calculate the actual UTP and LTP when resistors with standard values are selected. Take R_L as 10 k Ω and use a supply voltage of ± 15 V.

solution

From the $\mu\text{A}741$ data sheet in Appendix 1-11:

$$I_{B(\text{max})} = 500 \text{ nA}$$

For a stable level of V_2 , $I_2 \gg I_{B(\text{max})}$.

$$\begin{aligned} I_2 &= 100 \times 500 \text{ nA} \\ &= 50 \mu\text{A} \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{\text{UTP}}{I_2} = \frac{3 \text{ V}}{50 \mu\text{A}} \\ &= 60 \text{ k}\Omega \quad (\text{use } 56 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

Thus, I_2 becomes $3 \text{ V}/56 \text{ k}\Omega$, which is equal to $53.57 \text{ }\mu\text{A}$.

$$\begin{aligned}
 V_{R1} &= V_o - V_2 \\
 &= (V_{CC} - 1 \text{ V}) - V_2 \\
 &= 15 \text{ V} - 1 \text{ V} - 3 \text{ V} \\
 &= 11 \text{ V} \\
 R_1 &= \frac{V_{R1}}{I_2} = \frac{11 \text{ V}}{53.57 \text{ }\mu\text{A}} \\
 &= 205 \text{ k}\Omega \quad (\text{use } 220 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

$$\begin{aligned}
 \text{Actual UTP} &\simeq \frac{V_o R_2}{R_1 + R_2} \\
 &= \frac{14 \text{ V} \times 56 \text{ k}\Omega}{220 \text{ k}\Omega + 56 \text{ k}\Omega} = 2.8 \text{ V} \\
 \text{LTP} &\simeq -2.8 \text{ V}
 \end{aligned}$$

6-7.2 Adjusting the Trigger Points

A Schmitt trigger circuit in which the lower trigger point is clamped to -0.7 V is shown in Figure 6-8(a). When the output voltage becomes negative, diode D_1 is forward-biased. Thus, D_1 holds the noninverting input to 0.7 V below ground. When V_i (at the inverting input) drops below -0.7 V , the output again becomes positive. The LTP is now -0.7 V . The UTP is unaffected by the diode, since D_1 is reverse-biased when the output is positive.

The circuit can be designed for any desired UTP. Then, by use of a diode and potential divider, as shown in Figure 6-8(b), the LTP can be fixed at any desired level. A potentiometer placed between R_3 and R_4 [Figure 6-8(c)] provides an adjustable LTP. Finally, a diode connected in series with R_1 , as illustrated in Figure 6-8(d), gives an LTP which is very close to ground. When the output is negative, D_1 is reverse-biased and only the diode reverse leakage current I_R flows. The LTP now becomes $V_2 = -I_R R_2$. Since I_R normally is very small, and R_2 can be selected as low as a few kilohms, the LTP can be only millivolts from ground. By reversal of D_1 the UTP can be brought close to ground. Then, the LTP is specified by V_o , R_1 , and R_2 .

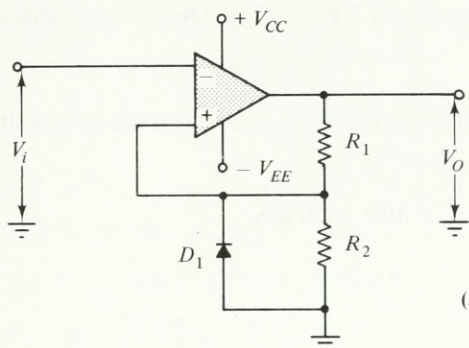
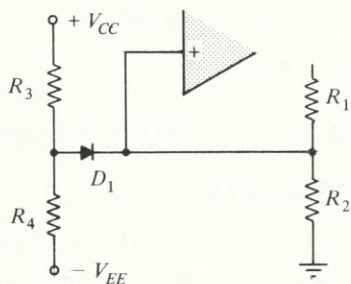
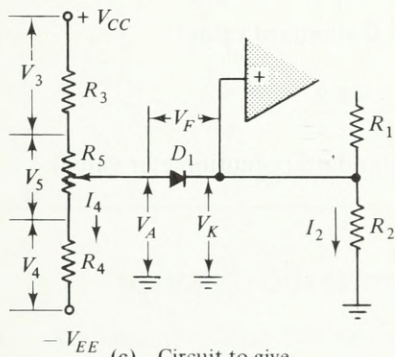
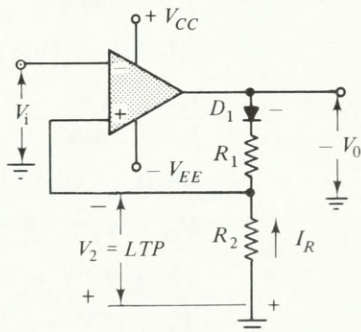

 (a) Circuit for
LTP ≈ -0.7 V

 (b) Circuit for LTP
at any desired level

 (c) Circuit to give
adjustable LTP

 (d) Circuit for LTP
close to ground

FIGURE 6-8. Operational amplifier Schmitt trigger circuits with various methods of setting LTP.

EXAMPLE 6-8

The Schmitt trigger circuit designed in Example 6-7 is to have the LTP adjustable over the range from 2 V to -2 V. Design a suitable circuit.

solution

Consider the circuit of Figure 6-8(c). For a stable bias voltage V_A , set $I_4 \gg I_2$. Let

$$\begin{aligned} I_4 &= 100 \times I_2 = 100 \times 50 \mu\text{A} \\ &= 5 \text{ mA} \end{aligned}$$

For

$$V_{K1} = -2 \text{ V}$$

$$\begin{aligned} V_{A1} &= V_{K1} + V_F \\ &= -2 \text{ V} + 0.7 \text{ V} \\ &= -1.3 \text{ V} \end{aligned}$$

$$V_4 = -1.3 \text{ V} - (-15 \text{ V}) = 13.7 \text{ V}$$

$$\begin{aligned} R_4 &= \frac{V_4}{I_4} = \frac{13.7 \text{ V}}{5 \text{ mA}} \\ &= 2.72 \text{ k}\Omega \quad (\text{use } 2.7 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

$$\begin{aligned} R_5 &= \frac{V_5}{I_4} = \frac{4 \text{ V}}{5 \text{ mA}} \\ &= 800 \Omega \quad (\text{use } 1 \text{ k}\Omega \text{ standard potentiometer value}) \end{aligned}$$

$$\begin{aligned} V_{A2} &= V_{K2} + V_F \\ &= 2 \text{ V} + 0.7 \text{ V} = 2.7 \text{ V} \end{aligned}$$

$$\begin{aligned} R_3 &= \frac{V_3}{I_4} = \frac{15 \text{ V} - 2.7 \text{ V}}{5 \text{ mA}} \\ &= 2.46 \text{ k}\Omega \quad (\text{use } 2.7 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

EXAMPLE 6-9

A Schmitt trigger circuit is to be designed to have UTP = 8 V, and LTP = 0 V. The available supply is ± 15 V. Using a $\mu\text{A}741$ operational amplifier, design a suitable circuit.

solution

Use the circuit as in Figure 6-8(d). From the μA741 data sheet (Appendix 1-11),

$$I_{B(\max)} = 500 \text{ nA}$$

$$I_2 \gg I_{B(\max)}$$

Make

$$\begin{aligned} I_2 &= 100 \times I_{B(\max)} \\ &= 100 \times 500 \text{ nA} = 50 \mu\text{A} \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{\text{UTP}}{I_2} = \frac{8 \text{ V}}{50 \mu\text{A}} \\ &= 160 \text{ k}\Omega \quad [\text{use } 150 \text{ k}\Omega \text{ standard value} \\ &\quad (\text{see Appendix 2-1})] \end{aligned}$$

I_2 now becomes $8 \text{ V} / 150 \text{ k}\Omega = 53.3 \mu\text{A}$ and

$$\begin{aligned} V_{R1} &= V_O - V_{D1} - \text{UTP} \\ &= (V_{CC} - 1 \text{ V}) - V_{D1} - \text{UTP} \\ &= 15 \text{ V} - 1 \text{ V} - 0.7 \text{ V} - 8 \text{ V} \\ &= 5.3 \text{ V} \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{V_{R1}}{I_2} = \frac{5.3 \text{ V}}{53.3 \mu\text{A}} \\ &= 99.4 \text{ k}\Omega \quad (\text{use } 100 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

REVIEW QUESTIONS AND PROBLEMS

- 6-1** Sketch a transistor Schmitt trigger circuit, and briefly explain its operation.
- 6-2** Define the terms, *upper trigger point*, *lower trigger point*, *hysteresis*, and *regeneration*.
- 6-3** Design a transistor Schmitt trigger circuit with $\text{UTP} = 6 \text{ V}$. Use a 2N3904 transistor with $I_C = 1 \text{ mA}$. The available supply is 15 V . Use standard value resistors.
- 6-4** Analyze the circuit designed in Problem 6-3 to determine the output voltage levels, and the actual UTP and LTP.

- 6-5** The circuit of Problem 6-3 is to have an LTP of 4 V. Make the necessary design modifications and select suitable standard value resistors.
- 6-6** Analyze the Schmitt trigger circuit, resulting from Problem 6-5, to determine the actual UTP and LTP.
- 6-7** Plot the output/input characteristics for the Schmitt trigger circuit designed in Problem 6-5.
- 6-8** (a) Briefly explain how a *speed-up capacitor* improves the switching time of a Schmitt trigger circuit. (b) The Schmitt trigger circuit designed in Problem 6-5 is to be triggered at a maximum frequency of 800 kHz. Determine the maximum size of the speed-up capacitor that may be employed.
- 6-9** (a) Sketch the circuit of an operational amplifier employed as a Schmitt trigger circuit. Briefly explain how it functions. (b) Show how this circuit could be modified so that (1) $LTP \simeq -0.7\text{ V}$, (2) $LTP \simeq 0\text{ V}$, (3) $UTP \simeq 0\text{ V}$.
- 6-10** Design a Schmitt trigger circuit using a $\mu\text{A}741$ operational amplifier. The supply voltage is to be $\pm 12\text{ V}$, and the trigger points $\pm 2\text{ V}$. Select standard value resistors and calculate the actual triggering levels.
- 6-11** Plot the output/input characteristics for the Schmitt trigger circuit designed in Problem 6-10.
- 6-12** The Schmitt trigger circuit designed in Problem 6-10 is to have an LTP adjustable over the range $\pm 1\text{ V}$. Suitably modify the circuit.
- 6-13** The circuit of Problem 6-10 has the following input waveforms:
(a) A triangular waveform with an amplitude of $\pm 5\text{ V}$;
(b) A square wave with an amplitude of 3 V ;
(c) A square wave with an amplitude of $\pm 4\text{ V}$;
(d) A sine wave with an amplitude of $\pm 10\text{ V}$;
(e) A sawtooth wave with an amplitude of $\pm 6\text{ V}$.
Sketch the above waveforms and the resultant output wave from the Schmitt trigger circuit for each case.
- 6-14** Using a $\mu\text{A}741$ IC operational amplifier, design a Schmitt trigger circuit to have $LTP = -2\text{ V}$ and $UTP = 0\text{ V}$. The available supply is $\pm 9\text{ V}$.

Chapter 7

Ramp Generators

INTRODUCTION

A simple ramp generator circuit can be constructed using a capacitor charged via a resistance, in conjunction with a discharge transistor. To improve the ramp output linearity, a transistor CONSTANT CURRENT CIRCUIT can be employed. When the discharge transistor is replaced by a UNIJUNCTION transistor, the circuit becomes a RELAXATION OSCILLATOR. The BOOTSTRAP RAMP GENERATOR, which produces a closely linear ramp, can be constructed using a transistor or an IC operational amplifier. An IC operational amplifier can also be employed in a Miller integrator.

7-1 CR RAMP GENERATOR

The simplest ramp generator circuit is a capacitor charged via a series resistance. A transistor must be connected in parallel with the capacitor

to provide a discharge path, as shown in the circuit of Figure 7-1(a). Capacitor C_1 is charged from V_{CC} via R_1 . Q_1 is biased *on* via R_B so the capacitor is normally in a discharged state. When a negative-going input pulse is coupled by C_2 to Q_1 base, the transistor switches *off*. Then, C_1 begins to charge; this provides an approximate ramp output until the input pulse ends [see Figure 7-1(b)]. At this point, Q_1 switches *on* again, and rapidly discharges the capacitor.

The output from a simple CR circuit is exponential rather than linear. For voltages very much less than the supply voltage, however, the output is approximately linear. When the transistor is *on*, the capacitor is discharged to $V_{CE(sat)}$. Hence, $V_{CE(sat)}$ is the starting level of the output ramp. Output amplitude adjustment can be provided by making the charging resistance (R_1) adjustable.

Capacitor C_2 , which couples the input pulse to the transistor base, should be selected as small as possible, both for minimum cost and smallest possible physical size. The minimum suitable size can be determined by allowing the base voltage of Q_1 to rise during the input pulse time, as shown in Figure 7-1(b). The base voltage starts approximately at 0.7 V when Q_1 is *on*. Then, V_{B2} is pulled negative by the input pulse, but starts to rise again as C_2 is charged through R_B . To ensure that Q_1 is still *off* at the end of the pulse time, V_{B2} should not rise above -0.5 V. This approach to coupling capacitor selection is outlined in Sec. 5-2.

EXAMPLE 7-1

Design a simple CR ramp generator to give an output that peaks at 5 V. The supply voltage is 15 V, and the load to be connected at the output is 100 k Ω . The ramp is to be triggered by a negative-going pulse with an amplitude of 3 V, PW = 1 ms, and time interval between pulse = 0.1 ms. Take the transistor $h_{FE(min)}$ as 50.

solution

This circuit is shown in Figure 7-1(a). The maximum output current is:

$$\begin{aligned} I_{L(max)} &= \frac{V_P}{R_L} \\ &= \frac{5 \text{ V}}{100 \text{ k}\Omega} = 50 \mu\text{A} \end{aligned}$$

Select the maximum capacitor charging current $I_1 \gg I_{L(max)}$. At peak output voltage, let

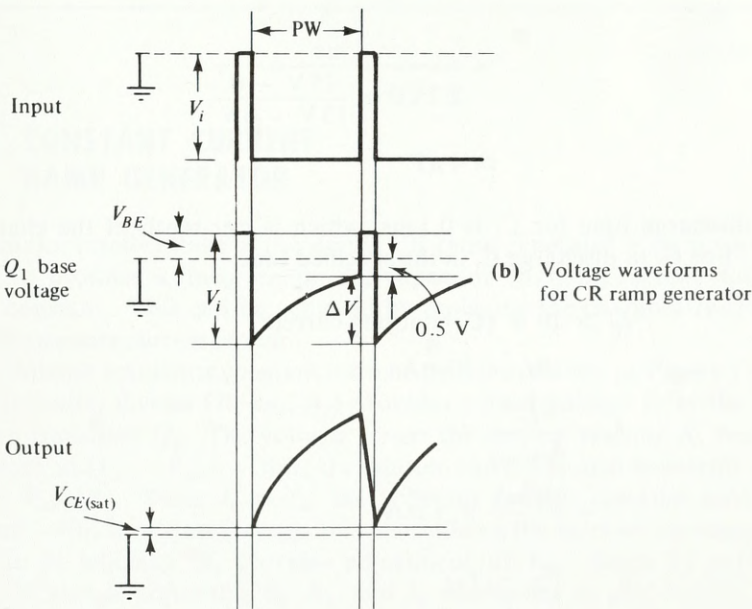
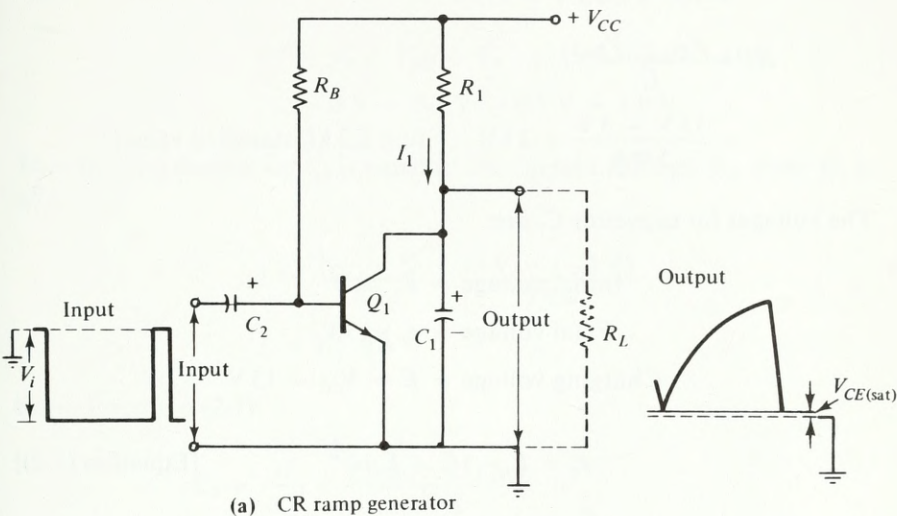


FIGURE 7-1. CR ramp generator circuit and voltage waveforms.

$$\begin{aligned}
 I_1 &= 100 \times I_{L(\max)} \\
 &= 100 \times 50 \mu\text{A} = 5 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 R_1 &= \frac{V_{CC} - V_P}{I_1} \\
 &= \frac{15 \text{ V} - 5 \text{ V}}{5 \text{ mA}} = 2 \text{ k}\Omega \quad (\text{use } 2.2 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

The voltages for capacitor C_1 are:

$$\text{Initial voltage} = E_o \simeq 0$$

$$\text{Final voltage} = e_c = 5 \text{ V}$$

$$\text{Charging voltage} = E = V_{CC} = 15 \text{ V}$$

$$e_c = E - (E - E_o)e^{\frac{-t}{CR}} \quad [\text{Equation (2-2)}]$$

$$\begin{aligned}
 C_1 &= \frac{t}{R \ln \frac{E - E_o}{E - e_c}} \\
 &= \frac{1 \text{ ms}}{2.2 \text{ k}\Omega \ln \frac{15 \text{ V} - 0}{15 \text{ V} - 5 \text{ V}}} \\
 &\simeq 1 \mu\text{F}
 \end{aligned}$$

The discharge time for C_1 is 0.1 ms, which is one-tenth of the charging time. For Q_1 to discharge C_1 in the specified time,

$$\begin{aligned}
 I_C &\cong 10 \times (C_1 \text{ charging current}) \\
 &= 10I_1 = 50 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 I_B &= \frac{I_C}{h_{FE(\min)}} \\
 &= \frac{50 \text{ mA}}{50} = 1 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 R_B &= \frac{V_{CC} - V_{BE}}{I_B} \\
 &= \frac{15 \text{ V} - 0.7 \text{ V}}{1 \text{ mA}} \\
 &= 14.3 \text{ k}\Omega \quad (\text{use } 12 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

For Q_1 to remain biased *off* at the end of the input pulse, let $V_B = -0.5$ V.

$$\begin{aligned}\therefore \quad \Delta V &= V_i - V_{BE} - V_B \quad [\text{See Figure 7-1(b)}] \\ &= 3 \text{ V} - 0.7 \text{ V} - 0.5 \text{ V} = 1.8 \text{ V}\end{aligned}$$

The charging current for C_2 is equal to the current through R_B when Q_1 is *off*:

$$\begin{aligned}I &\simeq \frac{V_{CC} - V_i}{R_B} = \frac{15 \text{ V} - (-3 \text{ V})}{12 \text{ k}\Omega} \\ &= 1.5 \text{ mA}\end{aligned}$$

From Equation (2-7):


$$\begin{aligned}C_2 &= \frac{It}{\Delta V} = \frac{1.5 \text{ mA} \times 1 \text{ ms}}{1.8 \text{ V}} \\ &= 0.83 \mu\text{F} \quad (\text{use } 1 \mu\text{F standard value})\end{aligned}$$

7-2 **CONSTANT CURRENT RAMP GENERATOR**


The major disadvantage of the simple CR ramp generator is its nonlinearity. To produce a linear ramp, the capacitor charging current must be held constant. This can be achieved by replacing the charging resistance with a *constant current circuit*.

A basic transistor constant current circuit is shown in Figure 7-2(a). The potential divider (R_1 and R_2) provides a fixed voltage V_1 at the base of *pnp* transistor Q_2 . The voltage across the emitter resistor R_3 remains constant at $(V_1 - V_{BE})$. Thus, the emitter current is also constant: $I_E = (V_1 - V_{BE})/R_3$. Since $I_C \simeq I_E$, the collector current remains constant. Figure 7-2(b) shows an arrangement that allows the level of constant current to be adjusted. R_4 provides adjustment of V_B . Since $V_3 = (V_B - V_{BE})$, V_3 also is adjustable by R_4 , and I_E can be set to any desired level over a range dependent upon R_4 .

Figure 7-3(a) shows a ramp generator that employs the constant current circuit. Note that because I_C of Q_2 is a constant charging current for C_1 ; the capacitor voltage V_o grows linearly. The simpler capacitor-charging equation, Equation (2-7), may now be used for C_1 calculations. The

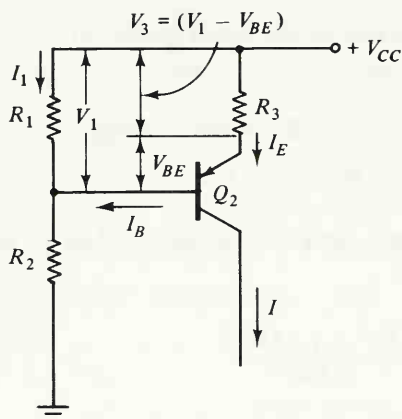

(a) Constant current circuit

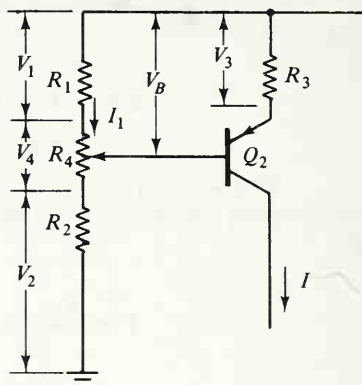

(b) Adjustable constant current circuit

FIGURE 7-2. Transistor fixed and adjustable constant current circuits.

circuit of Figure 7-3 (a) now functions like the simple CR ramp generator, with R_1 replaced by the constant current circuit.

The output voltage from the constant current ramp generator remains linear only if a sufficient voltage is maintained across Q_2 for it to operate in the active region of its characteristics. If Q_2 reaches saturation, the output stops at a constant level. Therefore, V_{CE2} should not fall below about 3 V. Because of this and the constant voltage V_3 across resistor R_3 , the maximum ramp output voltage obtainable from the circuit of Figure 7-3 is approximately $V_o = V_{CC} - V_3 - 3 \text{ V}$.

In the circuit of Figure 7-3(b) the input pulse is directly connected to the base of transistor Q_1 . When the input is at ground level, Q_1 is *off* and capacitor C_1 charges via Q_2 . When a positive input is applied, Q_1 is switched *on* and C_1 is rapidly discharged. Q_1 remains *on* during the positive input pulse; thus C_1 is held in a discharged condition, and the ramp generator output voltage remains at the $V_{CE(sat)}$ of Q_1 .

EXAMPLE 7-2


Using a constant current circuit, modify the ramp generator designed in Example 7-1 to produce a linear ramp output.

solution


Refer to the circuit of Figure 7-3 (a).

$$V_{O(\max)} = 5 \text{ V}$$
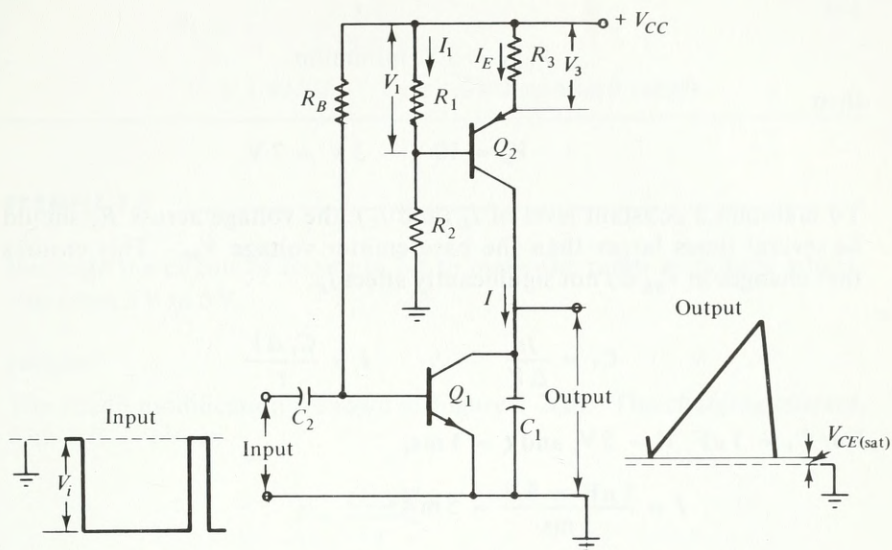
$$V_3 + V_{CE2} = V_{CC} - 5 \text{ V} = 10 \text{ V}$$



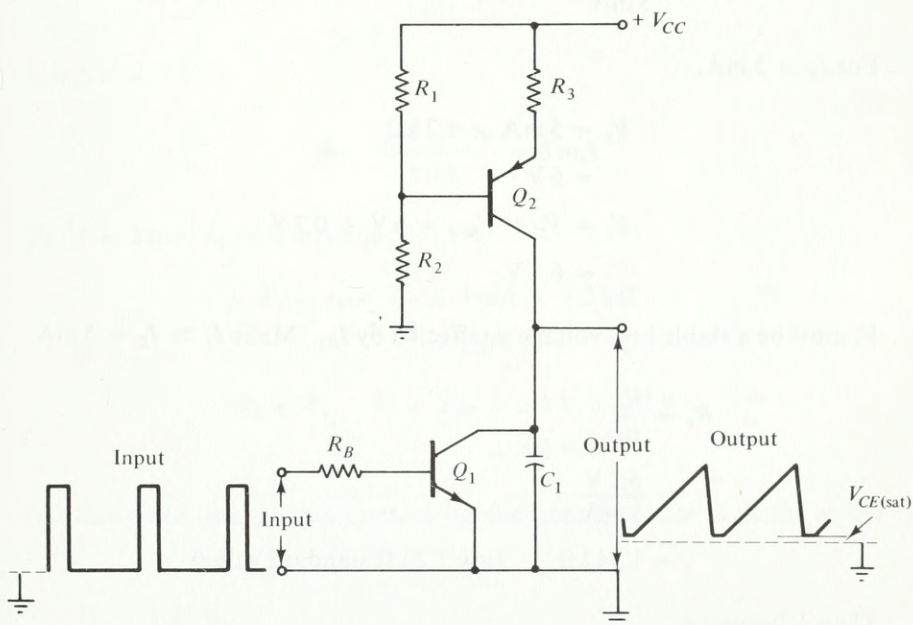(a) Constant current ramp generator with capacitor-coupled input



(b) Constant current ramp generator with direct-coupled input

FIGURE 7-3. Constant current ramp generators.

Let

$$V_{CE2} = 3 \text{ V, minimum}$$

then

$$V_3 = 10 \text{ V} - 3 \text{ V} = 7 \text{ V}$$

To maintain a constant level of I_E (and I_C), the voltage across R_3 should be several times larger than the base emitter voltage V_{BE} . This ensures that changes in V_{BE} do not significantly affect I_E .

$$C_1 = \frac{It}{\Delta V} \quad \therefore \quad I = \frac{C_1 \Delta V}{t}$$

For $C_1 = 1 \mu\text{F}$, $V = 5 \text{ V}$, and $t = 1 \text{ ms}$,

$$I = \frac{1 \mu\text{F} \times 5 \text{ V}}{1 \text{ ms}} = 5 \text{ mA}$$

$$R_3 \simeq \frac{7 \text{ V}}{5 \text{ mA}} = 1.4 \text{ k}\Omega \quad (\text{use } 1.2 \text{ k}\Omega \text{ standard value})$$

For $I_E = 5 \text{ mA}$,

$$\begin{aligned} V_3 &= 5 \text{ mA} \times 1.2 \text{ k}\Omega \\ &= 6 \text{ V} \end{aligned}$$

$$\begin{aligned} V_1 &= V_3 + V_{BE2} = 6 \text{ V} + 0.7 \text{ V} \\ &= 6.7 \text{ V} \end{aligned}$$

V_1 must be a stable bias voltage unaffected by I_{B2} . Make $I_1 \simeq I_E = 5 \text{ mA}$.

$$\begin{aligned} R_1 &= \frac{V_1}{I_1} \\ &= \frac{6.7 \text{ V}}{5 \text{ mA}} \\ &= 1.34 \text{ k}\Omega \quad (\text{use } 1.2 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

Then I_1 becomes

$$I_1 = \frac{6.7 \text{ V}}{1.2 \text{ k}\Omega} = 5.58 \text{ mA}$$

$$V_2 = V_{CC} - V_1 = 15 \text{ V} - 6.7 \text{ V} = 8.3 \text{ V}$$

$$\begin{aligned}
 R_2 &\simeq \frac{V_2}{I_1} = \frac{8.3 \text{ V}}{5.58 \text{ mA}} \\
 &= 1.49 \text{ k}\Omega \quad (\text{use } 1.5 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

EXAMPLE 7-3

Redesign the circuit of Example 7-2 to make the ramp amplitude adjustable from 3 V to 5 V.

solution

The circuit modification is shown in Figure 7-2(b). The charging current, with $\Delta V = 3 \text{ V}$, is:

$$\begin{aligned}
 I &= \frac{C_1 \Delta V}{t} \\
 &= \frac{1 \mu\text{F} \times 3 \text{ V}}{1 \text{ ms}} = 3 \text{ mA}
 \end{aligned}$$

For $\Delta V = 5 \text{ V}$,

$$I = \frac{1 \mu\text{F} \times 5 \text{ V}}{1 \text{ ms}} = 5 \text{ mA}$$

For $I = 3 \text{ mA}$, $I_E \simeq 3 \text{ mA}$ and

$$\begin{aligned}
 V_3 &= I_E \times R_3 = 3 \text{ mA} \times 1.2 \text{ k}\Omega \\
 &= 3.6 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_B = V_1 = V_3 + V_{BE} &= 3.6 \text{ V} + 0.7 \text{ V} \\
 &= 4.3 \text{ V}
 \end{aligned}$$

(At this point, the moving contact on the potentiometer is at the upper end.)

For $R_1 = 1.2 \text{ k}\Omega$,

$$I_1 = \frac{4.3 \text{ V}}{1.2 \text{ k}\Omega} \simeq 3.6 \text{ mA}$$

For $I = 5 \text{ mA}$,

$$\begin{aligned} V_3 &= 5 \text{ mA} \times 1.2 \text{ k}\Omega \\ &= 6 \text{ V} \end{aligned}$$

and

$$V_B = 6.7 \text{ V}$$

(At this point the potentiometer moving contact is at the lower end.)

$$V_B = V_1 + V_4$$

$$V_4 = 6.7 \text{ V} - 3.6 \text{ V} = 3.1 \text{ V}$$

and

$$\begin{aligned} R_4 &= \frac{V_4}{I_1} = \frac{3.1 \text{ V}}{3.6 \text{ mA}} \\ &= 0.86 \text{ k}\Omega \quad (\text{use a } 1 \text{ k}\Omega \text{ standard potentiometer value}) \end{aligned}$$

Then V_4 becomes

$$V_4 = I_1 R_4 = 3.6 \text{ mA} \times 1 \text{ k}\Omega = 3.6 \text{ V}$$

and

$$\begin{aligned} V_2 &= V_{CC} - V_1 - V_4 \\ &= 15 \text{ V} - 4.3 \text{ V} - 3.6 \text{ V} \\ &= 7.1 \text{ V} \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{V_2}{I_1} \\ &= \frac{7.1 \text{ V}}{3.6 \text{ mA}} \\ &= 1.97 \text{ k}\Omega \quad (\text{use } 2.2 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

7-3 UJT RELAXATION OSCILLATORS

7-3.1 The Unijunction Transistor

The basic construction of a unijunction transistor (UJT) and its equivalent circuit are shown in Figure 7-4. The device can be thought of as a

bar of lightly doped n -type silicon, with a small piece of heavily doped p -type joined to one side [see Figure 7-4(a)]. The p -type is named the *emitter*, while the two end terminals of the bar are designated bases 1 and 2 (B_1 and B_2), as shown. The silicon bar is represented as two resistors, r_{B1} and r_{B2} ; the pn junction, formed by the emitter and the bar, is represented by a diode in the equivalent circuit of Figure 7-4(b).

The ratio, $r_{B1}/(r_{B1} + r_{B2})$ is termed the *intrinsic standoff ratio* of the UJT, and is designated by η . Thus the voltage across r_{B1} is given by:

$$V_1 = V_{BB} \frac{r_{B1}}{r_{B1} + r_{B2}}$$

or

$$V_1 = V_{BB} \eta \tag{7-1}$$

The pn junction becomes forward-biased at a peak voltage, $V_p = V_{EB1} = V_1 + V_F$. When this peak is reached, the flow of charge carriers through r_{B1} causes its resistance to fall. Thus, a capacitor connected across E and B_1 is rapidly discharged. The flow of current into the emitter terminal continues until V_E falls to the *emitter saturation voltage* $V_{EB1(sat)}$, at which time the device switches off.

Two more important parameters for the UJT are *peak point current* I_p and the *valley point current* I_V . The peak point current is the minimum

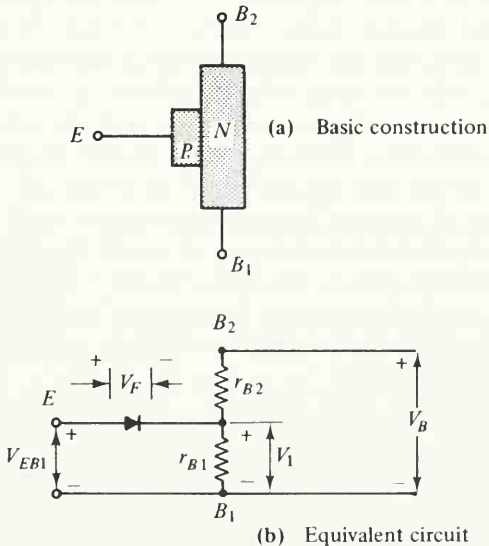


FIGURE 7-4. Basic construction and equivalent circuit of uni-junction transistor.

emitter current that must flow for the UJT to switch *on* or *fire*. This current occurs when V_E is at the *firing voltage*, that is, at peak point V_p . The valley point current is the emitter current that flows when V_E is at the emitter saturation voltage, $V_{EB1(sat)}$.

7-3.2 UJT Relaxation Oscillator

A unijunction transistor can be used in conjunction with a capacitor and a charging circuit, to construct an oscillator with an approximate ramp-type output. Figure 7-5(a) shows the simplest form of such a circuit, which is called a *UJT relaxation oscillator*. The UJT remains *off* until its emitter voltage V_{EB1} approaches the firing voltage V_p for the particular device. At this point, the UJT switches *on* and a large emitter current I_E flows. This causes capacitor C_1 to discharge rapidly. When the capacitor voltage falls to the emitter saturation level, the UJT switches *off*, allowing C_1 to begin to charge again.


The frequency of a relaxation oscillator can be made variable by switched selection of capacitors and/or by adjustment of the charging resistance [see Figure 7-5(b)]. The resistance R_2 , in series with UJT terminal B_1 , allows synchronizing input pulses to be applied. When an input pulse pulls B_1 negative, V_{EB1} is increased to the level at which the UJT fires. Once the UJT fires it will not switch *off* again until the capacitor is discharged.

In the design of a UJT relaxation oscillator, the charging resistance R_1 must be selected between certain upper and lower limits. Resistance R_1 must not be so large that the emitter current is less than the peak point current when V_{EB1} is at the firing voltage; otherwise, the device may not switch *on*. If R_1 is very small, then when V_{EB1} is at the emitter saturation level, a current greater than the valley point current might flow into the emitter terminal. In this case, the UJT may not switch *off*. Thus, for correct UJT operation, R_1 must be selected between two limits that allow the emitter current to be between a minimum of I_p and a maximum of I_v .


The UJT oscillator circuits shown in Figures 7-5(a) and (b) will produce exponential output waveforms because the capacitors are charged by resistances. Constant current circuits could be used here to generate linear ramp output waveforms.

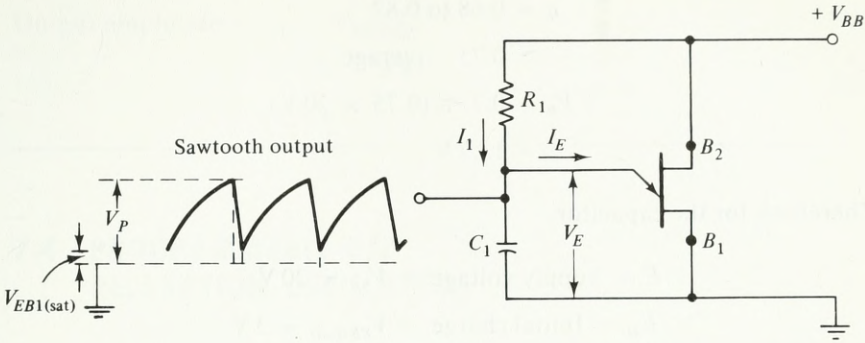EXAMPLE 7-4

The circuit of Figure 7-5(a) is to use a 2N3980 UJT. The supply voltage V_{BB} is 20 V, and output frequency is to be 5 kHz. Design a suitable circuit, and calculate the output amplitude.



(a) UJT relaxation oscillator

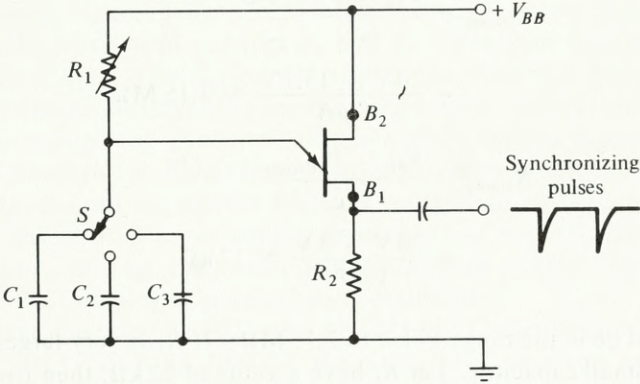

(b) Variable frequency UJT relaxation oscillator

FIGURE 7-5. Basic UJT relaxation oscillator and variable frequency circuit.

solution

Capacitor C_1 charges from $V_{EB1(sat)}$ to the firing voltage, $V_p = V_F + \eta V_{BB}$. The data sheet for the 2N3980 (Appendix 1-12) gives the following specifications:

$$V_{EB1(sat)} = 3 \text{ V maximum, } I_p = 2 \mu\text{A, } I_V = 1 \text{ mA}$$

and

$$\begin{aligned}
 \eta &= 0.68 \text{ to } 0.82 \\
 &\simeq 0.75 \quad \text{average} \\
 V_P &= 0.7 + (0.75 \times 20 \text{ V}) \\
 &= 15.7 \text{ V}
 \end{aligned}$$

Therefore, for the capacitor,

$$\begin{aligned}
 E &= \text{Supply voltage} = V_{BB} = 20 \text{ V} \\
 E_O &= \text{Initial charge} = V_{EB1(\text{sat})} = 3 \text{ V} \\
 e_c &= \text{Final charge} = V_P = 15.7 \text{ V}
 \end{aligned}$$

Now, to select R_1 :

$$\begin{aligned}
 R_{1(\text{max})} &= \frac{V_{BB} - V_P}{I_P} \\
 &= \frac{20 \text{ V} - 15.7 \text{ V}}{2 \mu\text{A}} \simeq 2.15 \text{ M}\Omega \\
 R_{1(\text{min})} &= \frac{V_{BB} - V_{EB1(\text{sat})}}{I_V} \\
 &= \frac{20 \text{ V} - 3 \text{ V}}{1 \text{ mA}} \simeq 17 \text{ k}\Omega
 \end{aligned}$$

So R_1 must be in the range $17 \text{ k}\Omega$ to $2.15 \text{ M}\Omega$. If R_1 is very large, C_1 must be a very small capacitor. Let R_1 have a value of $22 \text{ k}\Omega$; then from Equation (2-2)

$$\begin{aligned}
 C_1 &= \frac{t}{R_1 \ln \left(\frac{E - E_O}{E - e_c} \right)} \\
 t &= \frac{1}{\text{Output frequency}} = \frac{1}{5 \text{ kHz}} = 200 \mu\text{s}
 \end{aligned}$$

then

$$\begin{aligned}
 C_1 &= \frac{200 \mu\text{s}}{22 \text{ k}\Omega \ln \left(\frac{20 \text{ V} - 3 \text{ V}}{20 \text{ V} - 15.7 \text{ V}} \right)} \\
 &= 6600 \text{ pF} \quad [\text{use } 6800 \text{ pF standard capacitor} \\
 &\quad (\text{see Appendix 2-2})]
 \end{aligned}$$

$$\begin{aligned}
 \text{Output amplitude} &= V_P - V_{EB1(\text{sat})} \\
 &= 15.7 \text{ V} - 3 \text{ V} \\
 &= 12.7 \text{ V}
 \end{aligned}$$

7-4 PROGRAMMABLE UJT RELAXATION OSCILLATORS

The *programmable unijunction transistor* (PUT) is a silicon-controlled rectifier-type device used in a particular way to simulate a UJT. The interbase resistances r_{B1} and r_{B2} and the intrinsic standoff ratio η may be programmed to any desired values by selecting two resistors. This means that the device firing voltage V_P can also be programmed.

Consider Figures 7-6(a) and (b). The gate of the *pnpn* device is connected to the junction of resistors R_1 and R_2 . The gate voltage is $V_G = V_{BB} R_1 / (R_1 + R_2)$. The device will trigger *on* when the input voltage V_{AK} makes the anode (layer P_1) positive with respect to the gate (layer N_1). When this occurs, the anode-to-cathode voltage rapidly drops to a low level, and the device conducts heavily from anode to cathode. This situation continues until the current becomes too low to sustain conduction. With the anode used as an emitter terminal, and with R_1 and R_2 substituted for r_{B1} and r_{B2} , the circuit action simulates a UJT. Figure 7-6(c) shows the PUT employed in a relaxation oscillator.

A data sheet for 2N6027 and 2N6028 PUT devices is included in Appendix 1-13. For the 2N6027, the value of I_P is given as $1.25 \mu\text{A}$ typical, and I_V as $18 \mu\text{A}$ typical. The offset voltage, which is equivalent to $V_{EB1(\text{sat})}$, is typically 0.7 V .


EXAMPLE 7-5

Design a relaxation oscillator using a 2N6027 PUT. The supply voltage is 15 V , and the output is to be 5 V peak at 1 kHz .


solution

The circuit is as shown in Figure 7-6(c).

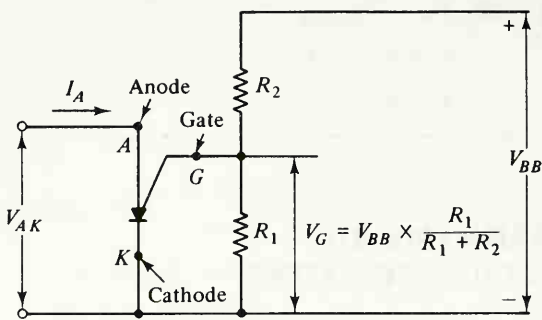
$$\begin{aligned}
 V_P &= V_G + (p_1 n_1 \text{ junction voltage drop}) \\
 5 \text{ V} &= V_G + 0.7 \text{ V} \\
 V_G &= 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}
 \end{aligned}$$



(a) Programmable UJT circuit

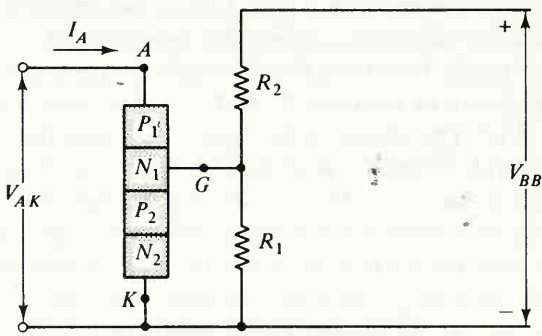

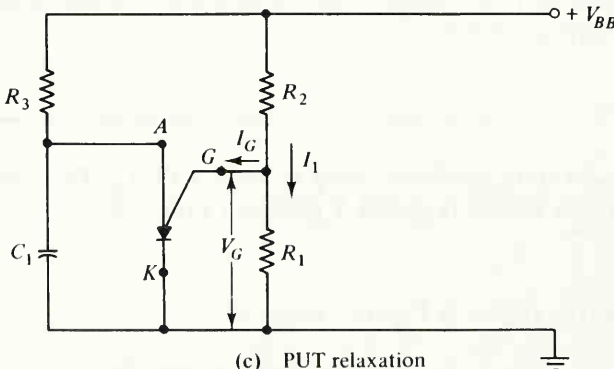(b) Four layer construction of programmable UJT



(c) PUT relaxation oscillator

FIGURE 7-6. Programmable UJT, four layer construction, and PUT relaxation oscillator circuit.

To provide a stable gate bias voltage the current through the potential divider (R_1 and R_2) must be much larger than the gate current at switch-on:

$$I_1 \gg I_G$$

Since $I_G \simeq 5 \mu\text{A}$ (typical), let

$$\begin{aligned} I_1 &= 100 \times I_G \\ &= 100 \times 5 \mu\text{A} = 0.5 \text{ mA} \\ R_1 &= \frac{V_G}{I_1} = \frac{4.3 \text{ V}}{0.5 \text{ mA}} \\ &= 8.6 \text{ k}\Omega \quad (\text{use } 8.2 \text{ k}\Omega \text{ standard}) \end{aligned}$$

Now, I_1 becomes

$$\begin{aligned} I_1 &= \frac{4.3 \text{ V}}{8.2 \text{ k}\Omega} = 524 \mu\text{A} \\ V_{R2} &= V_{BB} - V_G \\ &= 15 \text{ V} - 4.3 \text{ V} = 10.7 \text{ V} \\ R_2 &= \frac{V_{R2}}{I_1} = \frac{10.7 \text{ V}}{524 \mu\text{A}} \\ &= 20.4 \text{ k}\Omega \quad (\text{use } 18 \text{ k}\Omega \text{ standard}) \end{aligned}$$

Now V_G becomes

$$\begin{aligned} V_G &= \frac{15 \text{ V} \times 8.2 \text{ k}\Omega}{18 \text{ k}\Omega + 8.2 \text{ k}\Omega} \\ &= 4.69 \text{ V} \quad (\text{i.e., instead of } 4.3 \text{ V}) \end{aligned}$$

and

$$\begin{aligned} V_P &= V_G + 0.7 \text{ V} \\ &= 4.69 \text{ V} + 0.7 \text{ V} = 5.39 \text{ V} \end{aligned}$$

The valley voltage V_V is 0.7 V. For the capacitor C_1 ;

$$E = \text{Supply voltage} = V_{BB} = 15 \text{ V}$$

$$E_o = \text{Initial charge} = V_v = 0.7 \text{ V}$$

$$e_c = \text{Final charge} = V_p = 5.39 \text{ V}$$

For selection of R_3 :

$$\begin{aligned} R_{3(\max)} &= \frac{V_{BB} - V_p}{I_p} \\ &= \frac{15 \text{ V} - 5.39 \text{ V}}{1.25 \mu\text{A}} = 7.7 \text{ M}\Omega \end{aligned}$$

$$\begin{aligned} R_{3(\min)} &= \frac{V_{BB} - V_v}{I_v} \\ &= \frac{15 \text{ V} - 0.7 \text{ V}}{18 \mu\text{A}} = 790 \text{ k}\Omega \end{aligned}$$

Thus, R_3 must be in the range from 790 k Ω to 7.7 M Ω . Let $R_3 = 1 \text{ M}\Omega$.


$$t = \frac{1}{\text{Output frequency}} = \frac{1}{1 \text{ kHz}} = 1 \text{ ms}$$

and from Equation (2-2)


$$\begin{aligned} C_1 &= \frac{t}{R_3 \ln \left(\frac{E - E_o}{E - e_c} \right)} \\ &= \frac{1 \text{ ms}}{1 \text{ M}\Omega \ln \left(\frac{15 \text{ V} - 0.7 \text{ V}}{15 \text{ V} - 5.39 \text{ V}} \right)} \\ &= 0.0025 \mu\text{F} \quad (\text{standard value}) \end{aligned}$$

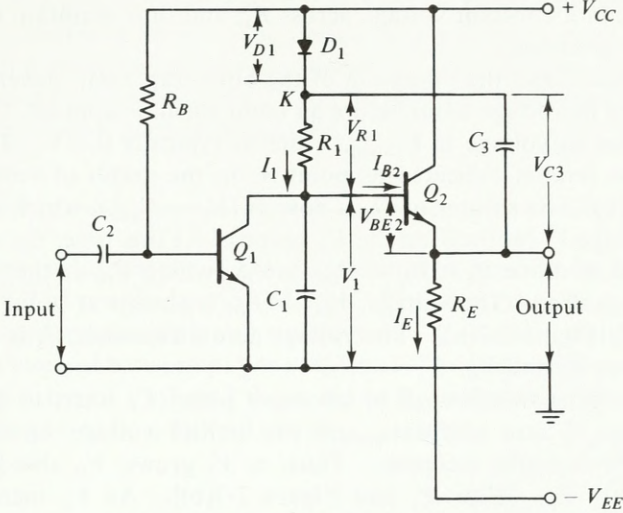7-5 TRANSISTOR BOOTSTRAP RAMP GENERATOR

The circuit of a transistor *bootstrap ramp generator* is shown in Figure 7-7(a). The ramp is generated across capacitor C_1 which is charged via resistance R_1 . The discharge transistor Q_1 holds the capacitor voltage V_1 down to $V_{CE(\text{sat})}$ until a negative input pulse is applied. Transistor Q_2 is an emitter follower that provides a low-output impedance. The emitter resistor R_E is connected to a negative supply level, rather than to ground. This is to ensure that Q_2 remains conducting when its base voltage V_1 is close to ground. Capacitor C_3 , known as the *bootstrapping capacitor*, has



(a) Bootstrap ramp generator

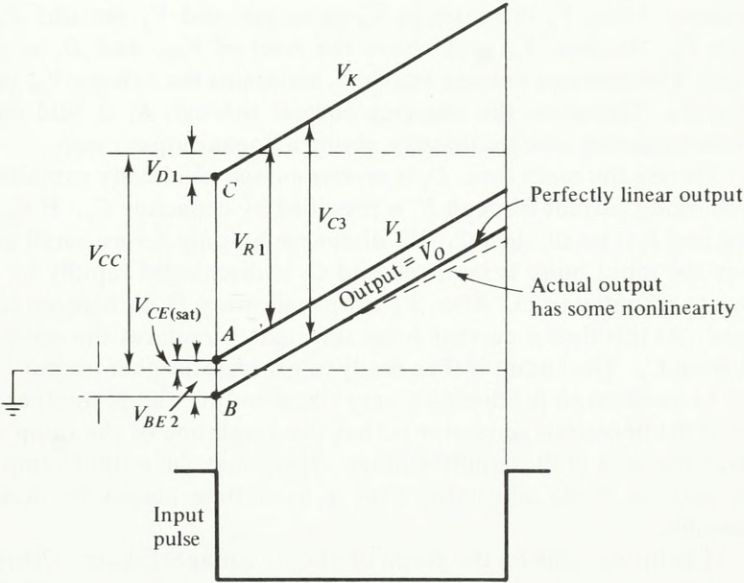

(b) Waveforms at various points in the circuit

FIGURE 7-7. Transistor bootstrap ramp generator and circuit waveforms.

a much larger capacitance than C_1 . The function of C_3 , as will be shown, is to maintain a constant voltage across R_1 , and thus maintain the charging current constant.

To understand the operation of the bootstrap ramp generator, first consider the dc voltage levels before an input signal is applied. Transistor Q_1 is *on*, and its voltage is $V_{CE(sat)}$, which is typically 0.2 V. Thus $V_1 = 0.2$ V. This level is indicated as point *A* on the graph of voltage V_1 in Figure 7-7(b). The emitter of Q_2 is now at $(V_1 - V_{BE2})$, which is also the output voltage V_o (point *B* on the V_o graph). At this time, the voltage at the cathode of diode D_1 is $V_K = V_{CC} - V_{D1}$, where V_{D1} is the diode forward voltage drop. The voltage, $V_{CC} - V_{D1}$ is shown at point *C* on the graph of V_K [Figure 7-7(b)]. The voltage across capacitor C_3 is the difference between V_K and V_o .

When Q_1 is switched *off* by an input pulse, C_1 starts to charge via R_1 . Voltage V_1 now increases, and the emitter voltage V_o of Q_2 (the emitter follower) also increases. Thus, as V_1 grows, V_o also grows, remaining only V_{BE} below V_1 [see Figure 7-7(b)]. As V_o increases, the lower terminal of C_3 is *pulled up*. Because C_3 is a large capacitor it retains its charge, and as V_o increases the voltage at the upper terminal of C_3 also increases. Thus, V_K increases as V_o increases, and V_K remains V_{C3} volts above V_o . In fact, V_K goes above the level of V_{CC} , and D_1 is reverse-biased. The constant voltage across C_3 maintains the voltage V_{R1} constant across R_1 . Therefore, the charging current through R_1 is held constant, and the capacitor charges linearly, giving a linear output ramp.

During the ramp time, D_1 is reverse-biased as already explained, and the charging current through R_1 is provided by capacitor C_3 . If C_3 is very large, and I_1 is small, then C_3 will discharge by only a very small amount. When the input pulse is removed and C_1 is discharged rapidly by Q_1 , V_o drops to its initial level. Also, V_K drops, allowing D_1 to become forward-biased. At this time a current pulse through D_1 replaces the small charge lost from C_3 . The circuit is then ready to generate another output ramp.

In addition to producing a very linear output ramp, another advantage of the bootstrap generator is that the amplitude of the ramp can approach the level of the supply voltage. Note that the output ramp amplitude may be made adjustable over a fixed time period by making R_1 adjustable.

The broken line on the graph of output voltage [Figure 7-7(b)] shows that the output, instead of being perfectly linear, may be slightly non-linear. If the difference between the actual output and the ideal output is 1% of the output peak voltage, then the ramp can be said to have 1% non-linearity. Some nonlinearity results from the slight discharge of C_3 that occurs during the ramp time. Another source of nonlinearity is the base current I_{B2} . As the capacitor voltage grows, I_{B2} increases. Since I_{B2} is part

of I_1 , the capacitor charging current decreases slightly as I_{B2} increases. Thus, the charging current does not remain perfectly constant, and the ramp is not perfectly linear. The design of a bootstrap ramp generator begins with a specification of ramp linearity. This dictates the charging current and the capacitance of C_3 . The percentage of nonlinearity usually is allocated in equal parts to ΔI_{B2} and ΔV_{C3} .

EXAMPLE 7-6

Design a transistor bootstrap ramp generator to provide an output amplitude of 8 V over a time period of 1 ms. The ramp is to be triggered by a negative-going pulse with an amplitude of 3 V, a pulse width of 1 ms, and a time interval between pulses of 0.1 ms. The load resistor to be supplied has a value of 1 k Ω and the ramp is to be linear within 2%. The supply voltage is to be ± 15 V. Take $h_{FE(\min)} = 100$.

solution

The circuit is shown in Figure 7-7(a).

$$R_E = R_L = 1 \text{ k}\Omega$$

When $V_O = 0$,

$$I_E \simeq \frac{V_{EE}}{R_E}$$

$$\frac{15 \text{ V}}{1 \text{ k}\Omega} = 15 \text{ mA}$$

When $V_O = V_P$,

$$I_E \simeq \frac{V_{EE} + V_P}{R_E}$$

$$= \frac{15 \text{ V} + 8 \text{ V}}{1 \text{ k}\Omega} = 23 \text{ mA}$$

$$I_{B2} \simeq \frac{I_{E2}}{h_{FE}}$$

At $V_O = 0$,

$$I_{B2} = \frac{15 \text{ mA}}{100} = 0.15 \text{ mA}$$

At $V_O = V_P$,

$$I_{B2} = \frac{23 \text{ mA}}{100} = 0.23 \text{ mA}$$

$$\Delta I_{B2} = 0.23 \text{ mA} - 0.15 \text{ mA} = 80 \mu\text{A}$$

Allow 1% nonlinearity due to ΔI_{B2} , (that is, ΔI_{B2} represents a loss of charging current to C_1)

$$\begin{aligned} I_1 &= 100 \times \Delta I_{B2} \\ &= 100 \times 80 \mu\text{A} \\ &= 8 \text{ mA} \end{aligned}$$

$$\begin{aligned} C_1 &= \frac{I_1 t}{\Delta V} = \frac{I_1 \times (\text{Ramp time})}{V_P} \\ &= \frac{8 \text{ mA} \times 1 \text{ ms}}{8 \text{ V}} \\ &= 1 \mu\text{F} \quad (\text{standard capacitor value}) \end{aligned}$$

$$\begin{aligned} V_{R1} &= V_{CC} - V_{D1} - V_{CE(\text{sat})} \\ &= 15 \text{ V} - 0.7 \text{ V} - 0.2 \text{ V} \\ &= 14.1 \text{ V} \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{V_{R1}}{I_1} = \frac{14.1 \text{ V}}{8 \text{ mA}} \\ &= 1.76 \text{ k}\Omega \quad (\text{use } 1.8 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

For 1% nonlinearity due to C_3 discharge,

$$\Delta V_{C3} = 1\% \text{ of initial } V_{C3} \text{ level}$$

$$V_{C3} \simeq V_{CC} = 15 \text{ V}$$

$$\Delta V_{C3} = \frac{15 \text{ V}}{100} = 0.15 \text{ V}$$

and C_3 discharge current is equal to $I_1 = 8 \text{ mA}$.

$$\begin{aligned} C_3 &= \frac{I_1 t}{\Delta V_{C3}} = \frac{8 \text{ mA} \times 1 \text{ ms}}{0.15 \text{ V}} \\ &= 53 \mu\text{F} \quad (\text{use } 56 \mu\text{F} \text{ standard capacitance value}) \end{aligned}$$

R_B and C_2 are calculated as they were for Example 7-1.

7-6 IC BOOTSTRAP RAMP GENERATOR

An IC operational amplifier (see Sec. 5-4) connected as a *voltage follower* forms part of the bootstrap ramp generator in Figure 7-8. When an operational amplifier is used as a voltage follower, the inverting input terminal is connected directly to the output. The input signal is applied at the noninverting input.

The operation of the voltage follower can best be understood if it is assumed that both input terminals are initially at ground level. The output is also at ground level at this time. *Note that the output from an operational amplifier is the amplified voltage difference between the two input terminals.* Now, suppose an input of 1 V is applied at the noninverting terminal. Since the amplifier has a very large gain, the output tends to move positively towards the saturation level. However, as the output increases positively, the voltage at the inverting terminal also increases positively. When the inverting terminal voltage equals the noninverting terminal voltage (*i.e.*, 1 V), there is no longer any voltage difference between the two input terminals. Consequently, there is no longer an input signal, and the output voltage ceases to increase. Thus, the output voltage *follows* the input very closely.

Actually, there is a small voltage difference between the input terminals of a voltage follower. This difference is equal to the output voltage divided by the amplifier gain. For a $\mu A741$ with an output of 10 V, the input difference would be typically:

$$\frac{10 \text{ V}}{200,000} = 50 \mu\text{V}$$

This means that the output voltage is only $50 \mu\text{V}$ behind the input voltage. This is a big improvement on the transistor emitter follower, where V_o is typically 0.7 V behind V_i .

It is seen that the voltage follower is an amplifier with a gain of 1, and that the output closely follows the input. The voltage follower also has the high input impedance and low output impedance characteristic of the IC operational amplifier.

The circuit of the IC operational amplifier bootstrap generator is almost exactly like that of the transistor bootstrap circuit. The voltage follower takes the place of the emitter follower. Note that although a $\pm V$ supply is still required, the load resistance R_L now can be grounded. Also note that the output ramp starts at $V_{CE(\text{sat})}$ instead of at $V_{CE(\text{sat})} - V_{BE}$. The low input current to the operational amplifier has an almost negligible effect on the charging current to C_1 in the IC bootstrap

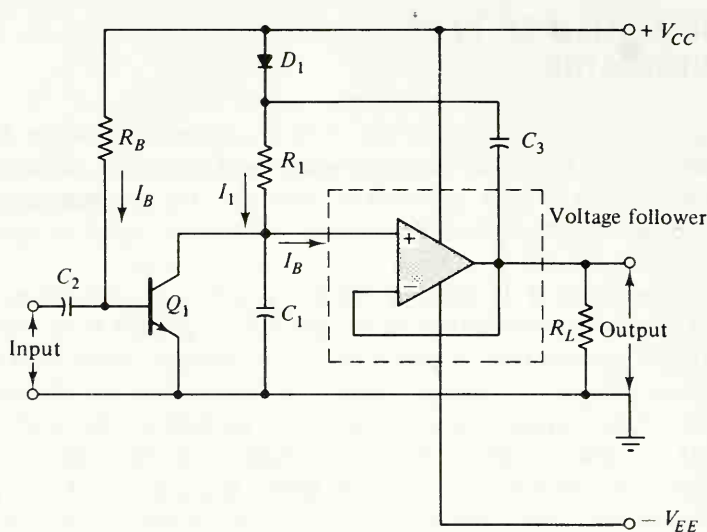


FIGURE 7-8. Bootstrap ramp generator using an IC operational amplifier.

circuit of Figure 7-8. In fact, the reverse leakage current of D_1 (when it is reverse-biased) is much more significant than the input bias current of the amplifier. Using a 1N914 diode (Appendix 1), I_R is typically $3\ \mu\text{A}$. For the $\mu\text{A}741$, the maximum input bias current is $500\ \text{nA}$. (Note that for the transistor bootstrap circuit, I_R of D_1 is very much smaller than I_B of transistor Q_2 .) The leakage current of D_1 becomes the starting point for the IC bootstrap circuit design. This results in a lower charging current to C_1 and in smaller values of C_1 , C_2 , and C_3 .

EXAMPLE 7-7

Design a bootstrap ramp generator using a $\mu\text{A}741$ operational amplifier. The specifications for the circuit are the same as those for the circuit of Example 7-6.

solution

The circuit is shown in Figure 7-8.

$$R_L = 1\ \text{k}\Omega$$

$$I_R = 3\ \mu\text{A} \quad (\text{when } D_1 \text{ is reverse-biased})$$

Allow 1% nonlinearity due to I_R :

$$\begin{aligned}
 I_1 &= 100 \times I_R \\
 &= 100 \times 3 \mu\text{A} = 300 \mu\text{A} \\
 C_1 &= \frac{I_1 t}{\Delta V} = \frac{I_1 \times (\text{Ramp time})}{V_P} \\
 &= \frac{300 \mu\text{A} \times 1 \text{ ms}}{8 \text{ V}} \\
 &= 0.0375 \mu\text{F} \quad (\text{use } 0.039 \mu\text{F standard value})
 \end{aligned}$$

$$\begin{aligned}
 V_{R1} &= V_{CC} - V_{D1} - V_{CE(\text{sat})} \\
 &= 15 \text{ V} - 0.7 \text{ V} - 0.2 \text{ V} \\
 &= 14.1 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 R_1 &= \frac{V_{R1}}{I_1} = \frac{14.1 \text{ V}}{300 \mu\text{A}} \\
 &= 47 \text{ k}\Omega \quad (\text{standard value})
 \end{aligned}$$

For 1% nonlinearity due to C_3 discharge:

$$\begin{aligned}
 \Delta V_{C3} &= 1\% \text{ of initial } V_{C3} \\
 V_{C3} &\simeq V_{CC} = 15 \text{ V} \\
 \Delta V_{C3} &= \frac{15 \text{ V}}{100} = 0.15 \text{ V}
 \end{aligned}$$

C_3 discharge current = $I_1 = 300 \mu\text{A}$

$$C_3 = \frac{I_1 t}{\Delta V_{C3}} = \frac{300 \mu\text{A} \times 1 \text{ ms}}{0.15 \text{ V}} = 2 \mu\text{F}$$

(standard value)

Compare this to $C_3 = 100 \mu\text{F}$ for the transistor circuit of Example 7-6. The discharge time of C_1 is equal to one-tenth of the charge time. Therefore, the discharge current of C_1 is ten times greater than the charge current.

$$\begin{aligned}
 \text{Minimum } I_c \text{ of } Q_1 &= 10 \times I_1 \\
 &= 10 \times 300 \mu\text{A} = 3 \text{ mA}
 \end{aligned}$$

$$I_B = \frac{I_C}{h_{FE}} = \frac{3 \text{ mA}}{100}$$

$$\begin{aligned}
 &= 30 \mu\text{A} \\
 R_B &= \frac{V_{CC} - V_{BE}}{I_B} \\
 &= \frac{15 \text{ V} - 0.7 \text{ V}}{30 \mu\text{A}} \\
 &= 477 \text{ k}\Omega \quad (\text{use } 470 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

During the input pulse, $\Delta V_{C_2} = 1.8 \text{ V}$ (see Example 7-1) and the charging current of C_2 can be expressed by:

$$\begin{aligned}
 I &= \frac{V_{CC} - V_i}{R_B} = \frac{15 \text{ V} - (-3 \text{ V})}{470 \text{ k}\Omega} \\
 &= 38 \mu\text{A}
 \end{aligned}$$


Thus,

$$\begin{aligned}
 C_2 &= \frac{It}{\Delta V} = \frac{38 \mu\text{A} \times 1 \text{ ms}}{1.8 \text{ V}} \\
 &= 0.02 \mu\text{F} \quad (\text{standard value})
 \end{aligned}$$

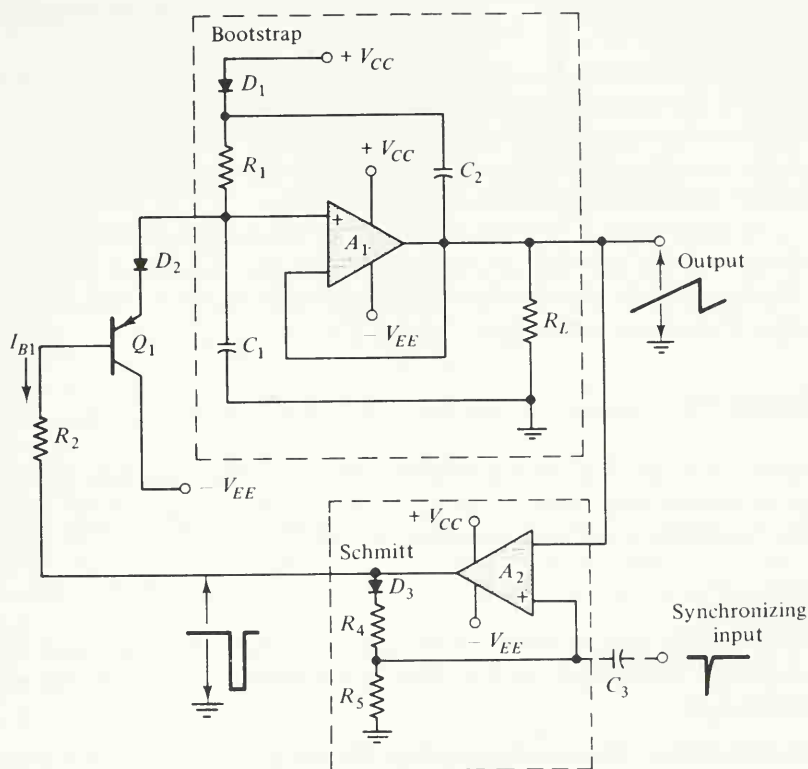
7-7 FREE-RUNNING RAMP GENERATOR

A bootstrap ramp generator may be made free-running by employing a Schmitt circuit to detect the output peak level and generate a capacitor discharge pulse. In the circuit shown in Figure 7-9(a) *pnp* transistor Q_1 discharges C_1 when the Schmitt circuit output is negative. Diode D_1 protects the base-emitter junction of Q_1 against excessive reverse bias when the Schmitt output is positive.


Consider the circuit waveforms shown in Figure 7-9(b). During the time that the Schmitt circuit output is positive, Q_1 remains *off* and C_1 charges; this provides a positive-going ramp output. When the ramp amplitude arrives at the UTP of the Schmitt circuit, the Schmitt output becomes negative. This causes I_{B1} to flow, biasing Q_1 *on* and discharging C_1 . As the voltage of capacitor C_1 falls, the ramp output also falls rapidly, and this continues until the Schmitt LTP is reached. The presence of D_3 makes the Schmitt circuit have an LTP close to ground (see Sec. 6-7.2). Therefore, when the ramp output falls to ground level, the Schmitt output goes positive again, switching Q_1 *off* and allowing ramp generation to commence again.



 
(a) Circuit of free-running ramp generator



(b) Circuit waveforms

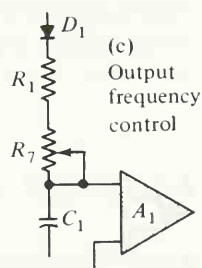

(c) Output frequency control

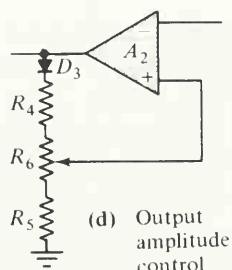

(d) Output amplitude control

FIGURE 7-9. Free-running ramp generator circuit, circuit waveforms, and controls.

The free-running ramp generator can be synchronized with another waveform by means of negative pulses coupled via capacitor C_3 . The presence of the negative pulse lowers the UTP of the Schmitt circuit, so that the Schmitt output becomes negative, causing the ramp to go to zero when the synchronizing pulse is applied.

Potentiometer R_7 [Figure 7-9(c)] allows the charging current to C_1 to be adjusted, thus controlling the ramp length and the output frequency. In Figure 7-9(d) R_6 affords adjustment of the Schmitt UTP. This provides control of the ramp amplitude.

EXAMPLE 7-8

Design a free-running ramp generator with an output frequency of 1 kHz and an output amplitude in the range 0 V to 8 V. Use $\mu A741$ operational amplifiers and a supply voltage of ± 15 V.

solution

Schmitt circuit. For an output of 0 V to 8 V, the Schmitt circuit must have an LTP of 0 V and a UTP of 8 V. Design the Schmitt circuit exactly as in Example 6-9.

Bootstrap circuit. The bootstrap output should go from 0 V to 8 V over a time period of 1/1 kHz. (i.e., 1 ms). Design the circuit as in Example 7-7, substituting a *pnp* transistor for Q_1 .

7-8 MILLER INTEGRATOR CIRCUIT

7-8.1 Miller Effect

Consider the circuit of Figure 7-10, in which an operational amplifier is connected as an *inverting amplifier*. Let the amplifier voltage gain be $-A_V$. Then,

$$V_o = -A_V V_i$$

Note that because of the amplifier phase shift, the voltage at the left-hand terminal of C_1 increases by V_i , while that at the right-hand terminal of the capacitor decreases by $A_V V_i$ when V_i is positive. This results in a total capacitor voltage change of:

$$\begin{aligned}\Delta V_1 &= V_i + A_v V_i \\ &= V_i(1 + A_v)\end{aligned}$$

Using the formula $Q = C \times \Delta V$, the charge supplied to the capacitor is:

$$\begin{aligned}Q &= C_1 \times \Delta V_1 \\ &= C_1 \times V_i(1 + A_v)\end{aligned}$$

or

$$= (1 + A_v)C_1 \times V_i$$

Thus it appears that the input has supplied a charge to a capacitor with a value of $(1 + A_v)C_1$, instead of C_1 alone. Capacitance C_1 is said to have been *amplified* by a factor of $(1 + A_v)$. This is known as the *Miller effect*.

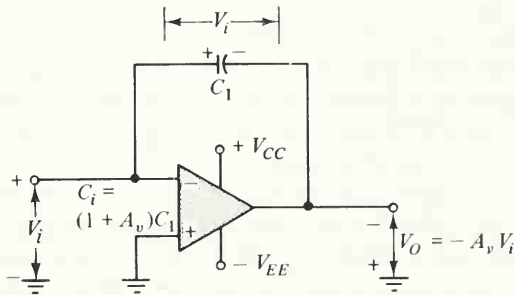


FIGURE 7-10. Miller effect or amplification of capacitance by inverting amplifier.

7-8.2 Miller Integrator

The *Miller integrator* utilizes the Miller effect to generate a linear ramp. In the circuit of Figure 7-11(a), a square wave input supplies charging current, alternatively positive and negative, to C_1 . The noninverting input terminal is grounded by a resistance R_2 equal to the resistance R_1 at the inverting input terminal. This is to ensure that the small bias currents cause equal voltage drops at each input terminal. Recall that, because of the very large gain of the operational amplifier, the voltage difference be-

tween the two input terminals is never greater than about $50\mu\text{V}$. Thus, it can be said that the inverting input terminal is always very close to ground level. The inverting terminal of an inverting operational amplifier is frequently termed a *virtual ground*, or *virtual earth*. Thus, the input voltage appears across R_1 and the input current is simply V_i/R_1 , which remains constant.

If the input current I_i is much greater than the input bias current of the amplifier, then I_i will not flow into the amplifier. Instead, effectively all of I_i flows through capacitor C_1 . For a positive input voltage, I_i flows into C_1 charging it positively on the left-hand side and negatively on the right-hand side [Figure 7-11(b)]. In this case the output voltage becomes negative, because the positive terminal, that is, the left-hand terminal, of the capacitor is held at the virtual ground level of the inverting input. A negative input voltage produces a flow of current out of C_1 [Figure 7-11(c)]. Thus the capacitor is charged negatively on the left-hand side and positively on the right-hand side. Now the output becomes positive, because the negative terminal of the capacitor is held at virtual ground.

Since I_i is a constant (+ or -) quantity, and since effectively all of I_i flows through the capacitor, C_1 is charged linearly. Thus the output voltage changes linearly, providing either a positive or negative ramp. When the input voltage is positive, the output is a negative-going ramp. When the input is negative, a positive-going output ramp is generated. Therefore, when the input is a square wave, the output waveform is triangular. This is illustrated in Figure 7-11(d).

Consider the Miller circuit of Figure 7-11(a). If the input is, say, $20\mu\text{V}$ away from ground level, then the output voltage could be $(A_v \times 20\mu\text{V}) = \pm(200,000 \times 20\mu\text{V}) = \pm 4\text{V}$. In this case the output is said to have *drifted* from its zero level. Even when the input terminal is maintained exactly at ground level, there could be a slight difference in the voltage at the amplifier inputs, due to small differences in the resistances of R_1 and R_2 , for example. Thus, because of the very high gain of the operational amplifier, its output voltage is very likely to drift from the zero level. The output voltage drift produces a charge on capacitor C_1 ; this charge gives the output an *offset* so that it is not symmetrical above and below ground (see Figure 7-12).

To minimize the output voltage drift, a large resistance [R_3 in Figure 7-11(a)] is connected between the output and the inverting input terminals. The effect of this resistance is to *cut down* the dc gain of the amplifier. When $R_3/R_1 = 10$, for example, the output drift will be only 10 times the input voltage difference. A ratio of 10:1 is typical for R_3/R_1 .

The presence of R_3 has the disadvantage that it affects the performance of the integrator at low frequencies. If the input frequency is so low that the capacitance impedance is very much larger than R_3 , then the

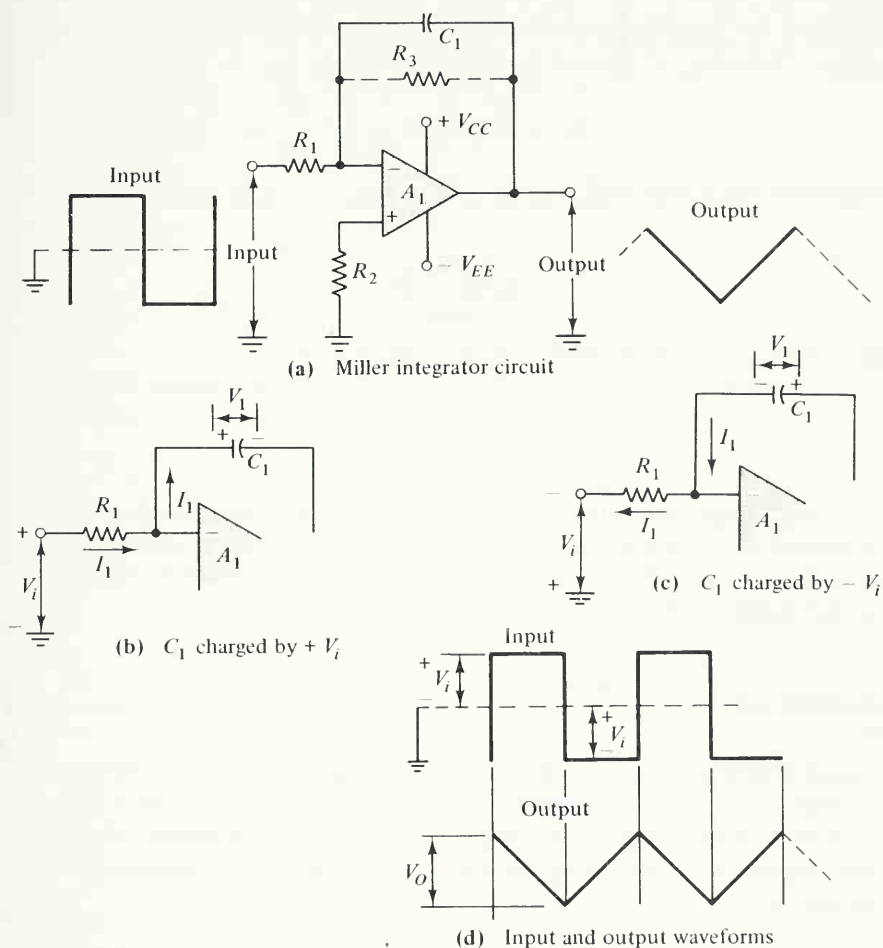


FIGURE 7-11. Miller integrator circuit, C_1 charging action, and waveforms.

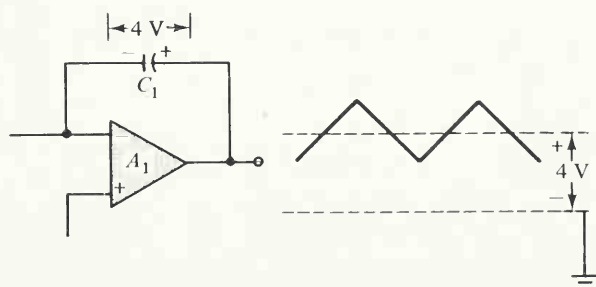


FIGURE 7-12. Effect of charge on C_1 due to output drift.

capacitor has a negligible effect and the circuit will not function as an integrator. Therefore, C_1 should be selected so that:

$$X_{C1} \ll R_3$$

As a lower limit, $X_{C1} = R_3/10$, so

$$\frac{1}{2\pi f C_1} = \frac{R_3}{10}$$

The lowest operating frequency of the integrator is

$$f = \frac{10}{2\pi C_1 R_3} \quad (7-2)$$

The design of a Miller integrator circuit begins with selection of the input current I_1 very much larger than the amplifier bias current. Then, R_1 is calculated as V_i/I_1 . From $C = It/V$, C_1 is determined using the desired output voltage, the time period, and the input current.

EXAMPLE 7-9

Design a Miller integrator circuit to produce a triangular waveform output with a peak-to-peak amplitude of 4 V. The input is a ± 10 V square wave with a frequency of 250 Hz. Use a $\mu A741$ operational amplifier with a supply of ± 15 V. Calculate the lowest operating frequency for the integrator.

solution

The circuit is shown in Figure 7-11(a). The $\mu A741$ data sheet in Appendix 1-11 gives the input bias current as:

$$I_B = 500 \text{ nA, maximum} \quad I_1 \gg I_B$$

Let

$$\begin{aligned} I_1 &= 1 \text{ mA} \\ R_1 &= \frac{V_i}{I_1} = \frac{10 \text{ V}}{1 \text{ mA}} \\ &= 10 \text{ k}\Omega \end{aligned}$$

Let

$$R_3 = 10 R_1 = 100 \text{ k}\Omega$$

$$R_2 = R_3 \parallel R_1 \simeq 10 \text{ k}\Omega$$

The ramp length is equal to one-half of the time period of the input, which is $1/(2f)$, or

$$\frac{1}{2 \times 250 \text{ Hz}} = 2 \text{ ms}$$

The ramp amplitude is equal to the peak-to-peak voltage output, which is 4 V.

$$C_1 = \frac{It}{\Delta V} = \frac{1 \text{ mA} \times 2 \text{ ms}}{4 \text{ V}} = 0.5 \mu\text{F}$$

Thus from Equation (7-2) the lowest operating frequency is

$$f = \frac{10}{2\pi \times 0.5 \mu\text{F} \times 100 \text{ k}\Omega}$$

$$= 32 \text{ Hz}$$

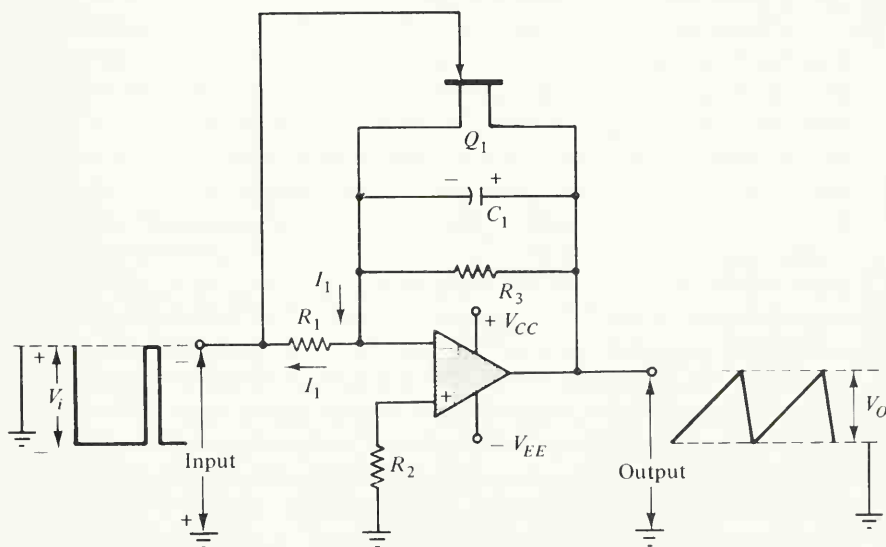


FIGURE 7-13. Miller integrator circuit as ramp generator.

The circuit in Figure 7-13 shows a Miller integrator operating as a ramp generator. The negative-going pulse generates the positive ramp by producing current I_1 in the direction shown. At this time n -channel FET (Q_1) is biased *off* by the negative input pulse. When the input goes to ground level, I_1 goes to zero and Q_1 is switched *on*. Q_1 discharges C_1 and keeps it discharged until the input becomes negative again. If C_1 is to be discharged in one-tenth of the charge time, then Q_1 must be able to pass a current ten times greater than the charge current I_1 . To ensure that Q_1 is biased *off* when the input pulse is present, the input pulse must have a negative amplitude greater than the FET pinchoff voltage.

7-9 TRIANGULAR WAVEFORM GENERATOR

A free-running triangular waveform generator can be constructed, using the output of the Miller circuit in Figure 7-11(a) to generate its own square wave input. Consider the circuit in Figure 7-14(a). The Miller integrator circuit used is exactly as discussed in the last section. The output of the Miller circuit is fed directly to an IC Schmitt trigger circuit. The Schmitt is designed to have a positive UTP and a negative LTP (see Sec. 6-7). An inverter connected directly following the Schmitt, inverts the Schmitt output and feeds it as an input to the Miller circuit.

Operation of the circuit is easily understood by considering the waveforms in Figure 7-14(b). At time t_1 the integrator output has reached the UTP (a positive voltage) and the Schmitt circuit output is negative at approximately $-(V_{EE} - 1\text{ V})$. This negative voltage produces a positive output from the inverter. The positive voltage from the inverter causes current I_1 to flow in the direction shown, charging C_1 positive on the left-hand side. As C_1 charges in this direction, the integrator output is a negative-going ramp. The integrator continues to produce a negative-going ramp while its input is a positive voltage. At time t_2 , the integrator output arrives at the LTP (negative voltage). The Schmitt trigger circuit output now becomes positive and causes the inverter output to become negative. The negative input to the integrator reverses the direction of I_1 . Thus the integrator output becomes a positive-going ramp. This positive-going ramp generation continues until the integrator output arrives at the UTP of the Schmitt circuit once again. Synchronizing pulses applied via C_2 lower the trigger point of the Schmitt circuit, causing it to trigger before the ramp arrives at its normal peak level.

The circuit described above generates a triangular waveform with a constant peak-to-peak output amplitude and a constant frequency. The

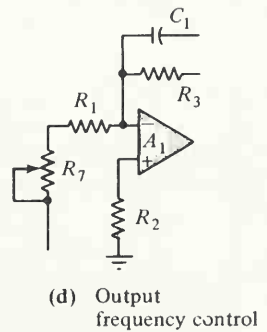
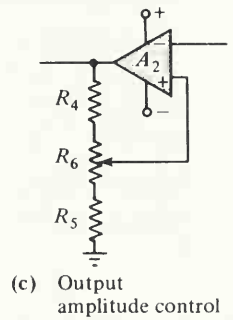
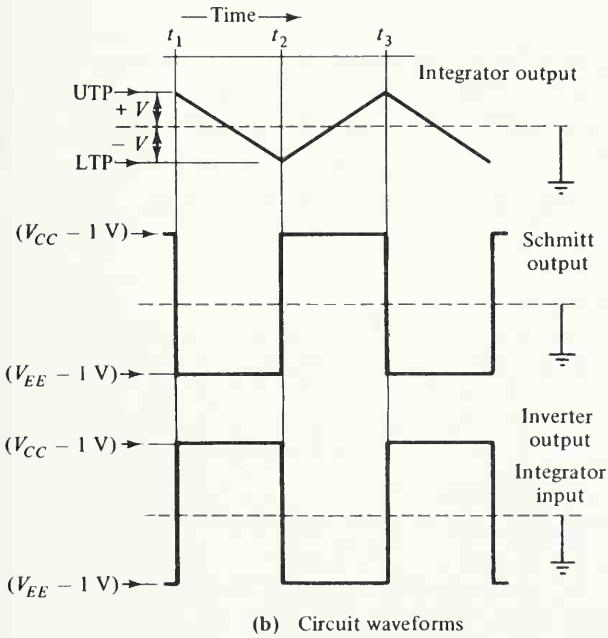
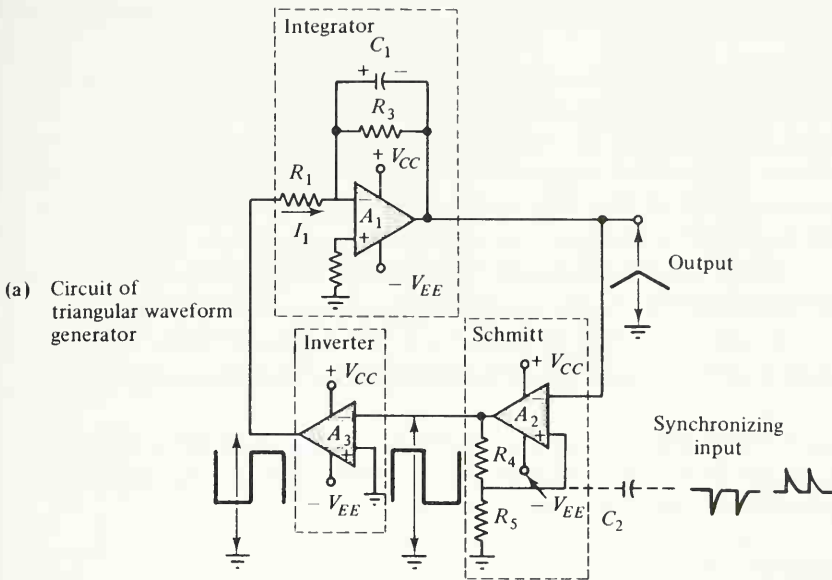


FIGURE 7-14. Triangular waveform generator circuit, circuit waveforms, and controls.

modifications shown in Figures 7-14(c) and (d) allow both frequency and amplitude adjustment. R_6 adjusts the UTP and LTP of the Schmitt circuit, and thus controls the peak-to-peak output amplitudes. R_7 affords adjustment of the input current to the integrator, and therefore controls the rate of charge of C_1 . This means that the ramp time period is controlled by adjusting R_7 .

In the design of a triangular waveform generator, each section must be treated separately.

EXAMPLE 7-10

Design a free-running triangular waveform generator to have a peak-to-peak output of 4 V at a frequency of 250 Hz. Use $\mu A741$ operational amplifiers and a supply voltage of ± 15 V.

solution

Schmitt circuit. For 4 V, p-to-p, the Schmitt circuit UTP = 2 V and LTP = -2 V. A Schmitt circuit can be designed as in Example 6-7 to give these desired trigger points.

Inverter circuit. The inverter is simply an operational amplifier connected as shown in Figure 7-14(a). The inverter output is approximately $+(V_{CC} - 1 \text{ V})$ and $-(V_{EE} - 1 \text{ V})$. That is, the inverter output $\simeq \pm(15 \text{ V} - 1 \text{ V}) \simeq \pm 14 \text{ V}$.

Miller integrator circuit. The input to the Miller circuit is the inverter output, that is, $\simeq \pm 14 \text{ V}$.

$$\begin{aligned}\text{Ramp amplitude} &= 4 \text{ V} \\ \text{Ramp time period} &= \frac{1}{2f} = \frac{1}{2 \times 250 \text{ Hz}} \\ &= 2 \text{ ms}\end{aligned}$$

Design the Miller circuit as in Example 7-9.

7-10 CRT TIME BASE

The need to synchronize a ramp generator is best understood by considering the time base for a cathode-ray oscilloscope. While the signal to be displayed provides vertical deflection of the electron beam, a ramp genera-

tor provides horizontal deflection. To obtain a correctly displayed signal, the electron beam must start at the left-hand side of the tube at the same instant that the input signal is going positive. Thus, the ramp must commence at this instant.

Figure 7-15 illustrates the process of obtaining synchronism of the ramp and the input signal. The signal normally is applied to a *vertical amplifier*, which controls the voltage on the vertical deflecting plates. This amplifier provides two equal output voltages, which are opposite in polarity, to the deflecting plates. One output is also fed to a Schmitt trigger which simply converts it to a square wave. The square wave is then dif-

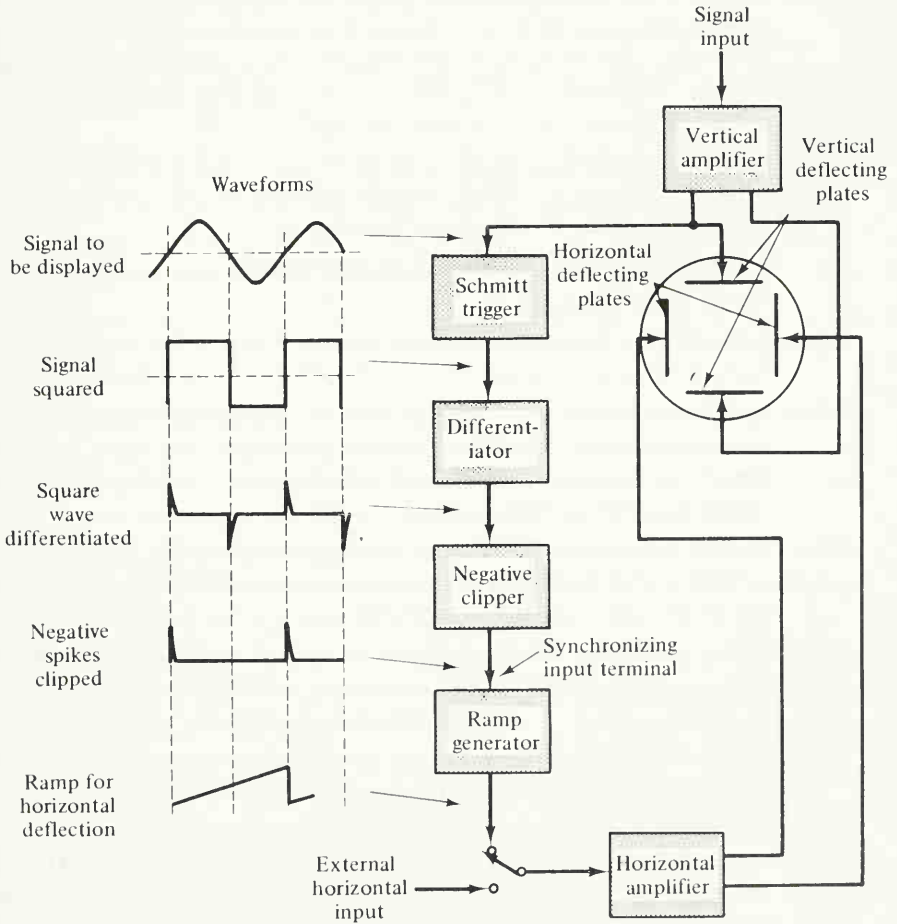


FIGURE 7-15. Automatic time base for cathode ray tube.

ferentiated to obtain a spike waveform, and the negative spikes are clipped off. This results in a series of positive spikes, each of which occurs exactly at the instant that the input signal is entering its positive half-cycle. These spikes are fed to the ramp generator synchronizing input terminal, causing the ramp to return instantaneously to its starting level.

REVIEW QUESTIONS AND PROBLEMS

- 7-1 Sketch the circuit of a simple CR ramp generator. Briefly explain its operation and its limitations. Also sketch the typical input and output waveforms.
- 7-2 Design a CR ramp generator to give an output of 3 V peak. The supply voltage is 20 V, and the load to be connected at the output is 330 k Ω . The ramp is to be triggered by a negative-going pulse with an amplitude of 4 V, PW = 3 ms, and time interval between pulses of 0.3 ms. Take the transistor $h_{FE(\min)} = 70$.
- 7-3 Sketch the circuit of a CR ramp generator using a transistor constant current circuit. Briefly explain how the circuit operates. Also sketch typical input and output waveforms.
- 7-4 Design a constant current circuit for the CR ramp generator designed in Problem 7-2.
- 7-5 Redesign the constant current circuit of Problem 7-4 to make the ramp amplitude adjustable from 2 V to 4 V.
- 7-6 Sketch the circuit of a UJT relaxation oscillator with adjustable output frequency. Sketch the output waveform, and show how the circuit can be synchronized by external pulses. Briefly explain the operation of the circuit.
- 7-7 Design a relaxation oscillator using a 2N3980 UJT. The supply voltage is 25 V and the output frequency is to be 2 kHz. Calculate the amplitude of the output waveform.
- 7-8 Using a 2N6027 PUT, design a relaxation oscillator to operate from a supply of 20 V. The output is to be 7 V peak at a frequency of 3 kHz.
- 7-9 Sketch the circuit of a transistor bootstrap ramp generator. Show the waveforms, and explain the operation of the circuit.
- 7-10 A transistor bootstrap generator is to produce an output of 7 V, with a time period of 2.5 ms. The load resistor is to be 1.2 k Ω , and the ramp is to be linear to within 3%. Design a suitable circuit using transistors with $h_{FE(\min)} = 120$ and $V_{CC} = \pm 20$ V.

- 7-11** Sketch the circuit of a bootstrap ramp generator using an IC operational amplifier. Briefly explain the operation of the circuit, drawing a comparison between it and the transistor bootstrap circuit.
- 7-12** Design a bootstrap generator using a $\mu A741$ operational amplifier. The circuit specification is the same as for the circuit in Problem 7-10.
- 7-13** Sketch the circuit of a free-running bootstrap ramp generator. Show the waveforms and carefully explain the operation of the circuit. Also, show how the input frequency and amplitude may be controlled.
- 7-14** Design a free-running bootstrap ramp generator using $\mu A741$ IC operational amplifiers. The output ramp is to have an amplitude of ± 3 V and frequency of 2 kHz. Use a supply voltage of ± 12 V.
- 7-15** Sketch the circuit of a Miller integrator, and explain its operation. Show output and input waveforms.
- 7-16** Design a Miller integrator circuit to produce a triangular output waveform with a peak-to-peak amplitude of 3 V. The input is a ± 8 V square wave with a frequency of 750 kHz. Use a $\mu A741$ operational amplifier with a supply of ± 12 V. Calculate the lowest operating frequency for the integrator.
- 7-17** Sketch a Miller integrator circuit connected to operate as a ramp generator. Show the input and output waveforms, and explain the circuit operation.
- 7-18** Sketch the circuit of a free-running triangular waveform generator using IC operational amplifiers. Show all the waveforms in the circuit, and carefully explain the overall circuit operation. Also, show how the output amplitude and frequency may be controlled.
- 7-19** Design a free-running triangular waveform generator to have an output of ± 2.5 V at a frequency of 500 Hz. Use $\mu A741$ operational amplifiers and a supply of ± 12 V.
- 7-20** Sketch the block diagram of an automatic time base for a cathode-ray tube. Show the waveforms at the various points in the diagram, and explain the operation of the system.

Chapter 8

Monostable and Astable Multivibrators

INTRODUCTION

The **MONOSTABLE MULTIVIBRATOR** has one stable state, and may be triggered temporarily into another state. When triggered, the circuit generates an output pulse of constant width and amplitude. In the collector-coupled monostable circuit, the transistors are switched into saturation. The emitter-coupled circuit may be designed for saturated or unsaturated operation. An IC operational amplifier may be employed as a monostable multivibrator by the external connection of appropriate resistances and capacitances. Integrated circuit units also are available for direct application as monostable multivibrators.

The **ASTABLE MULTIVIBRATOR** has no stable state; that is, the circuit oscillates between two temporary states. Astable circuits normally are designed to operate as square wave generators.

8-1 COLLECTOR-COUPLED MONOSTABLE MULTIVIBRATOR

The monostable multivibrator (also known as a *one-shot multivibrator*) has a single stable condition. One transistor is normally *on* and the other transistor is normally *off*. The condition can be reversed by application of a triggering pulse, which turns *on* the normally *off* transistor and switches *off* the normally *on* transistor. The reversed condition lasts only for a brief time period, dependent upon the circuit components.

Consider the *collector-coupled* monostable circuit shown in Figure 8-1. The circuit is described as collector-coupled because the collector terminal of Q_2 is coupled via R_1 and R_2 to the base terminal of Q_1 . In the normal dc condition of the circuit, base current I_{B2} is provided from V_{CC} to Q_2 via resistance R_B . Thus transistor Q_2 is normally *on*. At this time, diode D_1 is forward-biased and has no significant effect on Q_2 . The function of D_1 will become apparent later. With Q_2 *on* in saturation, the collector voltage of Q_2 is $(V_{CE(sat)} + V_{D1})$ above ground level. The base voltage V_{B1} of Q_1 is determined by the negative supply voltage V_{BB} and by R_1 and R_2 , as well as the collector voltage of Q_2 . With Q_2 collector near ground level, V_{B1} is likely to be negative (*i.e.*, Q_1 base is biased below its grounded emitter). Therefore, with Q_2 normally *on*, Q_1 is normally *off*.

When Q_1 is *off*, its collector current is zero. Therefore, there is no voltage drop across R_{L1} , and the collector of Q_1 is at the supply voltage level V_{CC} . Also, with Q_2 *on*, the base voltage of Q_2 is $V_{B2} = V_{BE} + V_{D1}$. On the right-hand terminal of capacitor C_1 the voltage is V_{B2} , and on the left-hand terminal it is V_{CC} . Hence the capacitor voltage is $E_o = V_{CC} - V_{B2}$, positive on the left-hand side as shown in Figure 8-1.

Now consider what would occur if Q_1 were triggered *on* to saturation for a brief instant. (This could be made to occur by, for example, capacitor-coupling a positive-going spike to the base of Q_1 as shown in Figure 8-1.) The collector voltage of Q_1 drops almost to ground level. Capacitor C_1 will not lose its charge E_o instantaneously; therefore, when the left-hand terminal of C_1 drops to $V_{CE(sat)}$ the right-hand terminal will drop to $(V_{CE(sat)} - E_o)$. Consequently, Q_2 base voltage goes to $(V_{CE(sat)} - E_o)$ —*i.e.*, Q_2 is biased *off*. With Q_2 *off*, there is no longer a collector current to produce a voltage drop across R_{L2} . Thus, V_{C2} rises, Q_1 base is biased above ground level, and Q_1 remains *on*. It is seen that when Q_1 is triggered *on* briefly, Q_2 goes *off* and Q_1 remains *on*. As will be seen Q_1 stays *on* only for a brief time.

The transistor switching process is illustrated by the waveforms in Figure 8-2. Prior to Q_1 being triggered *on*, the voltages are: $V_{B1} = -V$,

Refer again to the waveforms in Figure 8-2. It is seen that when the voltage at Q_2 collector is a positive-going pulse, that at Q_1 collector is a negative-going pulse. These two pulses are equal in width and either or both may be taken as output from the circuit. The pulse width of the output depends upon the values of C_1 and R_B . If R_B is made variable the output pulse width may be adjusted.

The monostable multivibrator now can be described as a circuit with one stable state capable of producing an output pulse when triggered. The output pulse width is constant, and can be made adjustable by making R_B adjustable (see Figure 8-3).

The purpose of D_1 is to protect the base-emitter voltage of transistor Q_2 against excessive reverse bias. When Q_1 is triggered on, V_{B2} falls to ap-

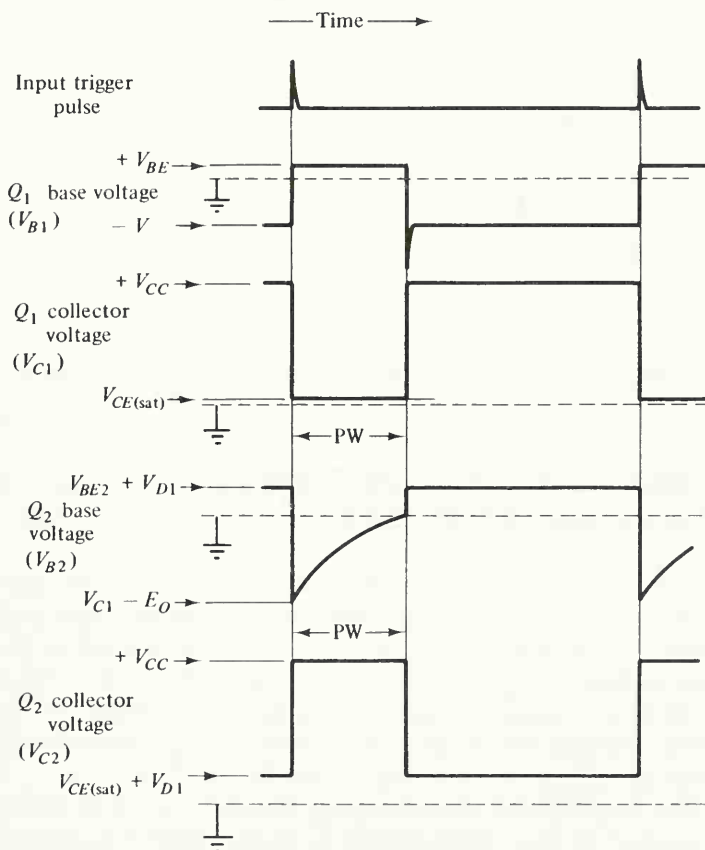


FIGURE 8-2. Monostable multivibrator circuit waveforms.

proximately $-V_{CC}$. Most transistors will not survive more than a reverse base-emitter voltage of 5 V, while most diodes might easily take reverse bias of 50 V without breaking down. Thus diode D_1 , in series with Q_2 emitter terminal, allows large negative voltages to be applied to Q_2 base. In some circuits, the reverse bias at the base of Q_1 may be excessive, and in this case a diode should be connected in series with Q_1 emitter.

Capacitor C_2 in Figure 8-1 is a speed-up capacitor to improve the transistor turn-on and turn-off times. The function of the speed-up capacitor is discussed in detail in Sec. 4-4.

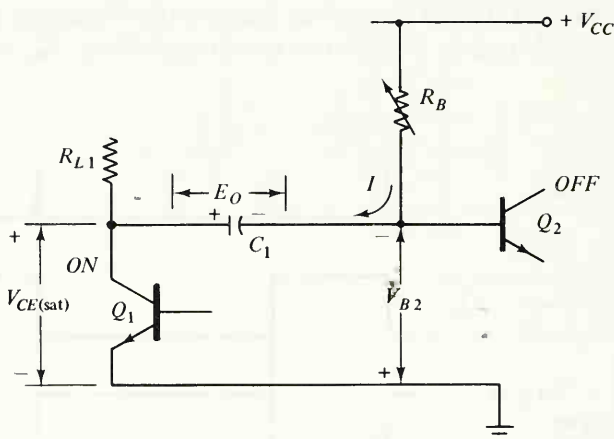


FIGURE 8-3. Negatively charged capacitor C_1 discharged via R_B when Q_1 is on and Q_2 is off.

8-2 DESIGN OF A COLLECTOR-COUPLED MONOSTABLE MULTIVIBRATOR

The design of a monostable multivibrator usually begins with specifications of the output pulse width, the supply voltage, the load, and, perhaps, the transistors to be employed. As with other circuits, it might be possible to connect the load directly into the circuit as either R_{L1} or R_{L2} . More frequently, the load is coupled to Q_2 collector, and R_{L2} is selected to be much smaller than the load resistance. Alternatively, I_{C2} may be selected to be much larger than the maximum output load current.

I_{C2} and R_{L2} must be chosen so that transistor Q_2 is in saturation, that is, $(I_{C2}R_{L2}) \simeq V_{CC}$. Base current I_{B2} is calculated as $I_{C2}/h_{FE(\min)}$, the minimum value of h_{FE} ensuring that I_{B2} is large enough to drive Q_2 to saturation. The base resistance R_{B2} is then calculated as $(V_{CC} - V_{B2})/I_{B2}$. R_{L1} usually is made equal to R_{L2} , and so $I_{C1} \simeq I_{C2}$.

Resistors R_1 and R_2 provide *on* or *off* bias to Q_1 base. For a stable bias voltage V_{B1} , the current I_2 that flows through R_1 and R_2 should be much larger than the base current to Q_1 . When Q_1 is *on*, I_{B1} flows through R_1 . If I_{B1} is not much smaller than I_2 , variations in I_{B1} may upset the bias voltage at Q_1 base. To achieve the condition $I_2 \gg I_{B1}$, R_1 and R_2 should be selected as small as possible. However, R_1 and R_2 also constitute a load on resistance R_{L2} ; thus to avoid overloading R_{L2} , R_1 and R_2 should be chosen as large as possible. These contradictory requirements are met by applying the rule-of-thumb that $I_2 \simeq I_{C2}/10$. Since $I_{C1} \simeq I_{C2}$, I_{B1} becomes $I_{C2}/h_{FE(\min)}$. Then, I_2 is $(h_{FE(\min)}/10) \times I_{B1}$. When a design is worked through, it will be seen that making $I_2 \simeq I_{C2}/10$ also results in R_1 and R_2 each being 5 to 10 times R_{L2} .

The output pulse width for a monostable circuit is dictated by the time taken for C_1 to discharge from its initial voltage level to approximately zero volt. Therefore, C_1 is calculated from Equation (2-2).

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}} \quad [\text{Equation (2-2)}]$$

For the collector-coupled monostable circuit,

$$e_c \simeq 0, \quad E = V_{CC}, \quad \text{and}$$

$$E_o = -(V_{CC} - V_{B2})$$

Note that C_1 is charged initially positive on the left-hand side and negative on the right-hand side. When Q_1 is *on* and Q_2 is *off*, C_1 tends to charge negative on the left-hand side, and positive on the right-hand side. Thus, the initial voltage E_o of C_1 must be taken as negative, and the charging voltage E as positive.

The initial value of Q_2 base voltage, that is, when Q_2 is *on*, is

$$V_{B2} = V_{BE} + V_{D1}$$

and

$$E_o = -(V_{CC} - V_{BE} - V_{D1})$$

$$t = \text{Specified PW}$$

$$C = C_1$$

$$R = R_B, \text{ which is}$$

the resistance through which C_1 is charged when Q_1 is *on* and Q_2 is *off*.

The speed-up capacitor C_2 is determined by a method similar to that employed for the inverter circuit and the Schmitt trigger circuit.

EXAMPLE 8-1

A collector-coupled monostable multivibrator is to operate from a $\pm 9\text{ V}$ supply. Transistor collector currents are to be 2 mA , and the transistors used have $h_{FE(\min)} = 50$. Neglecting the output pulse width, design a suitable circuit.

solution

The circuit is as shown in Figure 8-1. For Q_2 on and saturated [Figure 8-4(a)],

$$\begin{aligned} R_{L2} &\simeq \frac{V_{CC} - V_{D1}}{I_C} \\ &= \frac{9\text{ V} - 0.7\text{ V}}{2\text{ mA}} \\ &= 4.25\text{ k}\Omega \quad (\text{use } 4.7\text{ k}\Omega \text{ standard value}) \end{aligned}$$

$$\begin{aligned} I_{B2(\min)} &= \frac{I_C}{h_{FE(\min)}} \\ &= \frac{2\text{ mA}}{50} = 40\text{ }\mu\text{A} \end{aligned}$$

$$\begin{aligned} R_B &= \frac{V_{CC} - V_{BE} - V_{D1}}{I_{B2}} \\ &= \frac{9\text{ V} - 0.7\text{ V} - 0.7\text{ V}}{40\text{ }\mu\text{A}} \\ &= 190\text{ k}\Omega \quad (\text{use } 180\text{ k}\Omega \text{ standard value}) \end{aligned}$$

For Q_1 on and saturated [Figure 8-4(b)],

$$R_{L1} = R_{L2} = 4.7\text{ k}\Omega$$

To make $I_2 > I_{B1}$, let

$$\begin{aligned} I_2 &\simeq \frac{I_C}{10} \\ &= \frac{2\text{ mA}}{10} = 200\text{ }\mu\text{A} \end{aligned}$$

$$V_{B1} = V_{BE} = 0.7\text{ V} \quad (\text{when } Q_1 \text{ is on})$$

$$\begin{aligned}
 V_{R2} &= V_{B1} - V_{BB} \\
 &= 0.7 \text{ V} - (-9 \text{ V}) = 9.7 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 R_2 &= \frac{V_{R2}}{I_2} \\
 &= \frac{9.7 \text{ V}}{200 \mu\text{A}} \\
 &= 48.5 \text{ k}\Omega \quad (\text{use } 47 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

$$\begin{aligned}
 I_{B1} + I_2 &\simeq 200 \mu\text{A} + 40 \mu\text{A} \\
 &= 240 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 R_{L2} + R_1 &= \frac{V_{CC} - V_{B1}}{I_{B1} + I_2} \\
 &= \frac{9 \text{ V} - 0.7 \text{ V}}{240 \mu\text{A}} \\
 &= 34.6 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_1 &= (R_{L2} + R_1) - R_{L2} \\
 &= 34.6 \text{ k}\Omega - 4.7 \text{ k}\Omega \\
 &= 29.9 \text{ k}\Omega \quad (\text{use } 27 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

The circuit design is now complete (ignoring PW). V_{B1} should be calculated when Q_2 is *on* to determine that Q_1 is *off* at this time, and to check that the reverse bias is not excessive on Q_1 base-emitter junction.

When Q_2 is *on*,

$$\begin{aligned}
 V_{B1} &= V_{C2} - V_{R1} \\
 V_{C2} &= V_{D1} + V_{CE(\text{sat})} \\
 &\simeq 0.7 \text{ V} + 0.2 \text{ V} \\
 &= 0.9 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{R1} &= \frac{R_1}{R_1 + R_2} (V_{C2} - V_{BB}) \\
 &= \frac{27 \text{ k}\Omega}{27 \text{ k}\Omega + 47 \text{ k}\Omega} [0.9 \text{ V} - (-9 \text{ V})] \\
 &\simeq 3.6 \text{ V}
 \end{aligned}$$

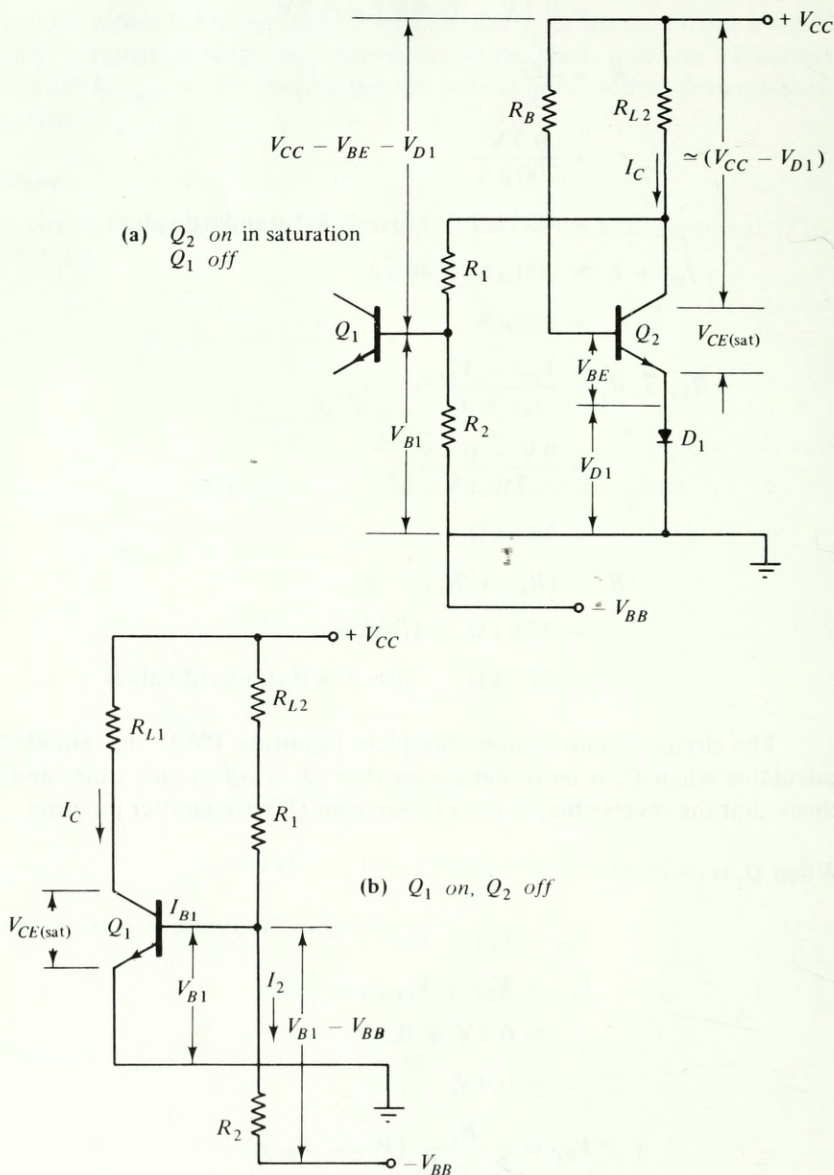


FIGURE 8-4. Monostable multivibrator circuit (a) for Q_2 on and (b) for Q_1 on.

$$\begin{aligned}\therefore V_{B1} &= 0.9 \text{ V} - 3.6 \text{ V} \\ &= -2.7 \text{ V}\end{aligned}$$

This value of V_{B1} is sufficient to ensure that Q_1 is biased *off* when Q_2 is *on*. Also -2.7 V is less than the typical limit of -5 V for a reverse-biased base-emitter junction.

EXAMPLE 8-2

For the circuit designed in Example 8-1, select a suitable capacitor to give an output pulse width of $250 \mu\text{s}$.

solution

By Equation (2-2)

$$e_c = E - (E - E_o)\epsilon^{\frac{-t}{CR}} \quad [\text{Equation (2-2)}]$$

$$(E - E_o)\epsilon^{\frac{-t}{CR}} = E - e_c$$

$$\epsilon^{\frac{-t}{CR}} = \frac{E - e_c}{E - E_o}$$

$$\epsilon^{\frac{t}{CR}} = \frac{E - E_o}{E - e_c}$$

$$\frac{t}{CR} = \ln \frac{E - E_o}{E - e_c}$$

$$C = \frac{t}{R \ln \left(\frac{E - E_o}{E - e_c} \right)}$$

$$e_c = 0 \text{ V}$$

$$E = V_{CC} = 9 \text{ V}$$

$$E_o = -(V_{CC} - V_{BE} - V_{D1})$$

$$= -(9 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V}) = -7.6 \text{ V}$$

$$t = 250 \mu\text{s}$$

$$R = R_B = 180 \text{ k}\Omega$$

$$\begin{aligned}
 \therefore C_1 &= \frac{250 \mu s}{180 \text{ k}\Omega \ln \left[\frac{9 \text{ V} - (-7.6 \text{ V})}{9 \text{ V} - 0 \text{ V}} \right]} \\
 &= 2.3 \times 10^{-9} \\
 &= 0.0023 \mu\text{F} \quad (\text{use } 0.0025 \mu\text{F standard capacitor value})
 \end{aligned}$$

8-3 TRIGGERING THE MONOSTABLE MULTIVIBRATOR

Monostable multivibrator triggering can be effected either by switching *off* the normally *on* transistor, or by turning *on* the normally *off* transistor. Figure 8-5(a) shows a positive-going spike capacitor coupled to the base of normally *off* transistor Q_1 . This raises Q_1 base above its grounded emitter, thus switching it *on*. Q_1 switch-*on* then causes Q_2 to switch *off*. The input spike “sees” resistances R_1 and R_2 in parallel as a load, as well as the transistor input resistance. Therefore, the spike has to supply current through R_1 and R_2 , as well as to supply base current to Q_1 . To ensure that Q_1 switches *on* and Q_2 switches *off*, the input current must be supplied for a time t equal to the turn-on time for Q_1 added to the turn-off time for Q_2 .

The arrangement in Figure 8-5(b) provides for Q_2 (the normally *on* transistor) to be switched *off*. In this case, the negative-going spike pulls Q_2 base below ground for the transistor turn-*off* time. During this brief time, C_1 behaves as a short circuit, so that the load “seen” by the input spike is $R_B \parallel R_{L1}$. This is greater than the load “seen” by the positive-going spike in Figure 8-5(a). Therefore, triggering by a negative-going spike at Q_{2B} requires a larger input current than triggering by a positive-going spike at Q_{1B} .

Perhaps the most effective monostable triggering circuit is that shown in Figure 8-5(c), in which an additional transistor Q_3 is employed. Q_3 normally is biased *off* by means of resistor R_3 shorting its base and emitter terminals together. Coupling capacitor C_c and resistor R_3 operate as a differentiating circuit (see Chapter 2), so that the pulse input is differentiated, as illustrated in the figure. Only the positive-going spike will turn *on* Q_3 . In the event that the negative-going spike is too large for Q_3 base-emitter, diode D_2 may be used to clip it off. When Q_3 switches *on*, its collector current causes a voltage drop across R_{L1} and the charge on capacitor C_1 causes Q_2 to be biased *off*. Thus Q_3 switch-*on* has the same

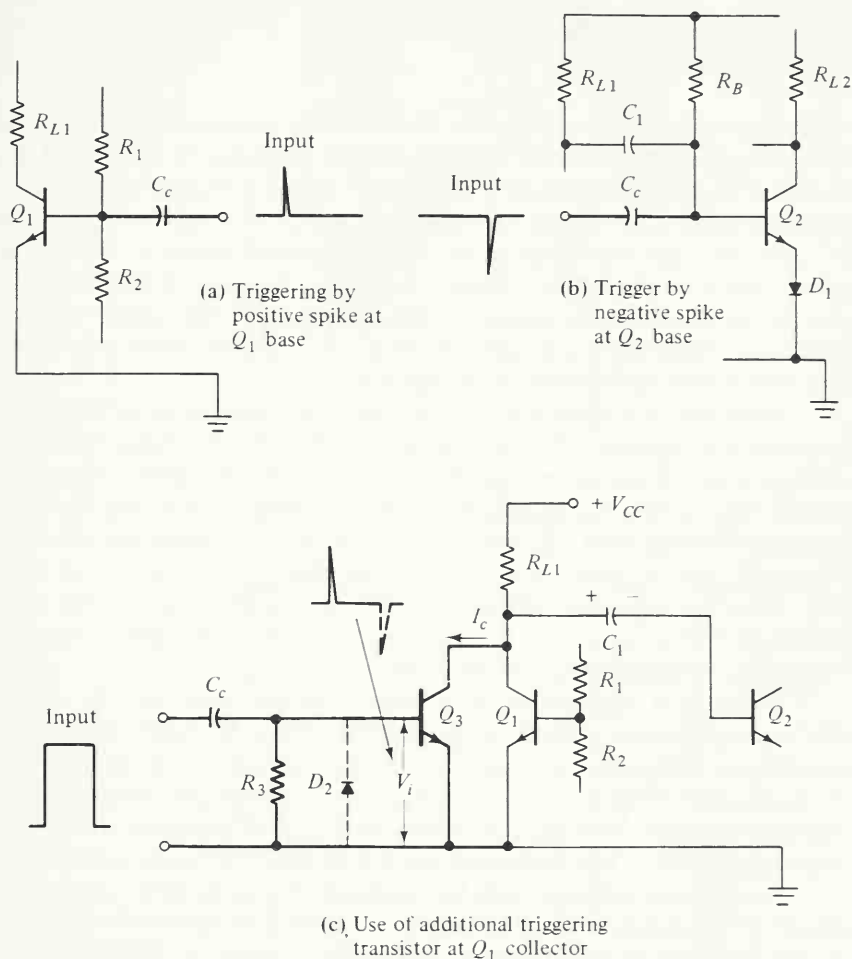


FIGURE 8-5. Various methods for triggering a monostable multivibrator.

effect as Q_1 switch-on. To correctly trigger the circuit of Figure 8-5(c) the input spike must hold Q_3 on for the turn-off time of Q_2 .

The design procedure for the triggering circuit of Figure 8-5(c) is similar to the capacitor-coupled inverter design in Example 5-5. This is also the procedure followed for selecting C_c in the circuit of Figure 8-5(a). Design of the circuit of Figure 8-5(b) is similar to the design given in Example 5-4.

8-4 EMITTER-COUPLED MONOSTABLE MULTIVIBRATOR

In the emitter-coupled monostable multivibrator (circuit in Figure 8-6), a resistance R_E connects both transistor emitter terminals to ground. Also, instead of R_2 being connected to a negative supply voltage, it now is connected to ground. The negative supply voltage is no longer required, and it is seen that one advantage of the emitter-coupled circuit is that it operates from a single supply voltage. Another advantage of this circuit is that the presence of R_E makes it easy to maintain the transistors unsaturated. Thus, the transistors can be made to switch faster than in the case of the collector-coupled multivibrator.

Reference to Figure 8-6(a) shows that transistor Q_2 is normally *on*, and that it is supplied with base current via R_B . At this time, there is a voltage drop V_E across resistor R_E , as shown in the figure. Also, the voltage drop across R_{L2} makes Q_2 collector voltage something less than the supply voltage level. Q_1 base is biased from Q_2 collector via potential divider R_1 and R_2 ; their ratio is such that with Q_2 *on*, V_{B1} is less than V_E . Therefore, Q_1 base voltage is below its emitter voltage, and Q_1 is biased *off*. With Q_1 *off*, its collector voltage equals the supply voltage. The initial voltage across C_1 at this time is $V_{CC} - V_{B2}^*$.

When Q_1 is triggered *on*, its collector voltage drops, and the charge on C_1 causes the base voltage of Q_2 to drop. When Q_2 begins to turn *off*, its collector voltage starts to rise, thus raising the base voltage of Q_1 . With Q_1 *on*, the new level of V_E is $V_{B1} - V_{BE1}$, and because the base of Q_2 is pushed below this level (by the charge on C_1) Q_2 is biased *off*. Then, Q_2 remains *off* until C_1 has discharged enough to allow V_{B2} to rise above V_E .

Speed-up capacitor C_2 may be employed, as for the collector-coupled circuit. If the supply voltage is kept low, the reverse base-emitter voltage for Q_2 may not be large enough to require a diode in series with the emitter terminal. Triggering methods for the emitter-coupled circuit are exactly the same as those for the collector-coupled multivibrator.

The design procedure for an emitter-coupled monostable multivibrator is similar to that for the collector-coupled circuit. When the circuit is designed for nonsaturated operation, a minimum V_{CE} level must be selected, and $h_{FE(\max)}$ must be used in the calculations.

A convenient arrangement for adjusting the output pulse width of an emitter-coupled monostable multivibrator is shown in Figure 8-7. V_{B1} is adjusted by means of potentiometer R_2 . The circuit is designed so that the maximum level of V_{B1} is less than the normal level of V_{B2} . When Q_1 is triggered *on*, the voltage drop at Q_1 collector and the charge on C_1 cause V_{B2} to be pushed below V_{B1} . Q_2 remains *off* until C_1 discharge allows V_{B2} to rise above V_{B1} again. The time for this to occur depends upon the

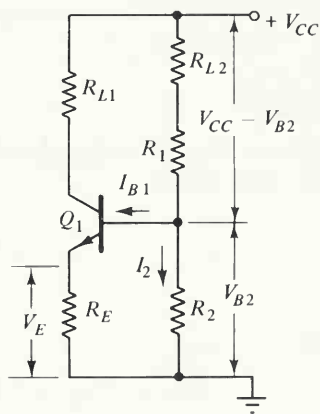
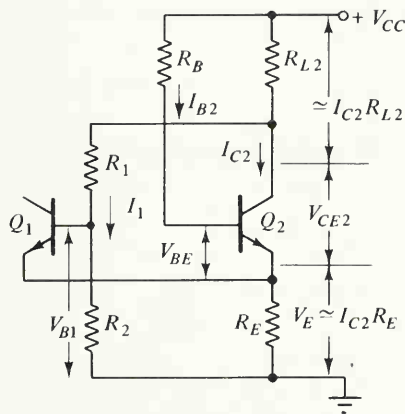
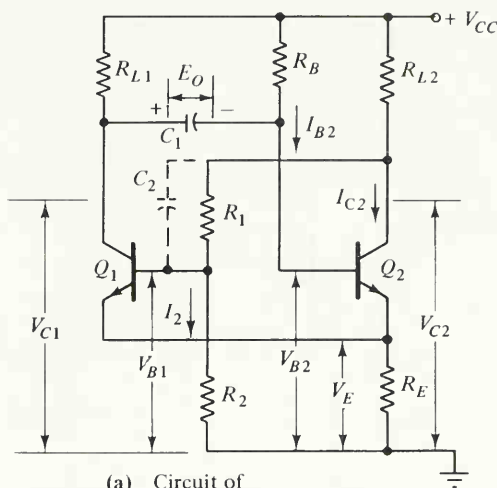


FIGURE 8-6. Emitter-coupled monostable multivibrator.

actual voltage level of V_{B1} . This time is also the output pulse width. Thus, control of V_{B1} provides pulse width control.

EXAMPLE 8-3

Design a nonsaturated emitter-coupled monostable multivibrator to operate from a 9 V supply. Transistor collector currents are to be 2 mA, and the transistors have $h_{FE(\max)} = 70$. Neglect the output pulse width.

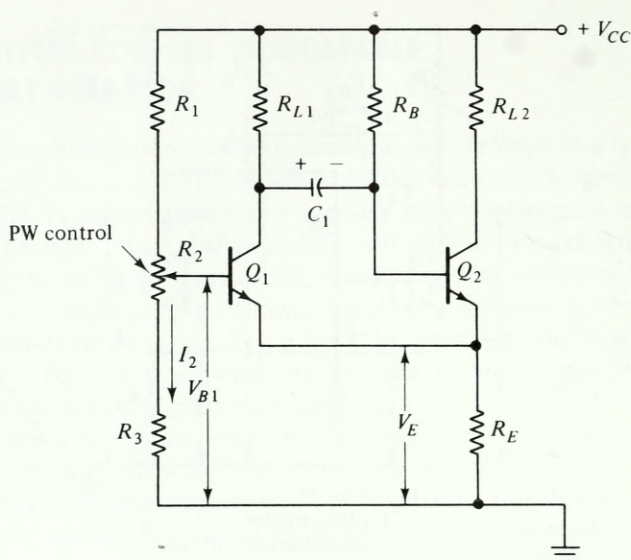


FIGURE 8-7. Emitter-coupled monostable multivibrator with PW control.

solution

Refer to Figure 8-6(b), showing Q_2 on. To avoid saturation, let $V_{CE2} = 3 \text{ V}$. This leaves

$$\begin{aligned} V_{RL2} + V_{RE} &= V_{CC} - V_{CE2} \\ &= 9 \text{ V} - 3 \text{ V} = 6 \text{ V} \end{aligned}$$

Let

$$V_{RE} = V_{RL2} = 3 \text{ V}$$

$$R_{L2} \simeq \frac{V_{RL2}}{I_C} = \frac{3 \text{ V}}{2 \text{ mA}} = 1.5 \text{ k}\Omega \quad (\text{standard value})$$

$$R_E = \frac{V_{RE}}{I_E} \simeq \frac{V_{RE}}{I_C} = 1.5 \text{ k}\Omega$$

$$I_{B(\max)} = \frac{I_{C2}}{h_{FE(\max)}} = \frac{2 \text{ mA}}{70} \simeq 28.6 \mu\text{A}$$

$$\begin{aligned} R_B &= \frac{V_{CC} - V_{B2}}{I_{B2}} \\ &= \frac{V_{CC} - (V_E + V_{BE})}{I_{B2}} \end{aligned}$$

$$\begin{aligned}
 &= \frac{9 \text{ V} - (3 \text{ V} + 0.7 \text{ V})}{28.6 \mu\text{A}} \\
 &= 185 \text{ k}\Omega \quad (\text{use } 180 \text{ k}\Omega \text{ standard resistance})
 \end{aligned}$$

Refer to Figure 8-6(c), showing Q_1 on. Let $I_2 = I_C/10$:

$$I_2 = \frac{2 \text{ mA}}{10} = 0.2 \text{ mA}$$

The reasons for this are explained in Sec. 8-2.

$$\begin{aligned}
 V_{B1} &= V_E + V_{BE} = 3 \text{ V} + 0.7 \text{ V} \\
 &= 3.7 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 R_2 &= \frac{V_{B1}}{I_2} = \frac{3.7 \text{ V}}{0.2 \text{ mA}} \\
 &= 18.5 \text{ k}\Omega \quad (\text{use } 18 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

Then I_2 becomes:

$$\begin{aligned}
 I_2 &= \frac{V_{B1}}{R_2} = \frac{3.7 \text{ V}}{18 \text{ k}\Omega} \\
 &= 0.206 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 I_{B1} &= \frac{I_{C1}}{h_{FE}} \\
 &= \frac{2 \text{ mA}}{70} \simeq 28.6 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 R_{L2} + R_1 &= \frac{V_{CC} - V_{B1}}{I_{B1} + I_2} \\
 &= \frac{9 \text{ V} - 3.7 \text{ V}}{28.6 \mu\text{A} + 0.206 \text{ mA}} \\
 &= 22.6 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_1 &= 22.6 \text{ k}\Omega - R_{L2} \\
 &= 22.6 \text{ k}\Omega - 1.5 \text{ k}\Omega = 21.1 \text{ k}\Omega \quad (\text{use } 22 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

Now check V_{BE1} when Q_2 is on. Refer again to Figure 8-6(b):

$$\begin{aligned}
 V_{CC} &= I_B R_B + V_{BE} + I_E R_E \\
 &= I_B R_B + V_{BE} + R_E (I_B + I_C) \\
 &= \frac{I_C}{h_{FE}} R_B + V_{BE} + R_E \left(\frac{I_C}{h_{FE}} + I_C \right)
 \end{aligned}$$

$$V_{CC} - V_{BE} = I_C \left[\frac{R_B}{h_{FE}} + R_E \left(\frac{1}{h_{FE}} + 1 \right) \right]$$

$$\begin{aligned}
 I_C &= \frac{V_{CC} - V_{BE}}{(R_B/h_{FE}) + R_E(1/h_{FE} + 1)} \\
 &= \frac{9 \text{ V} - 0.7 \text{ V}}{(180 \text{ k}\Omega/70) + 1.5 \text{ k}\Omega(1/70 + 1)} \\
 &\simeq 2.03 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 I_1 &= \frac{V_{C2}}{(R_1 + R_2)} \\
 &\simeq \frac{6 \text{ V}}{22 \text{ k}\Omega + 18 \text{ k}\Omega} \\
 &= 0.15 \text{ mA}
 \end{aligned}$$

$$I_C + I_1 = 2.03 \text{ mA} + 0.15 \text{ mA} = 2.18 \text{ mA}$$

$$\begin{aligned}
 V_{C2} &= V_{CC} - R_L(I_C + I_1) \\
 &= 9 \text{ V} - 1.5 \text{ k}\Omega(2.18 \text{ mA})
 \end{aligned}$$

$$V_{C2} = 5.73 \text{ V}$$

$$\begin{aligned}
 V_{B1} &= \frac{V_{C2} R_2}{R_1 + R_2} = \frac{5.73 \text{ V} \times 18 \text{ k}\Omega}{22 \text{ k}\Omega + 18 \text{ k}\Omega} \\
 &\simeq 2.6 \text{ V}
 \end{aligned}$$

and

$$\begin{aligned}
 V_E &= (I_B + I_C) R_E \\
 &= (I_C/h_{FE} + I_C) R_E \\
 &= (2.03 \text{ mA}/70 + 2.03 \text{ mA}) \times 1.5 \text{ k}\Omega \\
 &\simeq 3.1 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{BE1} &= V_{B1} + V_E \\
 &= 2.6 \text{ V} - 3.1 \text{ V} = -0.5 \text{ V} \quad (Q_1 \text{ is off})
 \end{aligned}$$

EXAMPLE 8-4

Determine the size of capacitor required if the circuit designed in Example 8-3 is to have $PW = 250 \mu s$.

solution

The initial capacitor voltage when Q_2 is *on* is:

$$\begin{aligned} E_o &= -(V_{CC} - V_{B2}) \\ &\simeq -(9 \text{ V} - 3.7 \text{ V}) \\ &= -5.3 \text{ V} \end{aligned}$$

Taking the initial charge as negative, the final capacitor voltage when Q_1 is *on* is:

$$\begin{aligned} e_c &= -(V_{C1} - V_{B1}) \\ &\simeq -(6 \text{ V} - 3.7 \text{ V}) \\ &= -2.3 \text{ V} \end{aligned}$$

Capacitor C_1 would eventually charge to E if Q_2 did not switch *on* again where

$$\begin{aligned} E &= V_{RL1} \\ &\simeq 3 \text{ V} \end{aligned}$$

This voltage is positive indicating that the capacitor voltage polarity is reversed from its initial state.

From Example 8-2:

$$\begin{aligned} C_1 &= \frac{t}{R_B \ln \left[\frac{E - E_o}{E - e_c} \right]} \\ &= \frac{250 \mu s}{180 \text{ k}\Omega \ln \left[\frac{3 \text{ V} - (-5.3 \text{ V})}{3 \text{ V} - (-2.3 \text{ V})} \right]} \\ &= 3.1 \times 10^{-9} \\ &\simeq 0.003 \mu\text{F} \quad (\text{standard capacitor value}) \end{aligned}$$

8-5 THE IC OPERATIONAL AMPLIFIER AS A MONOSTABLE MULTIVIBRATOR

An IC operational amplifier connected to function as a monostable multivibrator is shown in Figure 8-8(a). The inverting input terminal is grounded via resistance R_3 , and the noninverting terminal is biased above ground by resistances R_1 and R_2 . Since the noninverting terminal has a positive input, the output is saturated near the V_{CC} level. In Figure 8-8(b), it is seen that capacitor C_1 is normally charged positive on the right-hand side and negative on the left-hand side.

When a large enough positive-going input is coupled to the inverting terminal via C_2 , the inverting terminal voltage is raised above the level of the noninverting terminal. The output then switches rapidly to approximately $-(V_{EE} - 1 \text{ V})$. This pushes the noninverting terminal down to $-(V_{EE} - 1 \text{ V}) - E_o$, thus ensuring that the output remains negative until C_1 discharges. C_1 begins to discharge via R_1 and R_2 as soon as the output goes negative. Eventually C_1 will charge positive on the left-hand side and negative on the right-hand side. When the voltage on the left-hand side of C_1 rises above the voltage level at the inverting terminal, the noninverting terminal again has a positive input. Now, V_o rapidly returns to approximately $(V_{CC} - 1 \text{ V})$, and the circuit has returned to its original condition.

The output voltage of the circuit moved from its normal level of $(V_{CC} - 1 \text{ V})$ to a negative level $-(V_{EE} - 1 \text{ V})$, and eventually returned to $(V_{CC} - 1 \text{ V})$. Thus a negative output pulse is generated when the circuit is triggered. The output pulse width depends upon C_1 , the values of R_1 and R_2 , and the bias level at the inverting terminal.

Figure 8-9 shows a modification to the operational amplifier monostable circuit that facilitates pulse width control. Potentiometer R_4 provides for adjustment of the bias level at the inverting input terminal. When the circuit is triggered, and the output becomes negative, the condition is maintained until C_1 discharges sufficiently to allow the noninverting input terminal to rise above the inverting terminal bias voltage. Thus, if the bias voltage at the inverting terminal is adjustable, the time during which the output remains negative can be controlled. Thus the output pulse width is adjustable. The presence of R_4 also affects the minimum input amplitude that will trigger the circuit.

EXAMPLE 8-5

Design a monostable multivibrator using a $\mu\text{A}741$ operational amplifier with $V_{CC} = \pm 15 \text{ V}$. The circuit is to be triggered by a 1.5 V input spike, and the output pulse width is to be $200 \mu\text{s}$.

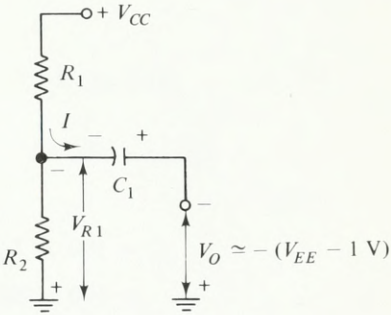
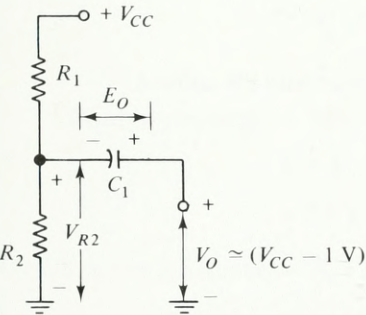
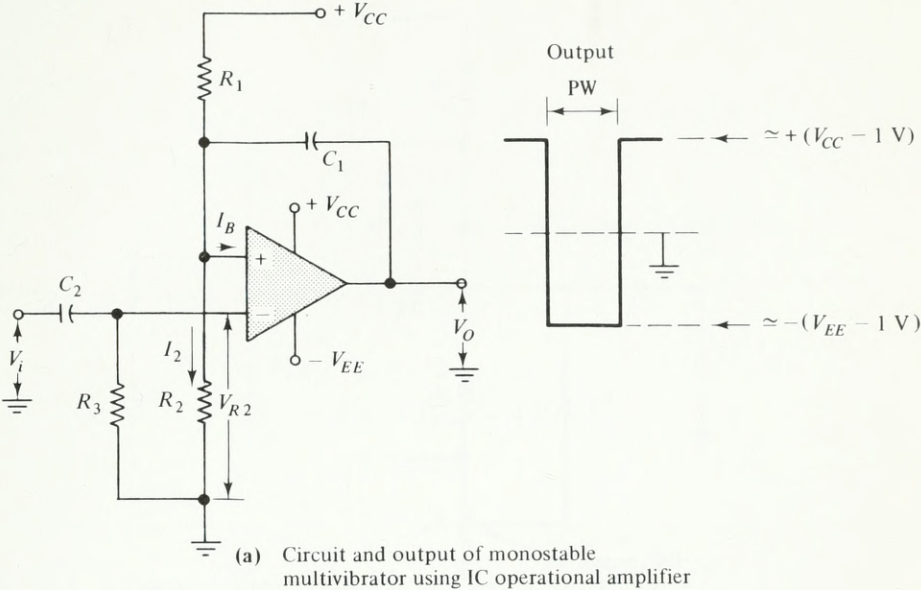


FIGURE 8-8. Monostable multivibrator using IC operational amplifier.

solution

To use a triggering input of 1.5 V, let

$$V_{R2} = 1 \text{ V} \quad [\text{See Figure 8-8(a).}]$$

Make $I_2 \gg I_B$. From the $\mu\text{A}741$ data sheet in Appendix 1-11,

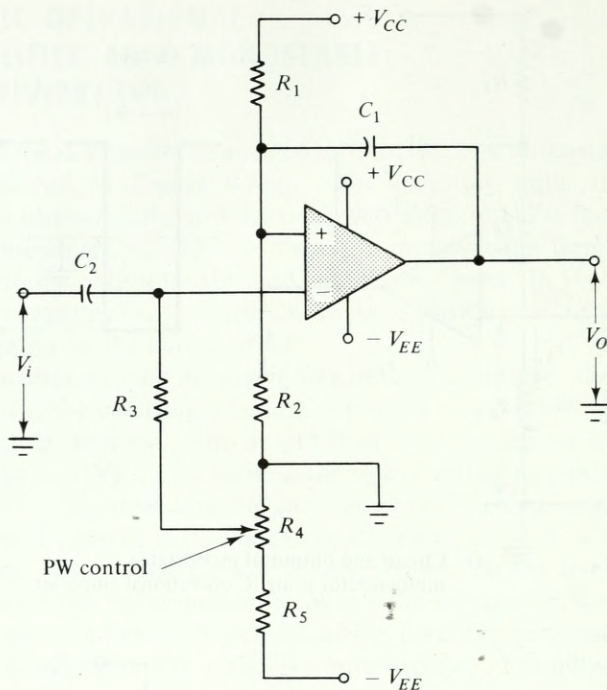


FIGURE 8-9. IC monostable circuit with PW control.

$$I_{B(\max)} = 500 \text{ nA}$$

Let

$$\begin{aligned} I_2 &= 100 \times I_{B(\max)} \\ &= 100 \times 500 \text{ nA} = 50 \mu\text{A} \end{aligned}$$

$$\begin{aligned} R_2 &= \frac{V_{R2}}{I_2} = \frac{1 \text{ V}}{50 \mu\text{A}} \\ &= 20 \text{ k}\Omega \quad (\text{use } 18 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

I_2 becomes

$$\begin{aligned} I_2 &= \frac{1 \text{ V}}{18 \text{ k}\Omega} \\ &\approx 56 \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{R1} &= V_{CC} - V_{R2} = 15 \text{ V} - 1 \text{ V} \\ &= 14 \text{ V} \end{aligned}$$

$$\begin{aligned}
 R_1 &= \frac{V_{R1}}{I_2} \\
 &= \frac{14 \text{ V}}{56 \mu\text{A}} = 250 \text{ k}\Omega \quad (\text{use } 270 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

$$\begin{aligned}
 R_3 &= R_1 \parallel R_2 = 18 \text{ k}\Omega \parallel 270 \text{ k}\Omega \\
 &\simeq 16.9 \text{ k}\Omega \quad (\text{use } 18 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

When V_o is positive, the initial charge on C_1 is

$$\begin{aligned}
 E_o &= V_{R2} - V_o \\
 &\simeq V_{R2} - (V_{CC} - 1 \text{ V}) \\
 &\simeq 1 \text{ V} - 15 \text{ V} + 1 \text{ V} \\
 &\simeq -13 \text{ V}
 \end{aligned}$$

When V_o is negative, the final charge on C_1 at switchover is

$$\begin{aligned}
 e_c &\simeq + (V_{EE} - 1 \text{ V}) \\
 &= +14 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{Charging voltage} &= E = V_{R2} - (-V_o) \\
 &= 1 \text{ V} + 14 \text{ V} \\
 &= 15 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{Charging resistance} &= R_1 \parallel R_2 \\
 &= 18 \text{ k}\Omega \parallel 270 \text{ k}\Omega \\
 &\simeq 16.9 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 C_1 &= \frac{t}{R \ln \left(\frac{E - E_o}{E - e_c} \right)} \\
 &= \frac{200 \mu\text{s}}{16.9 \text{ k}\Omega \ln \left[\frac{15 \text{ V} - (-13 \text{ V})}{15 \text{ V} - 14 \text{ V}} \right]} \\
 &= 3.55 \times 10^{-9} \\
 &= 0.00355 \mu\text{F} \quad (\text{use } 0.0036 \mu\text{F} \text{ standard value})
 \end{aligned}$$

8-6 IC MONOSTABLE MULTIVIBRATOR

Monostable multivibrators are available as single integrated circuit components. The MC951/MC851, made by Motorola, is typical of such components. Operating from a 5 V supply, the unit provides two output pulses which are complementary. The outputs have an amplitude of approximately 2 V, and are generated when a negative-going input signal is applied. Typically, the output pulse width is 100 ns, but can be extended by externally connecting an additional resistor and capacitor.

The circuit of the MC951/MC851 is shown in Figure 8-10. Supply voltage and ground terminals are pins #14 and #7 respectively. Output terminals are pins #1 and #6. Four input terminals are provided; pin #5 is a direct-coupled terminal, #2 is capacitor-coupled, and pins #3 and #4 are diode- and capacitor-coupled.

When no external components are employed, pin #9 is connected to V_{CC} . Then, the 9 k Ω resistance and 20 pF capacitance determine the output pulse width as approximately 100 ns. When an external capacitance is connected across pins #10 and #11 (i.e., in parallel with the 20 pF capacitance), the pulse width becomes:

$$PW \simeq 4.5(C_{ext} + 20)ns$$

where C_{ext} is in pF.

With pin #9 open-circuited, an external resistance with a value between 9 k Ω and 15 k Ω may be connected from pin #10 to V_{CC} . This is in addition to the external capacitor. The pulse width now becomes:


$$PW \simeq 0.5 R_{ext}(C_{ext} + 20)ns$$

where R_{ext} is in k Ω , and C_{ext} is in pF.

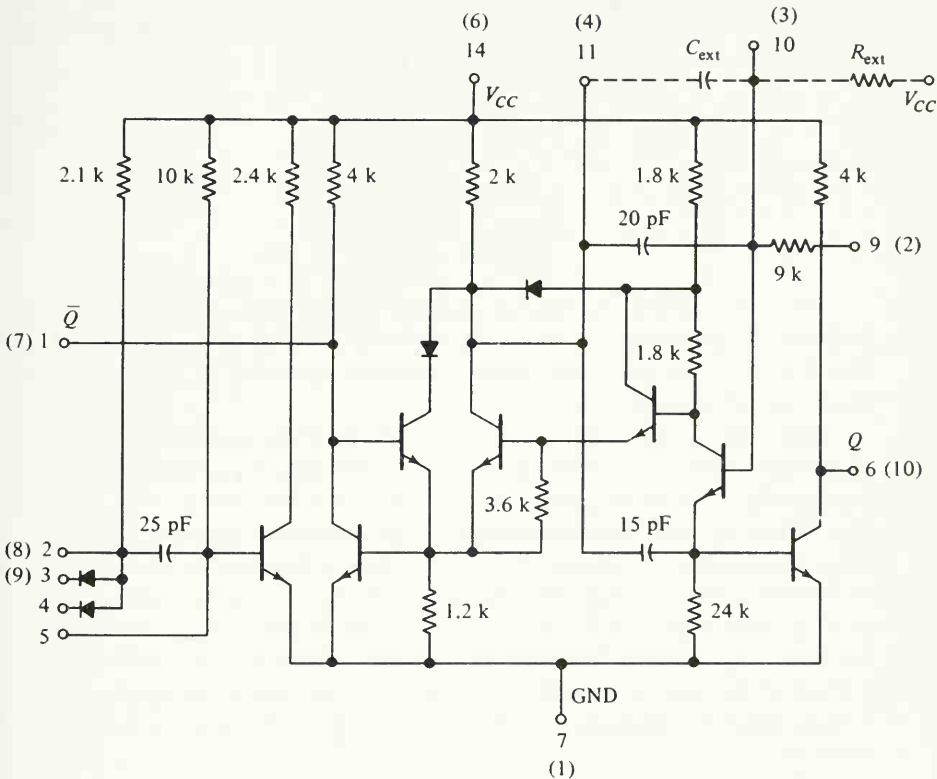8-7 ASTABLE MULTIVIBRATOR

The *astable multivibrator* has no stable state. Instead, the circuit oscillates between the states, (Q_1 on, Q_2 off) and (Q_2 on, Q_1 off). The output at the collector of each transistor is a square wave; therefore, the circuit is applied as a *square wave generator*.

Consider the circuit of a *collector-coupled astable multivibrator* shown in Figure 8-11(a). Each transistor has a bias resistance R_b and each is capacitor-coupled to the collector of the other transistor. This is similar to the arrangement of the normally *on* transistor in a monostable multivibrator. Consequently, each transistor in an astable circuit functions in



Note: When the internal timing resistor (9 k Ω) is to be used, connect Pin 9 to Pin 14 (flat and dual in-line packages) or pins 2 and 6 (can). Do not make this connection if using the external capacitor and resistor.

Number at end of terminal represents pin number for flat and dual in-line packages. Number in parenthesis indicates pin number for metal can.

FIGURE 8-10. MC951/MC851 IC monostable multivibrator.
(Courtesy of Motorola, Inc.)

the same way as the normally-on transistor in a monostable circuit. When Q_1 is on and Q_2 is off, capacitor C_1 is charged to $(V_{CC} - V_{BE1})$, positive on the right-hand side. For Q_2 on and Q_1 off, C_2 is charged to $(V_{CC} - V_{BE2})$, positive on the left-hand side.

Referring to the circuit waveforms in Figure 8-11(b), it is seen that prior to time t_1 , transistor Q_1 is on and its collector voltage is $V_{CE(sat)}$. Also, Q_2 is off, and its collector voltage is V_{CC} . Thus, capacitor C_1 is charged to $(V_{CC} - V_{BE1})$. At t_1 , the base voltage of transistor Q_2 rises

above ground causing Q_2 to switch *on*. The collector current I_{C2} now causes Q_2 collector voltage to fall to $V_{CE(sat)}$. Since C_1 will not discharge instantaneously, the base voltage of Q_1 becomes;

$$\begin{aligned} V_{B1} &= V_{C2} - (\text{Charge on } C_1) \\ &= V_{CE(sat)} - (V_{CC} - V_{BE1}) \\ &\simeq -V_{CC} \end{aligned}$$

With its emitter grounded, and its base at $-V_{CC}$, transistor Q_1 is biased *off*. Therefore, at time t_1 , the collector voltage of Q_1 raises to V_{CC} . The rise of V_{C1} is not instantaneous, because capacitor C_2 is charged via R_{L1} as Q_1 switches *off*.

Between times t_1 and t_2 , the base voltage of Q_2 remains at V_{BE} , and Q_2 remains biased *on*. During this time, however, C_1 discharges via resistance R_{B1} . Therefore, the voltage at Q_1 base rises from $-V_{CC}$ toward V_{CC} . When Q_1 base rises above ground, the transistor begins to switch *on*. The falling collector voltage of Q_1 is coupled to Q_2 base via capacitor C_2 , thus causing Q_2 to switch *off*. As Q_2 turns *off* its collector voltage rises, and C_1 is recharged via R_{L2} and Q_1 base. This pumps a large current into the base of Q_1 making it switch *on* very fast. Consequently, the collector voltage of Q_1 falls very rapidly at switch-*on*. The switchover process is reversed when C_2 discharges sufficiently to allow Q_2 base to rise above ground.

The output pulse width from either transistor is equal to the time during which the transistor is *off*. This is the time taken by the capacitor to discharge approximately from V_{CC} to zero volt.

$$t = CR \ln \left(\frac{E - E_o}{E - e_c} \right) \quad [\text{Equation (2-8)}]$$

In this equation,

$$t = \text{PW}, \quad C = C_1 = C_2, \quad R = R_{B1} = R_{B2}$$

and E , is equal to the supply voltage, V_{CC} ; E_o , the initial capacitor charge, is equal to $-V_{CC}$. (Note this is taken as negative, because the capacitor would eventually charge with reversed polarity to approximately $+V_{CC}$ if transistor switchover did not occur.)

The final capacitor charge at switchover, $e_c = 0 \text{ V}$.

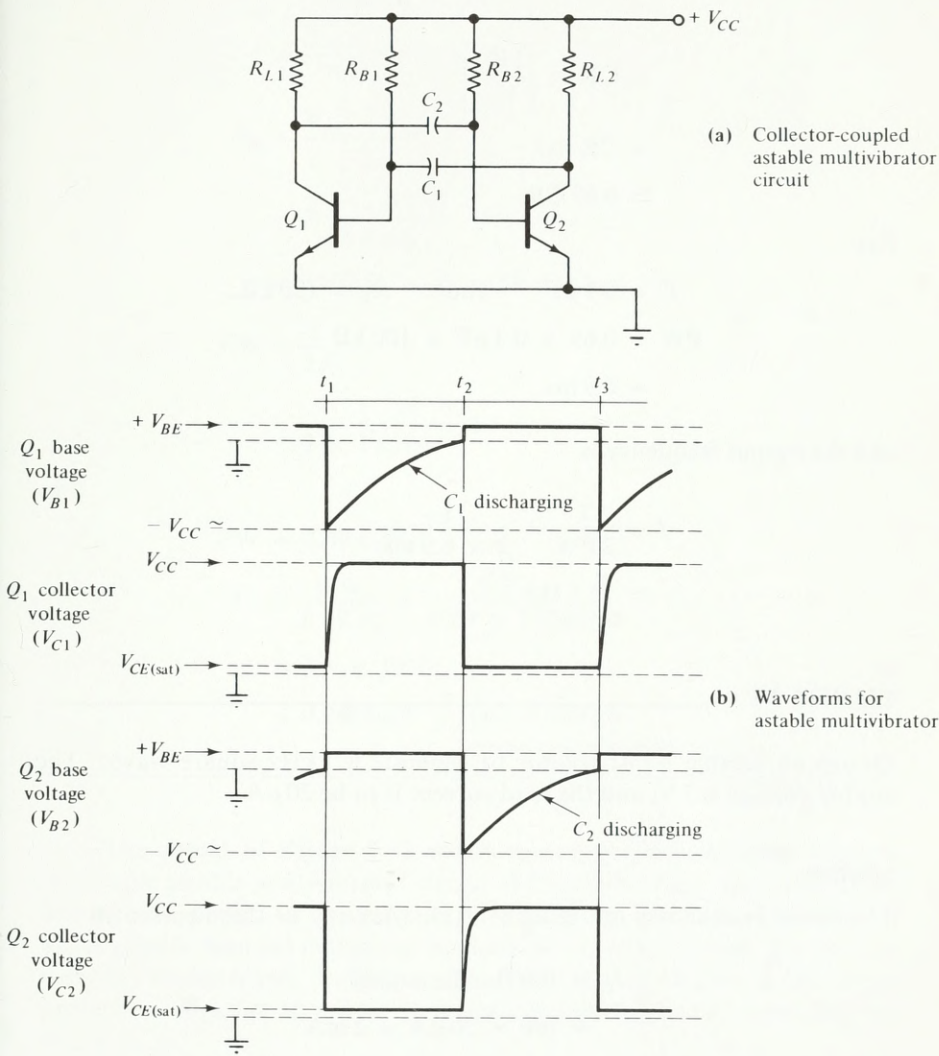


FIGURE 8-11. Circuit and waveforms of collector-coupled astable multivibrator.

$$\begin{aligned}
 PW &= CR \ln \left[\frac{V_{CC} - (-V_{CC})}{V_{CC} - 0} \right] \\
 &= CR \ln \left[\frac{2V_{CC}}{V_{CC}} \right] \\
 &= CR \ln 2 \\
 &\simeq 0.69 CR
 \end{aligned}$$

For

$$\begin{aligned}
 C &= 0.1 \mu\text{F} \quad \text{and} \quad R_B = 100 \text{ k}\Omega, \\
 PW &= 0.69 \times 0.1 \mu\text{F} \times 100 \text{ k}\Omega \\
 &= 6.9 \text{ ms}
 \end{aligned}$$

and the output frequency is

$$\begin{aligned}
 f &= \frac{1}{2 PW} = \frac{1}{2 \times 6.9 \text{ ms}} \\
 &\simeq 72.5 \text{ Hz}
 \end{aligned}$$

EXAMPLE 8-6

Design an astable multivibrator to generate a 1 kHz square wave. The supply voltage is 5 V, and the load current is to be 20 μA .

solution

The circuit is as shown in Figure 8-11(a). Make $I_C \gg$ (load current):

$$\begin{aligned}
 I_C &= 100 \text{ (load current)} \\
 &= 100 \times 20 \mu\text{A} = 2 \text{ mA}
 \end{aligned}$$

Use 2N3904 transistors which, from the data sheet in Appendix 1-4, have a value of $h_{FE(\min)}$ of 70.

$$\begin{aligned}
 R_L &\simeq V_{CC}/I_C = \frac{5 \text{ V}}{2 \text{ mA}} \\
 &= 2.5 \text{ k}\Omega \quad (\text{use } 2.7 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

$$\begin{aligned}
 I_{B(\min)} &= \frac{I_C}{h_{FE(\max)}} \\
 &= \frac{2 \text{ mA}}{70} \simeq 28.6 \mu\text{A} \\
 R_B &= \frac{V_{CC} - V_{BE}}{I_B} \\
 &= \frac{5 \text{ V} - 0.7 \text{ V}}{28.6 \mu\text{A}} \\
 &= 150 \text{ k}\Omega \quad (\text{standard value}) \\
 \text{PW} &= \frac{1}{2f} \\
 &= \frac{1}{2 \times 1 \text{ kHz}} = 0.5 \text{ ms}
 \end{aligned}$$

and

$$\begin{aligned}
 \text{PW} &= 0.69 C_1 R_B \\
 C_1 &= \frac{\text{PW}}{0.69 R_B} = \frac{0.5 \text{ ms}}{0.69 \times 150 \text{ k}\Omega} \\
 &= 4.8 \times 10^{-9} \\
 &= 0.0048 \mu\text{F} \quad (\text{use } 0.005 \mu\text{F} \\
 &\quad \text{standard capacitor value})
 \end{aligned}$$

The circuit of Figure 8-12 shows several possible modifications to the simple astable multivibrator circuit of Figure 8-11(a). Each transistor has its base biased to approximately $-V_{CC}$ when *off*. Consequently, if V_{CC} is greater than the maximum base-emitter reverse voltage, the transistors may be destroyed. Inclusion of diodes D_1 and D_2 (Figure 8-12), afford protection for the transistor base-emitter junctions, as explained in Sec. 8-1.

If C_1 and C_2 are not equal capacitors, one transistor will remain *off* for a longer time than the other one. In this case, the output is no longer a square wave, as the transistor with the largest capacitor at its base remains *off* longest. The output frequency of the circuit may be made adjustable by including a variable resistor R_1 in series with one of the base bias resistors. In Figure 8-12, R_1 controls the rate of discharge of capacitor C_1 ; thus R_1 can be used to adjust the *off*-time of Q_1 .

Occasionally the frequency of an astable multivibrator has to be synchronized to some external frequency. Figure 8-12 shows a negative-going synchronizing spike input capacitor-coupled to the base of Q_2 . When the spike input is applied, Q_2 is switched *off* and C_2 is recharged to its maximum voltage. Q_2 then remains *off* for its normal pulse width.

One problem with the collector-coupled astable circuit is that it may not always start oscillating when the supply voltage is switched *on*. Because of the circuit symmetry, it can happen that both transistors switch *on* and remain *on*. Oscillation can be started by shorting one of the transistor bases to its emitter terminal for a brief instant. However, this usually is not practical. The emitter-coupled astable multivibrator circuit shown in Figure 8-13 solves the problem. In this circuit, when one transistor begins to conduct, the other transistor has its emitter voltage raised and its base voltage reduced. Thus, it is almost impossible for the two to remain *on* at one time.

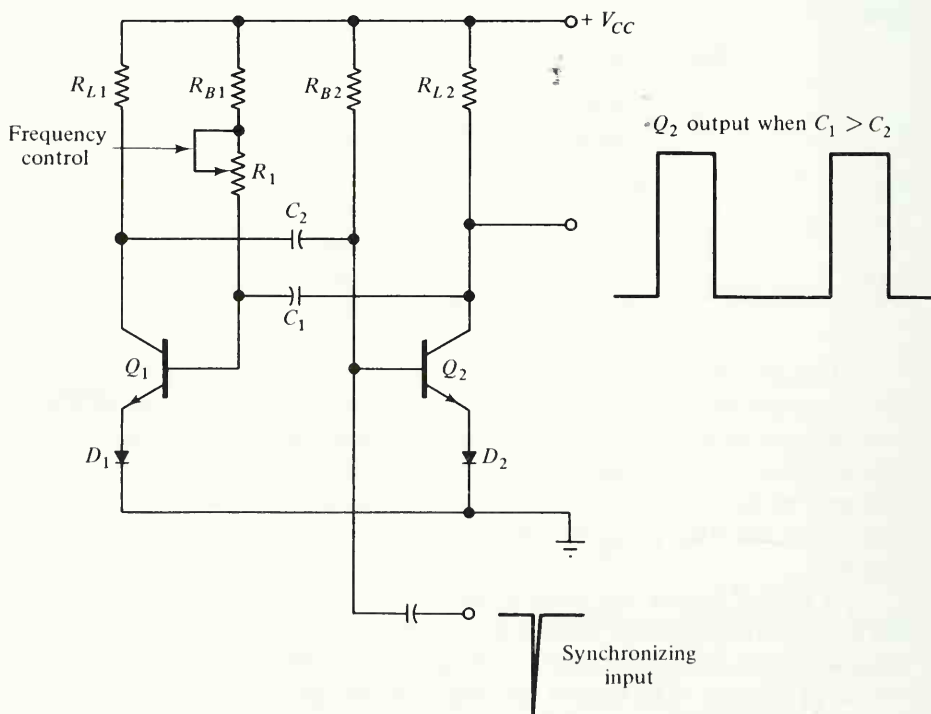


FIGURE 8-12. Astable multivibrator with frequency control, synchronizing input, and diodes for transistor protection.

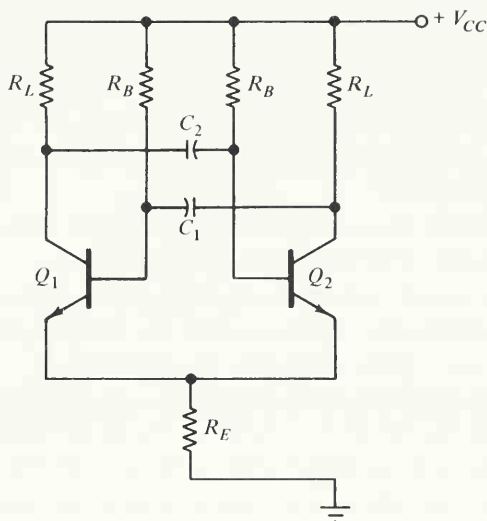


FIGURE 8-13. Emitter-coupled astable multivibrator.

REVIEW QUESTIONS AND PROBLEMS

- 8-1 Sketch the circuit of a collector-coupled monostable multivibrator. Sketch the waveforms and explain the operation of the circuit. Also explain the function of each component.
- 8-2 A collector-coupled monostable multivibrator is to operate from a ± 12 V supply. The transistor collector currents are to be 3 mA, and the transistors have $h_{FE(\min)} = 70$. Neglecting the output pulse width, design a suitable circuit.
- 8-3 Select suitable capacitors for the circuit in Problem 8-2 to give an output pulse of $330 \mu\text{s}$.
- 8-4 The monostable multivibrator designed for Problems 8-2 and 8-3 is to be triggered at $10 \mu\text{s}$ intervals between output pulses. Calculate the maximum size of the speed-up capacitor that may be employed.
- 8-5 Sketch and explain the various methods of triggering a monostable multivibrator. For the multivibrator in Problem 8-2, design a triggering system using an additional transistor. The triggering input is a 3 V, $10 \mu\text{s}$ pulse with a source resistance of $3.3 \text{ k}\Omega$.
- 8-6 Sketch the circuit of an emitter-coupled monostable multivibrator. Carefully explain how the circuit operates. Discuss the relative advantages and disadvantages of emitter-coupled and collector-

coupled monostable multivibrators. Show how the emitter-coupled circuit may be modified to provide pulse width control.

- 8-7** Design a nonsaturated emitter-coupled monostable multivibrator to operate from a 12 V supply. The transistor collector currents are to be 2 mA, and the transistors have $h_{FE(\max)} = 50$. Neglect the output pulse width.
- 8-8** Determine the size of capacitor required for the circuit in Problem 8-6 to give an output pulse width of 300 μ s.
- 8-9** Sketch the circuit of a monostable multivibrator employing an IC operational amplifier. Explain how the circuit operates; also show how the output pulse width may be controlled.
- 8-10** Design a monostable multivibrator using a μ A741 operational amplifier with $V_{CC} = \pm 9$ V. The circuit is to be triggered by a 0.5 V input spike, and the output pulse width is to be 300 μ s.
- 8-11** An MC951/MC851 IC monostable multivibrator is to have an output pulse width of 2 μ s. Select suitable external components, and show how they should be connected to the circuit.
- 8-12** Sketch the circuit of a collector-coupled astable multivibrator. Also sketch the waveforms of collector and base voltages. Carefully explain how the circuit operates.
- 8-13** Derive an expression for the output pulse width of an astable multivibrator. Design an astable multivibrator to have 5 kHz output square wave. The available supply is 9 V, and the load current is 50 μ A.
- 8-14** Sketch the circuit of an astable multivibrator in which the output frequency may be adjusted. Also show how the multivibrator frequency may be synchronized with an external frequency.
- 8-15** Sketch the circuit of an emitter-coupled astable multivibrator. Explain its operation, and discuss its advantages compared to a collector-coupled circuit.

Chapter 9

Bistable Multivibrators

INTRODUCTION

The BISTABLE MULTIVIBRATOR, also known as a FLIP-FLOP, is a switching circuit with two stable states. The circuit can be triggered from one state to the other by applying an input voltage via a suitable triggering circuit. The triggering input may be applied to the collectors, bases, or emitters of the transistors. Bistable multivibrators can be either collector-coupled or emitter-coupled circuits. They are also available in integrated circuit form. Because of its application in computing systems, the bistable multivibrator is the most important of all multivibrator circuits.

9-1 THE COLLECTOR-COUPLED BISTABLE MULTIVIBRATOR

The collector-coupled bistable multivibrator circuit, shown in Figure 9-1(a) has two stable states. Either Q_1 is *on* and Q_2 is *off*; or Q_2 is *on* and

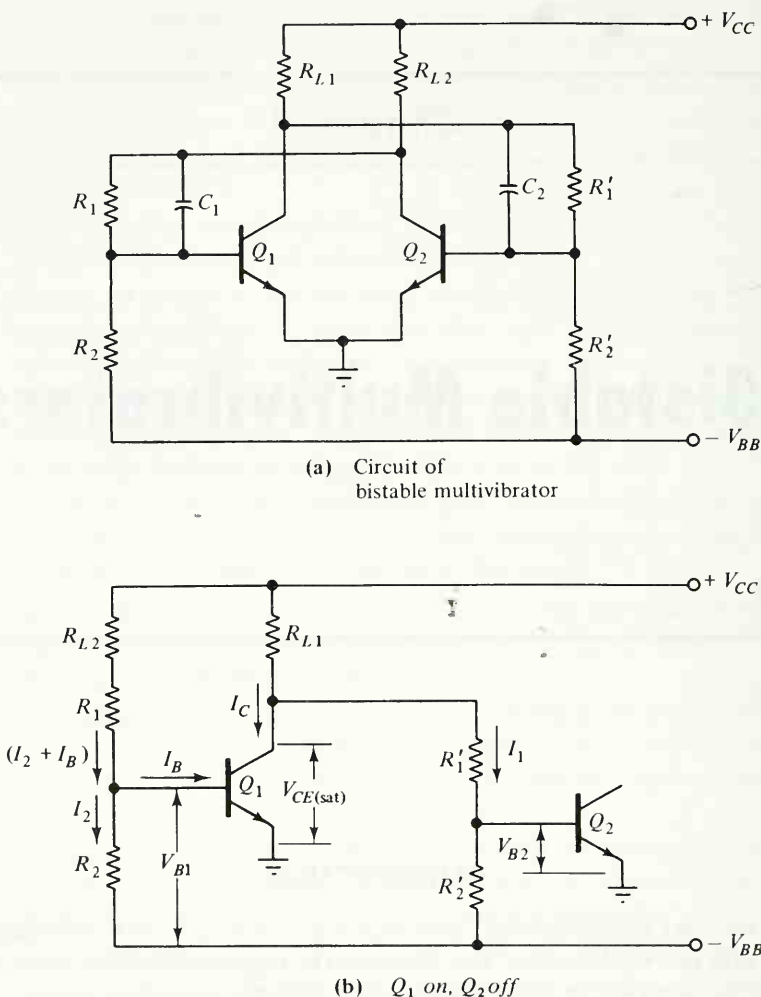


FIGURE 9-1. Collector-coupled bistable multivibrator circuit, and circuit condition when Q_1 is on and Q_2 is off.

Q_1 is biased off. The circuit is completely symmetrical. Load resistors R_{L1} and R_{L2} are equal, and potential dividers (R_1, R_2) and R'_1, R'_2 form similar bias networks at the transistor bases. Each transistor is biased from the collector of the other device. When either transistor is on, the other transistor is biased off.

Consider the condition of the circuit when Q_1 is on and Q_2 is off. With Q_2 off, there is no collector current flowing through R_{L2} . Therefore,

as shown in Figure 9-1(b), R_{L2} , R_1 , and R_2 can be treated as a potential divider biasing Q_1 base from V_{CC} and $-V_{BB}$. With Q_1 on in saturation, its collector voltage is $V_{CE(sat)}$, and R'_1 and R'_2 bias V_{B2} below ground level. Since the emitters of the transistors are grounded, Q_2 is off. The circuit can remain in this condition (Q_1 on, Q_2 off) indefinitely. When Q_1 is triggered off, Q_2 switches on, and remains on with its base biased via R_{L1} , R'_1 , and R'_2 . At this time, the base of Q_1 is biased negatively from Q_2 collector. Thus, Q_1 remains off and Q_2 remains on indefinitely. The output voltage at each collector is approximately V_{CC} .

Capacitors C_1 and C_2 operate as speed-up capacitors to improve the switching speed of the transistors. However, in the bistable circuit, C_1 and C_2 are also termed *commutating* or *memory capacitors*.

Consider the conditions when Q_1 is on and Q_2 is off. Capacitor C_1 is charged to the voltage across R_1 and C_2 is charged to the voltage across R'_1 . As will be seen when design of a bistable circuit is considered, the voltage across R_1 (at the base of the on transistor) is several volts greater than across R'_1 (at the base of the off transistor). Therefore, when Q_1 is on, C_1 is charged to a voltage greater than the voltage on C_2 . Now, consider what occurs when the on transistor is triggered off for a brief instant. With both transistors off, both collector voltages are approximately at the level of V_{CC} . Also, each base voltage becomes $V_B \simeq V_{CC} - (\text{Charge on the capacitor at the transistor base})$. Since C_2 has a smaller charge than C_1 , V_{B2} is greater than V_{B1} . One transistor must begin to switch on, and the one with the highest base voltage switches on first. Thus Q_2 (the formerly off transistor) switches on before Q_1 and, in doing so, it biases Q_1 off. Once switchover occurs, C_2 becomes charged to a greater voltage than C_1 .

It is seen that the charge on the capacitors enables them to "remember" which transistor was on and which was off, and facilitates the circuit changeover from one state to another.

9-2 DESIGN OF A COLLECTOR-COUPLED BISTABLE MULTIVIBRATOR

Design of a bistable multivibrator commences with a specification of supply voltage and load resistance. Alternatively, the output current may be specified, or I_C may simply be specified as a level much larger than the output current. As in the case of the monostable and Schmitt circuits, the bias resistances R_1 and R_2 must be chosen small enough to provide a stable bias level, and large enough so that they do not overload R_L . The rule-of-thumb that (bias current) $I_2 \simeq \frac{1}{10} I_C$ again can be applied, and the

circuit design procedure is then fairly simple. When the value of R_L is calculated, the next larger standard resistance should be selected. This will ensure sufficient voltage drop across R_L to have the transistor in saturation. The bias resistances should be selected as the next standard resistance size that is smaller than that calculated. This will provide slightly more base current than required for saturation.

The voltage on the commutating capacitors must not change significantly during the turn-off time of the transistors. If the capacitors are allowed to discharge by 10% of the difference between maximum and minimum capacitor voltages, Equation (2-10) may be applied.

$$t = 0.1 CR \quad [\text{Equation (2-10)}]$$

therefore,

$$C = \frac{t_{(\text{off})}}{0.1 R}$$

In this case, $C = C_1 = C_2$ and $t_{(\text{off})}$ is the turn-off time for the transistors; R is the resistance "seen" looking into the terminals of R_1 or R'_1 . With one transistor *on*, the minimum value of R approximates $R_1 \parallel R_2$. This gives

$$C_1 = C_2 = \frac{t_{(\text{off})}}{0.1(R_1 \parallel R_2)} \quad (9-1)$$

As for other switching circuits, the presence of capacitors limits the maximum frequency at which the bistable circuit may be triggered. To determine the maximum triggering frequency, the *recovery time* for the capacitors must be calculated. This is the time for the capacitors to discharge from maximum voltage to minimum voltage, or *vice versa*. The maximum triggering frequency is then calculated as $1/(\text{recovery time})$. Using Equation (2-9), the recovery time is calculated as:

$$t_{re} = 2.3 CR \quad [\text{Equation (2-9)}]$$

where again $R = (R_1 \parallel R_2)$ and maximum triggering frequency is:

$$f_{\max} = \frac{1}{t_{re}} = \frac{1}{2.3 C(R_1 \parallel R_2)} \quad (9-2)$$

EXAMPLE 9-1

Design a collector-coupled bistable multivibrator to operate from a ± 5 V supply. Use 2N3904 transistors, with $I_C = 2$ mA.

solution

Refer to Figure 9-1(b):

$$V_{CE(\text{sat})} = 0.2 \text{ V (typically)}$$

$$\begin{aligned} R_L &\simeq \frac{V_{CC} - V_{CE(\text{sat})}}{I_C} \quad (\text{i.e. neglecting } I_1) \\ &= \frac{5 \text{ V} - 0.2 \text{ V}}{2 \text{ mA}} \\ &= 2.4 \text{ k}\Omega \quad (\text{use } 2.7 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

From the 2N3904 data sheet in Appendix 1-4, $h_{FE(\text{min})} = 70$, so

$$\begin{aligned} I_{B(\text{min})} &= \frac{I_C}{h_{FE(\text{min})}} \\ &= \frac{2 \text{ mA}}{70} = 28.6 \mu\text{A} \end{aligned}$$

With Q_1 on,

$$\begin{aligned} V_{R2} &= V_{BE1} - V_{BB} \\ &= 0.7 \text{ V} - (-5 \text{ V}) = 5.7 \text{ V} \\ I_2 &\simeq \frac{1}{10} I_C = \frac{2 \text{ mA}}{10} = 200 \mu\text{A} \\ R_2 &= \frac{V_{R2}}{I_2} = \frac{5.7 \text{ V}}{200 \mu\text{A}} \\ &= 28.5 \text{ k}\Omega \quad (\text{use } 27 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

Now I_2 becomes

$$\begin{aligned} I_2 &= \frac{5.7 \text{ V}}{27 \text{ k}\Omega} \\ &= 211 \mu\text{A} \\ R_{L2} + R_1 &= \frac{V_{CC} - V_{BE}}{I_2 + I_B} \\ &= \frac{5 \text{ V} - 0.7 \text{ V}}{211 \mu\text{A} + 28.6 \mu\text{A}} \\ &= 17.9 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned}
 R_1 &= (R_{L2} + R_1) - R_{L2} \\
 &= 17.9 \text{ k}\Omega - 2.7 \text{ k}\Omega \\
 &= 15.2 \text{ k}\Omega \quad (\text{use } 15 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

Analysis.

$$V_{C(\text{on})} = V_{CE(\text{sat})} = 0.2 \text{ V}$$

$$V_{C(\text{off})} = V_{CC} - V_{RL2} \quad (\text{for } Q_2 \text{ off})$$

$$\begin{aligned}
 \text{Voltage across } (R_{L2} + R_1) &= V_{CC} - V_{BE1} \\
 &= 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{RL2} &= (V_{CC} - V_{BE1}) \times \frac{R_{L2}}{R_1 + R_{L2}} \\
 &= 4.3 \text{ V} \times \frac{2.7 \text{ k}\Omega}{15 \text{ k}\Omega + 2.7 \text{ k}\Omega} = 0.66 \text{ V}
 \end{aligned}$$

$$V_{C(\text{off})} = 5 \text{ V} - 0.66 \text{ V} = 4.34 \text{ V}$$

$$V_{B(\text{off})} = V_{CE(\text{sat})} - V_{R'1} \quad (\text{for } Q_2 \text{ off})$$


$$\begin{aligned}
 \text{Voltage across } (R'_1 + R'_2) &= V_{CE(\text{sat})} - V_{BB} \\
 &= 0.2 \text{ V} - (-5 \text{ V}) \\
 &= 5.2 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{R'1} &= (V_{CE(\text{sat})} - V_{BB}) \times \frac{R'_1}{R'_1 + R'_2} \\
 &= 5.2 \text{ V} \times \frac{15 \text{ k}\Omega}{15 \text{ k}\Omega + 27 \text{ k}\Omega} = 1.86 \text{ V}
 \end{aligned}$$


$$V_{B(\text{off})} = 0.2 \text{ V} - 1.86 \text{ V} = -1.66 \text{ V}$$

Figure 9-2(a) shows the bistable circuit as designed in Example 9-1, with resistor values and voltage levels indicated.

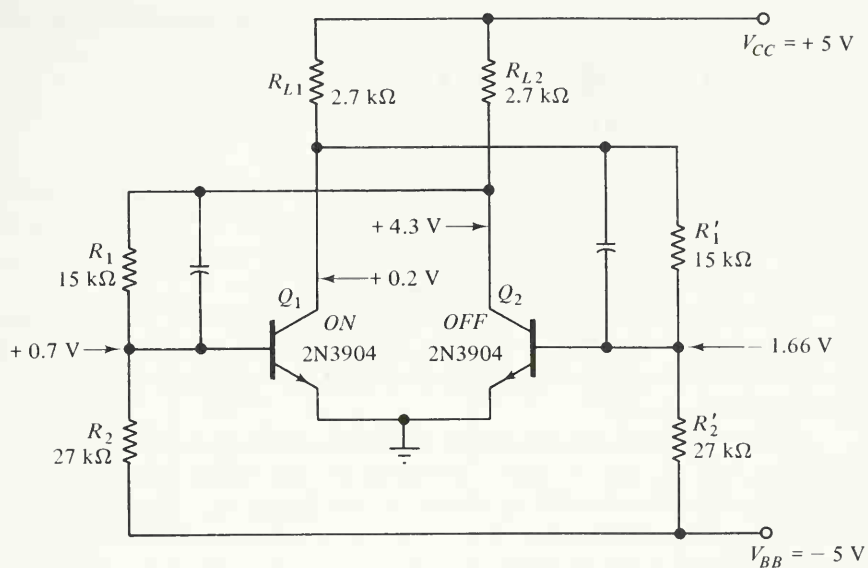In Figure 9-2(b) a bistable circuit using 2N3906 *pnp* transistors is shown. The circuit design is exactly the same as for the *nnp* circuit, except that all voltage polarities and current directions are reversed.



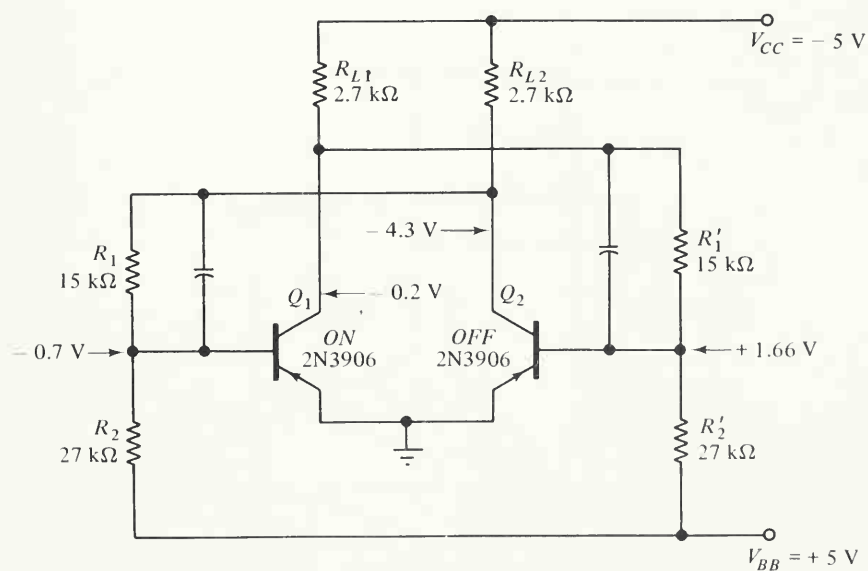(a) Bistable circuit using *NPN* transistors



(b) Bistable circuit using *PNP* transistors

FIGURE 9-2. Bistable multivibrator circuit designed in Example 9-1, using *npn* transistors and using *pnp* transistors.

9-3 EMITTER-COUPLED BISTABLE MULTIVIBRATOR

The emitter-coupled bistable multivibrator circuit (Figure 9-3) is the same as the collector-coupled circuit, except that an emitter resistor R_E has been added. Load resistors R_{L1} and R_{L2} are equal, as are capacitors C_1 and C_2 , and potential dividers (R_1, R_2) and (R'_1, R'_2) .

The presence of R_E allows the circuit to be operated from a single polarity supply. The emitter resistor also limits the collector current of the *on* transistor to any desired level, so that the transistor may be saturated or unsaturated.

Figure 9-4(a) shows the circuit conditions when Q_1 is *on* and Q_2 is *off*. Resistors R_{L2} , R_1 , and R_2 form a potential divider which biases Q_1 base. Q_2 base is then biased from Q_1 collector, via R'_1 and R'_2 . To analyze the circuit, potential divider R_{L1} , R_1 , and R_2 must be replaced with its open circuit output voltage (at Q_1 base) and its internal resistance. As shown in Figure 9-4(b), the open circuit output voltage of the potential divider is, $V_B = V_{CC}R_2/(R_1 + R_2 + R_{L2})$. Also the resistance of the potential divider, as "seen" from the transistor base is $R_B = R_2 \parallel (R_1 + R_{L2})$.

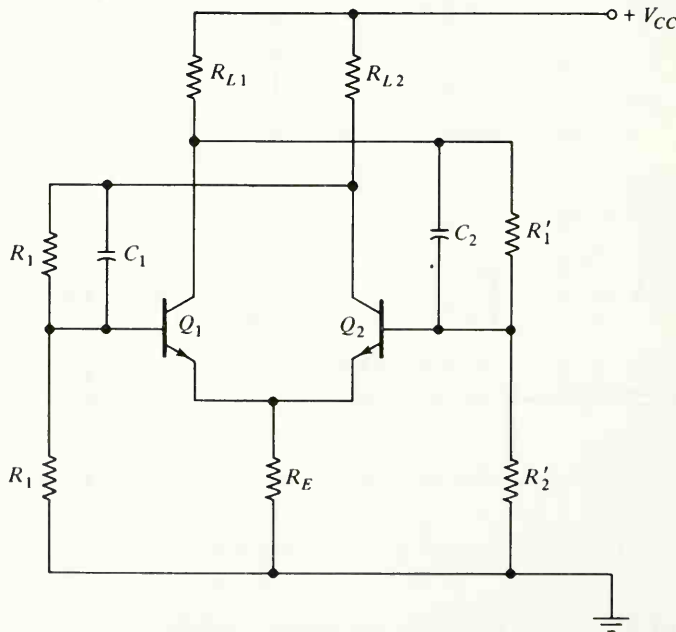


FIGURE 9-3. Emitter-coupled bistable circuit.

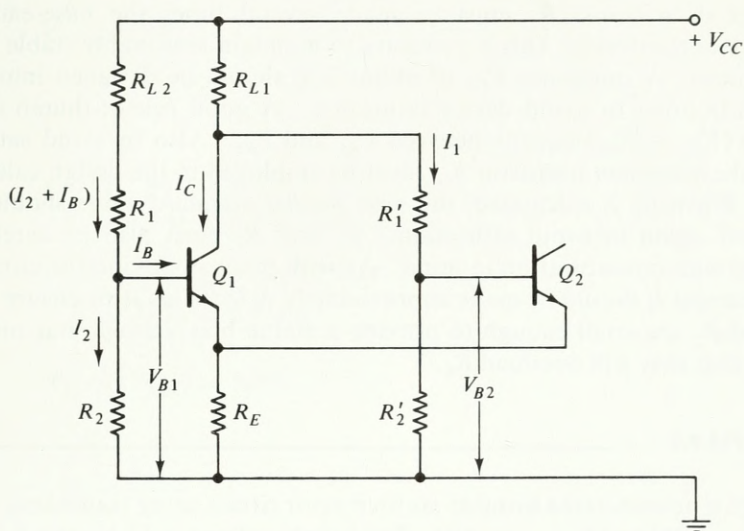
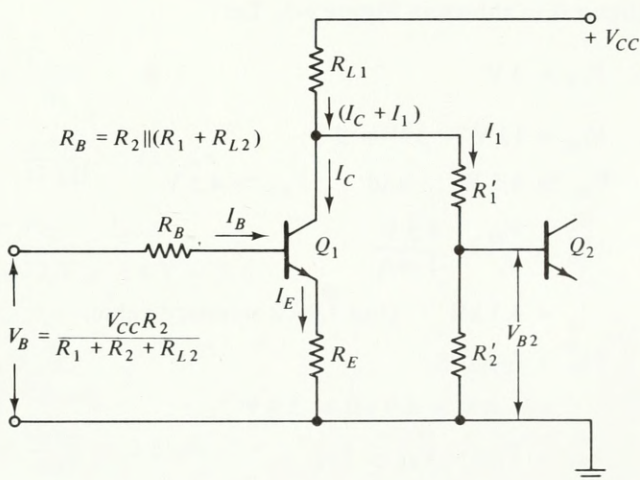

 (a) Q_1 on, Q_2 off

 (b) R_{L2} , R_1 and R_2 replaced by their equivalent circuit

FIGURE 9-4. Equivalent circuits for analysis of emitter-coupled bistable multivibrator.

In designing a nonsaturated emitter-coupled bistable circuit, the voltage drop across R_E must be made several times the base-emitter voltage of the device. This is necessary to maintain reasonably stable bias conditions. A minimum V_{CE} of about 3 V should be designed into the circuit in order to avoid device saturation. A good rule-of-thumb is to divide $(V_{CC} - V_{CE})$ equally between V_{RL} and V_{RE} . Also to avoid saturation, the *maximum* transistor h_{FE} must be employed in the design calculation. When R_L is calculated, the next *smaller* standard value should be selected, again to avoid saturation. R_1 and R_2 must also be carefully chosen with nonsaturation in mind. As with other multivibrator circuits, bias current I_2 should be made approximately $\frac{1}{10} I_C$. This is to ensure that R_1 and R_2 are small enough to provide a stable bias voltage, but not so small that they will overload R_L .

EXAMPLE 9-2

Design a nonsaturated bistable multivibrator circuit using transistors with $h_{FE(\min)} = 100$ and $h_{FE(\max)} = 400$. The supply voltage is 12 V, and I_C is to be 1 mA.

solution

The circuit is as shown in Figure 9-3. Let

$$V_{CE} = 3 \text{ V}$$

$$V_{CC} - V_{CE} = 12 \text{ V} - 3 \text{ V} = 9 \text{ V}$$

$$V_{RL} \simeq 4.5 \text{ V} \quad \text{and} \quad V_{RE} \simeq 4.5 \text{ V}$$

$$\begin{aligned} R_L &= \frac{V_{RL}}{I_C} = \frac{4.5 \text{ V}}{1 \text{ mA}} \\ &= 4.5 \text{ k}\Omega \quad (\text{use } 3.9 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

$$\begin{aligned} V_{RL} &= I_C R_L \\ &= 1 \text{ mA} \times 3.9 \text{ k}\Omega = 3.9 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{RE} &= V_{CC} - V_{RL} - V_{CE} \\ &= 12 \text{ V} - 3.9 \text{ V} - 3 \text{ V} = 5.1 \text{ V} \end{aligned}$$

Therefore,

$$\begin{aligned} R_E &\simeq \frac{V_{RE}}{I_C} = \frac{5.1 \text{ V}}{1 \text{ mA}} \\ &= 5.1 \text{ k}\Omega \quad (\text{use } 4.7 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

now

$$\begin{aligned} V_{RE} &\simeq I_C R_E \\ &= 1 \text{ mA} \times 4.7 \text{ k}\Omega = 4.7 \text{ V} \end{aligned}$$

and

$$\begin{aligned} V_{B(\text{on})} &= V_{RE} + V_{BE} \\ &= 4.7 \text{ V} + 0.7 \text{ V} = 5.4 \text{ V} \end{aligned}$$

Let

$$I_2 = \frac{1}{10} I_C = 0.1 \text{ mA}$$

$$V_{R2} = V_{B(\text{on})} = 5.4 \text{ V}$$

and

$$\begin{aligned} R_2 &= \frac{V_{B(\text{on})}}{I_2} \\ &= \frac{5.4 \text{ V}}{0.1 \text{ mA}} \\ &= 54 \text{ k}\Omega \quad (\text{use } 47 \text{ k}\Omega \text{ standard value}) \end{aligned}$$

Now,

$$\begin{aligned} I_2 &= \frac{V_{B(\text{on})}}{R_2} \\ &= \frac{5.4 \text{ V}}{47 \text{ k}\Omega} \simeq 115 \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{R1} + V_{RL} &= V_{CC} - V_{B(\text{on})} \\ &= 12 \text{ V} - 5.4 \text{ V} = 6.6 \text{ V} \end{aligned}$$

and

$$\begin{aligned} I_B &= \frac{I_C}{h_{FE(\text{max})}} \\ &= \frac{1 \text{ mA}}{400} = 2.5 \mu\text{A} \end{aligned}$$

$$\begin{aligned} R_1 + R_L &= \frac{V_{CC} - V_{B(\text{on})}}{I_2 + I_B} \\ &= \frac{6.6 \text{ V}}{115 \mu\text{A} + 2.5 \mu\text{A}} \\ &= 56.2 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned}
 R_1 &= 56.2 \text{ k}\Omega - R_L \\
 &= 56.2 \text{ k}\Omega - 3.9 \text{ k}\Omega \\
 &= 52.3 \text{ k}\Omega \quad (\text{use } 56 \text{ k}\Omega \text{ standard value to avoid saturation})
 \end{aligned}$$

EXAMPLE 9-3

Analyze the circuit designed in Example 9-2 to determine collector, base, and emitter voltages for the *on* and *off* transistors. Make the analysis (a) using maximum values of h_{FE} and (b) using minimum h_{FE} .

solution (a)

Refer to Figure 9-4(b):

$$\begin{aligned}
 V_B &= \frac{V_{CC}R_2}{R_1 + R_2 + R_{L2}} \\
 &= \frac{12 \text{ V} \times 47 \text{ k}\Omega}{56 \text{ k}\Omega + 47 \text{ k}\Omega + 3.9 \text{ k}\Omega} \\
 &= 5.28 \text{ V} \\
 R_B &= R_2 \parallel (R_1 + R_{L2}) \\
 &= 47 \text{ k}\Omega \parallel (56 \text{ k}\Omega + 3.9 \text{ k}\Omega) \\
 &= 26.3 \text{ k}\Omega \\
 V_B &= I_B R_B + V_{BE} + I_E R_E \\
 &= I_B R_B + V_{BE} + R_E(I_B + I_C) \\
 &= I_B R_B + V_{BE} + R_E(I_B + h_{FE}I_B) \\
 I_B &= \frac{V_B - V_{BE}}{R_B + R_E(1 + h_{FE})}
 \end{aligned}$$

For $h_{FE(\max)} = 400$:

$$\begin{aligned}
 I_B &= \frac{5.28 \text{ V} - 0.7 \text{ V}}{26.3 \text{ k}\Omega + 4.7 \text{ k}\Omega(1 + 400)} \\
 &= 2.4 \mu\text{A} \\
 I_C &= h_{FE}I_B \\
 &= 400 \times 2.4 \mu\text{A} = 0.96 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 V_E &= I_E R_E = R_E(I_B + I_C) \\
 &= 4.7 \text{ k}\Omega(2.4 \mu\text{A} + 0.96 \text{ mA}) \\
 &\simeq 4.5 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{B(\text{on})} &\simeq V_B - I_B R_B \\
 &= 5.28 \text{ V} - (2.4 \mu\text{A} \times 26.3 \text{ k}\Omega) \\
 &= 5.22 \text{ V}
 \end{aligned}$$

$$V_{C(\text{on})} = V_{CC} - R_L(I_C + I_1)$$

and

$$I_1 = \frac{V_{C(\text{on})}}{R_1 + R_2}$$

$$V_{C(\text{on})} = V_{CC} - R_L \left[I_C + \frac{V_{C(\text{on})}}{R_1 + R_2} \right]$$

$$V_{C(\text{on})} + \frac{R_L V_{C(\text{on})}}{R_1 + R_2} = V_{CC} - R_L I_C$$

$$V_{C(\text{on})} \left[1 + \frac{R_L}{R_1 + R_2} \right] = V_{CC} - R_L I_C$$

$$\begin{aligned}
 V_{C(\text{on})} &= \frac{V_{CC} - R_L I_C}{1 + \frac{R_L}{R_1 + R_2}} \\
 &= \frac{12 \text{ V} - (3.9 \text{ k}\Omega \times 0.96 \text{ mA})}{1 + \frac{3.9 \text{ k}\Omega}{56 \text{ k}\Omega + 47 \text{ k}\Omega}} \\
 &= 7.95 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{CE} &= V_{C(\text{on})} - V_E \\
 &= 7.95 \text{ V} - 4.5 \text{ V} \\
 &= 3.45 \text{ V} \quad (\text{the device is not saturated})
 \end{aligned}$$

$$V_{C(\text{off})} = V_{CC} - R_L(I_2 + I_B)$$

$$\begin{aligned}
 I_2 &= \frac{V_{B(\text{on})}}{R_2} \\
 &= \frac{5.22 \text{ V}}{47 \text{ k}\Omega} \\
 &= 111 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 I_2 + I_B &= 111 \mu\text{A} + 2.4 \mu\text{A} \\
 &= 113.4 \mu\text{A} \\
 V_{C(\text{off})} &= 12 \text{V} - 3.9 \text{k}\Omega (113.4 \mu\text{A}) \\
 &\simeq 11.6 \text{V} \\
 V_{B(\text{off})} &= V_{C(\text{on})} \times \frac{R_2}{R_1 + R_2} \\
 &= 7.95 \text{V} \times \frac{47 \text{k}\Omega}{56 \text{k}\Omega + 47 \text{k}\Omega} \\
 &= 3.6 \text{V}
 \end{aligned}$$

For the *off* transistor,

$$\begin{aligned}
 V_{BE(\text{off})} &= V_{B(\text{off})} - V_E \\
 &= 3.6 \text{V} - 4.5 \text{V} \\
 &= -0.9 \text{V} \quad (\text{the transistor is biased } \textit{off})
 \end{aligned}$$

solution (b)

For $h_{FE(\text{min})} = 100$:

$$\begin{aligned}
 I_B &= \frac{V_B - V_{BE}}{R_B + R_E(1 + h_{FE})} \\
 &= \frac{5.28 \text{V} - 0.7 \text{V}}{26.3 \text{k}\Omega + 4.7 \text{k}\Omega(1 + 100)} \\
 &= 9.1 \mu\text{A} \\
 I_C &= h_{FE} I_B \\
 &= 100 \times 9.1 \mu\text{A} = 0.91 \text{mA} \\
 V_E &= R_E(I_B + I_C) \\
 &= 4.7 \text{k}\Omega(9.1 \mu\text{A} + 0.91 \text{mA}) \\
 &\simeq 4.3 \text{V} \\
 V_{B(\text{on})} &= V_B - I_B R_B \\
 &= 5.28 - (9.1 \mu\text{A} \times 26.3 \text{k}\Omega) \\
 &= 5.04 \text{V}
 \end{aligned}$$

$$\begin{aligned}
 V_{C(\text{on})} &= \frac{V_{CC} - R_L I_C}{1 + \frac{R_L}{R_1 + R_2}} \\
 &= \frac{12 \text{ V} - (3.9 \text{ k}\Omega \times 0.91 \text{ mA})}{1 + \frac{3.9 \text{ k}\Omega}{56 \text{ k}\Omega + 47 \text{ k}\Omega}} \\
 &= 8.14 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{CE} &= V_{C(\text{on})} - V_E \\
 &= 8.14 \text{ V} - 4.3 \text{ V} \\
 &= 3.84 \text{ V} \quad (\text{again, the device is not saturated})
 \end{aligned}$$

$$\begin{aligned}
 V_{C(\text{off})} &= V_{CC} - R_L(I_2 + I_B) \\
 &= V_{CC} - R_L \left(\frac{V_B}{R_2} + I_B \right) \\
 &= 12 \text{ V} - 3.9 \text{ k}\Omega \left(\frac{5.04 \text{ V}}{47 \text{ k}\Omega} + 9.1 \mu\text{A} \right) \\
 &= 11.54 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{B(\text{off})} &= V_{C(\text{on})} \times \frac{R_2}{R_1 R_2} \\
 &= 8.14 \text{ V} \times \frac{47 \text{ k}\Omega}{56 \text{ k}\Omega + 47 \text{ k}\Omega} \\
 &= 3.71 \text{ V}
 \end{aligned}$$

For the *off* transistor,

$$\begin{aligned}
 V_{BE(\text{off})} &= V_{B(\text{off})} - V_E \\
 &= 3.71 \text{ V} - 4.3 \text{ V} \\
 &= -0.59 \text{ V} \quad (\text{the transistor is biased off})
 \end{aligned}$$

9-4 COLLECTOR TRIGGERING

Bistable multivibrator triggering circuits normally are designed to turn *off* the *on* transistor. The triggering may be *asymmetrical* or *symmetrical*. In *asymmetrical triggering*, two trigger inputs are employed, one to *set* the circuit in one particular state, and the other to *reset* to the opposite state. This process is sometimes referred to as *set-reset trigger-*

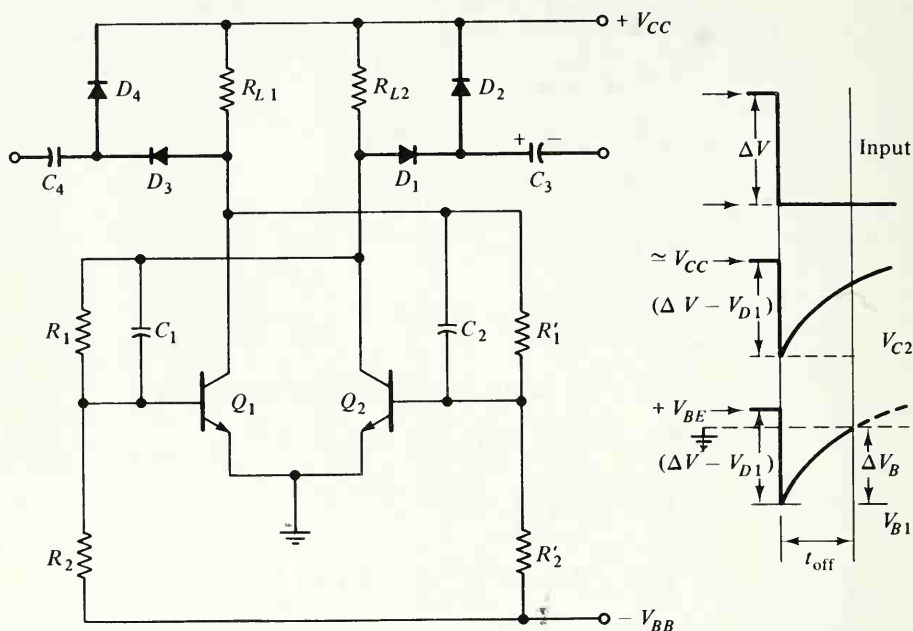


FIGURE 9-5. Asymmetrical collector triggering.

ing. Symmetrical triggering uses only one trigger input, and the state of the circuit is changed each time a trigger pulse is applied.

Refer to the asymmetrical collector trigger circuit shown in Figure 9-5, and assume that Q_1 is on and Q_2 is off. With Q_2 off, the voltage at its collector is approximately V_{CC} . The negative-going step input, coupled via C_3 , forward-biases D_1 and pulls its cathode down by ΔV . At this time, D_2 is reverse-biased by the negative-going input and has no function to perform. The anode of D_1 is pulled down by $\Delta V - V_{D1}$; that is, by ΔV minus the diode forward voltage drop. Thus, Q_2 collector voltage is changed from approximately V_{CC} to $[V_{CC} - (\Delta V - V_{D1})]$. See the waveforms in Figure 9-5. Capacitor C_1 , which does not discharge instantaneously, acts initially like a battery. Consequently, the voltage change at Q_2 collector also appears at Q_1 base. Q_1 base voltage initially is V_{BE} (with Q_1 on) and it falls by $\Delta V - V_{D1}$. Thus the input voltage at C_3 causes the base of Q_1 to be pushed below the level of its emitter voltage.

When the step input is applied, C_3 immediately starts to charge via R_{L2} (the polarity is shown in Figure 9-5). Both collector and base voltages rise from their minimum levels, as shown. To ensure that Q_1 switches off, its base voltage must remain below the emitter voltage level for the tran-

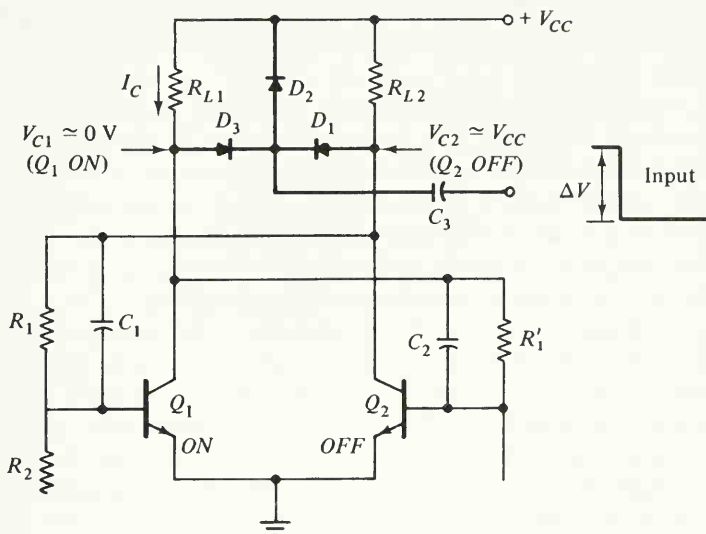


FIGURE 9-6. Symmetrical collector triggering.

sistor turn-off time t_{off} . This may be achieved by use of a large value coupling capacitor for C_3 . However, it is best to choose C_3 as small as possible. The smallest suitable capacitor is one that will allow V_B to rise to the level of the emitter voltage during the transistor turn-off time. The waveforms of Figure 9-5 show that V_{B1} rises to ground level during t_{off} .

When the triggering input becomes positive, returning to its normal dc level, D_1 is reverse-biased and the state of the bistable circuit is unaffected. The charge on C_3 which resulted from the negative-going input remains until the trigger input becomes positive. D_2 is then forward-biased by the capacitor charge, and C_3 is rapidly discharged via D_2 . The triggering circuit now is ready to receive another negative-going input. However, with Q_1 already *off*, the state of the circuit will not be altered by a triggering input via C_3 . Instead, Q_2 must be triggered *off* by an input applied to C_4 .

Symmetrical collector triggering is shown in Figure 9-6. With Q_1 on and Q_2 off, I_C flows through R_{L1} causing V_{C1} to be approximately zero volt. Also, V_{C2} is approximately V_{CC} . The amplitude of the negative-going trigger input does not exceed the voltage drop across R_L (i.e., less than V_{CC}), so that diode D_3 does not become forward-biased. However, diode D_1 is forward-biased by the negative-going input, as has been explained. Thus, Q_1 base is pushed down exactly as discussed for asymmetrical triggering and Q_1 is turned off. With Q_1 off, V_{C1} rises to approximately V_{CC} and V_{C2} drops to near zero. The next

negative-going input forward-biases D_3 and causes Q_2 base to be pushed below its emitter level. Hence, Q_2 switches *off* and the circuit returns to its original state.

It is seen that the circuit changes state each time a negative-going trigger voltage is applied. D_2 functions as before, becoming forward-biased and discharging C_3 each time the input returns to its upper level. A resistor could function in place of D_2 , but it would load the trigger signal and would take a relatively long time to discharge C_3 .

The design of collector triggering circuits mainly involves determination of the smallest suitable coupling capacitor. The allowable change in voltage at the base of the transistor to be switched *off* dictates the voltage through which the coupling capacitor may be charged.

Refer to Figures 9-5 and 9-6 again. Note that when the trigger voltage pulls the collector of Q_2 down to near ground level, capacitor C_1 begins to discharge via $R_1 \parallel R_2$. As already explained in Sec. 9-2, the commutating capacitor voltage should not be allowed to discharge by more than 10% of the difference between maximum and minimum capacitor voltages. Equation (9-1) can be applied to calculate C_1 and C_2 .

EXAMPLE 9-4

The saturated collector-coupled flip-flop designed in Example 9-1 is to be triggered by the collector output of a previous similar stage. Design a suitable symmetrical collector triggering circuit.

solution

The waveforms of the triggering voltage as it appears at various points in the circuit are shown in Figure 9-7. From Example 9-1, the collector voltage of the flip-flop changes from 4.3 V to 0.2 V. This change is used as an input triggering voltage (see Figure 9-7).

$$V_i = 4.3 \text{ V} - 0.2 \text{ V} = 4.1 \text{ V}$$

At the diode cathodes,

$$\Delta V_K \simeq 4.1 \text{ V}$$

$$\begin{aligned} \Delta V_{C2} &= \Delta V_K - V_{D1} \\ &= 4.1 \text{ V} - 0.7 \text{ V} = 3.4 \text{ V} \end{aligned}$$

$$\Delta V_{B1} = \Delta V_{C2} = 3.4 \text{ V}$$

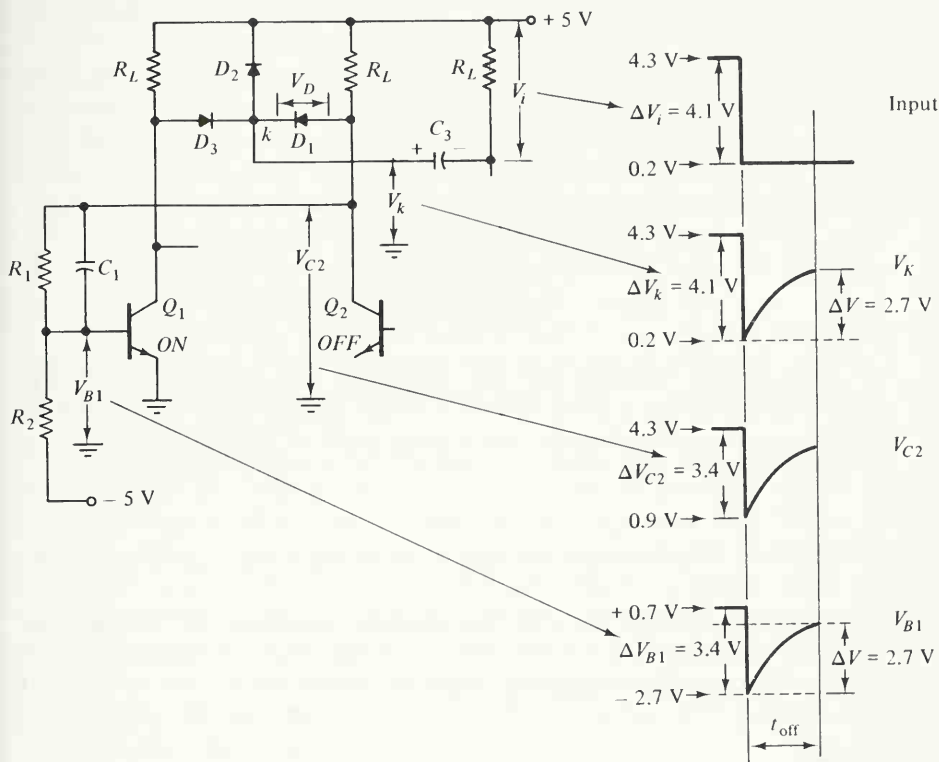


FIGURE 9-7. Triggering voltage waveforms for symmetrical collector triggering design.

To keep $V_{B1} < V_E$ during $t_{(off)}$:

$$\begin{aligned}\Delta V &= \Delta V_{B1} - V_{BE} \\ &= 3.4 \text{ V} - 0.7 \text{ V} = 2.7 \text{ V}\end{aligned}$$

$\therefore C_3$ can charge by 2.7 V during $t_{(off)}$.

For C_3 :

$$\text{Initial voltage} = E_o \simeq 0 \text{ V}$$

$$\text{Final voltage} = e_c \simeq \Delta V = 2.7 \text{ V}$$

$$\text{Charging voltage} = E = \Delta V_i - V_{D1} = 3.4 \text{ V}$$

$$\text{Charging resistance} \simeq R_L = 2.7 \text{ k}\Omega$$

$$\text{Turn-off time (for 2N3904)} = t_{(off)} = 250 \text{ ns}$$

From Equation (2-8):

$$\begin{aligned}
 C_3 &= \frac{t}{R_L \ln \left(\frac{E - E_o}{E - e_c} \right)} \\
 &= \frac{250 \text{ ns}}{2.7 \text{ k}\Omega \times \ln \left(\frac{3.4 \text{ V} - 0}{3.4 \text{ V} - 2.7 \text{ V}} \right)} \\
 &\simeq 59 \text{ pF} \quad (\text{use } 62 \text{ pF standard value})
 \end{aligned}$$

The diodes required for the triggering are low-current devices capable of surviving a peak inverse voltage greater than V_{CC} . 1N914 diodes are more than adequate (see the data sheet in Appendix 1-1).

EXAMPLE 9-5

Determine the value of suitable commutating capacitors for the flip-flop designed in Example 9-1 when collector triggering is employed. Also calculate the maximum triggering frequency for the circuit.

solution

By Equation (9-1),

$$\begin{aligned}
 C_1 = C_2 &= \frac{t_{(\text{off})}}{0.1(R_1 \parallel R_2)} \\
 &= \frac{250 \text{ ns}}{0.1(15 \text{ k}\Omega \parallel 27 \text{ k}\Omega)} = 259 \text{ pF} \quad (\text{use } 270 \text{ pF standard value})
 \end{aligned}$$

By Equation (9-2),

$$\begin{aligned}
 f_{(\text{max})} &= \frac{1}{2.3 C(R_1 \parallel R_2)} \\
 &= \frac{1}{2.3 \times 270 \text{ pF}(15 \text{ k}\Omega \parallel 27 \text{ k}\Omega)} \\
 &= 167 \text{ kHz}
 \end{aligned}$$

9-5 BASE TRIGGERING

Base triggering circuits are subdivided into *asymmetrical base triggering*, *symmetrical base triggering*, and *collector-steered base triggering* circuits. The first two of these are shown schematically in Figure 9-8. In Figure 9-8(a), a negative-going input coupled via C_3 forward-biases D_1 and pulls Q_2 base below its emitter voltage level. C_3 charges via R_{L1} (C_2 by-passes R'_1) and allows the base voltage to rise to ground over a time period equal to the transistor turn-off time. C_3 is discharged via D_2 when the input becomes positive to return to its normal dc level.

In Figure 9-8(a), the negative-going input to C_3 can only switch Q_2 off. To turn Q_1 off, a negative-going input must be coupled via C_4 and D_3 . Positive-going inputs at either terminal reverse bias D_1 or D_3 and have no effect on the bistable circuit.

For the symmetrical base triggering circuit in Figure 9-8(b), D_2 is common and the input is applied to the common cathode terminal of D_3 and D_1 . If Q_1 is off, its base voltage is biased negatively with respect to ground. Thus, if the input signal is kept small enough, D_3 does not become forward-biased. Q_2 base is at V_{BE} with respect to ground (with Q_2 on), so that the negative-going input forward-biases D_1 and pulls the transistor base below its emitter level. When Q_2 is off and Q_1 is on, D_3 is forward-biased by the triggering input, and D_1 remains reverse-biased. D_2 becomes forward-biased only when the input becomes positive. At this time, C_3 is discharged.

The amplitude of the trigger input to the symmetrical base triggering circuit is very critical. The input must be greater than 0.7 V in order to switch off the on transistor. If the base voltage of the off transistor is, say, -1.5 V, then the input voltage should be less than 1.5 V to avoid affecting the off transistor. The collector-steered base triggering circuit overcomes the problem of critical triggering amplitude.

In the collector-steered base triggering circuit, shown in Figure 9-9, diode D_2 has its anode connected to Q_2 base and its cathode connected via *steering resistance* R'_5 to Q_2 collector. Similarly, the anode of D_1 is connected to Q_1 base, and the cathode is connected via R_5 to Q_1 collector. The common triggering signal is applied to D_1 and D_2 cathodes via separate capacitors C_3 and C_4 , respectively.

Consider the circuit conditions for Figure 9-9 when Q_1 is off and Q_2 is on. With Q_1 off, the voltage at its collector is approximately V_{CC} . Therefore, the cathode of D_1 is approximately at V_{CC} . In this case, triggering inputs with amplitude less than V_{CC} will not forward-bias D_1 . Since Q_2 is on, its collector voltage is $V_{CE(sat)}$ above ground level; consequently the cathode of D_2 is at $V_{CE(sat)}$. A negative-going trigger input with an ampli-

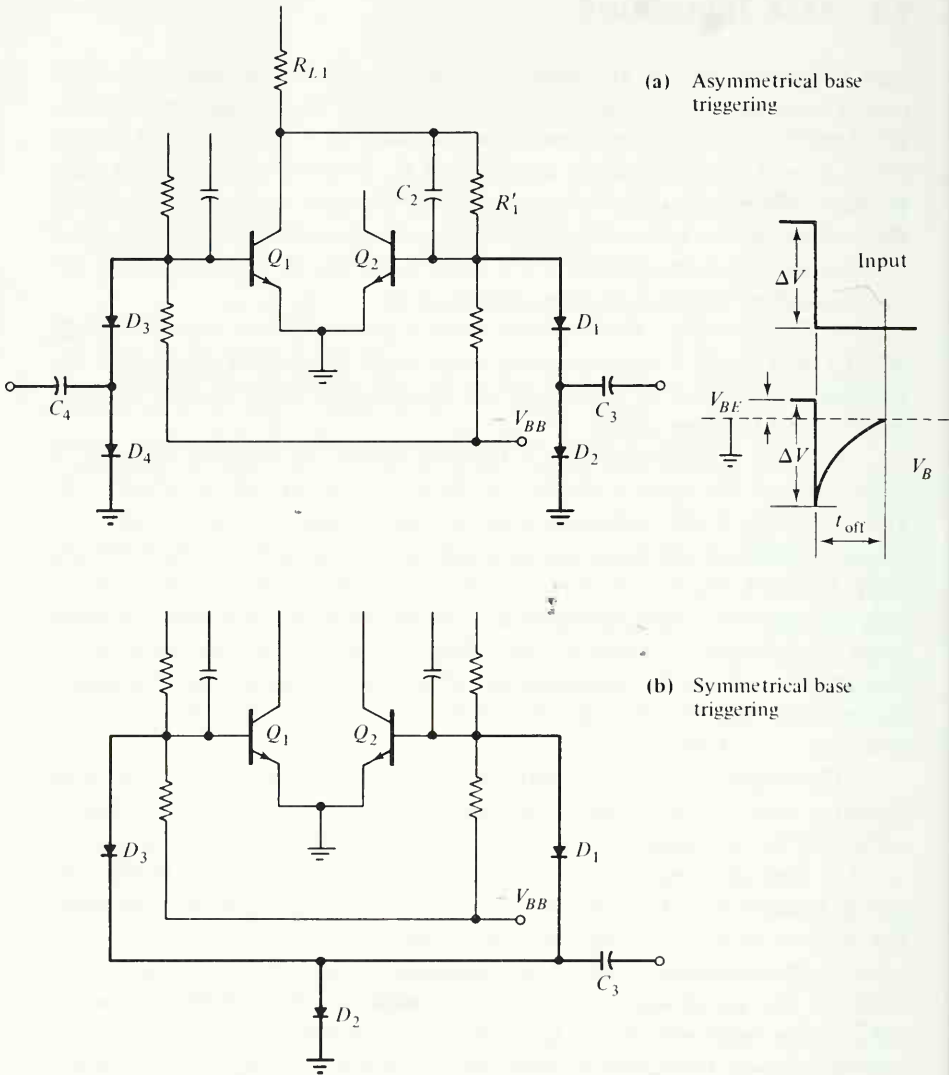


FIGURE 9-8. Asymmetrical and symmetrical base triggering.

tude of a few volts will forward-bias D_2 and pull the base of Q_2 below ground. Thus, to cause the circuit to correctly change state, the trigger voltage amplitude can have a value anywhere between about 2 V and V_{CC} .

Now consider the triggering waveforms shown in Figure 9-9. When the input changes negatively by ΔV , the voltage at the cathode of D_2 falls

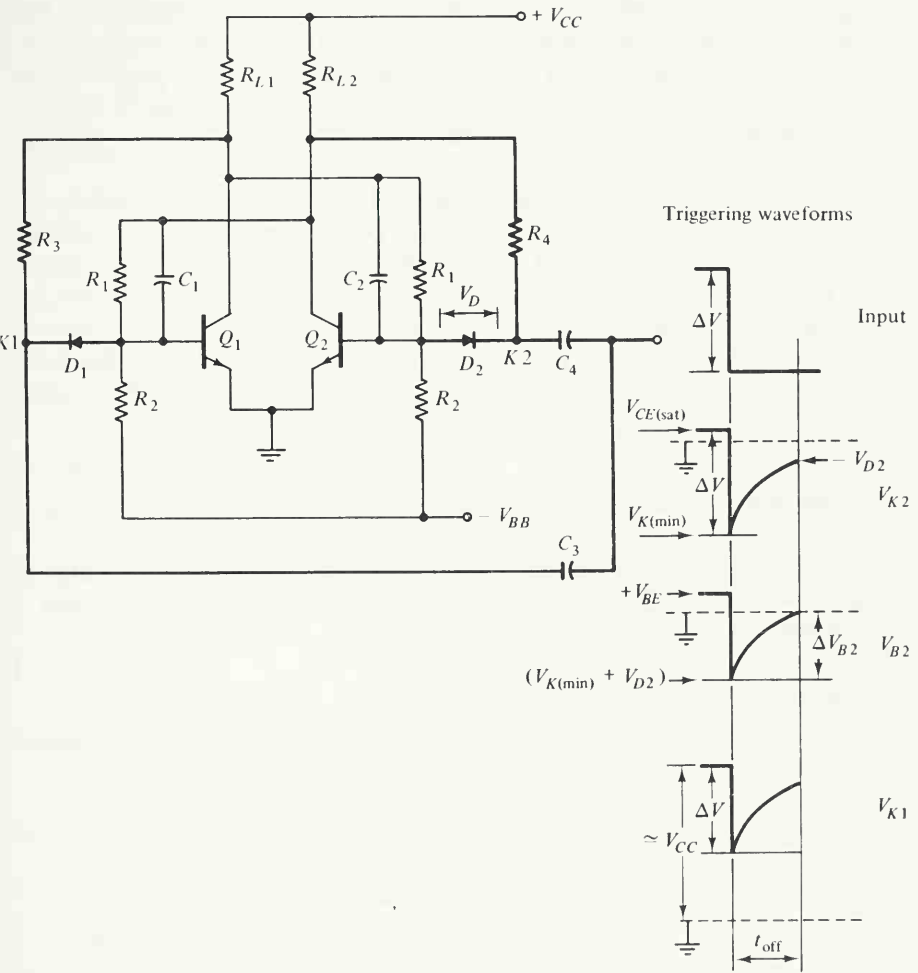


FIGURE 9-9. Collector-steered base triggering circuit and waveforms when Q_2 is initially on.

by ΔV from its initial level of $V_{CE(sat)}$ (i.e., when Q_2 is on). Q_2 base voltage is pulled down from V_{BE} to $(V_{K(min)} + V_{D2})$. If Q_2 base rises by ΔV_{B2} to ground level, C_4 charges by $(V_{K(min)} + V_{D2})$ during the transistor turn-off time. Since the voltage on commutating capacitor C_2 should change very little during $t_{(off)}$, C_2 may be regarded as a short circuit. Consequently, R_1 is shorted out and the charging resistance for C_4 becomes

$R_{L1} || R'_2 || R'_s$, which is approximately equal to R_L . To find the charging voltage, it is necessary to assume that Q_1 remains *off*, and that C_2 behaves as a short circuit, while C_4 continues to charge via R_L . In this case, C_4 would charge toward $+(V_{CC} - V_{D2})$ on the LHS and V_i minimum on the RHS. In Figure 9-9, note that when the triggering voltage is applied, V_{K1} falls by ΔV from approximately V_{CC} . Thus, D_1 does not become forward-biased.

For collector-steered base triggering (Figure 9-9), R_s should be selected much larger than R_L . This is to ensure that R_s does not constitute a significant load on R_{L1} and R_{L2} . When Q_2 base voltage is pulled down by the input trigger voltage, commutating capacitor C_2 commences to charge via R_L . Since Q_2 is to be switched *off*, C_2 voltage can be allowed to increase slightly. However, the charge on C_1 (at the base of the transistor that is to switch *on*) should not change significantly. Once again Equation (9-1) applies.

EXAMPLE 9-6

Design a collector-steered base triggering circuit for the flip-flop designed in Example 9-1. The trigger input is to be the collector output from a previous similar stage.

solution

From Example 9-1, the collector output voltage from a previous flip-flop is 4.3 V to 0.2 V.

Refer to Figure 9-9.

$$\Delta V = 4.3 \text{ V} - 0.2 \text{ V} = 4.1 \text{ V}$$

At D_2 cathode,

$$\begin{aligned} V_{K(\min)} &= V_{CE(\text{sat})} - \Delta V \\ &= 0.2 \text{ V} - 4.1 \text{ V} \\ &= -3.9 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{B2(\min)} &= \Delta V_{B2} = V_{K(\min)} + V_{D2} \\ &= -3.9 \text{ V} + 0.7 \text{ V} = -3.2 \text{ V} \end{aligned}$$

With K_2 at $V_{CE(\text{sat})}$, and V_i at 4.3 V, the initial charge on C_4 is

$$E_O = 0.2 \text{ V} - 4.3 \text{ V} = -4.1 \text{ V} \quad (\text{negative on LHS})$$

With V_i at 0.2 V and Q_1 *off*, the charging voltage E to C_4 is

$$\begin{aligned} E &= V_{C1} - V_{D2} - V_{CE(\text{sat})} \\ &= 4.3 \text{ V} - 0.7 \text{ V} - 0.2 \text{ V} = 3.4 \text{ V} \quad (\text{positive on LHS}) \end{aligned}$$

The final voltage e_c on C_4 , after time $t_{(\text{off})}$, is

$$\begin{aligned} e_c &= E_O - \Delta V_{B2(\text{min})} \\ &= -4.1 \text{ V} - (-3.2 \text{ V}) \\ &= 0.9 \text{ V} \quad (\text{negative on LHS}) \end{aligned}$$

Charging resistance $\simeq R_L = 2.7 \text{ k}\Omega$

Turn-off time $= t_{(\text{off})} = 250 \text{ ns}$

From Equation (2-8),

$$\begin{aligned} C_4 &= \frac{t}{R_L \ln \left(\frac{E - E_o}{E - e_c} \right)} \\ &= \frac{250 \text{ ns}}{2.7 \text{ k}\Omega \ln \left(\frac{3.4 \text{ V} - (-4.1 \text{ V})}{3.4 \text{ V} - (-0.9 \text{ V})} \right)} \end{aligned}$$

Thus,

$$C_3 = C_4 \simeq 166 \text{ pF} \quad (\text{use } 180 \text{ pF standard value})$$

Since $R_S \gg R_L$, take

$$\begin{aligned} R_S &= 10 \times R_L \\ &= 10 \times 2.7 \text{ k}\Omega = 27 \text{ k}\Omega \end{aligned}$$

9-6 **EMITTER TRIGGERING**

The simplest triggering method of all is provided by capacitor-coupling a positive-going input signal to the common emitter terminal of an emitter-coupled bistable circuit. Figure 9-10 shows the emitter triggering method. The positive-going voltage pushes the emitter above the level of the bias voltage at the base of the *on* transistor. Thus, the *on* transistor is switched *off*, and the charges on the commutating capacitors dictate that the formerly *off* transistor be switched *on*.

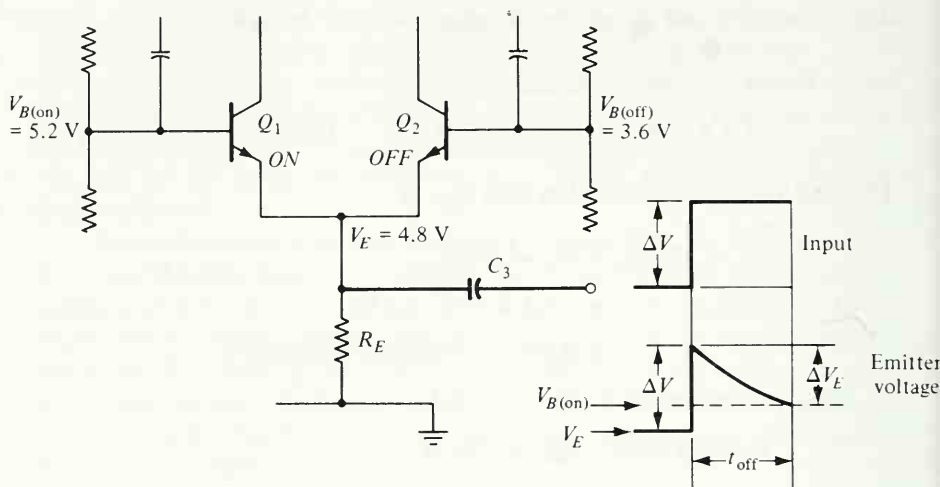


FIGURE 9-10. Emitter triggering.

For the emitter-coupled circuit analyzed in Example 9-3, the levels of base and emitter voltages are shown in Figure 9-10. $V_{B(off)}$ is less than $V_{B(on)}$. Consequently, when the transistor emitters are raised by the triggering voltage the reverse bias at the base of the *off* transistor is greater than that at the *on* transistor. A typical maximum reverse base-emitter voltage for most transistors is 5 V. Therefore, the triggering voltage should not push the emitters above $(V_{B(off)} + 5\text{ V})$. The triggering voltage must keep the base-emitter of the *on* transistor reverse-biased for the duration of the transistor turn-off time to effect switch-off. This can be accomplished by raising the emitter voltage by ΔV , and allowing it to fall to $V_{B(on)}$ during $t_{(off)}$ (see the waveforms in Figure 9-10). The fall in the emitter voltage is due to capacitor C_3 charging via R_E .

EXAMPLE 9-7

Design an emitter triggering circuit for the bistable multivibrator designed in Example 9-3. Take the transistor turn-off time as 300 ns.

solution

From the circuit analysis in Example 9-3:

$$V_{B(on)} \simeq 5.2\text{ V} \quad (\text{maximum})$$

$$V_{B(off)} \simeq 3.6\text{ V}$$

$$V_E \simeq 4.5 \text{ V}$$

$$V_{B(\text{off})} = 3.6 \text{ V}$$

$$V_{E(\text{max})} < (3.6 + 5 \text{ V})$$

$$V_{E(\text{max})} < 8.6 \text{ V}$$

This restriction on $V_{E(\text{max})}$ is made to avoid a reverse V_{BE} in excess of 5 V. A reverse bias of 2 V at the *on* transistor will drive $V_{E(\text{max})}$ to $(V_{B(\text{on})} + 2 \text{ V})$, that is, to $(5.2 \text{ V} + 2 \text{ V}) = 7.2 \text{ V}$. This satisfies the requirement that $V_{E(\text{max})} < 8.6 \text{ V}$.

To reverse bias $V_{BE(\text{on})}$ by 2 V, V_E must rise from 4.5 V to 7.2 V, that is,

$$\Delta V = (7.2 \text{ V} - 4.5 \text{ V}) = 2.7 \text{ V}$$

V_E can be allowed to fall to $V_{B(\text{on})}$ during the transistor turn-off time. That is, $\Delta V_E = 2 \text{ V}$ during $t_{(\text{off})}$.

From Equation (2-8):

$$C = \frac{t_{(\text{off})}}{R \ln \left(\frac{E - E_o}{E - e_c} \right)}$$

$$t_{(\text{off})} = 300 \text{ ns}$$

$$R = R_E = 4.7 \text{ k}\Omega$$

$$E = \Delta V = 2.7 \text{ V} \quad (\text{positive on RHS})$$

$$E_o = V_E = -4.5 \text{ V} \quad (\text{negative on RHS})$$

The initial charge on C_3 when the input is zero volts is $E_o = -4.5 \text{ V}$, which is negative compared to E .

$$\begin{aligned} e_c &= E_o + \Delta V_E \\ &= -4.5 \text{ V} + 2 \text{ V} = -2.5 \text{ V} \end{aligned}$$

$$C_3 = \frac{300 \text{ ns}}{4.7 \text{ k}\Omega \ln \left(\frac{2.7 \text{ V} + 4.5 \text{ V}}{2.7 \text{ V} + 2.5 \text{ V}} \right)}$$

$$\simeq 197 \text{ pF} \quad (\text{use } 200 \text{ pF standard value})$$

9-7 IC FLIP-FLOPS

When used as a logic element, the bistable multivibrator usually is termed a *flip-flop*. Flip-flops are available as integrated circuits in a wide variety of forms and combinations. Logic symbols for the various types of flip-flops are shown in Figure 9-11.

9-7.1 T Flip-Flop

The *toggle*, or *T*, flip-flop is simply a flip-flop that is symmetrically triggered by an input to one terminal. Any one of the symmetrically triggered bistable multivibrators already studied could be employed as a *T* flip-flop. The logic symbol for the toggle flip-flop is shown in Figure 9-11(a). The *T* terminal is the triggering input terminal, and the output terminals are the transistor collectors. The *1* and *0* at the outputs identify one particular state of the flip-flop. Logic *1* may indicate a positive voltage, and logic *0* a zero voltage level.

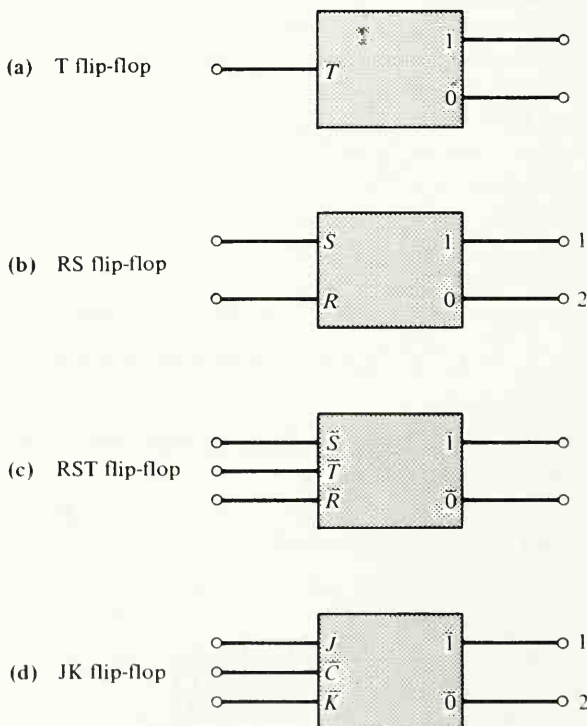


FIGURE 9-11. Logic symbols for various types of flip-flops.

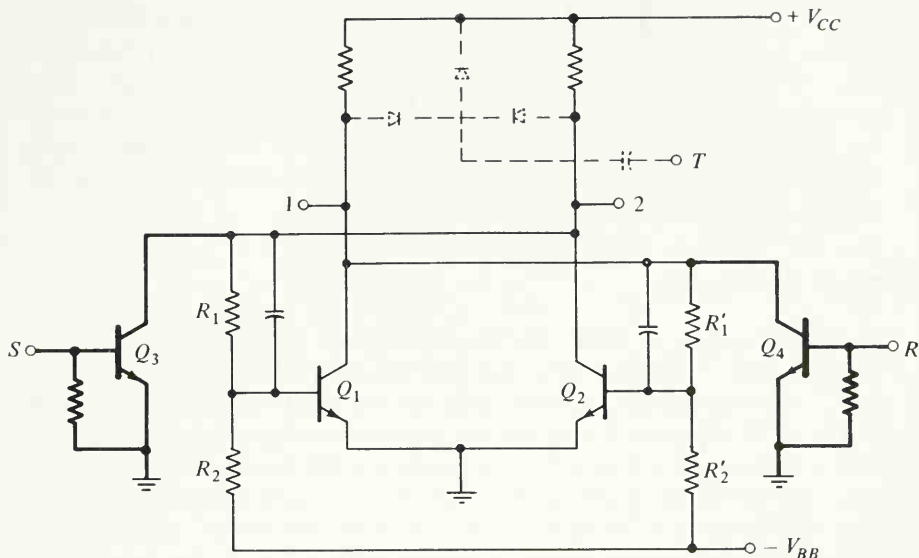


FIGURE 9-12. Reset-set flip-flop with addition of toggle circuit (broken lines).

9-7.2 RS Flip-Flop

The *reset-set*, or *RS*, flip-flop illustrated in Figure 9-11(b) could have a circuit similar to the asymmetrically triggered flip-flop in Figure 9-5. Previous consideration of that circuit showed that it can be triggered into one particular state (*i.e.*, it could be *set*) when a trigger voltage is applied to one input terminal. Also, it can be triggered (or *reset*) into the opposite state by a voltage applied to the other input terminal. Another name for the RS flip-flop is *set-clear*, or *SC*, flip-flop.

A better illustration for an RS flip-flop is the circuit of Figure 9-12. In this circuit, the *reset-set* function is performed by transistors Q_3 and Q_4 . Terminals 1, 2, S , and R correspond with the logic diagram terminals in Figure 9-11(b). It is assumed that logic 1 represents a positive voltage level, and that logic 0 represents approximately zero volts. When both inputs are at 0, both triggering transistors Q_3 and Q_4 are *off*, and the flip-flop could be in either state. When a 1 input is applied to terminal S , transistor Q_3 is biased *on* into saturation. This causes Q_2 collector to be pulled down; consequently Q_1 is biased *off* via R_1 and R_2 , and Q_2 switches *on* into saturation. The output at terminal 1 (from Q_1 collector) is now a positive voltage, *i.e.*, logic 1. The output at terminal 2 (from Q_2 collector) is near zero volt, or logic 0. The flip-flop is now in *set* condition, and this was obtained by applying a 1 input to terminal S , the *set* terminal.

If a 0 input is applied to terminal S , the circuit remains *set*. Also further 1 inputs to terminal S do not affect the *set* condition of the flip-flop. A 1 input to terminal R , the *reset* terminal, switches Q_4 on. This pulls the collector of Q_1 down, biasing Q_2 off (via R'_1 and R'_2) and switching Q_1 on. The output is now 0 at terminal 1 and 1 at terminal 2, and the circuit is said to be *reset*. To return to the *set* condition, 1 must be applied to the S input while the R input is at 0.

9-7.3 RST Flip-Flop

A *reset-set-toggle*, or *RST*, flip-flop is one that combines the triggering facilities of a *T* flip-flop with the reset-set arrangement of an RS flip-flop. Another name sometimes used for the RST flip-flop is *set-clear-toggle (SCT) flip-flop*. The symmetrical collector triggering circuit, shown with a broken line in Figure 9-12, converts the RS flip-flop to an RST circuit. The combination allows the toggle function only when both *set* and *reset* inputs are at 0. With a 1 at S , the circuit remains in *set* condition, and the flip-flop cannot toggle. Similarly, with a 1 at R , the flip-flop remains in *reset* condition. Figure 9-11(c) shows the logic diagram for the RST flip-flop.

9-7.4 JK Flip-Flop

The JK flip-flop is similar to the RST flip-flop in that it has a *toggle* input as well as *set* and *reset* inputs. However, the circuit condition changes only when an input appears at the T terminal. Suppose the flip-flop is in *set* condition, and a *reset* input is applied, the circuit remains in *set* condition until a *toggle* input is received, then it changes to *reset*. Further *toggle* inputs will not cause the flip-flop to change from the *reset* condition. Similarly, a *set* input will not be effective until a *toggle* signal is applied, and then the circuit changes to and remains in *set* condition. With *set* and *reset* inputs at 0, the flip-flop condition cannot be altered by a *toggle* input. Only when both *set* and *reset* inputs are 1 can the circuit be triggered continuously by a *toggle* input.

In the logic diagram for the JK flip-flop [Figure 9-11(d)], the *toggle* input terminal is identified as C for *clock*. This is the logic term for an accurate trigger frequency source. The *set* and *reset* inputs are identified as J and K .

The schematic diagram of Figure 9-13 is the basic circuit of a JK flip-flop. Transistors Q_3 and Q_4 perform *set* and *reset* functions, as already explained for the RS flip-flop. In Figure 9-13, however, base resistors R_B tend to bias Q_3 and Q_4 on. Diodes D_7 and D_8 , in series with

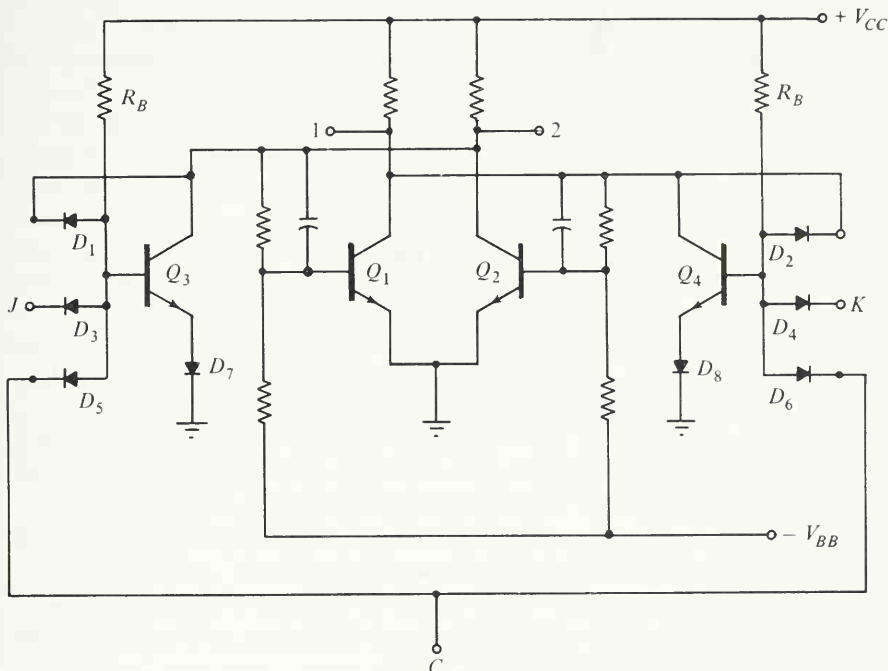


FIGURE 9-13. Basic circuit of a JK flip-flop.

the emitters of Q_3 and Q_4 , ensure that the transistors will not switch *on* until the base voltage is approximately $V_{BE} + V_D$. Thus, V_{B3} and V_{B4} must be about 1.4 V for switch-*on*.

When the J and K inputs are 0 (i.e., zero volt), D_3 and D_4 are forward-biased, and they hold the transistor bases below the level for switch-*on*. A clock input of 1 (i.e., a positive voltage) will only reverse-bias D_5 and D_6 and will have no effect on the state of the flip-flop. Now suppose a 1 input is applied to J , while K is at 0. Also, assume that the flip-flop is in *reset* condition with Q_1 *on* and Q_2 *off*. With Q_2 *off*, its collector voltage is positive, and diode D_1 is reverse-biased. When a 1 input is applied to the clock, D_5 and D_6 are again reverse-biased. Transistor Q_4 is unaffected, because the 0 input at K holds Q_4 *off*. However, all the diodes at Q_3 base are reverse-biased during the clock input. Therefore, Q_3 is biased *on* via R_B . When Q_3 switches *on*, it pulls the collector of Q_2 down, causing Q_1 to switch *off* and Q_2 to switch *on*, that is, the flip-flop returns to *set* condition. Once Q_2 switches *on*, D_1 becomes forward-biased, so that Q_3 is held *off*. Any more inputs to the clock terminal have no effect on the state of the flip-flop.

The circuit can be reset again by applying a clock input, when J is at 0 and K is at 1. Once again, only one pulse of clock frequency will be effective in changing the state of the circuit. When both J and K have 1 inputs, diodes D_3 and D_4 are reverse-biased. If Q_2 is *on* and Q_1 is *off*, D_1 is forward-biased and holds Q_3 *off*, but D_2 is reverse-biased. Consequently, a clock input reverses D_6 and causes Q_4 to switch on. Q_4 then switches Q_2 *off* and Q_1 *on*. Now D_1 is reverse-biased and D_2 is forward-biased. The next clock input switches Q_3 *on*, and once again changes the state of the flip-flop. It is seen that with 1 inputs at J and K the flip-flop can be toggled continuously by a clock input.

Appendix 1-14 shows the data sheet for the MC663P dual JK flip-flop manufactured by Motorola. The unit contains two separate JK flip-flops. As well as all of the input and output terminals discussed above, each flip-flop has a *direct reset* terminal identified as \bar{R}_D . A logic 0 input applied to the *direct reset* terminal resets outputs to logic 0 at terminal Q , and logic 1 at \bar{Q} (see the diagram on the data sheet). This reset occurs no matter what the voltage levels on the JK and C inputs. For normal operation of the flip-flop input \bar{R}_D must be kept high.

The MC663P flip-flop uses a supply of 15 V and dissipates a total of 200 mW. The low output voltage V_{OL} is a maximum of 1.5 V, and the high output voltage V_{OH} is a minimum of 12.5 V.

9-7.5 Flip-Flop Loading

Consider the data sheet for the MC663P dual JK flip-flop (Appendix 1-14). The current taken by a single input terminal is the *forward current* I_F listed as -1.2 mA maximum. The negative sign indicates that this current must flow *out* of the input terminal. Reference to the circuit diagram in the data sheet (or to the basic JK flip-flop in Figure 9-13) shows that the input voltage level must be *low* in order to forward bias an input diode. Consequently, the input current is actually flowing out of the input terminal.

When one of these flip-flops is to be triggered from another similar flip-flop, the output level of the triggering flip-flop must be *low* when triggering occurs. Thus, the (negative) input current to the triggered flip-flop actually flows *into* the output terminal of the triggering circuit. The test current I_{OL} flowing into the output terminal of an MC663P flip-flop when the output is low is listed as 10.8 mA. This means that when the flip-flop output is low, it can "take in" a total load current of 10.8 mA. This condition is sometimes referred to as *current sinking*. Since each input terminal must have a maximum of 1.2 mA of current "pulled-out" from it when triggering occurs, the total number of flip-flop inputs that may be connected to one output can be calculated as

$$\begin{aligned}\text{Output loading factor} &= \frac{I_{OL}}{I_F} \\ &= \frac{10.8 \text{ mA}}{1.2 \text{ mA}} = 9\end{aligned}$$

The output loading factor is listed as 9 on the data sheet.

REVIEW QUESTIONS AND PROBLEMS

- 9-1 Sketch the circuit of a collector-coupled bistable multivibrator employing *npn* transistors. Explain how the circuit operates.
- 9-2 Repeat Problem 9-1 for a circuit using *pnp* transistors.
- 9-3 Repeat Problem 9-1 for an emitter-coupled circuit.
- 9-4 Design a collector-coupled bistable multivibrator to operate from a $\pm 6 \text{ V}$ supply. Use 2N3904 transistors and make $I_C \simeq 1 \text{ mA}$.
- 9-5 Design a collector-coupled bistable multivibrator using 2N3906 transistors. The supply voltage is $\pm 9 \text{ V}$, and the collector current is to be approximately 2 mA .
- 9-6 Design a nonsaturated bistable multivibrator using a supply of 18 V . The silicon *pnp* transistors to be employed have $h_{FE(min)} = 70$, and $h_{FE(max)} = 300$.
- 9-7 Analyze the circuit designed for Problem 9-6 to determine maximum and minimum levels of collector, base, and emitter voltages for both transistors. I_C is to be 1.5 mA .
- 9-8 Sketch the circuit for asymmetrical collector triggering. Show the triggering waveforms, and explain how the circuit functions.
- 9-9 Repeat Problem 9-8 for symmetrical collector triggering.
- 9-10 The bistable multivibrator designed for Problem 9-4 is to use symmetrical collector triggering. The trigger input is to be the collector output of a previous similar stage. Design a suitable triggering circuit.
- 9-11 Calculate the value of the commutating capacitors for the flip-flop and triggering circuits designed for Problems 9-4 and 9-10. Also, calculate the maximum triggering frequency that should be employed.
- 9-12 Sketch the circuits for asymmetrical base triggering and symmetrical base triggering. Explain how each circuit operates, and discuss the major disadvantages of symmetrical base triggering.
- 9-13 Sketch a collector-steered base triggering circuit. Show the triggering waveforms, and explain how the circuit operates.

- 9-14 Design a collector-steered base triggering circuit for the flip-flop designed for Problem 9-4. The triggering input is to be the collector output from a previous similar stage.
- 9-15 Determine the value of suitable commutating capacitors for the flip-flop and triggering circuits designed for Problems 9-4 and 9-14. Also calculate the maximum triggering frequency for the circuits.
- 9-16 Design an emitter triggering circuit for the flip-flop designed for Problem 9-6. Take the transistor turn-off time as 400 ns.
- 9-17 Select commutating capacitors for the circuit designed for Problem 9-16. Also determine the maximum triggering frequency for the circuit.
- 9-18 List the various basic logic type flip-flops, and sketch the logic symbol for each of them. Explain the function of each flip-flop.
- 9-19 Sketch the basic circuit for an RST flip-flop and explain its operation.
- 9-20 Sketch the basic circuit for a JK flip-flop and explain its operation.
- 9-21 Explain the term *loading factor* as applied to a flip-flop.

Chapter 10

Logic Gates

INTRODUCTION

The two basic logic gates are the AND gate and the OR gate. The AND gate produces a change in output voltage only when appropriate input voltages are applied to all of its input terminals. With the OR gate, an output is generated when any one of its input terminals receives a signal. NAND and NOR gates function in a slightly different way from AND and OR gates, respectively. Each type of gate has its own logic symbol.

Logic gates can be constructed by use of diodes and resistors (DIODE LOGIC), by use of resistors and transistors (RESISTOR TRANSISTOR LOGIC), or by using combinations of transistors (TRANSISTOR TRANSISTOR LOGIC). Other logic families are named according to the circuit configurations, and all are available as integrated circuits. The performances of the various IC logic families are expressed in terms of switching speed, power dissipation, noise immunity, and fan-out.

10-1 DIODE AND GATE

The circuit of a diode *AND* gate with three input terminals is shown in Figure 10-1(a). If one or more of the input terminals (*i.e.*, diode cathodes) are grounded, then the diode (or diodes) are forward-biased. Consequently, the output voltage V_O is equal to the diode forward voltage drop V_D . Suppose an input of 5 V is applied to terminal *A*, while terminals *B* and *C* are grounded. Diode D_1 is reverse-biased while D_2 and D_3 remain forward-biased, and $V_O = V_D$. If levels of 5 V are applied to all three inputs, no current flows through R_1 , and $V_O = V_{CC} = 5$ V. Thus, a *high* output voltage is obtained from the *AND* gate only when high input voltages are present at input *A*, *AND* at input *B*, *AND* at input *C*. Hence the name *AND* gate.

An *AND* gate may have as few as two or a great many input terminals. In all cases an output is obtained only when the correct input voltage levels are provided at every input terminal.

For all logic gates, the level of input and output voltages usually are described as either *high* or *low*. Depending upon the particular gate circuit, a *high* level might be between 3V and 6 V, while a *low* voltage level might be less than 1 V. The high level is usually designated *1*, and the low level is designated *0*. The logic symbol for the *AND* gate is shown in Figure 10-1(b). When one or more of the input levels is *0*, the gate output is also *0*. When all three input levels are *1*, the output also goes to *1*.

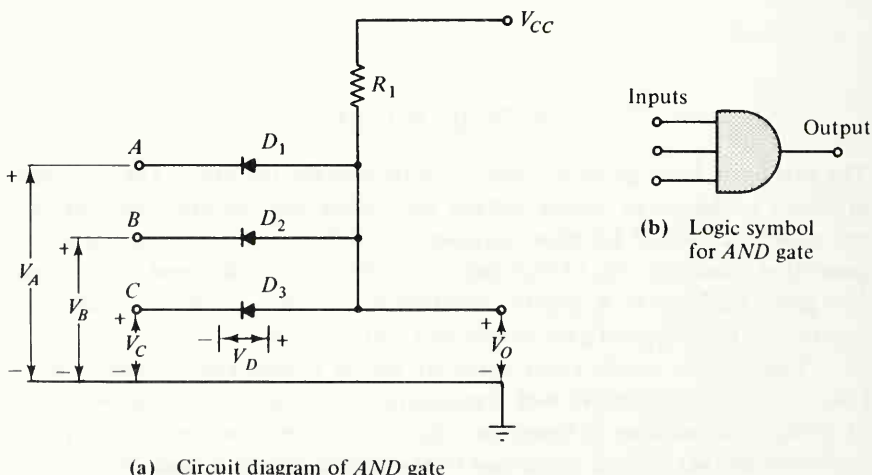


FIGURE 10-1. Circuit of a three-input diode *AND* gate and logic symbol for the *AND* gate.

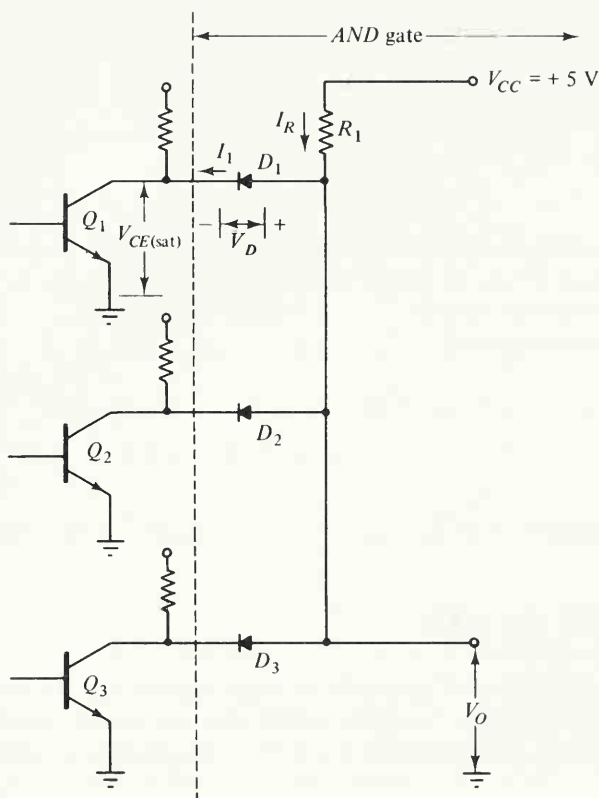


FIGURE 10-2. Diode AND gate with inputs controlled by transistors.

EXAMPLE 10-1

An AND gate has three input terminals which are connected to the collectors of saturated transistors. The transistors can take an *additional* collector current of 0.5 mA. Design a suitable circuit and determine the low and high output levels from the gate. Use $V_{CC} = 5$ V.

solution

The circuit is as shown in Figure 10-2. In the figure, maximum additional collector current I_1 flows through Q_1 when Q_1 is *on* and Q_2 and Q_3 are *off*.

$$I_R = I_{1(\max)}$$

$$V_{CC} = (I_R R_1) + V_D + V_{CE(\text{sat})}$$

$$\begin{aligned}
 R_1 &= \frac{V_{CC} - V_D - V_{CE(\text{sat})}}{I_R} \\
 &= \frac{5 \text{ V} - 0.7 \text{ V} - 0.2 \text{ V}}{0.5 \text{ mA}} \\
 &= 8.2 \text{ k}\Omega
 \end{aligned}$$

This is the minimum value for R_1 to limit the transistor additional collector current to 0.5 mA. R_1 could be made larger than 8.2 k Ω , in which case the current would be smaller.


Output voltages are:

$$\begin{aligned}
 V_{O(\text{low})} &= V_{CE(\text{sat})} + V_D \\
 &= 0.2 \text{ V} + 0.7 \text{ V} = 0.9 \text{ V}
 \end{aligned}$$

$$V_{O(\text{high})} = V_{CC} = 5 \text{ V}$$

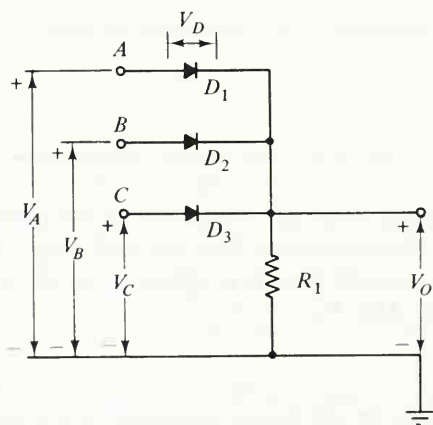10-2 DIODE OR GATE

A three input diode OR gate and its logic symbol are shown in Figure 10-3. It is obvious, from the gate circuit, that the output is zero when all three inputs are at ground level. If a 5 V input is applied to terminal A, D_1



(a) Circuit diagram for OR gate

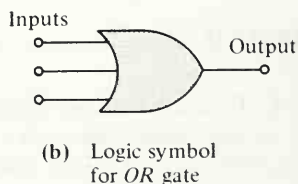


FIGURE 10-3. Circuit of a three-input diode OR gate and logic symbol for the OR gate.

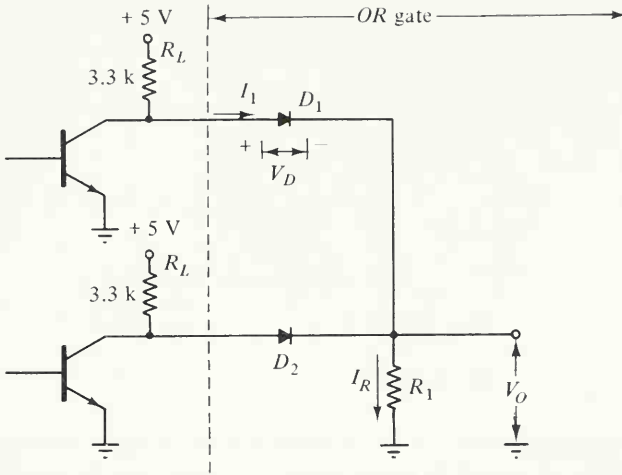


FIGURE 10-4. Diode OR gate with inputs controlled by transistors.

is forward-biased, and V_O becomes $(5\text{ V} - V_D)$. If terminals B and C are grounded at this time, diodes D_2 and D_3 are reverse-biased. Instead of terminal A , the positive input might be applied to terminal B or C to obtain a positive output voltage. A *high* output voltage is obtained from an OR gate, when a high input is applied to terminal A , OR to terminal B , OR to terminal C . Hence the name OR gate.

As in the case of the AND gate, an OR gate may have only two or a great many input terminals.

EXAMPLE 10-2

An OR gate has two input terminals, each of which are supplied from flip-flops having $R_L = 3.3\text{ k}\Omega$. The supply voltage to the flip-flops is $V_{CC} = 5\text{ V}$. The gate output voltage is to be at least 3.5 V . Design a suitable circuit.

solution

Refer to the circuit shown in Figure 10-4. When one input is *high*,

$$V_O = V_{CC} - (I_1 R_L) - V_D$$

and

$$I_R = I_1 = \frac{V_{CC} - V_D - V_O}{R_L}$$

$$I_R = \frac{5 \text{ V} - 0.7 \text{ V} - 3.5 \text{ V}}{3.3 \text{ k}\Omega} = 0.24 \text{ mA}$$

Also;

$$R_1 = \frac{V_O}{I_R}$$

$$= \frac{3.5 \text{ V}}{0.24 \text{ mA}}$$

$$\simeq 14.6 \text{ k}\Omega$$

This is a minimum value for R_1 to maintain the output voltage at a minimum of 3.5 V. R_1 could be made larger, in which case V_O would be larger.

10-3 POSITIVE LOGIC AND NEGATIVE LOGIC

The diode *AND* and *OR* gates already discussed both provide positive outputs when positive input signals are applied. This is referred to as *positive logic*. When negative input and output voltages are involved, the operation is termed *negative logic*.

Consider the situation with the diode *AND* gate shown in Figure 10-5. In this case, there is no supply voltage and the load resistance is grounded. If a negative input voltage V_A is now applied to terminal A , diode D_1 is forward-biased, and the output is pulled negatively. Therefore, a negative output is obtained when a negative input is applied to

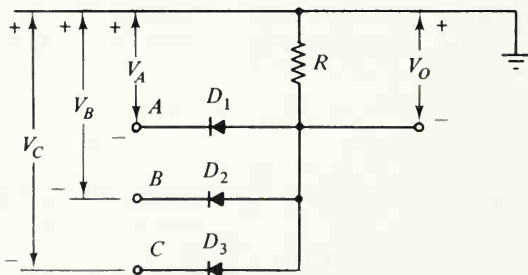
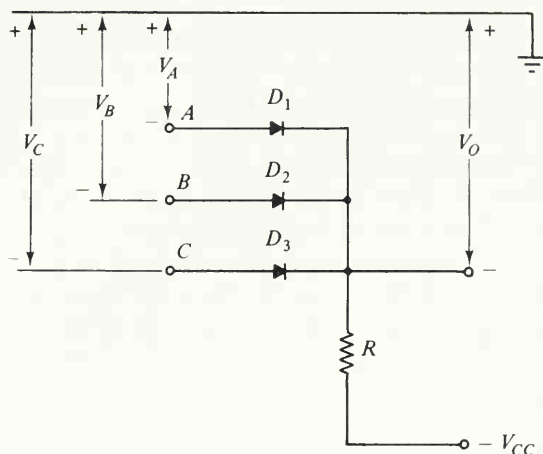


FIGURE 10-5. Negative logic *OR* gate.

FIGURE 10-6. Negative logic *AND* gate.

terminal *A*, OR terminal *B*, OR terminal *C*. Thus, the positive logic *AND* gate is also a negative logic *OR* gate.

The *OR* gate of Figure 10-3 is reproduced in Figure 10-6 with a negative supply connected to *R* and the input terminals grounded. While any of the inputs remain at ground level, one diode is forward-biased and the output remains $V_O = -V_D$. A (large) negative output voltage is obtained only when negative inputs are applied to terminal *A*, AND to terminal *B*, AND to terminal *C*. Thus, the positive logic *OR* gate can also be used as a negative logic *AND* gate.

10-4 DIODE TRANSISTOR LOGIC (DTL)

10-4.1 NAND Gate

As already explained, a positive logic diode *AND* gate has a low voltage output when one or more of its inputs are low, and a high output when all inputs are high. If a transistor inverter is connected at the output of the *AND* gate, the inverter output is high when one or more of the *AND* inputs are low, and low when all *AND* gate inputs are high. Used in this fashion, the inverter is termed a *NOT* gate. The combination of the *NOT* gate and the *AND* gate is then referred to as a *NOT AND* gate, or a *NAND* gate.

Figure 10-7(a) shows an integrated circuit *NAND* gate composed of

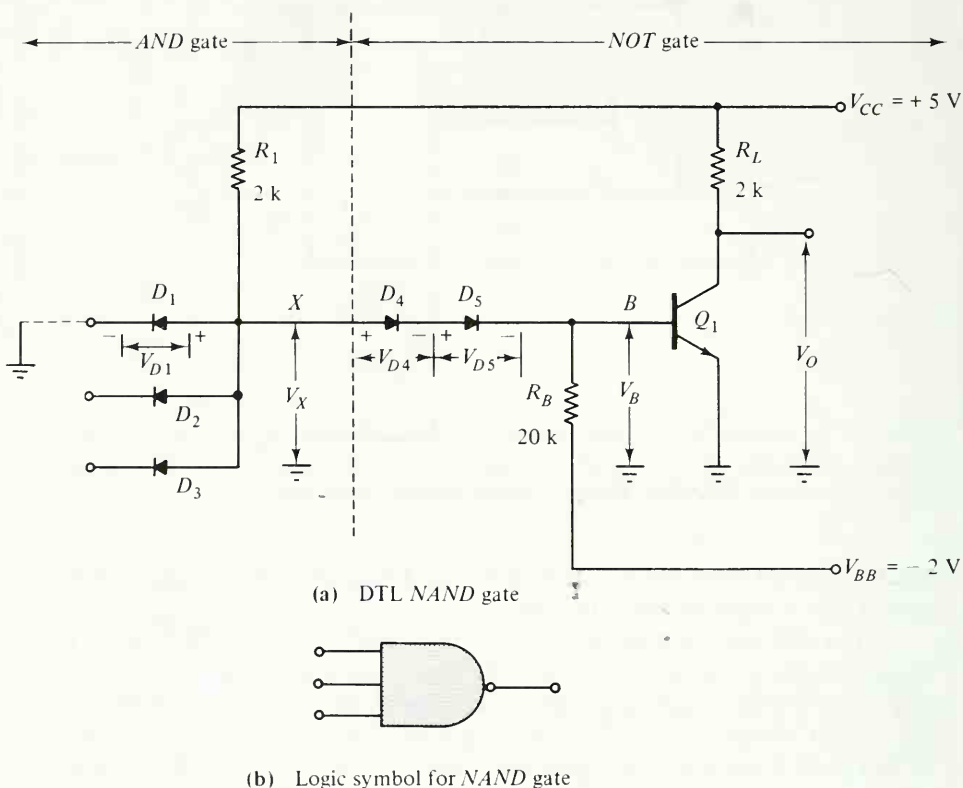


FIGURE 10-7. Diode transistor *NAND* gate and logic symbol.

a diode *AND* gate and an inverter. R_1 , D_1 , D_2 , and D_3 constitute the *AND* gate. The inverter is formed by transistor Q_1 with load resistor R_L and bias resistor R_B . When all input terminals are at ground level, the voltage at point X is the voltage drop across the input diodes (i.e., $V_X = V_D$). If diodes D_4 and D_5 were not present, V_D would be sufficient to forward-bias the base-emitter junction of Q_1 . The negative supply $-V_{BB}$ keeps diodes D_4 and D_5 forward-biased, so that when the inputs are at 0 V the transistor base voltage is:

$$\begin{aligned} V_B &= V_X - (V_{D4} + V_{D5}) \\ &= V_D - V_{D4} - V_{D5} \end{aligned}$$

For silicon devices,

$$\begin{aligned} V_B &\simeq 0.7 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V} \\ &= -0.7 \text{ V} \end{aligned}$$

Therefore, when any one input to the *NAND* gate is at 0 V, Q_1 is biased off, and the output voltage is V_{CC} .

Suppose all inputs to the *NAND* gate are made sufficiently positive to reverse-bias D_1 , D_2 , and D_3 . Now V_B depends upon the values of R_1 and R_2 , and upon the levels of V_{CC} and $-V_{BB}$. If these quantities are all correctly selected, V_B is positive at this time, Q_1 is driven into saturation, and the output voltage goes to $V_{CE(sat)}$. When any one input to the *NAND* gate is at logic 0, the gate output is at 1. When input *A* AND input *B* AND input *C* are at 1, the output of the *NAND* gate is level 0. The logic symbol employed for a *NAND* gate is shown in Figure 10-7(b). The symbol is simply that of an *AND* gate with a small circle at the output to indicate that the output voltage is inverted.

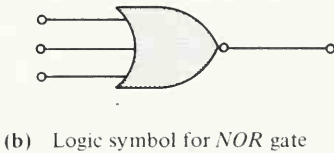
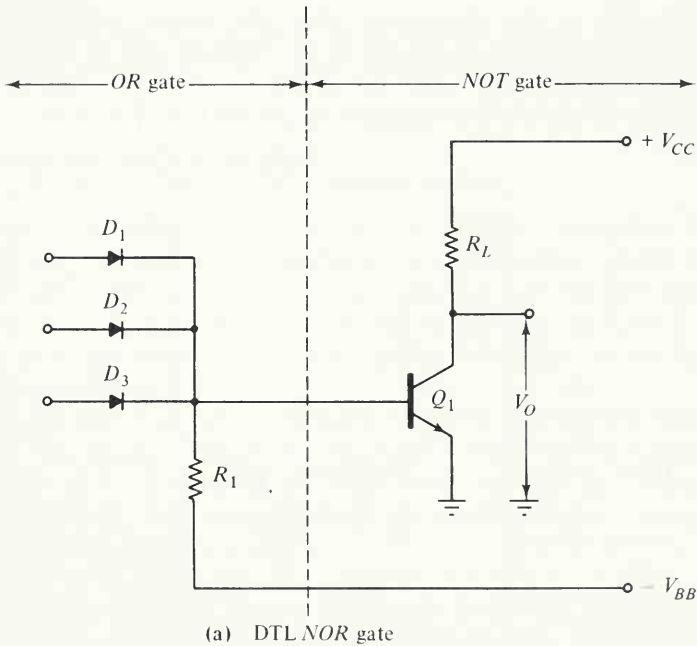



FIGURE 10-8. Diode transistor *NOR* gate and logic symbol.

10-4.2 NOR Gate


A transistor inverter (or *NOT* gate) connected at the output of a positive logic *OR* gate, generates a negative-going output when any one of the inputs is positive. The circuit is termed a *NOT OR* gate or *NOR* gate. A diode transistor *NOR* gate is shown in Figure 10-8(a), with its logic symbol shown in Figure 10-8(b). As in the case of the *NAND* gate, a small circle is employed to denote the polarity inversion at the output.

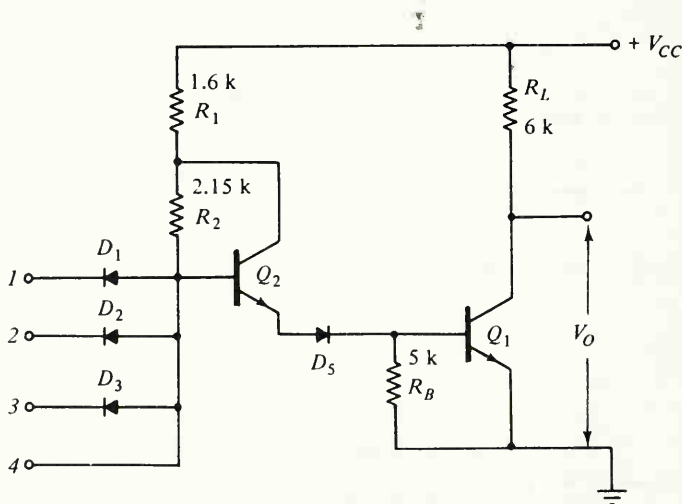10-4.3 Propagation Delay Time

The switching speed of a logic gate is defined in terms of a *propagation delay time*. This is the time required for the gate to switch from its *low* output state to its *high* output state, or *vice versa*. The quantity varies with the transistor collector current and output load conditions. The switching time is also dependent upon the circuit configuration; for example, the transistors may have to be switched out of saturation, or they may be unsaturated. In DTL, the transistors are saturated. Typical propagation delay time for integrated circuit DTL is 25 to 30 ns.



(a) Modified DTL *NAND* gate

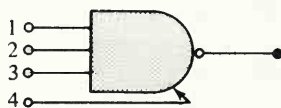

(b) Logic symbol for expandable gate

FIGURE 10-9. Modified DTL gate and logic symbol.

10-4.4 Modified DTL NAND Gate

A modified version of the DTL *NAND* gate is shown in Figure 10-9. Now, resistor R_B is on the order of 5 k Ω instead of 20 k Ω , and it simply ties the transistor base terminal to the emitter, that is, to ground level. Diode D_4 (in Figure 10-7) is replaced by *emitter follower* Q_2 in Figure 10-9. The emitter follower provides base current to Q_1 and allows R_1 to be replaced by a larger resistance, $R_1 + R_2$, thus reducing the maximum drive current to each input. The base-emitter voltage of Q_2 substitutes for the voltage drop across diode D_4 in Figure 10-7.

Input terminal 4 in Figure 10-9(a) is a direct connection to the diode anodes. Thus it provides for the connection of additional diodes to increase the number of input terminals. With this facility the gate is said to be *expandable*. Terminal 4 is shown on the logic symbol as a direct input [Figure 10-9(b)].

The advantages of modified DTL are operation from a single supply voltage, greater output current, lower power dissipation, and lower input current.

10-5 FAN-IN AND FAN-OUT

Since logic gates usually are connected in complex combinations, the output of each circuit must be capable of driving the inputs of many other similar circuits. The number of similar gates that any one gate can drive is limited. This limit is termed the *fan-out* of the gate. If I_L is the total output current that a gate can handle, and I_i is the drive current for each input, then *fan-out* = I_L/I_i .

The *fan-in* of a gate is the number of inputs that can be connected to a gate. The circuit in Figure 10-7 has three input terminals; therefore, it has a *fan-in* of 3. *Expandable* IC gates have facilities for connections of additional input. The stated *fan-in* for the gate is then the total number of inputs that may be connected.

Figure 10-10 shows one DTL *NAND* gate driving another similar gate. Note that the load current I_L actually flows *into* the collector of transistor Q_1 , and *out of* the input terminal of the gate being controlled. In this situation the transistor is sometimes referred to as a *current sink*. From a knowledge of the supply voltage, resistor values, and transistor $h_{FE(\min)}$, the *fan-out* of the circuit can be calculated.

EXAMPLE 10-3

Assuming that Q_1 has $h_{FE(\min)} = 20$, determine the fan-out for the DTL *NAND* gates shown in Figure 10-10.

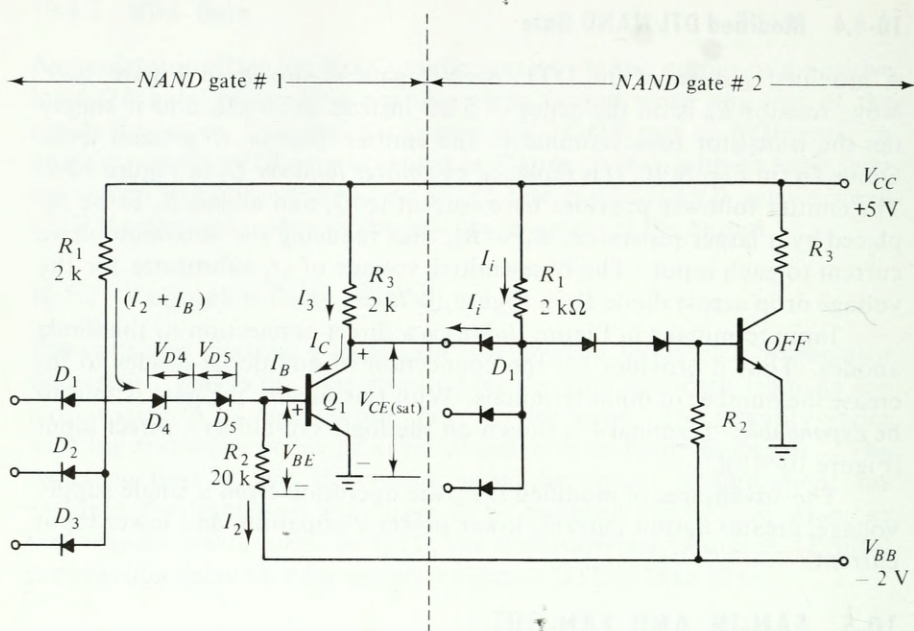


FIGURE 10-10. A DTL NAND gate driving another NAND gate.

solution

$$I_2 = \frac{V_{BE} - V_{BB}}{R_2}$$

$$= \frac{0.7 \text{ V} + 2 \text{ V}}{20 \text{ k}\Omega}$$

$$= 135 \mu\text{A}$$

$$I_2 + I_B = \frac{V_{CC} - V_{BE} - V_{D4} - V_{D5}}{R_1}$$

$$= \frac{5 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V}}{2 \text{ k}\Omega}$$

$$= 1.45 \text{ mA}$$

and

$$I_B = (I_2 + I_B) - I_2$$

$$= 1.45 \text{ mA} - 135 \mu\text{A}$$

$$= 1.315 \text{ mA}$$

$$I_{C1} = h_{FE} I_B$$

$$= 20 \times 1.315 \text{ mA} = 26.3 \text{ mA}$$

$$I_3 = \frac{V_{CC} - V_{CE(\text{sat})}}{R_3}$$

$$= \frac{5 \text{ V} - 0.2 \text{ V}}{2 \text{ k}\Omega} = 2.4 \text{ mA}$$

$$\text{Maximum output current} = I_L = I_{C1} - I_3$$

$$= 26.3 \text{ mA} - 2.4 \text{ mA}$$

$$\simeq 23.9 \text{ mA}$$

$$\text{Input current} = I_i = \frac{V_{CC} - V_{D3} - V_{CE(\text{sat})}}{R_1}$$

$$= \frac{5 \text{ V} - 0.7 \text{ V} - 0.2 \text{ V}}{2 \text{ k}\Omega}$$

$$= 2.05 \text{ mA}$$

$$\frac{I_L}{I_i} = \frac{23.9 \text{ mA}}{2.05 \text{ mA}} \simeq 11.6$$

Eleven similar gates can be driven from the output of one gate (*i.e.*, *fan-out* = 11).

It is obvious from Example 10-3 that a gate can operate with a load less than the fan-out. When the fan-out is exceeded, the gate may not operate correctly. Even when the fan-out is not exceeded, each additional load connected to a gate output increases the capacitance at the transistor collector and hence increases the gate switching time. For high speed operation IC manufacturers usually recommend a maximum *loading factor* which is less than the dc fan-out capability of the circuit.

Appendix 1-15 shows the data sheet for the Motorola MC 930/830 series integrated circuit DTL gates. These gates are described as *expandable dual 4-input gates*. Use of the term *dual* simply means that there are two complete gate circuits in each IC package. The schematic diagram on the data sheet also shows two separate gate circuits. Each gate has four input terminals connected to diode cathodes. Each also has a directly connected input terminal which may be used to *expand* the number of inputs.

The data sheet lists the output loading factor as 8 for the MC 930/830 circuit, and as 7 for the MC 961/861 circuit. Typical propagation

delay times are listed as 30 ns for the MC 930/830 and 25 ns for the MC 961/861. Output voltages are designated *low output voltage* V_{OL} and *high output voltage* V_{OH} . For both circuit types at 25°C, V_{OL} is a maximum of 0.4 V and V_{OH} is a minimum of 2.6 V.

10-6 HIGH THRESHOLD LOGIC (HTL)

The minimum input voltage at which a logic gate switches is termed the *threshold voltage*. Consider the DTL gate in Figure 10-11(a). For Q_1 to be switched *on*, Q_2 must also be *on* and D_5 must be forward-biased. For this to occur, the minimum input voltage at the cathode of D_3 is:

$$\begin{aligned} V_i &= V_{BE2} + V_{D5} + V_{BE1} - V_{D3} \\ &= 0.7 \text{ V} + 0.7 \text{ V} + 0.7 \text{ V} - 0.7 \text{ V} = 1.4 \text{ V} \end{aligned}$$

Therefore, the threshold voltage for a DTL gate is approximately 1.4 V.

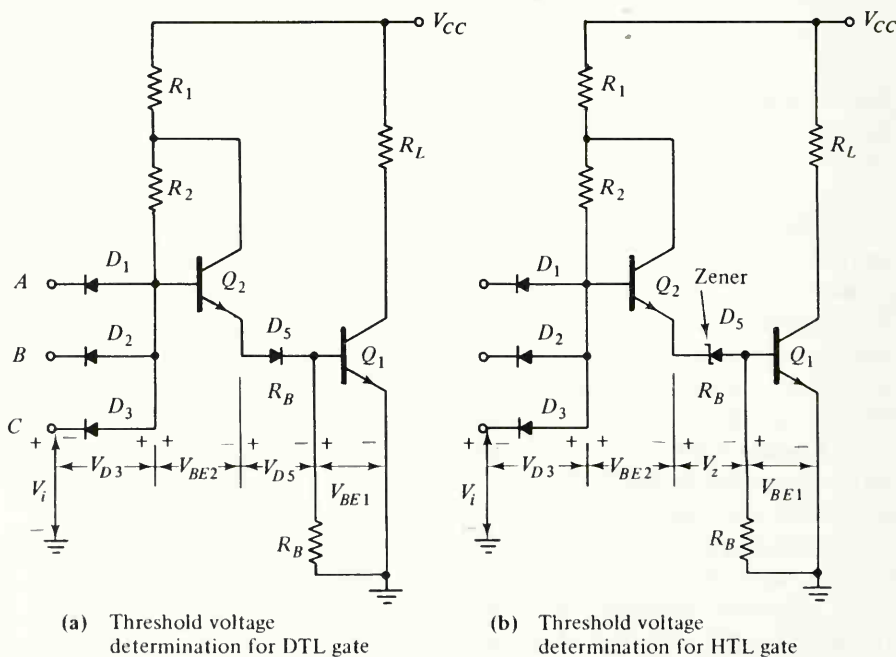


FIGURE 10-11. Comparison of DTL and HTL gates.

Under some circuit conditions *noise spikes* greater than 1.4 V may be present, and these could produce unwanted gate switching. To avoid this possibility, *high threshold logic* (HTL) was developed. It should be noted that the noise immunity of a logic gate does not depend solely on the threshold voltage. Where a circuit has a low input impedance, noise spikes are potentially divided, and therefore are less likely to cause switching. Similarly, a gate that is driven from a low impedance source may be more immune to noise voltages. Also, a gate that switches slowly is less sensitive to fast spikes than one that has a very short propagation delay time. It is seen that many factors are involved in the *ac noise immunity* for any given circuit. Instead of attempting to rate the noise immunity of a circuit in terms of voltage levels, switching time, and impedance, noise immunity is best described as *poor*, *fair*, *good*, or *excellent*.

In the HTL circuit in Figure 10-11(b), D_5 is a Zener diode with $V_z \simeq 6.8\text{ V}$. For Q_1 on, the Zener diode must be in breakdown and Q_2 must be on. Now, the minimum input voltage for Q_1 and Q_2 on is

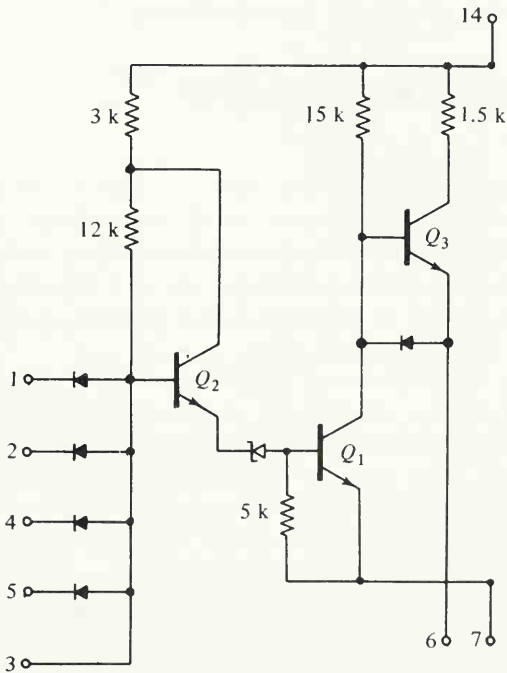


FIGURE 10-12. MC660 integrated circuit HTL NAND gate. (Courtesy of Motorola, Inc.)

$$\begin{aligned}
 V_i &= V_{BE2} + V_z + V_{BE1} - V_{D2} \\
 &= 0.7 \text{ V} + 6.8 \text{ V} + 0.7 \text{ V} - 0.7 \text{ V} \\
 &= 7.5 \text{ V}
 \end{aligned}$$

The threshold voltage for the HTL gate is approximately 7.5 V. It is obvious that the HTL gate is more immune than the DTL circuit to noise spikes. Note also that because of the presence of the Zener diode the HTL circuit uses $V_{CC} = 15 \text{ V}$, compared to $V_{CC} = 5 \text{ V}$ for DTL gates.

Figure 10-12 shows the circuit of a MC660 expandable four-input integrated circuit HTL gate manufactured by Motorola. The circuit is similar to that shown in Figure 10-11(b), with the exception that emitter follower Q_3 has been added at the output to improve the fan-out. The emitter follower is said to provide *active output pull-up*. The diode connected from Q_1 collector to the output terminal ensures that the output is *pulled down* rapidly when Q_1 is driven into saturation. The MC660 series HTL has a typical propagation delay time of 110 ns, which is much slower than the 25 to 30 ns for DTL. However, the longer switching time also provides the circuit with greater noise immunity.

10-7 RESISTOR TRANSISTOR LOGIC (RTL)

The *resistor transistor logic* circuit shown in Figure 10-13(a) has a *high* output voltage when all three inputs are at ground level. All three transistors are biased *off* so that no collector current flows, and $V_o \simeq V_{CC}$. A collector current flows and the output drops to a *low* level, if a positive input voltage is applied to terminal *A* OR terminal *B* OR terminal *C*. Thus the circuit is that of a *NOR* gate.

RTL gates are available as integrated circuits. However, an RTL *NOR* gate using discrete components is quite easy to design. Resistor R_1 should be selected much smaller than the load resistance to be supplied. This is because R_1 must pull up the output voltage when the gate transistors are biased *off*. If the desired gate output current I_o is known, then I_C should be made about ten times larger than I_o . This keeps R_1 small enough for good pull-up. I_B is calculated using $I_{C(\max)}$ and $h_{FE(\min)}$ as for all saturated transistors. Then R_B is determined from I_B , V_{BE} , and the threshold voltage for the circuit.

EXAMPLE 10-4

An RTL *NOR* gate is to have an output which goes from approximately 0 V to 3 V. The load supplied by the gate output (when the output is

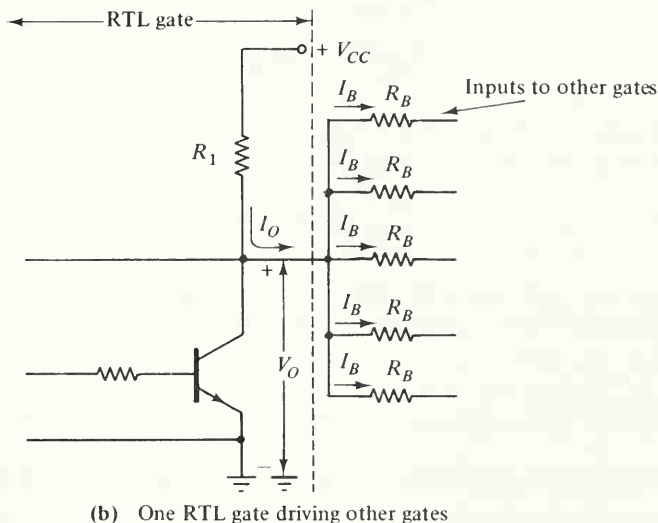
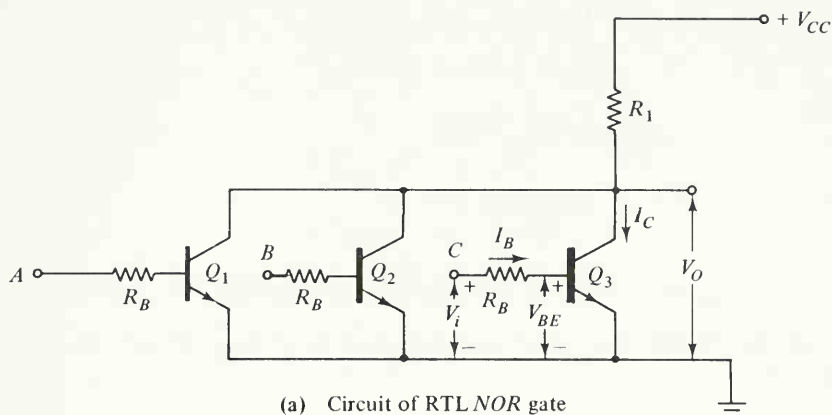


FIGURE 10-13. Circuit of RTL NOR gate and several gates driven from the output of one gate.

high) is 1 mA, and the gate input threshold voltage is to be ≈ 2 V. Using 2N3903 transistors, design a suitable circuit.

solution

Refer to Figure 10-13(a). For $V_O \approx 3$ V, use $V_{CC} = 3$ V. Make $I_c \gg$ load supplied. Let

$$\begin{aligned}
 I_C &\simeq 10 \times I_O \\
 &= 10 \times 1 \text{ mA} = 10 \text{ mA} \\
 R_I &= \frac{V_{CC} - V_{CE(\text{sat})}}{I_C} \\
 &= \frac{3 \text{ V} - 0.2 \text{ V}}{10 \text{ mA}} \\
 &= 280 \, \Omega \quad (\text{use } 270 \, \Omega \text{ standard value})
 \end{aligned}$$

From the 2N3903 data sheet in Appendix 1-4, at $I_C = 10 \text{ mA}$, $h_{FE(\text{min})} = 50$, and

$$\begin{aligned}
 I_{B(\text{min})} &= \frac{I_C}{h_{FE(\text{min})}} \\
 &= \frac{10 \text{ mA}}{50} = 200 \, \mu\text{A} \\
 R_B &= \frac{V_i - V_{BE}}{I_B} \\
 &= \frac{2 \text{ V} - 0.7 \text{ V}}{200 \, \mu\text{A}} \\
 &= 6.5 \text{ k}\Omega \quad (\text{use } 5.6 \text{ k}\Omega \text{ standard value})
 \end{aligned}$$

EXAMPLE 10-5

Determine the maximum fan-out of the circuit designed in Example 10-4.

solution

Refer to Figure 10-13(b). The input current to one input terminal of the gate is:

$$\begin{aligned}
 I_B &= \frac{V_i - V_{BE}}{R_B} \\
 &= \frac{2 \text{ V} - 0.7 \text{ V}}{5.6 \text{ k}\Omega} \\
 &= 232 \, \mu\text{A}
 \end{aligned}$$

When the output is *high* (at 2 V),

$$V_o = V_i(\text{to other gates}) = 2 \text{ V}$$

$$\begin{aligned} I_o &= \frac{V_{CC} - V_i}{R_L} \\ &= \frac{3 \text{ V} - 2 \text{ V}}{270 \, \Omega} \\ &= 3.7 \text{ mA} \end{aligned}$$

The maximum number of gate inputs that can be supplied by I_o is

$$\begin{aligned} \text{Total inputs} &= \frac{I_o}{I_B} \\ &= \frac{3.7 \text{ mA}}{232 \, \mu\text{A}} = 15.9 \end{aligned}$$

$$\text{Maximum fan-out} = 15$$

This is the absolute maximum number of gates that can be driven from the output of one gate as designed. For best switching speed and noise rejection, the fan-out should be kept well below the maximum.

The minimum input voltage that will begin to switch any one transistor *on* is the normal transistor V_{BE} of approximately 0.7 V. Although this voltage cannot drive the output to $V_{CE(\text{sat})}$, it could affect the input current to other gates [*i.e.*, those being driven from the output, as in Figure 10-13(b)]. Therefore, an RTL gate may be susceptible to noise voltages around 0.7 V.

Typical integrated circuit RTL uses a supply of 3 V, has a fan-out of 5, gate power dissipation of approximately 20 mW, and propagation delay time of 12 ns.

10-8 TRANSISTOR TRANSISTOR LOGIC (TTL)

In *transistor transistor logic* (TTL or T²L), the input signals are applied directly to transistor terminals.

Consider the basic TTL circuit shown in Figure 10-14(a). The output transistor Q_2 is controlled by the voltage at the collector terminal of transistor Q_1 . When the input terminal (*i.e.*, Q_1 emitter) is grounded, sufficient base current I_B flows to keep Q_1 in saturation. The collector

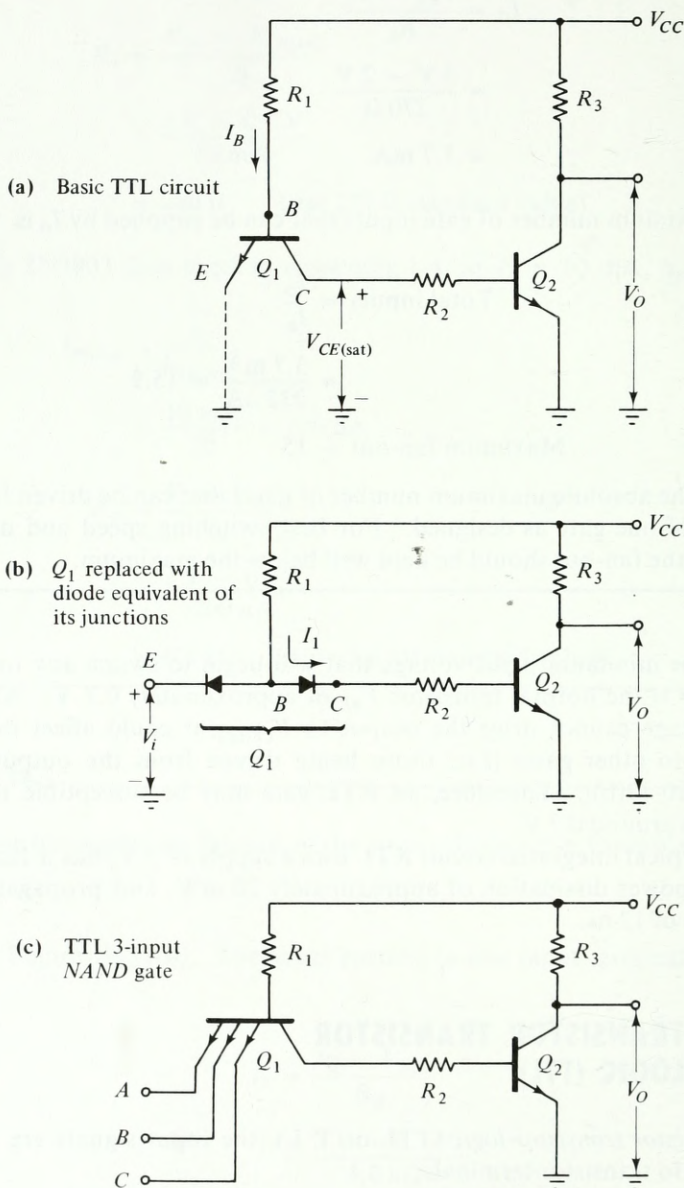


FIGURE 10-14. TTL gate circuits.

voltage of Q_1 is $V_{CE(sat)}$ above ground. Typically, $V_{CE(sat)}$ is 0.2 V which is not high enough to bias Q_2 on. Therefore, when the input voltage is low, Q_2 is off and the output level is high.

If a positive voltage is applied to the input terminal, Q_1 remains in saturation (I_B is still large enough) and Q_1 collector voltage goes to $V_i + V_{CE(sat)}$. Dependent upon the actual level of input voltage, sufficient base current can be supplied to Q_2 to drive it into saturation. Figure 10-14(b) shows Q_1 replaced by diodes representing the base-emitter and collector-base junctions. The arrangement is similar to that of a DTL circuit. It is seen that the input voltage could easily be made large enough to reverse-bias the base-emitter junction. When this occurs the collector-base junction remains forward-biased, and base current flows to saturate the output transistor.

Figure 10-14(c) shows a basic three-input TTL circuit. Q_1 is seen to be a transistor with three emitter terminals. This is fabricated easily in integrated circuit form. The three emitters are the input terminals to the gate. For Q_1 collector to rise above $V_{CE(sat)}$, input A AND input B AND input C must be high positive levels. Because of this, and because the output voltage level goes from high to low, the circuit is a NAND gate.

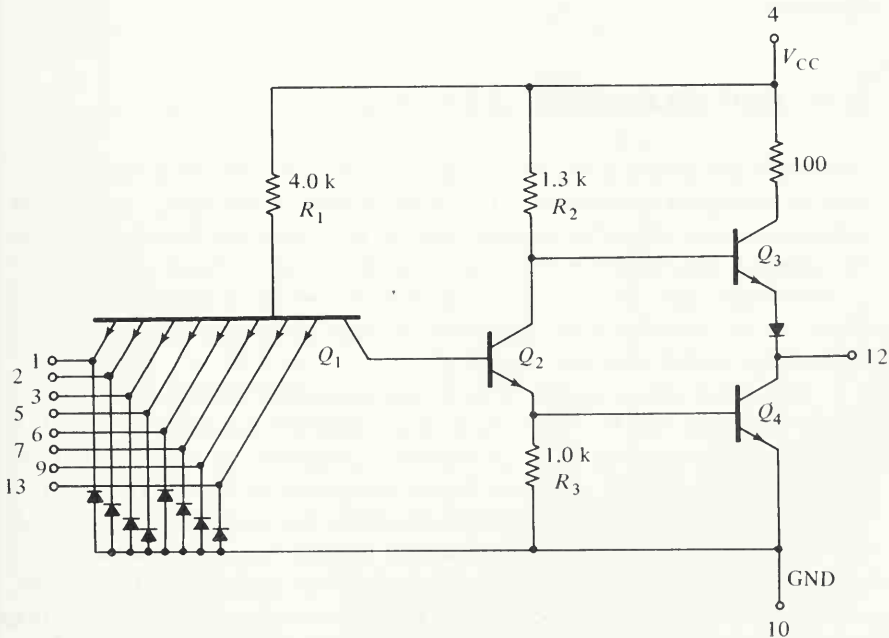


FIGURE 10-15. MC500/400 integrated circuit eight-input TTL NAND gate. (Courtesy of Motorola, Inc.)

The circuit of an eight-input integrated circuit TTL *NAND* gate is shown in Figure 10-15. The diodes connected from ground to each input terminal become forward-biased only when the input voltage goes negative. Their function is to limit the amplitude of negative spikes appearing at the gate inputs. Transistors Q_2 , Q_3 , and Q_4 function as follows: When Q_2 is *off*, R_3 biases Q_4 *off*, and R_2 biases Q_3 *on*. Thus Q_3 provides active pull-up (or low output impedance) when the gate output voltage is *high*. When Q_2 is *on* in saturation, base current supplied to Q_4 drives it into saturation. Consequently, the output voltage is pulled down, and Q_4 offers a low output impedance when the gate output is in its *low* state. At this time, Q_3 is biased *off* by the voltage drop across R_2 .


The multi-emitter input transistor used with TTL is always in saturation, even when all the input voltages are *high*. Since it never has to be switched out of saturation, there is no *storage time* involved when the transistor is switched. This is one reason why TTL tends to switch considerably faster than DTL. The typical propagation delay time for the MC500/400 gate (Figure 10-15) is 10 ns. The circuit operates from a 5 V supply, dissipates approximately 15 mW, and has a fan-out ranging from 6 to 15. Because the gate input terminals are transistor emitters, they have a low impedance; consequently, TTL is said to have good ac noise immunity.

10-9 EMITTER-COUPLED LOGIC (ECL)

One major limitation to the switching speed of logic circuits is the *storage time* of saturated transistors. The storage time is the time required to drive a transistor out of saturation, that is, to reverse the forward bias on the collector-base junction. In *emitter-coupled logic* (ECL), also termed *current mode logic*, the transistors are maintained in an unsaturated condition. This eliminates the transistor storage time, and results in logic gates which switch very fast indeed.

The schematic diagram of a typical integrated circuit ECL gate is shown in Figure 10-16. The circuit uses a negative supply $-V_{EE}$ and the positive supply terminal V_{CC} is grounded. Transistor Q_5 has its base bias voltage provided by the potential divider composed of R_5 , R_6 , D_1 , and D_2 . The diodes provide temperature compensation for changes in the V_{BE} of Q_5 . Q_5 operates as an emitter follower to provide a low impedance bias to the base of transistor Q_4 . With a constant bias voltage at Q_4 base, the voltage drop across emitter resistor R_2 is also maintained constant so long as the input voltages are low enough to keep transistors Q_1 , Q_2 , and Q_3 in the *off* state. In this circumstance, the emitter current and collector current of Q_4 are held constant and the transistor is maintained in an un-

(a) Integrated circuit ECL OR/NOR gate

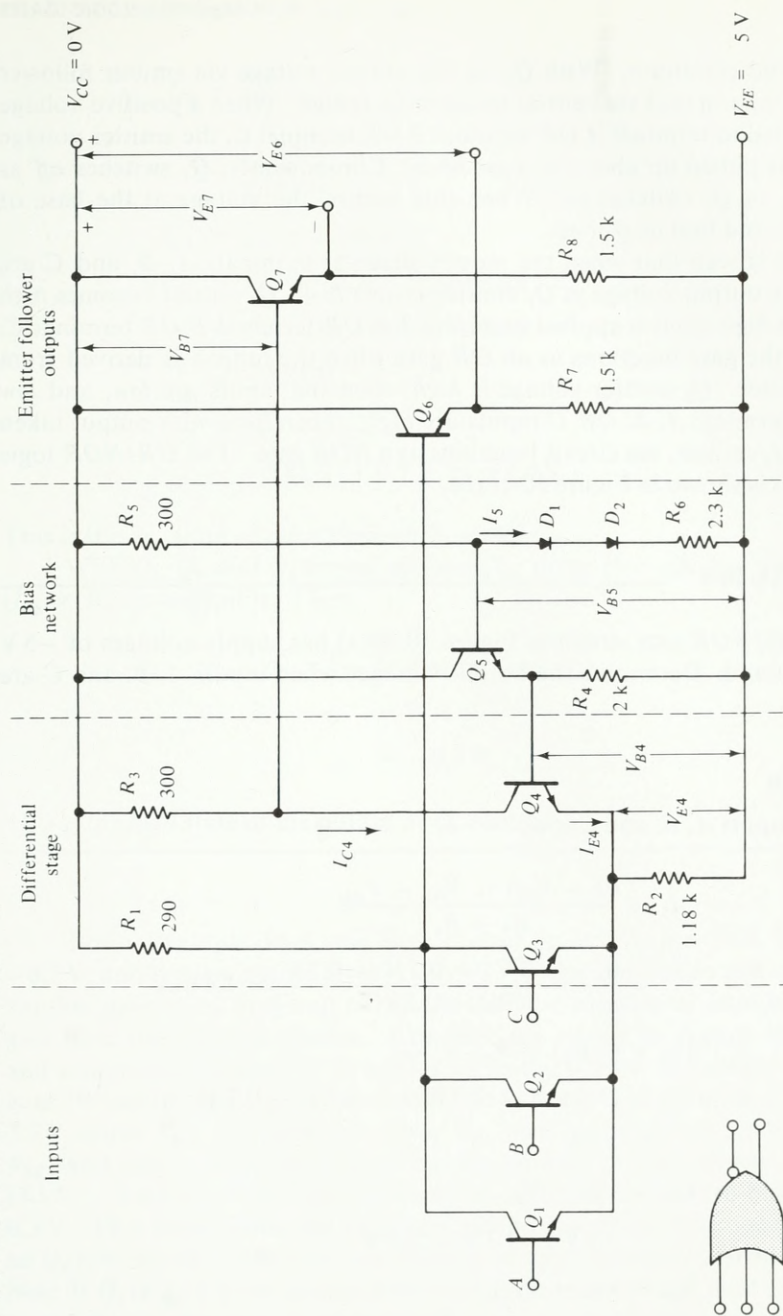

(b) OR/NOR gate logic symbol

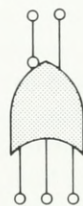


FIGURE 10-16. Circuit and logic symbol for ECL OR/NOR gate.

saturated condition. With Q_4 on, the output voltage via emitter follower Q_7 is low, and that via emitter follower Q_6 is high. When a positive voltage is applied to terminal A OR terminal B OR terminal C , the emitter voltage of Q_4 is pulled up above its base level. Consequently, Q_4 switches off as Q_1 , Q_2 , or Q_3 switches on. When this occurs, the voltage at the base of Q_6 falls and that at Q_7 rises.

It is seen that when the input voltage at terminals A , B , and C are low, the output voltage at Q_7 emitter is also low. Q_7 output becomes high when a high input is applied to terminal A OR terminal B OR terminal C . Thus, the gate functions as an OR gate when the output is derived from Q_7 emitter. Q_6 emitter voltage is high when the inputs are low, and low when terminal A , B , OR C inputs are high. Therefore, with output taken from Q_6 emitter, the circuit functions as a NOR gate. The OR/NOR logic symbol is shown in Figure 10-16(b).

EXAMPLE 10-6

The OR/NOR gate circuit in Figure 10-16(a) has supply voltages of -5 V and ground. Determine the output voltages when inputs A , B , and C are low.

solution

With inputs A , B , and C low,

$$\begin{aligned} I_5 &= \frac{(0 - V_{EE}) - V_{D1} - V_{D2}}{R_5 + R_6} \\ &= \frac{0 - (-5\text{ V}) - 0.7\text{ V} - 0.7\text{ V}}{300\Omega + 2.3\text{ k}\Omega} \simeq 1.4\text{ mA} \end{aligned}$$

$$\begin{aligned} V_{B5} &= (I_5 R_6) + V_{D1} + V_{D2} \\ &= (1.4\text{ mA} \times 2.3\text{ k}\Omega) + 0.7\text{ V} + 0.7\text{ V} \\ &\simeq 4.6\text{ V} \end{aligned}$$

$$\begin{aligned} V_{B4} &= V_{B5} - V_{BE5} \\ &= 4.6\text{ V} - 0.7\text{ V} = 3.9\text{ V} \end{aligned}$$

$$\begin{aligned} V_{E4} &= V_{B4} - V_{BE4} \\ &= 3.9\text{ V} - 0.7\text{ V} \\ &= 3.2\text{ V} \end{aligned}$$

$$\begin{aligned}
 I_{E4} &= \frac{V_{E4}}{R_2} \\
 &= \frac{3.2 \text{ V}}{1.18 \text{ k}\Omega} \simeq 2.7 \text{ mA} \\
 I_{C4} &\simeq I_{E4} = 2.7 \text{ mA} \\
 V_{B7} &\simeq V_{CC} - I_{C4}R_3 \quad (\text{neglect } I_{B7}) \\
 &= 0 \text{ V} - (2.7 \text{ mA} \times 300\Omega) \\
 &= -0.81 \text{ V} \\
 V_{E7} &= V_{B7} - V_{BE7} \\
 &= -0.81 \text{ V} - 0.7 \text{ V} \simeq -1.5 \text{ V}
 \end{aligned}$$

This is the *low* state of the output at Q_7 emitter.

With Q_1 , Q_2 , and Q_3 biased *off*, only I_{B6} flows through R_1 . Consider ($I_{B6} \times R_1$) as negligible. Then,

$$\begin{aligned}
 V_{E6} &\simeq V_{CC} - V_{BE6} \\
 &= 0 - 0.7 \text{ V} \\
 &= -0.7 \text{ V}
 \end{aligned}$$

This is the *high* state of the output at Q_6 emitter.

From Example 10-6, the *high* output level for the ECL gate is -0.7 V , and the *low* output level is -1.5 V . When applied to the input of another gate, these *high* and *low* levels must be capable of switching the gate from one state to another. Consider the circuit in Figure 10-16(a), and assume that terminal C is connected to the output of another similar gate. When the *low* output level (-1.5 V) is applied to terminal C , V_{B3} is 3.5 V above V_{EE} . In Example 10-6, V_{E4} was found to be 3.2 V above V_{EE} , and this is also the voltage at the emitter of Q_3 . Since, $V_{BE3} = (3.5 \text{ V} - 3.2 \text{ V}) = 0.3 \text{ V}$, Q_3 base-emitter actually is forward-biased by 0.3 V . This is not sufficient to bias a silicon transistor into conduction, so Q_3 remains *off*. However, an increase of approximately 250 mV at the base of Q_3 (e.g., a noise spike) could cause the transistor at least partially to switch *on*. A similar analysis of the circuit conditions when Q_3 is *on* and Q_4 is *off* shows that switching could again occur with a -250 mV spike.

The principal drawback of integrated circuit ECL compared to other IC logic families is now evident. That drawback is its sensitivity to low level noise on the order of ± 250 mV. The high input resistance and very fast switching speed of ECL also contributes to its low noise immunity. However, the low output resistance of ECL improves the noise immunity at the input of another gate that is being driven. Another aspect of the noise sensitivity of logic gates is that most types of logic circuits generate noise spikes when transistors are switched into or out of saturation. This is not the case with ECL, because each time one transistor is switched *off* another is switched *on*. Thus the current drawn from the supply remains approximately constant.


Another disadvantage of ECL is its relatively high power dissipation, approximately 30 mW per gate. The major advantage of ECL over other types of logic undoubtedly is the very fast switching speed. Because of the nonsaturated condition of the *on* transistors, the propagation delay time can be 2 ns or less.

Appendix 1-16 shows the data sheet for MC306.MC307 3-input ECL gates manufactured by Motorola. In the schematic diagram on the data sheet, the three transistors with their bases connected to terminals 6, 7, and 8 correspond to Q_1 , Q_2 , and Q_3 in Figure 10-16(a). Also, the transistor with its base connected to terminal 1 corresponds to Q_4 in Figure 10-16(a). The remaining two transistors in the MC306.MC307 circuit are the emitter follower outputs. No bias network is provided in this IC gate. Instead, an external bias driver must be connected to terminal 1.

The listed electrical characteristics of the MC306.MC307 show that the low output voltage (NOR logic 0) is -1.750 V. The high output voltage (NOR logic 1) is -0.795 V. This gives an output voltage change of 0.955 V. The shortest propagation delay time for the MC306.MC307 is listed as 5.5 ns.

10-10 COMPLEMENTARY MOSFET LOGIC (CMOS)

CMOS is the abbreviation for *complementary metal oxide semiconductor*. As already discussed in Secs. 4-6 and 4-7, MOSFET switches have an extremely high input resistance, very small drain to source voltage drop, and very little power dissipation. The *n*-channel *enhancement mode* MOSFET is normally *off* when its gate is at the same potentials as its substrate. When the gate is made positive with respect to the substrate, an *n*-type channel is produced from drain to source, and drain current flows. Similarly, the *p*-channel device has no drain current while its gate and sub-

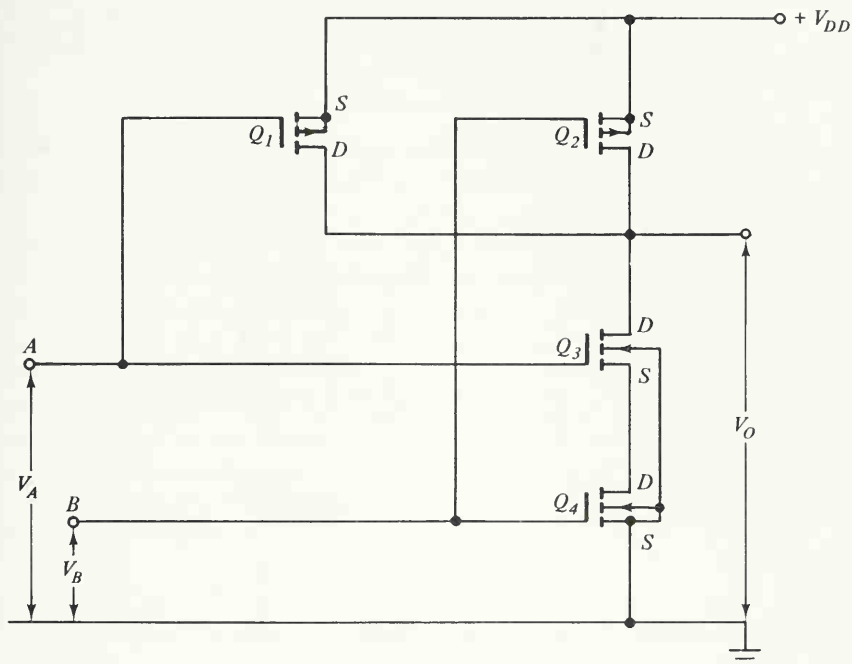FIGURE 10-17. CMOS *NAND* gate.

strate are at the same potential. The *p*-type channel appears when the gate is made negative with respect to the substrate.

The CMOS *NAND* gate shown in Figure 10-17 employs two *p*-channel MOSFETs (Q_1 and Q_2) and two *n*-channel devices (Q_3 and Q_4). When input terminals A and B are grounded, the *p*-channel devices (Q_1 and Q_2) are biased *on*, and the *n*-channel FETs are *off*. This means that the drain terminals of Q_1 and Q_2 are at the same potential as their source terminals (i.e., V_{DD}). Therefore, when both A and B are grounded, $V_o \simeq V_{DD}$. Actually, V_o is about 10 mV less than V_{DD} at this time. When an input equal to V_{DD} is applied to terminal A , Q_3 is biased *on* and Q_2 is biased *off*. However, with terminal B grounded, Q_4 is still *off* and Q_1 is still *on*. Consequently, the output voltage remains at V_{DD} . When the positive input (equal to V_{DD}) is applied to terminal A and to terminal B , both *p*-channel devices are biased *off* and both *n*-channel transistors are biased *on*. The output now goes to 0 V plus approximately a 10 mV drop along the channels of Q_3 and Q_4 .

The circuit of a CMOS *NOR* gate is shown in Figure 10-18. Once again, two *p*-channel devices (Q_1 and Q_2) and two *n*-channel transistors

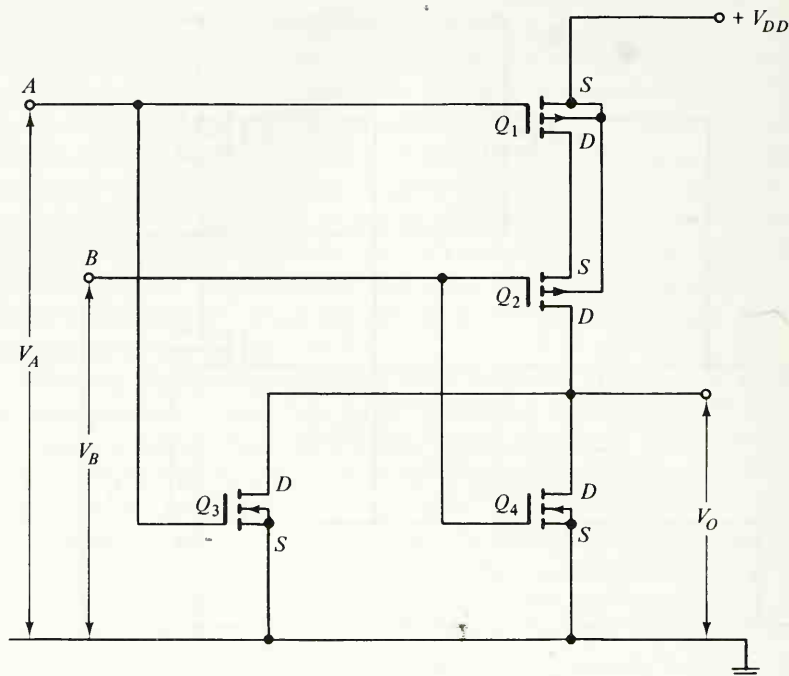


FIGURE 10-18. CMOS NOR gate.

(Q_3 and Q_4) are employed. When both inputs are at ground level, Q_3 and Q_4 are biased *off*, and Q_1 and Q_2 are *on*. In this condition there is about a 10 mV drop from drain to source terminals in the p -channel transistors, and V_O is very close to V_{DD} . When terminal A has a positive input (equal to V_{DD}), Q_1 switches *off* and Q_3 switches *on*. The series combination of Q_1 and Q_2 now is open-circuited, and the output is shorted to ground via Q_3 . Similarly, if terminal A remains grounded and terminal B has V_{DD} applied, Q_2 switches *off* and Q_4 switches *on*. Again the output goes to ground level.

The major advantage of integrated circuit CMOS logic over bipolar logic circuits is its extremely low power dissipation. Ranging from $2.5 \mu\text{W}$ to $10 \mu\text{W}$ per gate, the low dissipation allows greater circuit density within a given size of IC package. The resultant low supply current demand also makes CMOS ideal for battery-operated instruments. Typical supply voltages employed for CMOS are 5 V to 10 V; however, operation with a supply of 1 V to 18 V is possible. The circuitry is immune to noise levels as high as 30% of the supply voltage. The extremely high input resistance of MOSFETs gives CMOS gates typical input resistances of $10^9 \Omega$, and this makes it possible to have fan-outs greater than 50. Typical propagation delay time for CMOS is 25 ns.

10-11 COMPARISON OF MAJOR
 TYPES OF IC LOGIC

The major integrated circuit logic families are compared in Table 10-1. In applications for which high speed is important, either RTL or TTL may be suitable. Although RTL is less expensive, TTL is superior in noise immunity and fan-out. When very high speed is desirable, ECL is the only choice. Also, it offers large fan-out but relatively high power dissipation and only fair noise immunity. If switching speed is not the paramount consideration, then DTL or CMOS might be suitable. In situations where noise is unavoidable, either HTL or CMOS are appropriate. CMOS is very much superior to both DTL and HTL in fan-out and switching speed and offers low power dissipation. Also, CMOS is relatively inexpensive to manufacture, and because of the extremely low power dissipation CMOS integrated circuits can be produced with a much greater density than any other type of logic.

Table 10-1
COMPARISON OF TYPICAL
CHARACTERISTICS OF IC LOGIC

	<i>DTL</i>	<i>RTL</i>	<i>HTL</i>	<i>TTL</i>	<i>ECL</i>	<i>CMOS</i>
Propagation delay time	30 ns	12 ns	119 ns	12 ms	2 ns	25 ms
Power dissipation per gate	15 mW	15 mW	50 mW	15 mW	40 mW	5 μ W
Noise immunity	Good	Poor	Excellent	Good	Fair	Excellent
Fan-out	8	5	10	10	25	> 50

REVIEW QUESTIONS AND PROBLEMS

- 10-1 Sketch the circuit and logic symbol for a diode *AND* gate. Briefly explain the operation of the circuit.
- 10-2 Design a four-input diode *AND* gate using a 9 V supply. The gate inputs are to be controlled from the collectors of saturated transistors which can pass an additional collector current of 1 mA. Determine the *low* and *high* output levels for the gate.
- 10-3 Sketch the circuit and logic symbol for a diode *OR* gate. Briefly explain the operation of the circuit.
- 10-4 A diode *OR* gate is to have an output voltage which goes from a

low level of 0 V to a *high* level of at least 2 V. The inputs to the *OR* gate are connected to flip-flops with $R_L = 4.7 \text{ k}\Omega$ and $V_{CC} = 9 \text{ V}$. Design a suitable circuit.

- 10-5 Explain *positive logic* and *negative logic*. Sketch the circuits of negative logic *AND* and *OR* gates. Compare these to positive logic circuits.
- 10-6 Sketch the circuit and logic symbol for a DTL *NAND* gate. Carefully explain the operation of the circuit and discuss the function of each component.
- 10-7 Repeat Problem 10-6 for a DTL *NOR* gate.
- 10-8 Sketch the circuit and logic symbol for a *modified* DTL *NAND* gate, with facility for fan-in expansion. Compare the modified and unmodified DTL gates.
- 10-9 Define *fan-in* and *fan-out* and discuss their relationships to gate switching speed.
- 10-10 Calculate the fan-out for the modified DTL *NAND* gate shown in Figure 10-9. Assume that the transistors have $h_{FE(\min)} = 20$ and $V_{CC} = 5 \text{ V}$.
- 10-11 Calculate the fan-out for the DTL *NOR* gate shown in Figure 10-8. Take $R_L = 2 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, $V_{CC} = 5 \text{ V}$, and $V_{BB} = -2 \text{ V}$.
- 10-12 Explain the need for *high threshold logic* and discuss the other factors relating to the *ac noise immunity* of logic gates.
- 10-13 Sketch the circuit of a typical HTL *NAND* gate, and carefully explain the function of every component.
- 10-14 Sketch the circuit of a two-input RTL *NOR* gate, and explain its operation.
- 10-15 An RTL *NOR* gate is to have an output which goes approximately from 0 V to 5 V. The load to be supplied by the gate output (when *high*) is 0.5 mA, and the gate input threshold voltage is to be $\approx 3 \text{ V}$. Using 2N3904 transistors, design a suitable circuit.
- 10-16 Using illustrations, explain the principle of TTL. Discuss the reasons for the fast switching speed and good *ac noise immunity* of TTL.
- 10-17 Sketch the circuit of a typical integrated circuit TTL gate. Explain the function of each component.
- 10-18 Sketch the complete circuit and logic symbol for an ECL *OR/NOR* gate. Carefully explain the operation of the circuit, and discuss the major advantages and disadvantages of ECL.
- 10-19 Sketch the circuits of CMOS *NAND* and *NOR* gates. Carefully

explain the operation of each circuit, and list the advantages and disadvantages of CMOS logic.

- 10-20** Define *propagation delay time*, and discuss the characteristics that affect the switching speed of the various logic circuits.
- 10-21** Compare the various types of IC logic in terms of propagation delay time, power dissipation, noise immunity, and fan-out.

Chapter 11

Sampling Gates

INTRODUCTION

A SAMPLING GATE is a switching circuit which usually is employed to sample the amplitude of dc or low-frequency signals. Sampling gate circuits can be constructed using diodes, bipolar transistors, or FETs. For large signal voltages, diodes or bipolar transistors may be satisfactory. For very small signals, JFETs or MOSFETs produce the best results.

11-1 DIODE SAMPLING GATE

A very simple diode gate which may be applied to voltage level sampling is shown in Figure 11-1. The signal V_s to be sampled is applied to the cathode of D_1 . The output voltage V_o is derived from the cathode of D_2 . A pulse control input V_1 is applied via R_1 to the anodes of D_1 and D_2 . The

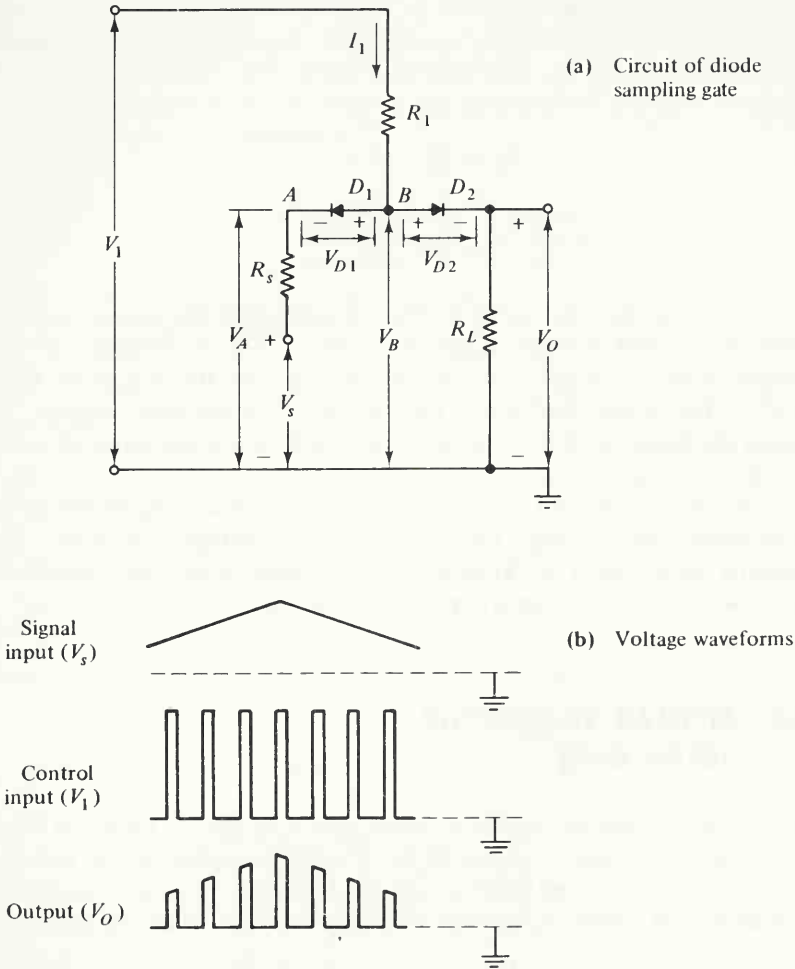


FIGURE 11-1. Circuit and waveforms for diode sampling gate.

signal source resistance is R_s , and the load is R_L . When the control voltage is zero or negative, diodes D_1 and D_2 are reverse-biased, and $V_o \simeq 0$ V. When the control voltage becomes positive, D_1 and D_2 are forward-biased. Then,

$$V_A = V_s + I_s R_s$$

if

$$I_s R_s \ll V_s, \quad V_A \simeq V_s$$

and

$$\begin{aligned}
 V_B &= V_A + V_{D1} \\
 &\simeq V_s + V_{D1} \\
 V_o &= V_B - V_{D2} \\
 &\simeq V_s + V_{D1} - V_{D2} \\
 &\simeq V_s
 \end{aligned}$$

It is seen that the signal voltage is passed to the output terminals when the control voltage pulses positively. The waveforms of input voltage, control voltage, and output voltage are illustrated in Figure 11-1(b). The circuit shown can sample only positive input signals. Reversing the diodes and the control input would permit sampling of a negative signal voltage.

The diode sampling gate has errors due to differences in the voltage drops across each diode, and due to diode leakage currents. Consequently, diode gates are applicable only where large signal amplitudes are involved and where accuracy is not important.

11-2 BIPOLAR TRANSISTOR SERIES GATE

The circuit of a bipolar transistor series sampling gate is shown in Figure 11-2. The low-frequency signal to be sampled is applied to the collector, and the output is derived from the emitter terminal. A pulse waveform at the base acts as a control, driving the transistor into saturation and cutoff.



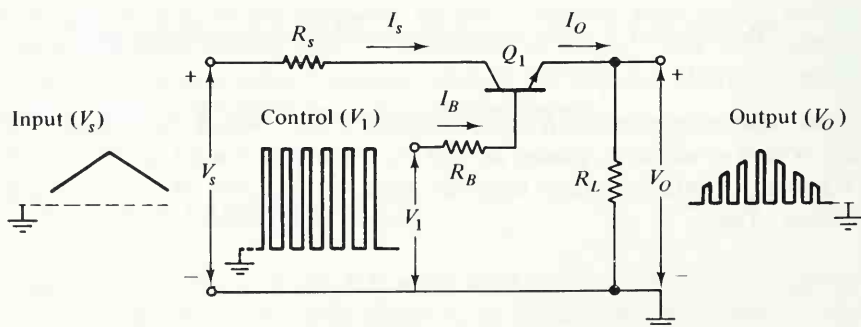


FIGURE 11-2. Bipolar transistor series sampling gate.

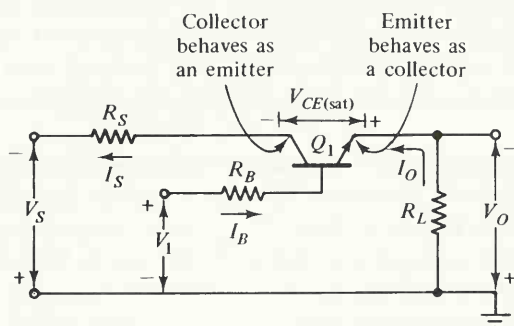When the control voltage is positive, Q_1 is biased *on*. When the control voltage goes to zero, Q_1 is *off*. At transistor saturation, the output voltage is $V_o \simeq V_s$. At cutoff, the output becomes zero. It is seen that the transistor is operating as a switch, and that the output from the gate is a series of samples of the input amplitude.



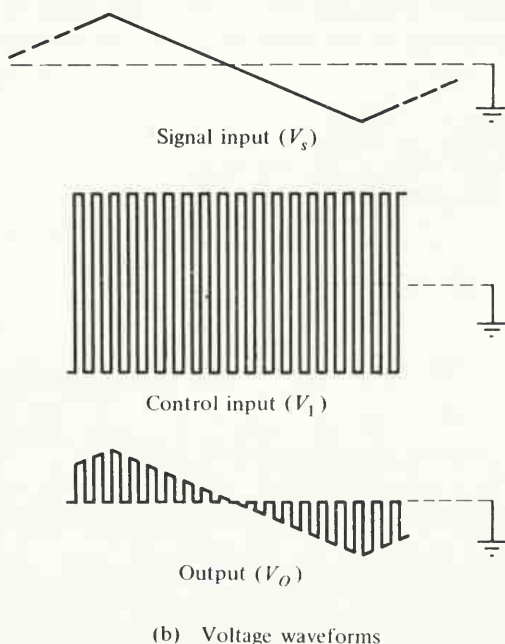(a) Series gate with a negative signal voltage




(b) Voltage waveforms

FIGURE 11-3. Series gate with negative signal voltage and transistor in *inverted* mode.


The waveforms in Figure 11-2 are drawn for a positive input signal. If the input becomes negative, as shown in Figure 11-3(a), then the transistor operates in the *inverted mode*. The emitter terminal acts as the collector, and the collector operates as the transistor emitter. This, by no means, is an efficient way to operate a transistor used for amplification. However, as a saturated switch with a large base current, the transistor performs satisfactorily in inverted mode. To ensure that the device will switch *off*, the negative swing of the control voltage must be greater than the negative peak of the signal voltage. For a signal with positive and negative components, the circuit waveforms are as illustrated in Figure 11-3(b).

The input signal applied to a sampling gate is frequently a very low level voltage. Since the transistor saturation voltage constitutes a loss of signal amplitude [see Figure 11-4(a)], $V_{CE(sat)}$ (also termed the *offset voltage*) must be maintained as small as possible. Reference to the transistor characteristics in Figure 4-2 shows that for the smallest $V_{CE(sat)}$, I_C must be kept small and I_B must be relatively large. For $I_C = 1$ mA and $I_B = 0.1$ mA, a typical $V_{CE(sat)}$ is 0.2 V. Another source of error is the emitter-base leakage current I_{EO} that flows when the device is biased *off*. I_{EO} causes an unwanted output voltage to develop across load resistance R_L [see Figure 11-4(b)]. A typical level of I_{EO} for a switching transistor is 50 nA at 25°C.

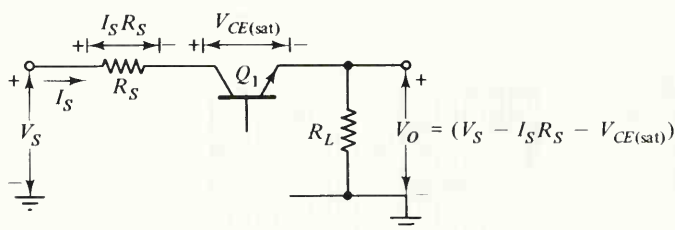In the design of a series sampling gate, the load resistance R_L should



(a) Q_1 on

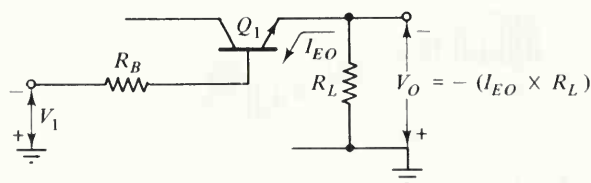

(b) Q_1 off

FIGURE 11-4. Error sources in bipolar transistor series gate.

be selected much larger than the signal source resistance R_s . This will avoid large signal currents which would cause a significant voltage drop across R_s . The signal current can be reduced to a minimum if I_B is made equal to the output current I_E . The amplitude of the control voltage should be greater than the peak signal voltage. The sampling frequency (i.e., the control voltage frequency) should be several times the frequency of the signal to be sampled.

EXAMPLE 11-1

Design a transistor series gate to sample a signal with a peak amplitude of 2 V, and a source resistance of 100 Ω . Also calculate the output errors due to $V_{CE(sat)}$ and I_{EO} .

solution

$$R_L \gg R_s$$

Let

$$R_L = 100 \times R_s = 100 \times 100 \Omega = 10 \text{ k}\Omega$$

When the transistor is on,

$$V_o \simeq V_s$$

$$\therefore I_o = \frac{V_s}{R_L} = \frac{2 \text{ V}}{10 \text{ k}\Omega} = 200 \mu\text{A}$$

Let

$$I_B = I_o = 200 \mu\text{A}$$

The control voltage $V_1 > V_s$. Let

$$V_1 = 2 \times V_s = 2 \times 2 \text{ V} = 4 \text{ V}$$

$$I_B = \frac{V_1 - V_{BE} - V_o}{R_B}$$

$$200 \mu\text{A} = \frac{4 \text{ V} - 0.7 \text{ V} - 2 \text{ V}}{R_B}$$

and

$$R_B = \frac{1.3 \text{ V}}{200 \mu\text{A}} = 6.5 \text{ k}\Omega \quad (\text{use } 6.8 \text{ k}\Omega \text{ standard value})$$

Typically, $V_{CE(sat)} = 0.2 \text{ V}$, and $I_{EO} = 50 \text{ nA}$.

$$\begin{aligned}\text{Error due to } V_{CE(sat)} &= \frac{V_{CE(sat)}}{V_s} \times 100\% \\ &= \frac{0.2 \text{ V}}{2 \text{ V}} \times 100\% = 10\%\end{aligned}$$

$$\begin{aligned}\text{Error due to } I_{EO} &= \frac{(I_{EO} R_L)}{V_s} = 100\% \\ &= \frac{50 \text{ nA} \times 10 \text{ k}\Omega}{2 \text{ V}} \times 100\% \\ &= 0.025\%\end{aligned}$$

11-3 BIPOLAR TRANSISTOR SHUNT GATE


The series sampling gate is suitable for signals having a low source resistance. For signals with a very high source resistance, the series gate requirement that R_L be much larger than R_s is difficult to fulfill. In this case, a shunt sampling gate is most suitable.

In the shunt sampling gate (Figure 11-5), transistor Q_1 shorts the input to ground when it is switched into saturation. When Q_1 is *off*, current flows from the signal source to the load resistance. Therefore, the shunt sampling gate essentially is a *current switch*, whereas the series sampling gate is a *voltage switch*. The transistor offset voltage results in a load current $V_{CE(sat)}/R_L$ when the transistor is *on* [Figure 11-6(a)]. When the device is *off*, some of the signal current is lost as I_{CO} through the transistor [Figure 11-6(b)]. If the input signal becomes negative, the transistor operates in the inverted mode, as in the case of the series gate.


The load resistance for a shunt sampling gate should be selected such that $I_O R_L$ is much larger than $V_{CE(sat)}$. For transistor saturation and for minimum $V_{CE(sat)}$, I_B can be approximately equal to I_O . As in the case of the series gate, the sampling frequency should be at least several times the signal frequency. The transistor leakage current I_{CO} should be very much smaller than I_O .

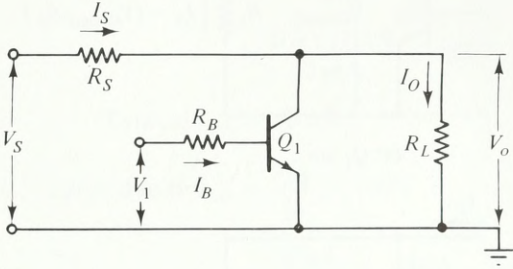EXAMPLE 11-2

Design a transistor shunt gate to sample a signal current having a peak amplitude of 2 mA. Also, calculate the output errors due to $V_{CE(sat)}$ and I_{CO} .



(a) Shunt gate circuit

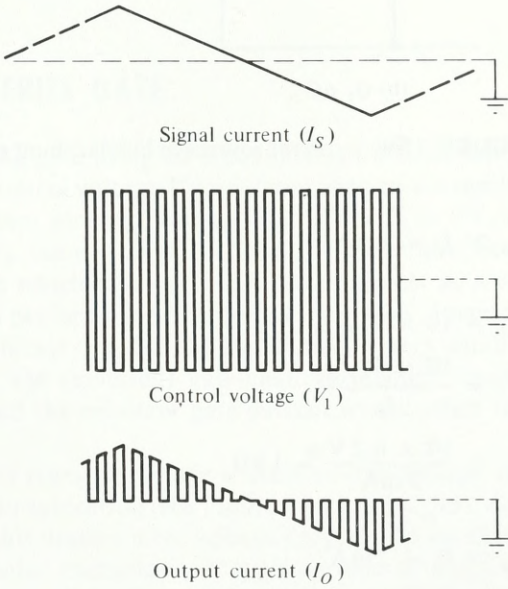

(b) Current and voltage waveforms

FIGURE 11-5. Bipolar transistor shunt gate and waveforms.

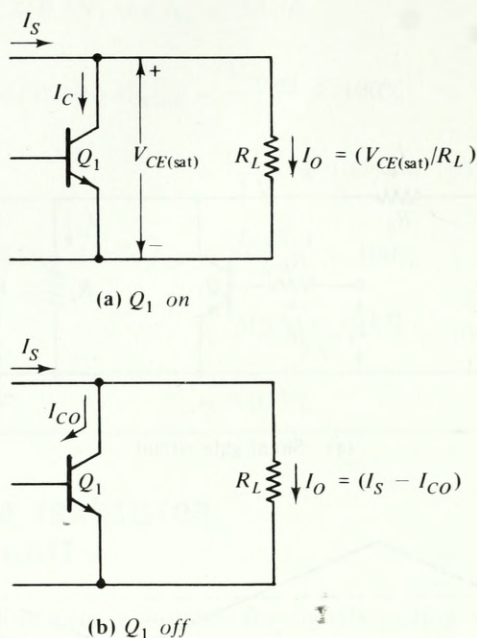


FIGURE 11-6. Error sources in bipolar shunt gate.

solution

$$I_O \simeq I_s = 2 \text{ mA}$$

Let

$$I_O R_L = 10 \times V_{CE(\text{sat})}$$

$$R_L = \frac{10 \times V_{CE(\text{sat})}}{I_O}$$

$$= \frac{10 \times 0.2 \text{ V}}{2 \text{ mA}} = 1 \text{ k}\Omega$$

Let

$$I_B \simeq I_O = 2 \text{ mA}$$

Take

$$V_1 = 4 \text{ V}$$

$$I_B = \frac{V_1 - V_{BE} - V_O}{R_B}$$

$$2 \text{ mA} = \frac{4 \text{ V} - 0.7 \text{ V} - 2 \text{ V}}{R_B}$$

$$R_B = \frac{1.3 \text{ V}}{2 \text{ mA}} = 650 \Omega \quad (\text{use } 680 \Omega \text{ standard value})$$

$$\text{Error current due to } V_{CE(\text{sat})} = \frac{V_{CE(\text{sat})}}{R_L}$$

$$\begin{aligned}\text{Error due to } V_{CE(\text{sat})} &= \frac{V_{CE(\text{sat})}/R_L}{I_O} \times 100\% \\ &= \frac{0.2\text{V}/1\text{ k}\Omega}{2\text{ mA}} \times 100\% = 10\%\end{aligned}$$

$$\text{Typical } I_{CO} = 50\text{ nA}$$

$$\begin{aligned}\text{Error due to } I_{CO} &= \frac{I_{CO}}{I_O} \times 100\% \\ &= \frac{50\text{ nA}}{2\text{ mA}} \times 100\% = 0.0025\%\end{aligned}$$

11-4 JFET SERIES GATE

A series sampling gate using an n -channel JFET is shown in Figure 11-7. Note that the control voltage V_1 goes from zero to a negative level greater than the transistor pinchoff voltage V_p . When $V_1 = 0\text{ V}$, the FET is *on*. When $-V_1 > V_p$, the device is *off*. The JFET can also be operated in inverted mode, in which case the drain terminal acts as a source, and the source terminal performs the function of the drain. Inverted operation of a JFET is satisfactory only if the signal level is very small. If the signal becomes large, the (inverted) gate-channel junction could become forward-biased, and the resultant gate current would affect the drain-source voltage.

Field effect transistors have a drain-source voltage drop of $I_D R_{D(\text{on})}$ when biased into saturation [see Figure 11-7(b) and Sec. 4-5]. With small drain current, this drain-source voltage drop can be much smaller than the $V_{CE(\text{sat})}$ of a bipolar transistor. A typical value of $R_{D(\text{on})}$ for a switching FET is $30\ \Omega$, although devices with $R_{D(\text{on})}$ as low as $5\ \Omega$ are available. For a load current of $200\ \mu\text{A}$, as in Example 11-1, the typical FET offset voltage is $(200\ \mu\text{A} \times 30\ \Omega) = 6\text{ mV}$. This is only 0.3% of a 2 V signal, compared to the 10% loss due to the $V_{CE(\text{sat})}$ of the bipolar transistor. When the JFET is biased *off* there is a gate-source leakage current I_{GSS} , which corresponds to I_{EO} in a bipolar transistor [Figure 11-7(c)]. Thus, I_{GSS} constitutes an unwanted load current. For a switching JFET I_{GSS} can be 0.2 nA or less, which is superior to the typical 50 nA of a bipolar device. The performance specification for some switching JFETs is given below:

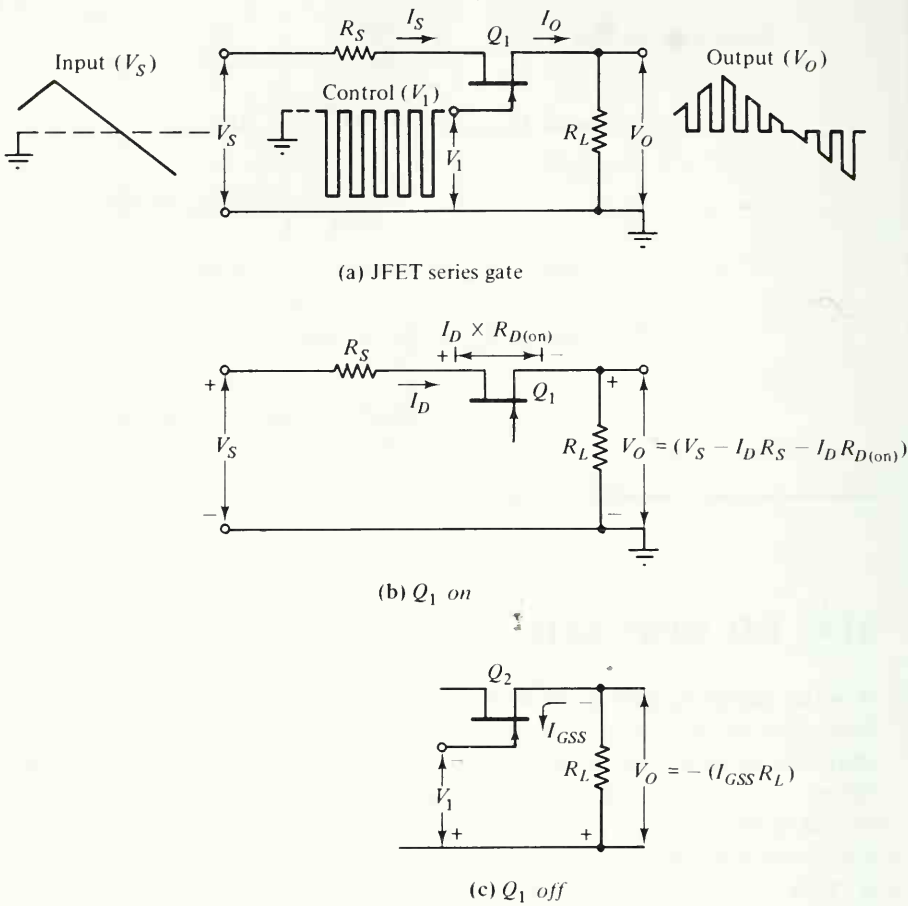


FIGURE 11-7. Circuit, waveforms, and error sources for JFET series gate.

	Maximum pinchoff voltage $V_{P(\text{max})}$	Drain-source on resistance $R_{D(\text{on})}$	Gate-source leakage I_{GSS}	Drain-source leakage $I_{D(\text{off})}$
2N4391	10 V	30Ω	0.1 nA	0.1 nA
2N5433	9 V	7Ω	0.2 nA	0.2 nA

Note that the data sheet for the 2N4391 is in Appendix 1-10.

EXAMPLE 11-3

A low-frequency signal with a peak amplitude of 1 V is applied to a voltage follower with a very low output resistance. The signal is to be sam-

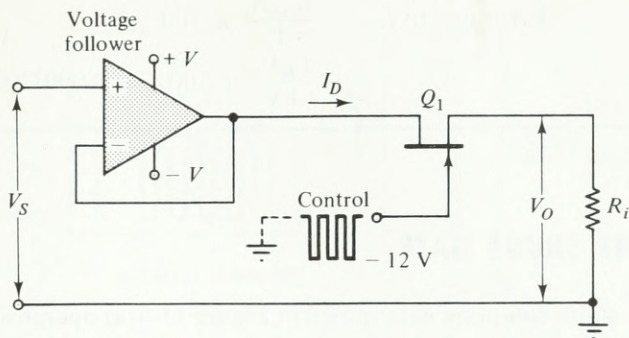


FIGURE 11-8. FET series gate.

pled at the output of the voltage follower and fed to a circuit with $R_i = 10 \text{ k}\Omega$. Design a suitable FET gate circuit and estimate the output errors.

solution

The circuit is as shown in Figure 11-8. For the 2N4391 FET, the control voltage $V_1 > (V_{P(\text{max})} = 10 \text{ V})$. Let

$$V_1 \simeq -12 \text{ V}$$

With Q_1 on,

$$\begin{aligned} I_D &= \frac{V_s}{R_s + R_i} \\ &\simeq \frac{1 \text{ V}}{0 \Omega + 10 \text{ k}\Omega} = 0.1 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_{DS(\text{on})} &= I_D R_{D(\text{on})} \\ &= 0.1 \text{ mA} \times 30 \Omega = 3 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{Error due to } V_{DS(\text{on})} &= \frac{V_{DS(\text{on})}}{V_s} \times 100\% \\ &= \frac{3 \text{ mV}}{1 \text{ V}} \times 100\% \\ &= 0.3\% \end{aligned}$$

With Q_1 off,

$$\begin{aligned} I_O &= I_{GSS} = 0.1 \text{ nA} \\ V_O &= I_{GSS} R_i \\ &= 0.1 \text{ nA} \times 10 \text{ k}\Omega = 1 \mu\text{V} \end{aligned}$$

$$\begin{aligned}\text{Error due to } I_{GSS} &= \frac{I_{GSS} R_i}{V_s} \times 100\% \\ &= \frac{1 \mu\text{V}}{1 \text{ V}} \times 100\% = 0.0001\%\end{aligned}$$

11-5 JFET SHUNT GATE

The JFET shunt sampling gate shown in Figure 11-9(a) operates in a similar way to the bipolar shunt circuit. Like the bipolar shunt gate, the JFET shunt gate is essentially a current switch. When the FET is *on*, the output of the gate is shorted to ground. The output voltage at this time actually is $I_D R_{D(\text{on})}$, and this produces an unwanted output current ($I_D R_{D(\text{on})}/R_L$) [see Figure 11-9(b)]. However, for the shunt FET gate, the unwanted output is much less than the minimum possible with a bipolar circuit. When the transistor is *off*, the drain-source leakage current $I_{D(\text{off})}$ diverts signal current from the load [see Figure 11-9(c)]. Again, this usually is less than the corresponding bipolar leakage current.

EXAMPLE 11-4

A low-frequency current with an amplitude of 0.1 mA is to be sampled and fed to the input of a circuit with $R_i = 10 \text{ k}\Omega$. Design a suitable FET shunt gate, and estimate the output voltage errors due to the transistor.

solution

Use a 2N4391 FET. Let the control voltage be -12 V as in Example 11-3. When Q_1 is *on*,

$$\begin{aligned}V_O &= I_s R_{D(\text{on})} \\ &= 0.1 \text{ mA} \times 30 \Omega = 3 \text{ mV}\end{aligned}$$

and when Q_1 is *off*,

$$\begin{aligned}V_O &= I_s R_i \\ &= 0.1 \text{ mA} \times 10 \text{ k}\Omega = 1 \text{ V}\end{aligned}$$

The error when Q_1 is *on* is given by

$$\frac{3 \text{ mV} \times 100}{1 \text{ V}} = 0.3\%$$

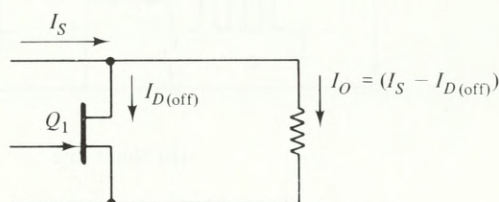
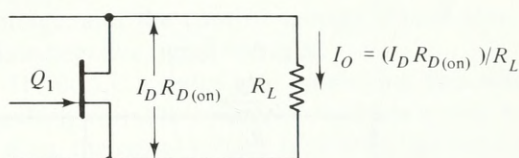
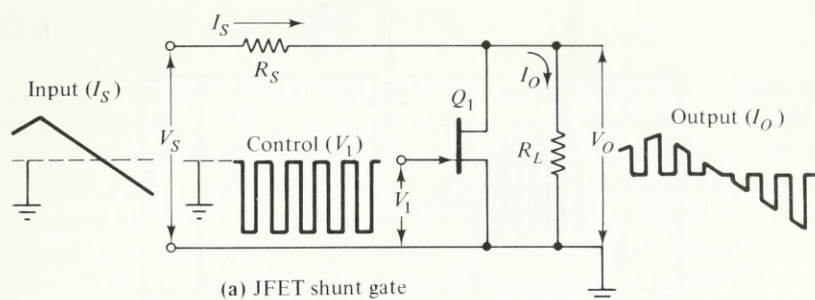


FIGURE 11-9. Circuit, waveforms, and error sources for JFET shunt gate.


When Q_1 is off,

$$I_D = I_{D(\text{off})} = 0.1 \text{ nA}$$


$$I_O = I_S - I_{D(\text{off})}$$

$$= 0.1 \text{ mA} - 0.1 \text{ nA}$$

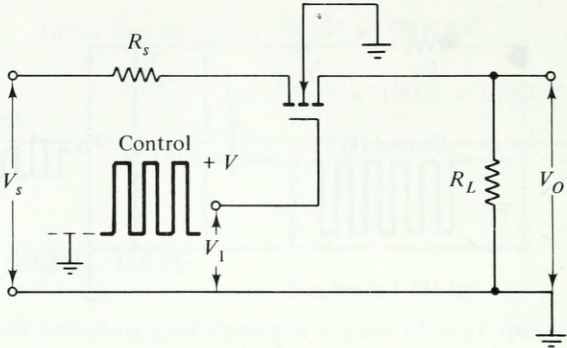
$$\text{Error} = \frac{0.1 \text{ nA}}{0.1 \text{ mA}} \times 100 = 0.0001\%$$



(a) Series gate

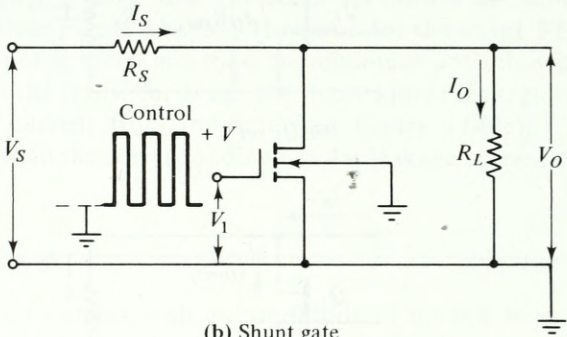

(b) Shunt gate

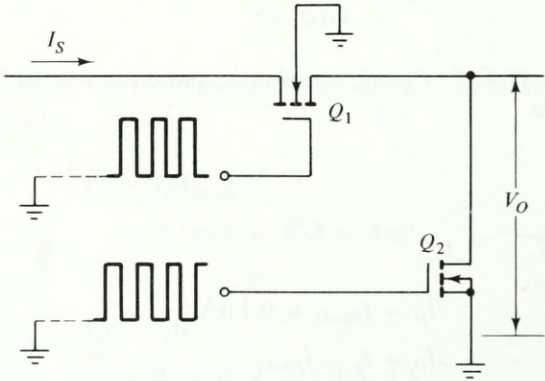

(c) Series – shunt gate

FIGURE 11-10. MOSFET sampling gate.

11-6 MOSFET SAMPLING GATES

MOSFETs are almost ideal devices for use as sampling gates. They have the same low $R_{D(\text{on})}$ characteristic as JFETs, and the *enhancement mode* devices are normally *off* while the gate is at the same potential as the substrate. Figure 11-10(a) shows the circuit of a series sampling gate using an *n*-channel MOSFET. With the substrate at ground potential, the control voltage should go from 0 V to a positive voltage to switch the gate from *off* to *on*. When the input signal can be either negative or positive, the substrate should be taken to a negative bias voltage and the control voltage should start at the bias level. A MOSFET shunt sampling gate is shown in Figure 11-10(b). Here, again, the substrate terminal of the FET can be taken to a negative bias voltage, and the control voltage should start at the bias level to accommodate negative signal voltages.

The circuit in Figure 11-10(c) is a series gate employing two MOSFETs. This circuit is particularly suitable where the load has a very high input resistance. When Q_1 is *on*, the signal voltage is switched to the load, and Q_2 is *off*. When Q_1 is *off*, the load voltage should be zero. With Q_2 *on* at this time, the output voltage is

$$(I_{D(\text{off})} \text{ for } Q_1) \times (R_{D(\text{on})} \text{ for } Q_2)$$

When typical values of 0.1 nA and 30 Ω are used, the unwanted output voltage is only 3 nV.

REVIEW QUESTIONS AND PROBLEMS

- 11-1 Sketch the circuit of a diode sampling gate. Show the voltage waveforms, explain the operation of the circuit, and discuss the error sources.
- 11-2 Repeat Problem 11-1 for a bipolar transistor series sampling gate.
- 11-3 Explain how a bipolar transistor series sampling gate functions when the input signal is alternately positive and negative with respect to ground.
- 11-4 Design a bipolar transistor series gate to sample a signal with a peak amplitude of 3 V and a source resistance of 200 Ω . Calculate the output errors due to $V_{CE(\text{sat})}$ and I_{EO} .
- 11-5 Repeat Problem 11-1 for a bipolar transistor shunt sampling gate.
- 11-6 Design a bipolar transistor shunt gate to sample a signal current with a peak amplitude of 1 mA. Calculate the output errors due to $V_{CE(\text{sat})}$ and I_{CO} .

- 11-7** Repeat Problem 11-1 for a JFET series sampling gate. State the precautions necessary for inverted operation of the JFET.
- 11-8** A signal of 1.5 V with a very low source resistance is to be sampled and passed to a circuit with $R_i = 20\text{ k}\Omega$. Design a suitable JFET gate circuit, and estimate the output errors.
- 11-9** Repeat Problem 11-1 for a JFET shunt sampling gate.
- 11-10** A $200\text{ }\mu\text{A}$ signal current is to be sampled and passed to a circuit with $R_i = 15\text{ k}\Omega$. Design a suitable JFET gate, and estimate the output errors.
- 11-11** Sketch circuits for MOSFET shunt, series, and series-shunt sampling gates. Show waveforms and explain the operation of the circuits.
- 11-12** Compare the performances of bipolar transistors, JFETs, and MOSFETs as sampling gates.

Chapter 12

Digital Counting

INTRODUCTION

Because the bistable multivibrator, or flip-flop, has two stable states, it can be used to count up to two. A cascade of four flip-flops can count up to sixteen. The SCALE-OF-16 COUNTER can be modified to produce a decade counter, which has an output in the form of a BINARY NUMBER. For counting in decimal form, a binary number must be converted to decimal. A further conversion stage usually is necessary to drive a numerical display. Decade counters and their numerical displays can be cascaded to construct systems for counting to hundreds, thousands, tens of thousands, etc.

12-1 FLIP-FLOPS IN CASCADE

The schematic diagram of four flip-flops (FF) connected in cascade is shown in Figure 12-1. Each flip-flop is a collector-coupled circuit, and

each has symmetrical collector triggering. Negative-going input pulses are applied to FF1 via coupling capacitor C_1 . Each time an input pulse is applied, FF1 will change state. The triggering circuit for FF2 is coupled via capacitor C_2 to transistor Q_2 in FF1. When Q_2 switches *off*, its collector voltage rises, applying a positive voltage step to C_2 . Since a negative-going voltage is required to trigger these flip-flops (see Chapter 9), FF2 is not affected by the positive-going voltage. When Q_2 switches *on*, its collector voltage drops, thus applying a negative voltage step to FF2 via C_2 . This negative voltage change triggers FF2. In a similar way, FF3 is triggered from FF2, and FF4 is triggered from FF3. It is seen that each flip-flop is triggered from each preceding stage.

The four-stage cascade in Figure 12-1 can have a number of combinations of flip-flop states. In Figure 12-2, the flip-flops are shown in block form with the arrowheads indicating that each is triggered from the previous stage. The state of each of the four flip-flops is best indicated by using the *binary* number system, where 0 represents a voltage at or near ground level and 1 represents a positive voltage level (see Figure 12-2). When a transistor is *on*, its collector voltage is low and is represented by 0. An *off* transistor, on the other hand, has a high collector voltage and is designated 1. In the decimal system, counting goes from 0 to 9, then the next count is indicated by 0 in the first column and 1 in the next leftward column. In the binary system, the count in all columns can go only from 0 to 1. Thus the count for 1 in both binary and decimal systems is 1; in the binary system, the count for decimal 2 is indicated by 0 in the first column and 1 in the next leftward column. Thus, *binary 10* is equivalent to *decimal 2*. The next count in a binary system is 11 and is followed by 100. The table of 0's and 1's showing the state of the flip-flops at each count is known as a *truth table*.

Suppose, before any pulses are applied, the state of the flip-flops is such that all even-numbered, (*i.e.*, left-hand) transistors are *on*. Reading only the even-numbered transistors (*i.e.*, in Figure 12-2) from left to right, the binary count is 0000. At this time the decimal count is 0 and the binary count is 0.

The first trigger pulse causes Q_1 to switch *on* and Q_2 to switch *off*. Thus, Q_2 reads as 1 (positive), and the binary count and decimal count are both 1. The second input trigger pulse causes FF1 to change state again, so that Q_1 goes *off* and Q_2 switches *on*. When Q_2 switches *on*, a negative step is applied to FF2 triggering Q_3 *on* and Q_4 *off*. Now the binary count is 10, and the decimal count is 2. The third input pulse triggers Q_1 *on* and Q_2 *off* once again. This produces a positive output from FF1, which does not affect FF2. At this time, the binary count is 11, for a decimal count of 3. The fourth trigger pulse applied to the input, switches Q_1 *off* and Q_2 *on*. Q_2 coming *on* produces a negative step which causes Q_3 to

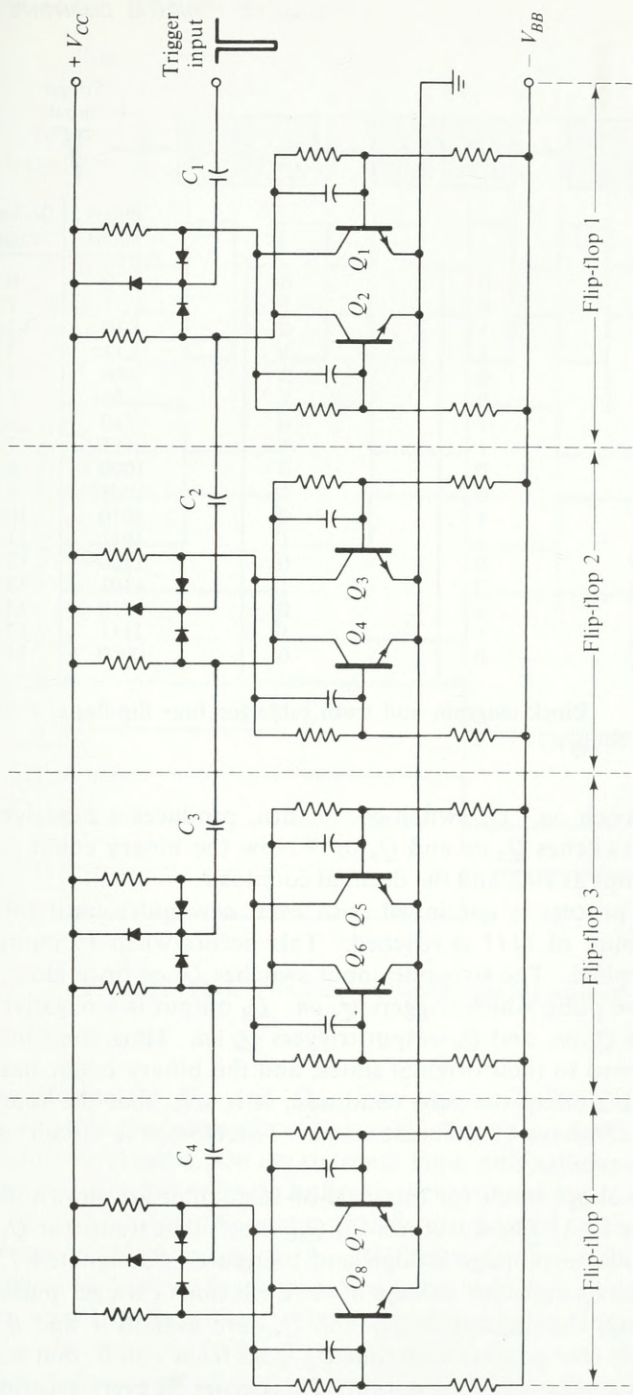


FIGURE 12-1. Cascade of four flip-flops.

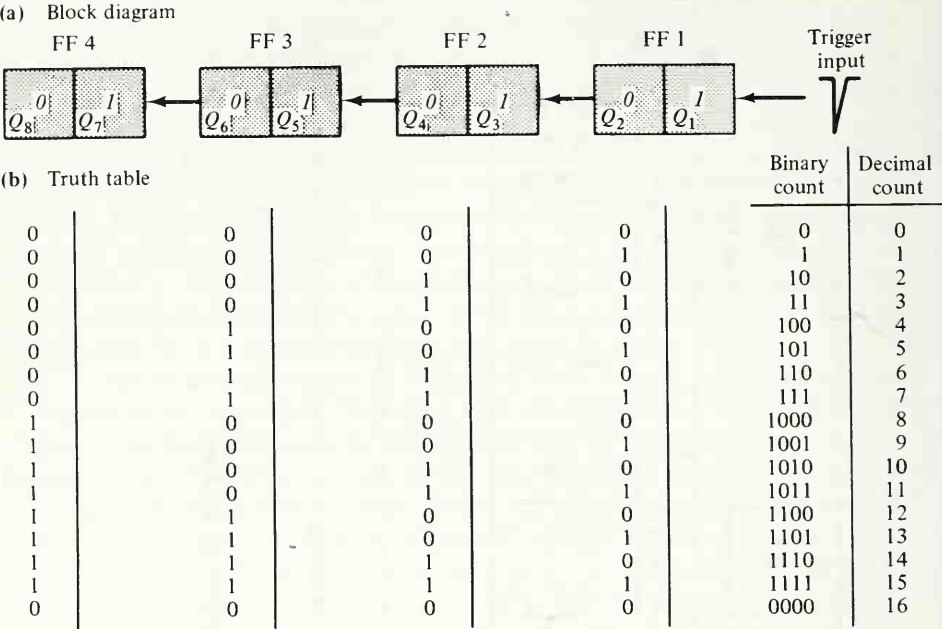


FIGURE 12-2. Block diagram and truth table for four flip-flops as a scale-of-16 counter.

go *off* and Q_4 to switch *on*. Q_4 switch-*on*, in turn, produces a negative voltage step which switches Q_5 *on* and Q_6 *off*. Now the binary count is read from the flip-flops as 100, and the decimal count is 4.

The counting process is continued with each new pulse until the maximum binary count of 1111 is reached. This occurs when 15 input pulses have been applied. The sixteenth input switches Q_2 *on* once more, producing a negative pulse which triggers Q_4 *on*. Q_4 output is a negative pulse which triggers Q_6 *on*, and Q_6 output triggers Q_8 *on*. Thus, the four flip-flop have returned to their original states, and the binary count has returned to 0000. Including the zero condition, it is seen that the four flip-flop in cascade can have 16 different states. Therefore, the circuit is termed a *scale-of-16 counter*.

The collector voltage levels for the scale-of-16 counter are shown as waveforms in Figure 12-3. The waveform for Q_{1C} shows that transistor Q_1 is initially *off*; its collector voltage is high and therefore is designated 1. Q_2 is initially *on*, with its collector voltage at 0. Each time a trigger pulse is applied, Q_1 and Q_2 change state. Q_{3C} and Q_{4C} are initially 1 and 0, respectively, and they change state each time Q_{2C} goes from 1 to 0, that is, when FF1 produces a negative-going output. This occurs on every second input pulse. Q_{5C} starts as 1 and Q_{6C} as 0, and they change state only when Q_{4C} goes from 1 to 0, which is at every fourth input pulse. Finally, the

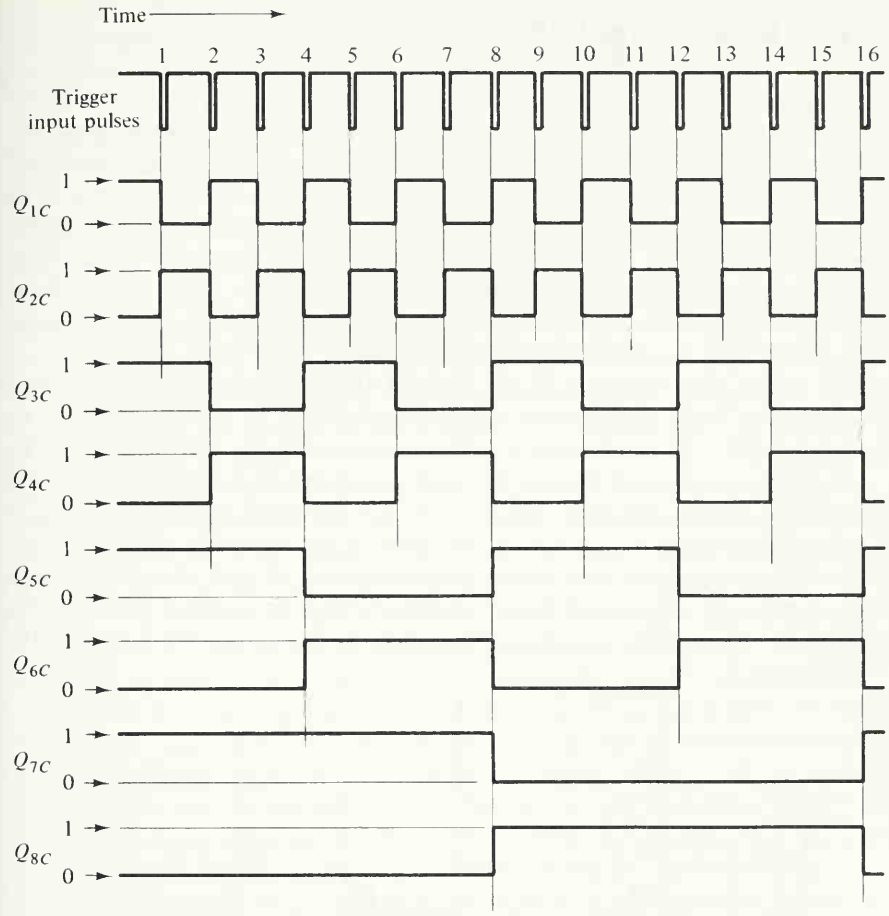


FIGURE 12-3. Collector waveforms for scale-of-16 counter.

waveforms for Q_{7C} and Q_{8C} show that initially Q_{7C} is 1 and Q_{8C} is 0, and that they change state when Q_{6C} becomes negative, that is, at every eighth input pulse. On the sixteenth input pulse all flip-flops change state, and the collector voltages return to their original levels.

The scale-of-16 counter actually can be used to divide the input pulse frequency by a factor of 16. Reference to the collector waveforms in Figure 12-3 shows that a negative-going voltage is produced at Q_8 collector after 16 input pulses. Another negative-going step will occur again at Q_{8C} after another 16 input pulses. Hence, the name *divide-by-16 counter* is sometimes applied to this circuit. An output taken from FF3 will produce a pulse frequency which is the input PRF divided by 8. Similarly, the output of FF2 divides the input by 4.

12-2 DECADE COUNTER

The scale-of-16 counter has many applications. However, there are also a great many instances in which a *scale-of-10*, or *decade*, counter is required. A decade counter also requires the use of a cascade of four flip-flops. Three flip-flops would count only up to seven, and then on the eighth pulse the count would revert to the 000 starting condition. This can be seen in Figure 12-2. Therefore, to produce a decade counter, a scale-of-16 must be modified to eliminate six of the sixteen states. This can be done by eliminating either the first six states or the last six states, or, perhaps, by eliminating some of the intermediate states.

When the first six states of a scale-of-16 counter are to be eliminated, the counter must always have an initial condition of 0110 (decimal 6 in Figure 12-2). To obtain this condition, transistors Q_4 and Q_6 must be in the *off* state. Q_4 and Q_6 can be reset to *off* by the asymmetrical base triggering circuit shown in Figure 12-4. (Asymmetrical base triggering is discussed in Sec. 9-5.) When Q_8 switches *on*, its collector voltage drops, providing a negative step which forward-biases D_1 and D_3 , and triggers Q_6 and $Q_4 *off*. Figures 12-2 and 12-3 show that Q_8 switches *on* when the sixteenth input pulse is applied. Therefore, at the end of the count of 16,$

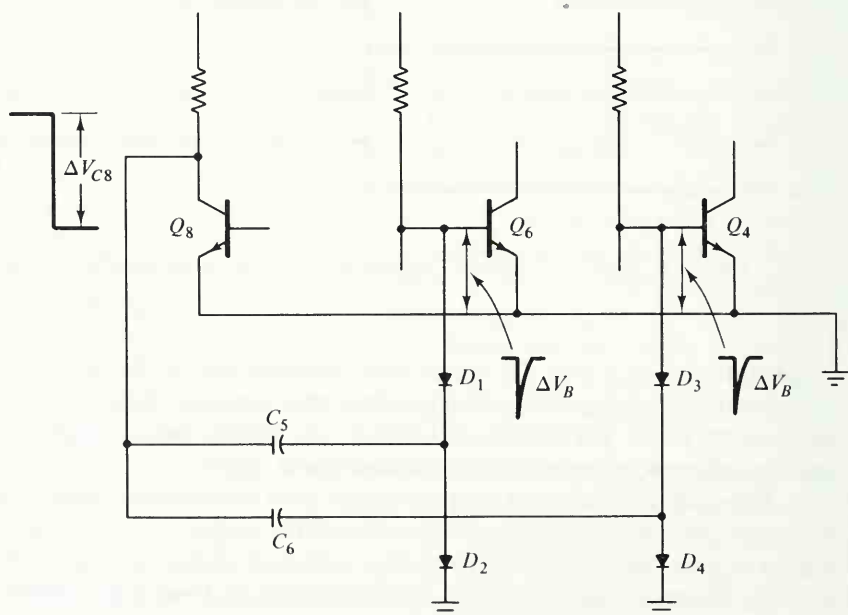


FIGURE 12-4. Resetting Q_4 and Q_6 from Q_8 .


the flip-flops are set to 0110. The block diagram, truth table, and collector waveforms for the decade counter are shown in Figure 12-5.

In Figure 12-5(a), the line from FF4 to FF2 and FF3 indicates that these flip-flops are reset by the output from FF4. The initial state of the four flip-flops (*i.e.*, at decimal 0) is read in Figure 12-5(b) as 0110. The first input pulse now changes the state of FF1 causing Q_2 to switch *off*. Thus the collector of Q_2 becomes 1 (*i.e.*, high positive), and the condition of the counter is 0111. This also is illustrated by the collector waveforms in Figure 12-5(c). The second input pulse (decimal 2) again changes the state of FF1, this time causing Q_2 to switch *on*. The output from Q_2 is a negative step which triggers FF2 switching Q_4 *on*. This, in turn, produces a negative step which triggers FF3 from Q_6 *off* to Q_6 *on*. The output from FF3 triggers FF4. Counting continues in this way, exactly as explained for the scale-of-16 counter, until the tenth pulse. The ninth pulse sets the counter at 1111, and the tenth pulse changes it to 0000. However, as Q_8 switches *on*, it provides the negative output step which resets FF2 and FF3. The flip-flops have then returned to their initial conditions of 0110, and it is seen that the circuit has only ten different states.

The waveforms in Figure 12-5(c) indicate that a negative output step is generated at Q_{8C} each time the tenth input pulse is applied. Thus, the decade counter can be employed as a *divide-by-10 counter*. Before counting begins, a decade counter (or scale-of-16 counter) must have its flip-flops set in the correct starting condition. This can be accomplished by the manual resetting arrangement shown in Figure 12-6(a). When switch S_1 is closed, the diodes are forward-biased and the transistor bases are pulled below ground level. Thus, transistors Q_1 , Q_4 , Q_6 , and Q_7 are switched *off* giving the desired initial condition for the decade counter.

The flip-flops can also be reset automatically in their initial condition by the CR circuit addition in Figure 12-6(b). When the supply voltages are first switched *on*, the capacitor behaves as a short-circuit. Therefore, the diode cathode voltages are at $-V$, and the transistors are biased *off*. After a brief time period, C_1 charges to $+V$ via resistor R . Now the diodes are all reverse-biased, and the reset circuit has no further effect.

Figure 12-7 shows a further modification of the circuit for resetting the flip-flops. Diode D_5 serves to isolate R and C from the rest of the reset circuit. When the cathodes of D_1 to D_4 are pulled down, D_5 is reverse-biased. D_6 and D_7 , together with coupling capacitor C_2 , form a triggering circuit. A negative-going voltage step applied to C_2 generates a negative pulse at the cathode of D_6 . This forward-biases D_6 , D_1 , D_2 , D_3 , and D_4 , causing the flip-flop to reset. Thus, as well as being reset to its starting condition when the supply is switched *on*, the counter can be reset to *zero* at any time by the application of a negative voltage step.

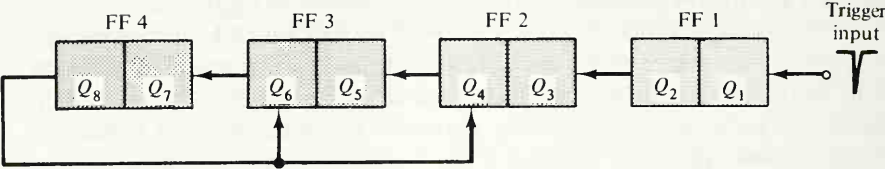

Q_{8C}	Q_{6C}	Q_{4C}	Q_{2C}	Decimal count
0	1	1	0	0
0	1	1	1	1
1	0	0	0	2
1	0	0	1	3
1	0	1	0	4
1	0	1	1	5
1	1	0	0	6
1	1	0	1	7
1	1	1	0	8
1	1	1	1	9
Reset 0	0	0	0	10
0	1	1	0	0 =

(b) Truth table showing state of transistor collector

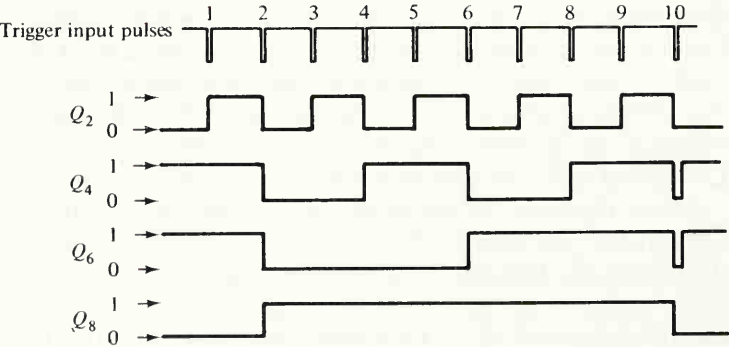


FIGURE 12-5. Block diagram and truth table for four flip-flops as decade counter.

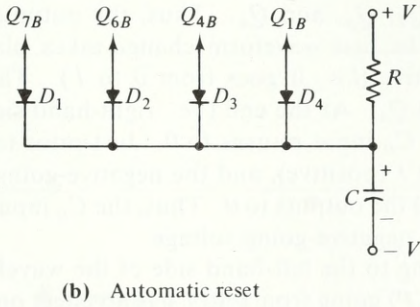
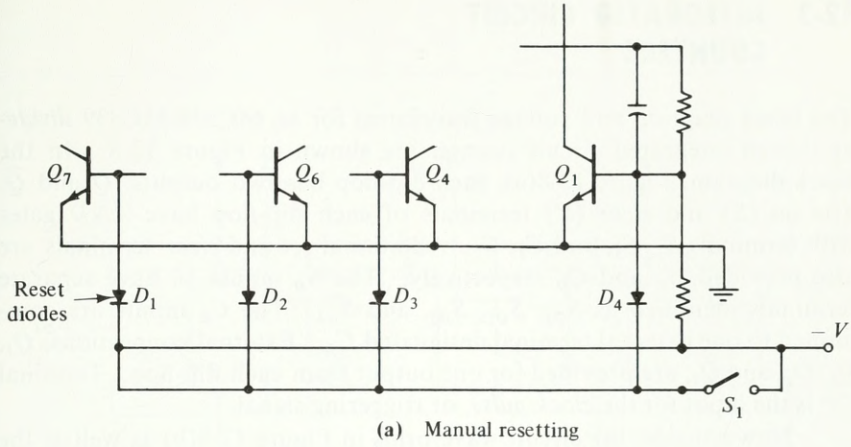


FIGURE 12-6. Resetting a decade counter to zero.

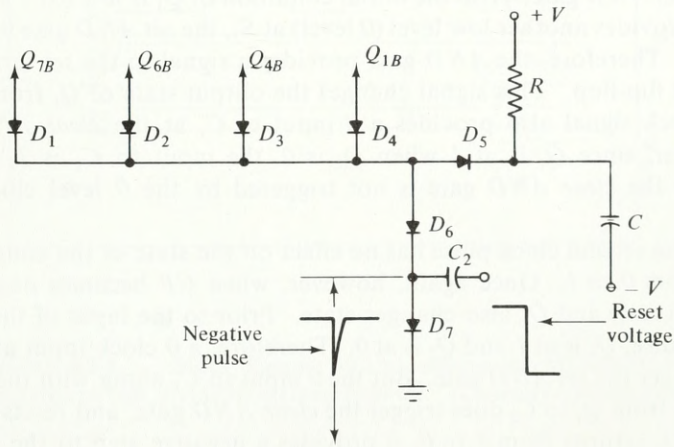


FIGURE 12-7. Resetting to zero by pulse.

12-3 INTEGRATED CIRCUIT COUNTERS

The block diagram and voltage waveforms for an MC939, MC839 *divide-by-sixteen* integrated circuit counter are shown in Figure 12-8. In the block diagram, Figure 12-8(a), each flip-flop has two outputs, Q and \bar{Q} . The *set* (S) and *clear* (C) terminals of each flip-flop have *AND* gates with terminals S_1 , S_2 , and C_1 , C_2 . Additional *set* and *clear* terminals are also provided, S_D and C_D respectively. The S_D inputs all have separate terminals identified as S_{D1} , S_{D2} , S_{D3} , and S_{D4} . The C_D inputs are commoned to one external terminal designated C_D . External connections, Q_1 , Q_2 , Q_3 , and Q_4 , are provided for one output from each flip-flop. Terminal CP is the input for the *clock pulse*, or triggering signal.

Now consider the circuit waveforms in Figure 12-8(b) as well as the block diagram. The waveforms show that the starting voltages are low at outputs Q_1 , Q_2 , Q_3 , and Q_4 . Thus, the outputs can all be represented as logic 0. The first waveform change takes place when the C_D input becomes positive (*i.e.*, it goes from 0 to 1). This has no effect on the outputs Q_1 to Q_4 . At the end (*i.e.*, right-hand side) of the waveforms illustrated, the C_D input returns to 0. Just prior to this, the outputs Q_1 to Q_4 were all at 1 (positive), and the negative-going C_D input has the effect of resetting all the outputs to 0. Thus, the C_D input is a *clear* or *reset* input triggered by a negative-going voltage.

Returning to the left-hand side of the waveform diagram, the clock pulse input (CP) going from 0 to 1 has no effect on the state of the counter outputs. When CP becomes negative (1 to 0), Q_1 output goes from 0 to 1. To see why this occurs, note that Q_1 is connected back to S_1 at the input of the *set AND* gate. Also the initial condition of Q_1 is low (0). When the pulse provides another low level (0 level) at S_2 , the *set AND* gate has two 0 inputs. Therefore, the *AND* gate provides a signal to the *set* terminal of the first flip-flop. This signal changes the output state of Q_1 from 0 to 1. The clock signal also provides a 0 input to C_1 at the *clear AND* gate. However, since \bar{Q}_1 is at 1 when Q_1 is 0, the input to C_2 is 1. Consequently the *clear AND* gate is not triggered by the 0 level clock pulse input.

The second clock pulse has no effect on the state of the counter as it goes from 0 to 1. Once again, however, when CP becomes negative Q_1 changes state and Q_2 also changes state. Prior to the input of the second clock pulse, Q_1 is at 1 and \bar{Q}_2 is at 0. Therefore, a 0 clock input at S_2 cannot trigger the *set AND* gate. But the 0 input to C_1 along with the 0 input applied from \bar{Q}_1 to C_2 does trigger the *clear AND* gate, and resets Q_1 to 0. When Q_1 returns from 1 to 0, it provides a negative step to the S_2 input terminal of the second flip-flop. Since the input to S_1 at this time is also 0 (from Q_2), the second flip-flop is triggered, and Q_2 goes from 0 to 1.

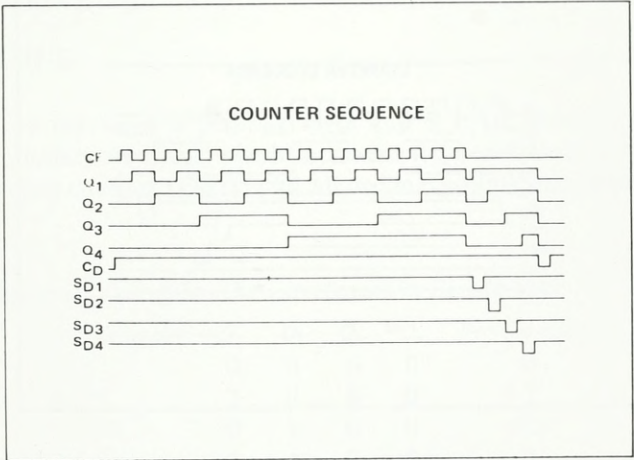
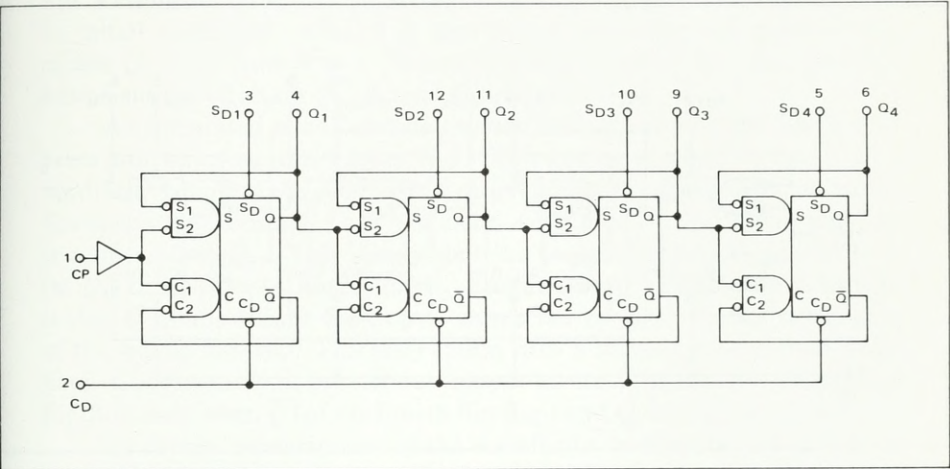


FIGURE 12-8. Block diagram and waveforms for MC939/MC839 integrated circuit divide-by-sixteen counter. (Courtesy of Motorola, Inc.)

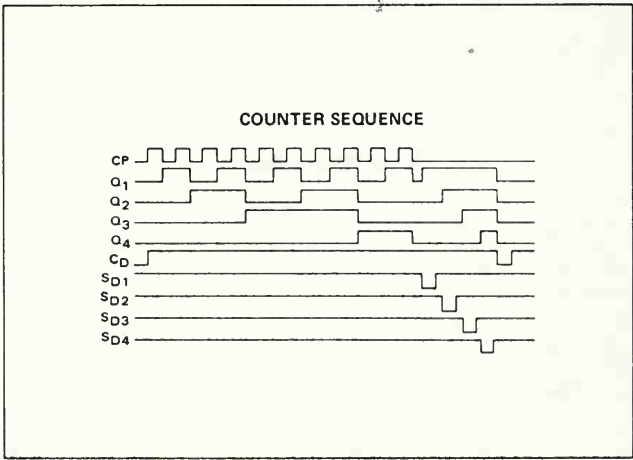
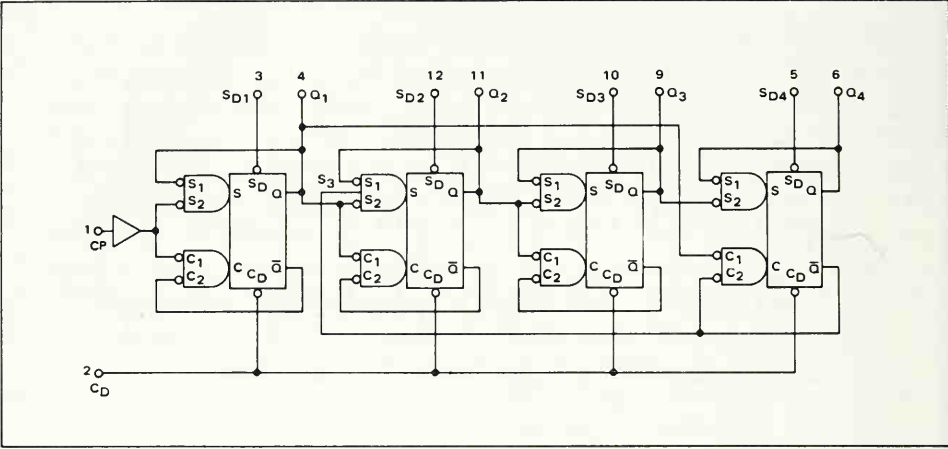


FIGURE 12-9. Block diagram and waveforms for MC938/MC838 integrated circuit decade counter. (Courtesy of Motorola, Inc.)

The changing state of the counter at each negative-going edge of the clock pulse can be examined by continuing the process discussed above. The waveforms show that the sixteenth clock pulse returns the counter to its initial condition. Also, it is seen that a negative-going pulse at S_{D1} causes Q_1 to go from 0 to 1. Negative-going pulses at S_{D2} , S_{D3} , and S_{D4} have a similar effect on Q_2 , Q_3 , and Q_4 , respectively.

An integrated circuit *decade counter* is illustrated by the block diagram and waveforms of Figure 12-9. This can be thought of simply as a modified version of the *divide-by-16 counter* considered above. One modification is that terminal C_1 at the *clear AND* gate of the fourth flip-flop is connected to Q_1 . This means that the fourth flip-flop is cleared to 0 (at Q_4) only when Q_1 and \overline{Q} (at C_2) are both at 0. Another modification is that \overline{Q} of the fourth flip-flop is connected to S_3 at the *set AND* gate of the second flip-flop. This (*set*) gate is now a three-input terminal *AND* gate. Consequently, it provides an output to the S terminal of the second flip-flop only when \overline{Q} (of the fourth flip-flop) and Q_1 and Q_2 are all at 0.

By careful consideration of the waveforms in Figures 12-8 and 12-9, it is found that the last six states of the divide-by-16 counter are eliminated in the decade counter.

Each of the two counters analyzed above operates from a 5 V supply, and dissipates 150 mW (typical). The maximum counting frequency for each is 30 MHz.

EXAMPLE 12-1 _____

Using 1 to represent a positive level and 0 to represent ground level, write the binary numbers which represent the conditions of Q_1 to Q_4 for the I_C decade counter. Do this for all decimal counts from 0 to 10.

solution

The solution is taken from the waveforms in Figure 12-9:


Terminals \rightarrow	Q_1	Q_2	Q_3	Q_4	Decimal count
	0	0	0	0	0
	1	0	0	0	1
	0	1	0	0	2
	1	1	0	0	3
	0	0	1	0	4
	1	0	1	0	5
	0	1	1	0	6
	1	1	1	0	7
	0	0	0	1	8
	1	0	0	1	9
	0	0	0	0	10

12-4 DIGITAL DISPLAYS OR READOUTS


12-4.1 Light Emitting Diode Display

Charge carrier recombination occurs at a *pn*-junction as *electrons* cross from the *n*-side and recombine with *holes* on the *p*-side. When recombination takes place, the charge carriers give up energy in the form of heat and light. If the semiconductor material is translucent the light is emitted, and the junction is a light source, that is, a *light emitting diode* (LED).


Figure 12-10(a) shows a cross-sectional view of a typical LED. Charge carrier recombinations takes place in the *p*-type material; there-

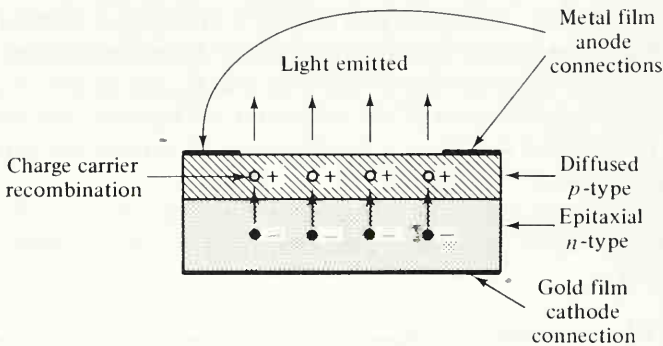

(a) LED cross-section

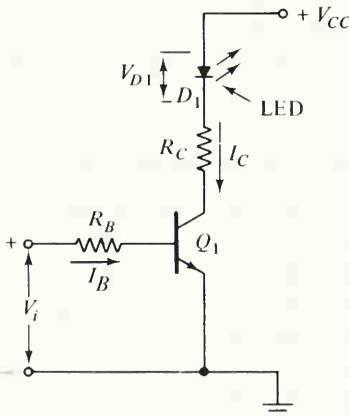

 (b) LED controlled by a transistor switch



(c) LED numerical display

FIGURE 12-10. Light emitting diode (LED) cross-section, control circuit, and seven-segment numerical display.

fore, the p -region becomes the surface of the device. For maximum light emission, a metal film anode is deposited around the edge of the p -type material, or sometimes in a comb-shaped pattern at the center of the surface. The cathode connection for the device usually is a gold film at the bottom of the n -type region; this helps reflect the light to the surface. Semiconductor material used for LED manufacture is *gallium arsenide phosphide* (Gs AsP) which emits either red or yellow light, or *gallium arsenide* (Ga As) for green or red light emission.

The LED circuit symbol is shown in Figure 12-10(b). Figure 12-10(c) illustrates the arrangement of a seven-segment LED numerical display. Each segment has several LEDs connected in series, and a single LED may be used as a decimal point. Passing a current through the appropriate segments allows any numeral from 0 to 9 to be displayed. The typical voltage drop across a forward-biased LED is 1.2 V, and typical forward current for reasonable brightness is about 20 mA. This relatively large current requirement is a major disadvantage of LED displays. Some advantages of LEDs over other type of displays are the ability to operate from a low voltage dc supply, ruggedness, rapid switching ability, and small physical size. The data sheet for a typical 7-segment LED display is shown in Appendix 1-17.

The simple transistor switch shown in Figure 12-10(b) is a suitable *on/off* control for LEDs. Q_1 is driven into saturation by input current I_B . Resistor R_C limits the current through the devices.

EXAMPLE 12-2

The LED shown in Figure 12-10(b) is to have a maximum forward current of 20 mA. The diode has a forward voltage drop of 1.2 V, and transistor Q_1 has $h_{FE(\min)} = 100$. Using $V_{CC} = 5$ V and $V_i = 5$ V, determine suitable values for R_C and R_B .

solution

$$V_{CC} = V_{D1} + I_C R_C + V_{CE(\text{sat})}$$

$$R_C = \frac{V_{CC} - V_{D1} - V_{CE(\text{sat})}}{I_C}$$

$$= \frac{5 \text{ V} - 1.2 \text{ V} - 0.2 \text{ V}}{20 \text{ mA}}$$

$$= 180\Omega \quad (\text{standard value})$$

$$I_B = \frac{I_C}{h_{FE(\min)}}$$

$$= \frac{20 \text{ mA}}{100} = 200 \mu\text{A}$$

$$V_i = I_B R_B + V_{BE}$$

$$R_B = \frac{V_i - V_{BE}}{I_B}$$


$$= \frac{5 \text{ V} - 0.7 \text{ V}}{200 \mu\text{A}} = 21.5 \text{ k}\Omega \quad (\text{use } 18 \text{ k}\Omega \text{ standard value})$$

12-4.2 Liquid Crystal Displays


Liquid crystal cell displays (LCD) usually are arranged in the same seven-segment numerical format as the LED display. There are two types of liquid crystal display, the *dynamic scattering type* and the *field effect type*. The construction of a dynamic scattering type liquid crystal cell is illustrated in Figure 12-11(a). The liquid crystal material may be one of several organic compounds which exhibit the optical properties of a crystal though they remain in liquid form. Liquid crystal is layered between glass sheets with transparent electrodes deposited on the inside faces. When a potential is applied across the cell, charge carriers flowing through the liquid disrupt the molecular alignment and produce turbulence. When not activated, the liquid crystal is transparent. When activated, the molecular turbulence causes light to be scattered in all directions, so that the cell appears quite bright. The phenomenon is termed *dynamic scattering*.

The construction of a *field effect* liquid crystal display is similar to that of the dynamic scattering type, with the exception that two thin polarizing optical filters are placed at the inside surface of each glass sheet. The liquid crystal material in the field effect cell is also a different type from that employed in the dynamic scattering cell. Known as *twisted nematic*, this liquid crystal material actually twists the light passing through the cell when the cell is not energized. This allows light to pass through the optical filters, and the cell appears bright (it can also be made to appear dark). When the cell is energized, no twisting of the light occurs and the cell remains dull.

Liquid crystal cells may be *transmittive* or *reflective*. In the *transmittive type* cell, both glass sheets are transparent, so that light from a rear source is scattered in the forward direction when the cell is activated. The *reflective type* cell has a reflecting surface on one of the glass sheets. In this case, incident light on the front surface of the cell is dynamically scattered by an activated cell. When activated, both the transmittive and reflective type cells appear quite bright even under high ambient light conditions.

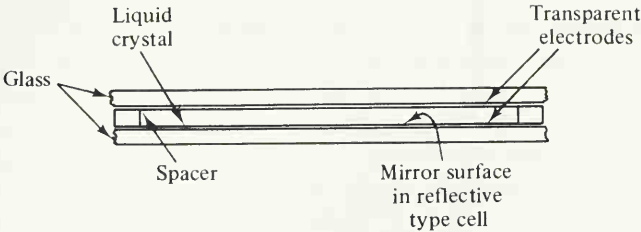

(a) Construction of liquid crystal cell

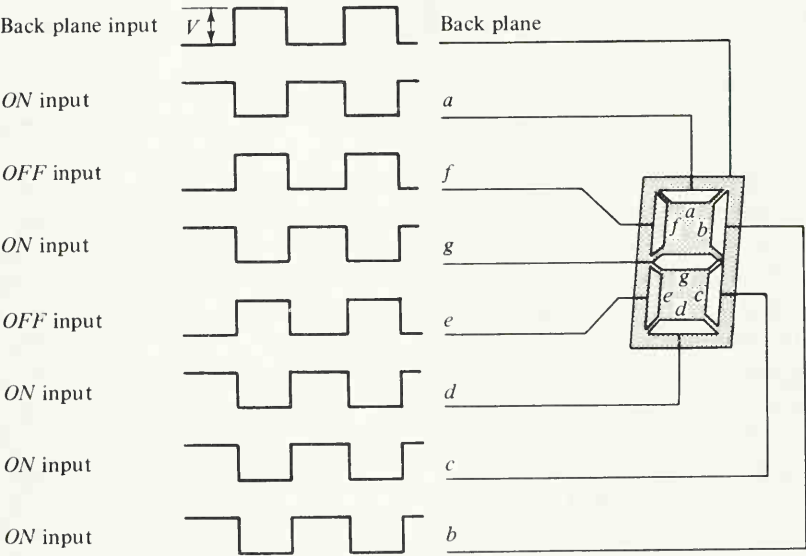

(b) Square wave drive method for liquid crystal cell 7-segment display

FIGURE 12-11. Construction and electrical drive arrangement for liquid crystal cells.

Since liquid crystal cells are light reflectors or transmitters rather than light generators, they consume very small amounts of energy. The only energy required by the cell is that needed to activate the liquid crystal. The total current flow through four small 7-segment displays is typically about 25 μA for dynamic scattering cells and 300 μA for field effect cells. However, the LCD requires an ac voltage supply, either in the form of a sine wave or a square wave. This is because a direct current produces a plating of the cell electrodes, which could damage the device.

A typical supply for a dynamic scattering LCD is a 30 V peak-to-peak square wave with a frequency of 60 Hz. A field effect cell typically uses 8V peak-to-peak. Figure 12-11(b) illustrates the square wave drive method for liquid crystal cells. The *back plane*, which is one terminal common to all cells, is supplied with a square wave. The other cell terminals each have square waves applied which are either in phase or in antiphase with the back plane square wave. Those cells with waveforms in phase with the back plane waveform [cells *e* and *f* in Figure 12-11(b)] have no voltage developed across them; therefore they are *off*. The cells with square waves in antiphase with the back plane input have an ac voltage developed across them (e.g., positive square waves with 15 V peak effectively produce 30 V peak-to-peak when in antiphase). Therefore, the cells which have square wave inputs in antiphase with the back plane input are energized and appear bright.

The data sheet for the series 1603-02 liquid crystal display manufactured by Industrial Electronic Engineers, Inc., is shown in Appendix 1-18. The maximum power consumption is listed as 20 μ W per segment, giving 140 μ W per numeral when all seven segments are energized. Comparing this to the typical 400 mW per numeral for a LED display (see Appendix 1-17), the major advantage of liquid crystal displays is obvious. Perhaps the major disadvantage of the liquid crystal display is the decay time of 150 ms (or more). This is very slow compared to the 10 ns rise and fall times for the LED display. In fact it is so slow that the human eye can observe the fading-out of segments switching *off*. At low temperatures the response time of liquid crystal cells is considerably increased.

The series 1603-02 LCD is described in the data sheet as a $3\frac{1}{2}$ *decade display*. This means that the three righthand units are complete 7-segment units while the fourth (lefthand) unit is only a single segment which indicates numeral 1 when energized. This unit is referred to as a half unit, and the entire display is then described as a $3\frac{1}{2}$ decade display. The maximum number that can be indicated by such a display is 1999.

12-4.3 Tungsten Display

Tungsten (or *incandescent*) numerical displays consist of seven small tungsten filament lamps placed behind lenses arranged in seven-segment format. The construction of a seven-segment tungsten display is illustrated in Figure 12-12, and the data sheet is shown in Appendix 1-19. The data sheet lists the power consumption for this device as 1.2 W maximum, which is three times the power consumed by the LED specified in Appendix 1-17. However, the tungsten display shown is approximately twice the size of the LED display considered.

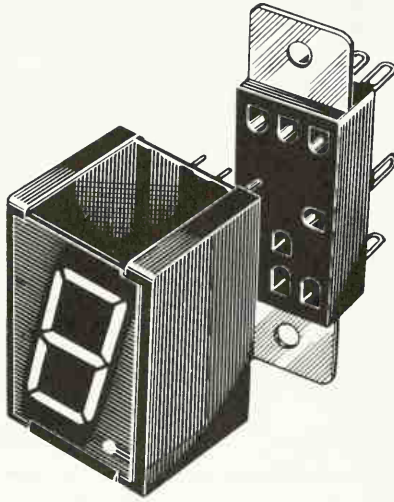


FIGURE 12-12. Seven-segment incandescent readout. (*Courtesy of Alco Electronic Products, Inc.*)

12-4.4 Digital Indicator Tube

The basic construction of a *digital indicator tube* is shown in Figure 12-13(a), and its schematic symbol is illustrated in Figure 12-13(b). (Other names applied to this device are *cold cathode tube* and *glow tube*.) A flat metal plate with a positive voltage supply functions as an anode, and there are 10 separate wire cathodes, each in the shape of a numeral from 0 to 9. The electrodes are enclosed in a gas-filled glass envelope with connecting pins at the bottom. *Neon* gas usually is employed and it gives an orange-red glow when the tube is activated; however, other colors are available with different gases.

When a voltage is applied across the anode and one cathode, electrons are accelerated from cathode to anode. These electrons collide with gas atoms, and cause other electrons to be emitted from the gas atoms. The effect is termed *ionization by collision*. Since the ionized atoms have lost electrons they are positively charged. Consequently, they accelerate toward the (negative) cathode, where they cause secondary electrons to be emitted when they strike. The secondary emitted electrons cause ionization and electron-atom recombination in the region close to the cathode. This results in energy being released in the form of light and produces a visible glow around the cathode. Since the cathodes are in the shape of numerals, a glowing numeral appears depending upon which cathode is energized. A transistor gate is usually employed at each

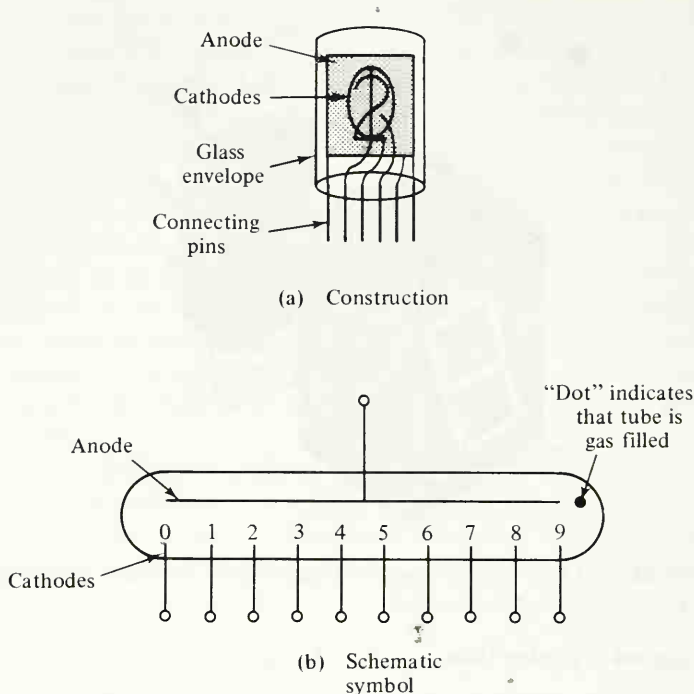



FIGURE 12-13. Digital indicator tube, construction, and schematic symbol.

cathode, so that the desired numeral can be switched *on* by a small input voltage.

The circuitry for driving digital indicator tubes is simpler than that for seven-segment devices. However, high voltages (140 V to 200 V) are required for these tubes, and in general they are much bulkier than comparable seven-segment devices.

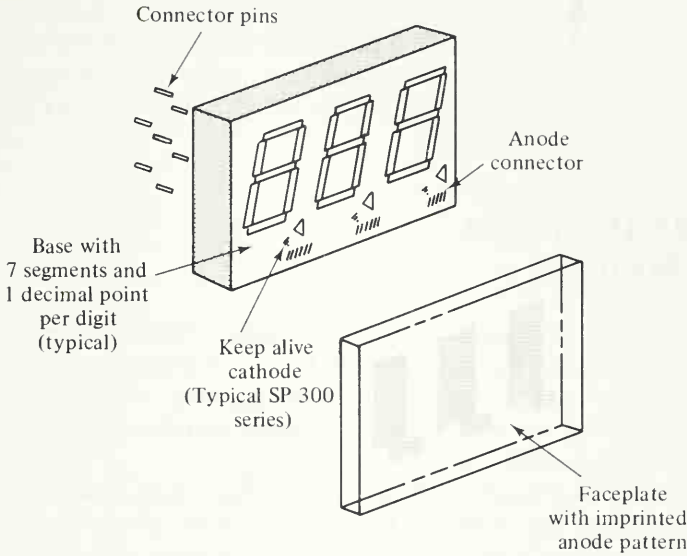12-4.5 Seven-segment Gas Discharge Displays

Gas discharge displays also are available in seven-segment format. Integrated circuits have been developed to drive these devices and to handle the high voltages involved. The mechanical construction of a seven-segment gas discharge display is illustrated in Figure 12-14(a). It is seen that separate cathodes are provided in seven-segment (and decimal point) form on a base. Each seven-segment group has a single anode deposited on the covering face plate. The gas is contained in the space between the anodes and cathodes, and rear connecting pins are provided for all electrodes. A *keep alive cathode* is also enclosed with each group of segments.



(a) Construction of 7-segment gas discharge display
(Courtesy of Beckman Instruments, Inc.)

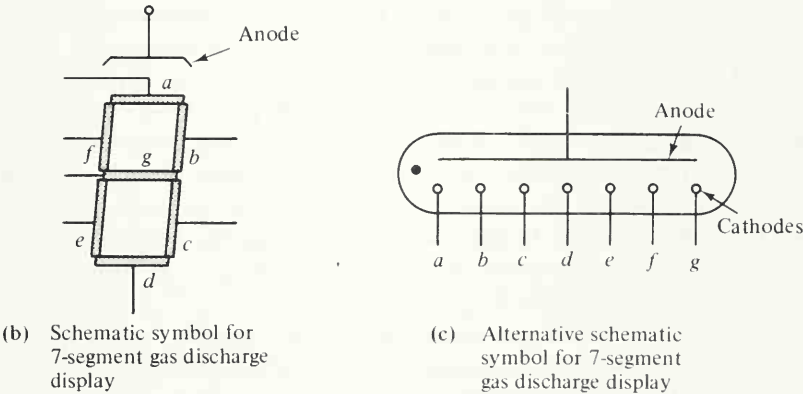


FIGURE 12-14. Mechanical construction and circuit symbols for seven-segment gas discharge display.

A 50 μA current maintained through the *keep alive cathode* provides a source of ions which improves the switch-on speed of the display. Two circuit symbols in general use for seven-segment gas discharge displays are shown in Figures 12-14(b) and (c).

The supply voltage required to operate gas discharge displays ranges from about 140 V to 200 V, and this is the most serious disadvantage of

these devices. High-voltage transistors must be employed as switches for the cathodes, and usually a separate high-voltage supply must be provided. Offsetting the disadvantage of high voltages is the fact that bright displays can be achieved with tube currents as low as $200\ \mu\text{A}$. Thus the drain on power supplies is minimal.

12-5 BINARY TO DECIMAL CONVERSION

The output of a decade counter can be given in binary form if collector voltages are read as 1 when high and 0 when low. For display purposes, it is necessary to convert this binary number to decimal. Figure 12-15 shows the various binary states of a decade counter, and the circuitry required to convert each state to a decimal indication.

The *diode matrix* consists of diodes D_1 to D_{40} which have their cathodes connected to the collectors of the transistors in the decade counter. The anodes of the diodes are connected to the bases of gate transistors Q_{10} to Q_{19} . When one transistor is switched *on*, it grounds the selected cathode in the digital indicator tube. Since the anode of the indicating tube has a positive supply, anode current flows when one of the cathodes is grounded and the cathode glows. The transistor emitters are commoned and connected to ground via diode D_{41} . The presence of D_{41} ensures that the base voltage of each transistor has to be approximately $2V_{BE}$ above ground level for it to switch *on*. Each gate transistor has four diodes connected to its base. When the cathode of one or more of these diodes is at 0 (i.e., near ground level), the transistor base is held below the switching voltage. In this condition the transistor cannot switch *on*. When the cathodes of all four diodes connected to the base of any gate transistor are at 1 , the diodes are reverse-biased, and the transistor is biased *on* via base resistance R_B .

Consider the collector voltage levels and decimal count for the decade counter illustrated in Figure 12-15. For a decimal count of 0 , reading all transistor collector levels, Q_8 to Q_1 are read as $01\ 10\ 10\ 01$. Now, look at diodes D_1 , D_2 , D_3 , and D_4 , which are connected to the base of Q_{10} . The cathode of D_1 is connected to Q_7 collector. The collector voltage of Q_7 is at 1 (i.e., positive); therefore D_1 is reverse-biased. The cathode of D_2 is connected to Q_{6C} , which is also at 1 , so D_2 is also reverse-biased. The cathode of D_3 is connected to Q_{4C} , and since Q_{4C} is at 1 , D_3 is reverse-biased. Finally, D_4 has its cathode connected to Q_{1C} , which is also at 1 . Thus all four diodes at the base of Q_{10} are reverse-biased. Base current flows from V_{BB} via R_B into the base of Q_{10} . With Q_{10} *on*, the 0 cathode in the digital tube glows, indicating that the decimal count is 0 .

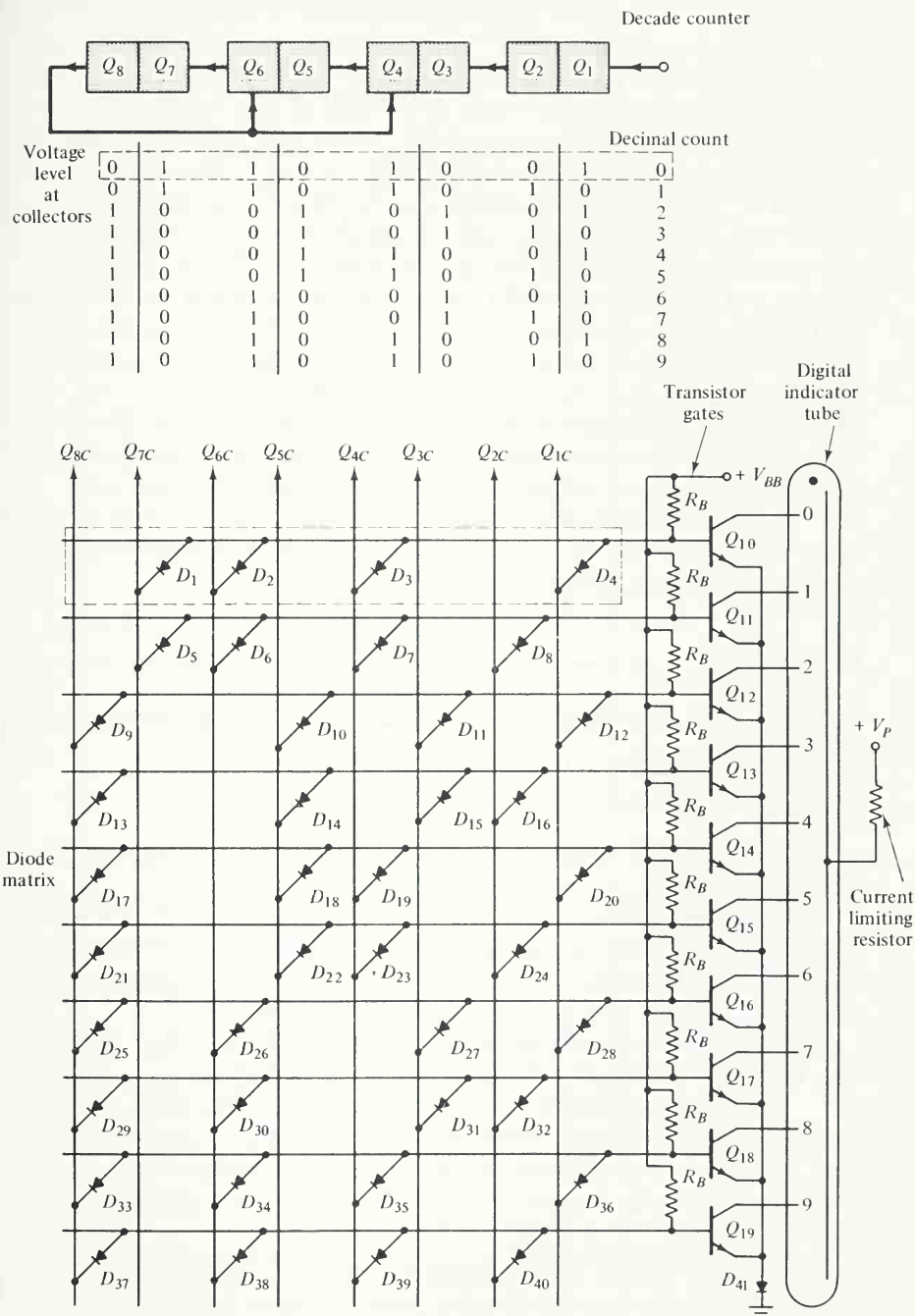


FIGURE 12-15. Binary to decimal conversion.

For a correct 0 indication, all other gate transistors (Q_{11} to Q_{19}) must be biased *off*. To check that this is the case, it is necessary to identify only one forward-biased diode at the base of each transistor. Consider diodes D_5 to D_8 at the base of Q_{11} . The cathodes of D_5 , D_6 , and D_7 are connected to transistor collectors which are at 1 when the decimal count is 0. Therefore, all three are reverse-biased. D_8 cathode is connected to Q_2 collector, which is at 0. Consequently, D_8 is forward-biased, and transistor Q_{11} is held in the *off* condition. For Q_{12} , the cathodes of D_9 , D_{10} , and D_{11} are connected to transistor collectors which are at 0 while the decimal count remains 0. Thus Q_{12} is biased *off*. Other diodes with 0 at their cathodes when the decade counter is in its decimal 0 condition are D_{13} , D_{14} , D_{15} , D_{16} , D_{17} , D_{18} , D_{21} , D_{22} , D_{24} , D_{25} , D_{27} , D_{29} , D_{31} , D_{32} , D_{33} , D_{37} , D_{40} . It is seen that while the decimal count is 0, all transistors except Q_{10} have at least one forward-biased diode at their bases. Therefore, only Q_{10} is biased *on*, and only the 0 cathode glows in the digital indicator tube.

A careful examination of the circuit conditions for any given decimal count shows that only the correct cathode is energized. All other cathodes have their transistor gates biased *off*.

EXAMPLE 12-3

In Figure 12-15, identify the forward-biased and reverse-biased diodes for a decimal count of 5.

solution

For decimal 5, the transistor collectors in the decade counter read 10 01 10 10.

At the base of transistor Q_{15} , diodes D_{21} , D_{22} , D_{23} , and D_{24} have their cathodes connected to Q_8 , Q_5 , Q_4 , and Q_2 , respectively. All these transistors have collectors at 1; therefore, diodes D_{21} to D_{24} are reverse-biased, Q_5 is biased *on*, and cathode 5 in the digital tube glows.

Other reverse-biased diodes are D_3 , D_7 , D_8 , D_9 , D_{10} , D_{13} , D_{14} , D_{16} , D_{17} , D_{18} , D_{19} , D_{25} , D_{29} , D_{32} , D_{33} , D_{35} , D_{37} , D_{39} , D_{40} .

The forward-biased diodes and their associated transistor gates are D_1 , D_2 , D_4 — Q_{10} ; D_5 , D_6 — Q_{11} ; D_{11} , D_{12} — Q_{12} ; D_{15} — Q_{13} ; D_{20} — Q_{14} ; D_{26} , D_{27} , D_{28} — Q_{16} ; D_{30} , D_{31} — Q_{17} ; D_{34} , D_{36} — Q_{18} ; D_{38} — Q_{19} .

Figure 12-16 is a logic diagram for binary to decimal conversion. The flip-flop blocks have terminals as follows: *trigger input T*, *set S*, *reset R*, and outputs identified by their normal *set* conditions of 0 and 1 as shown. The triggering input pulses are applied to terminal *T* of FF1. Each

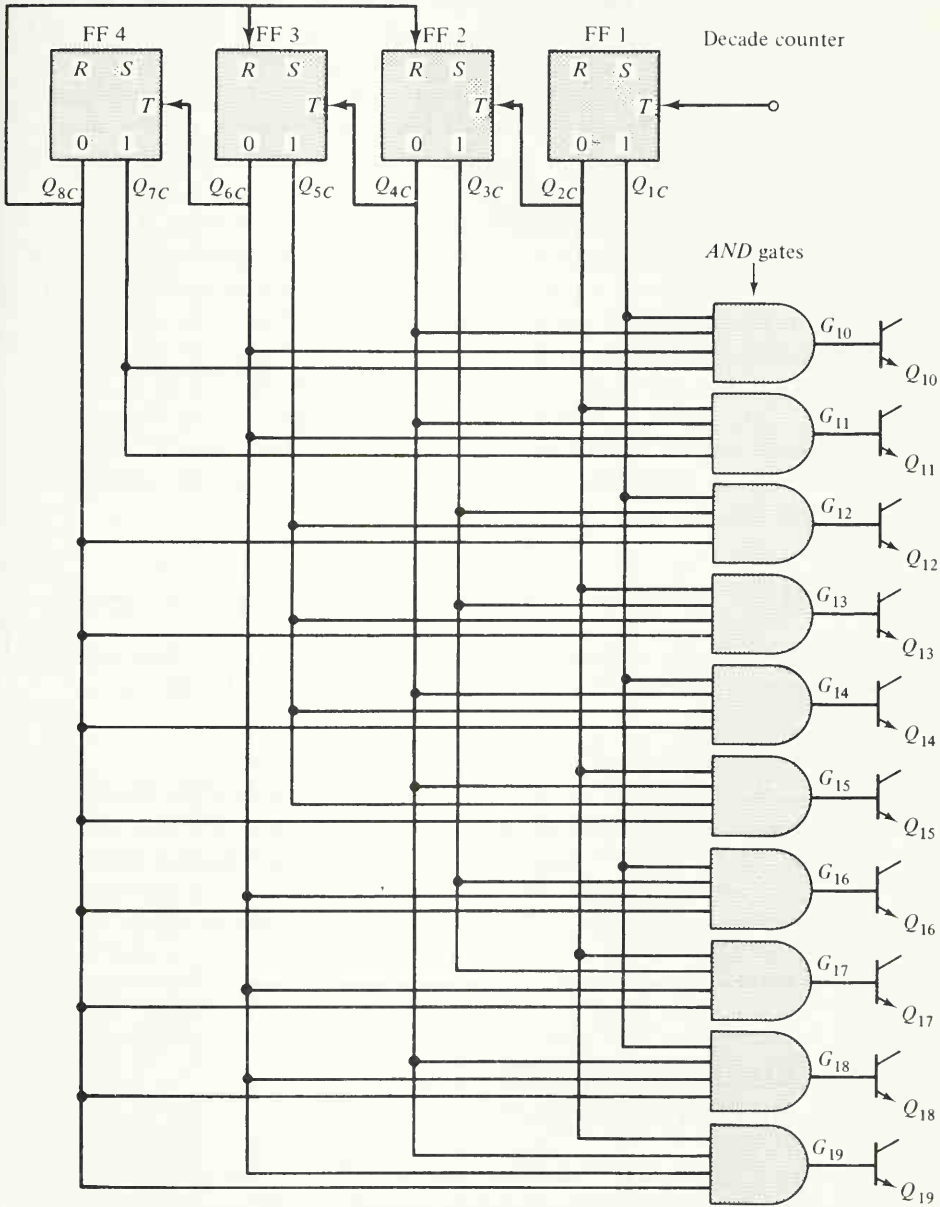


FIGURE 12-16. Logic diagram for binary to decimal conversion.

succeeding flip-flop has its trigger terminal connected to the 0 output of the preceding stage. This arrangement can be compared to the cascaded flip-flops in Figure 12-1, where each stage is triggered from the second transistor in the previous stage. The *reset* terminals of FF2 and FF3 are connected to the output of FF4. This corresponds with the *reset* circuitry in Figure 12-4. In Figure 12-16, the output terminals of the decade counter are identified as Q_{1C} , Q_{2C} , etc. to show the correspondences with Figure 12-15.

Diodes D_1 , D_2 , D_3 , and D_4 in Figure 12-15 constitute an *AND* gate. In Figure 12-16, these diodes are replaced by the *AND* gate symbol. Thus gate G_{10} represents D_1 to D_4 . Also gate G_{11} represents diodes D_5 to D_8 , G_{12} represents D_9 to D_{12} , etc. In Figure 12-16 the input terminals of *AND* gate G_{10} are connected to the decade counter terminals in the same configuration as D_1 to D_4 in Figure 12-15. Thus, the inputs to G_{10} are Q_{1C} , Q_{4C} , Q_{6C} , and Q_{7C} . Similarly, gate G_{11} in Figure 12-16 is connected to the same decade counter terminals as D_5 to D_8 in Figure 12-15. The output of each *AND*-gate is connected to the base of the appropriate transistor gate.

EXAMPLE 12-4

From the collector voltage levels shown in Figure 12-15, determine the input terminal connections for *AND* gate G_{19} in Figure 12-16.

solution

Gate G_{19} should provide an output to transistor Q_{19} only when the decimal count is 9. For G_{19} to produce an output, all its input terminals must be positive (*i.e.*, 1). From Figure 12-15, at the decimal count of 9, transistors Q_8 , Q_6 , Q_4 , and Q_2 all have their collectors at 1. Therefore, the inputs of G_{19} should be connected to the 0 0 0 0 output terminals of the decade counter in Figure 12-16.

12-6 SEVEN-SEGMENT LED DISPLAY DRIVER

The binary to decimal conversion circuitry already discussed is suitable for driving a digital indicating tube. However, it is not suitable for driving a seven-segment display. Binary to decimal conversion is necessary for a seven-segment display, but in addition another diode matrix is required to convert from decimal to seven-segment format. The required diode matrix configuration is shown in Figure 12-17.

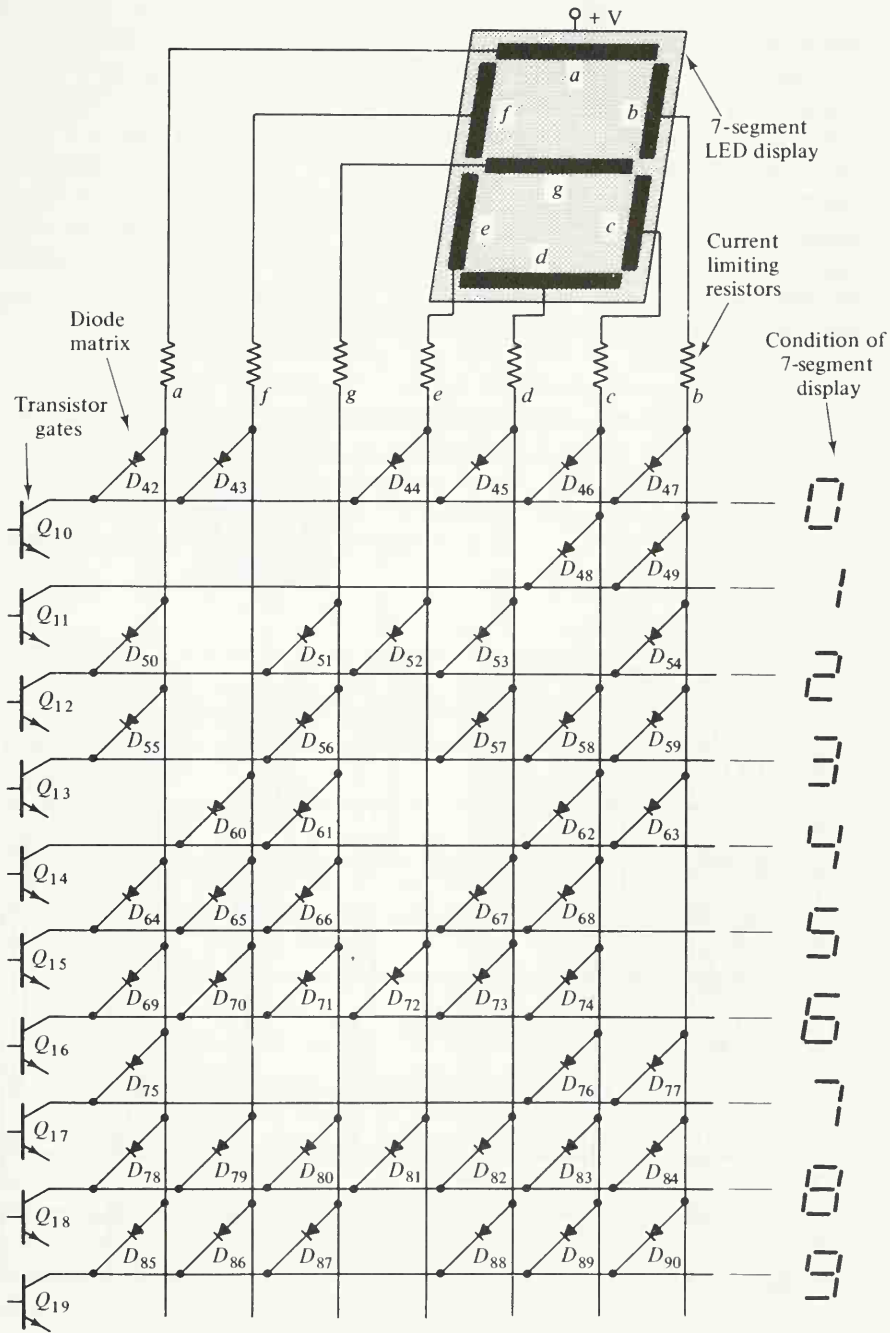


FIGURE 12-17. Decimal to seven-segment display conversion.

For the seven-segment display shown in Figure 12-17, the anodes of the light emitting diodes are commoned and have a positive supply voltage ($+V$). The cathodes from each segment (lettered a to g) have separate terminals. The transistor gates Q_{10} to Q_{19} of Figures 12-15 and 12-16 are shown again in Figure 12-17. When the decimal count is 0, gate Q_{10} is *on*. When the count is 1, gate Q_{11} is *on*, etc. For a 0 indication, LED segments a , b , c , d , e , and f should be energized. Therefore, these segments are connected via diodes D_{42} to D_{47} to the collector of transistor Q_{10} . The cathodes of the diodes are connected to the transistor collector so that they are forward-biased when Q_{10} is *on*. With this transistor *on* the seven-segment display indication is \square as illustrated in Figure 12-17.

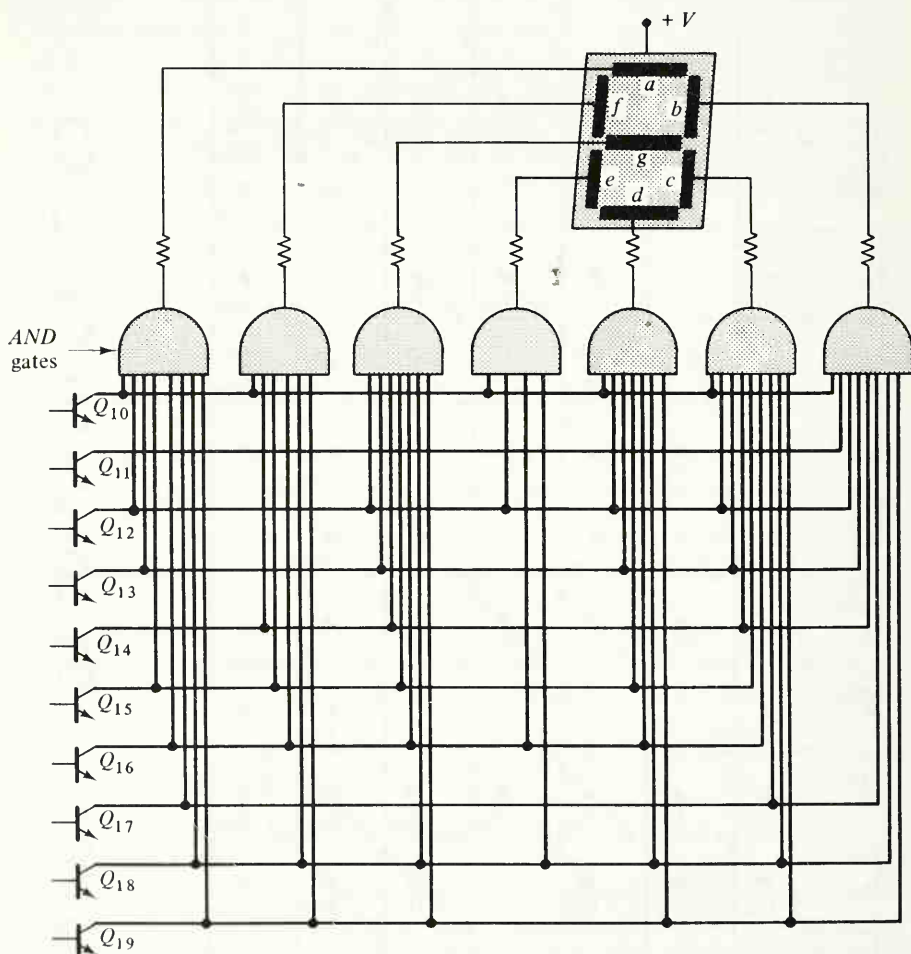


FIGURE 12-18. Logic diagram for decimal to seven-segment display conversion.

When the decimal count is 1, segments b and c should be energized. These segments are connected via diodes D_{48} and D_{49} to the collector of transistor Q_{11} . At the collector of transistor Q_{12} , diodes D_{50} to D_{54} connect to LED segments a , b , d , e , and g . When transistor Q_{12} is *on*, these segments are energized and display the numeral 2 as shown in the figure. At this time, only diodes D_{50} to D_{54} are conducting. No other diodes are conducting because only transistor Q_2 is *on*. Figure 12-17 shows the LED segments that are energized for each decimal count.

Consideration of the diode matrix in Figure 12-17 reveals that the diodes connected to each LED segment constitute an *AND* gate. For segment e , for example, diodes D_{44} , D_{52} , D_{72} , and D_{81} provide a *low* level at the segment cathode when any one of the diodes has a low input level. The segment cathode is *high* only when the inputs to all four diodes are *high*. The diode matrix can be replaced by a group of *AND* gates, as shown in the logic diagram of Figure 12-18. The *AND* gate inputs for each segment are the same as the cathode connections for the diodes associated with the segments in Figure 12-17.

EXAMPLE 12-5

Determine the input terminal connections for the *AND* gate connected to segment b in Figure 12-18.

solution

Consideration of the 0 to 9 display arrangements shows that segment b must be energized for display of numerals 0, 1, 2, 3, 4, 7, 8, 9. Therefore, the *AND* gate input for segment b must be connected to transistors Q_{10} , Q_{11} , Q_{12} , Q_{13} , Q_{14} , Q_{17} , Q_{18} , and Q_{19} .

12-7 SCALE-OF-10,000 COUNTER

One decade counter together with a seven-segment display and the necessary binary to seven-segment conversion circuitry can be employed to count from 0 to 9. Each time the tenth input pulse is applied, the display goes from 9 to 0 again. When this occurs, the output of the final transistor in the decade counter goes from 1 to 0 (see Figure 12-5). This is the only time that the final transistor produces a negative-going output, and this output can be used to trigger another decade counter.

Consider the block diagram of the scale-of-10,000 counter shown in Figure 12-19. The system consists of four complete decade counters and

displays. Starting from 0, all four counters can be set at their normal starting conditions. This gives an indication of 0000. The first 9 input pulses register only on the first (right-hand side) display. On the tenth input pulse, the first display goes to 0, and a negative-going pulse output from the first decade counter triggers the second decade counter. The

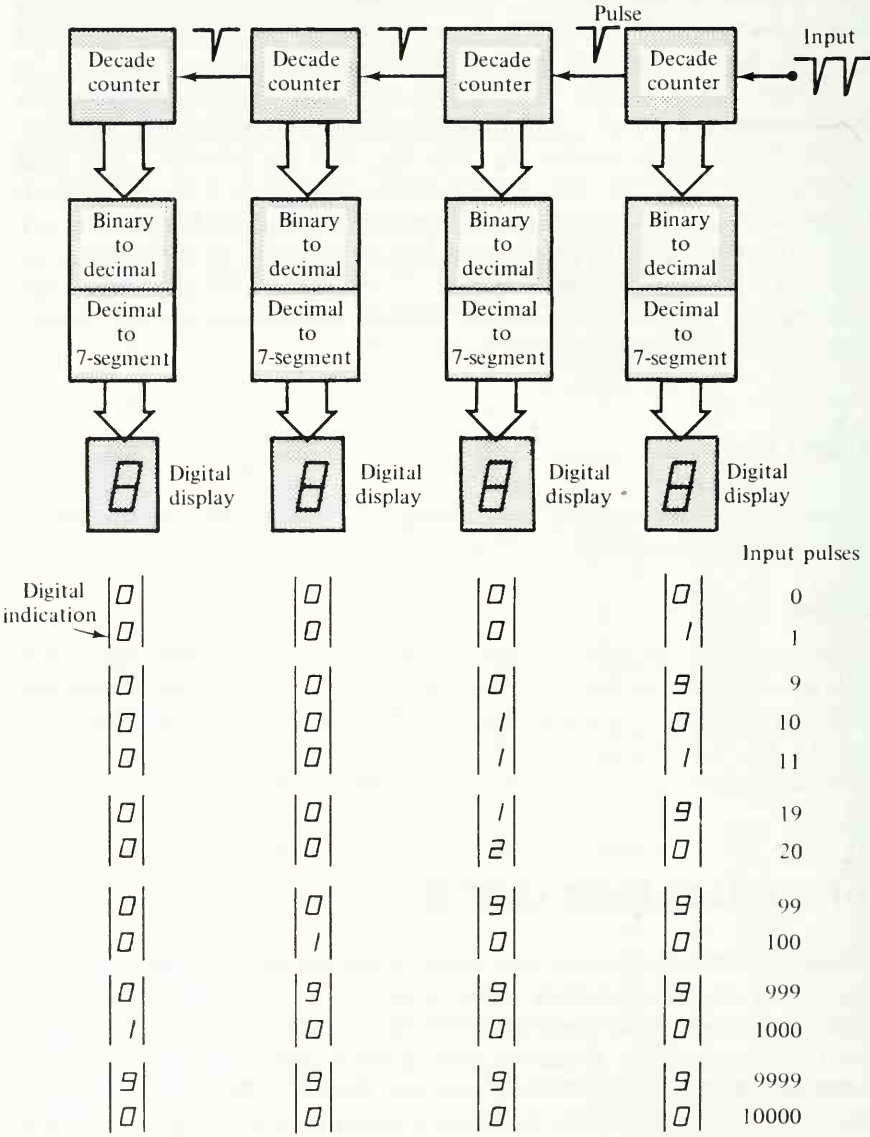


FIGURE 12-19. Scale-of-10,000 counter.

display of the second counter now registers *1*, so that the complete display reads *0010*. The counter has counted to *10*, and has also registered *10* on the display system.

The next nine input pulses cause the first counter to go from *0* to *9*, so that the display reads *0019* on the nineteenth pulse. The twentieth pulse causes the first display to go to *0* again. At this time, the final transistor in the first decade counter puts out another negative pulse, which again triggers the second decade counter. The total display now reads *0020*, which indicates the fact that 20 pulses have been applied to the input of the first decade counter. It is seen that the second decade counter and display is counting *tens* of input pulses.

Counting continues as described until the display indicates *0099* after the ninety-ninth input pulse. The one-hundredth input pulse causes the first two displays (from the right) to go to *0*. The second decade counter emits a negative pulse at this time, which triggers the third decade counter. Therefore, the count reads *100*. It is seen that the system shown in Figure 12-19 can count to a maximum of *9999*. One more pulse causes the display to return to its initial *0000* condition. To increase the maximum count to *99999*, it is necessary to add one more decade counter, together with a display, and binary to seven-segment conversion circuitry.

12-8 COUNTER CONTROLS

A simple system for switching the counter input pulses *on* and *off* is shown in Figure 12-20. The pulses to be counted are applied to one input of an *AND* gate. The voltage level at the other input of the gate is controlled by the output of a flip-flop. The input triggering pulses pass through the gate

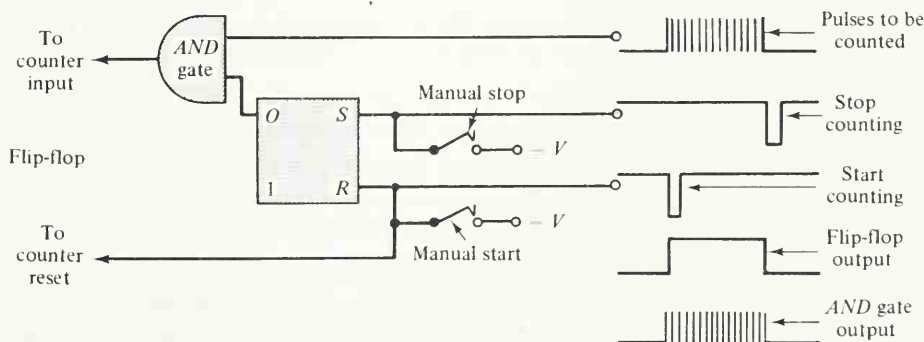


FIGURE 12-20. Starting and stopping a counter.

to the counter only when the flip-flop output is at its 1 level, that is, when it is high. The flip-flop can be reset to 1 output by switching a negative input voltage to the *reset R* terminal. The *manual start* control shown in the figure is provided for this purpose. A connection to the *reset* input of each decade counter (see Figure 12-7) ensures that the counting circuits return to 0 condition before counting begins. The *manual stop* control provides a negative voltage which returns the flip-flop to its original *set* condition. This applies a 0 to the *AND* gate input, and thus stops the pulses to be counted from passing through.

The flip-flop can also be triggered, and consequently counting can be started, by means of a negative *start-counting* pulse applied to the *reset* terminal as shown in Figure 12-20. Similarly, a negative pulse applied to the *set* terminal of the flip-flop interrupts the passage of pulses to the counter. The waveforms in the figure show that counting pulses pass through the *AND* gate only during the time interval between application of *start-counting* and *stop-counting* pulses.

REVIEW QUESTIONS AND PROBLEMS

- 12-1 Sketch the complete circuitry for four cascaded flip-flops. Briefly explain the triggering process.
- 12-2 Sketch a block diagram for a scale-of-16 counter. Reading only the left-hand transistors in each flip-flop, prepare a truth table showing the state of the counter after each input pulse from 0 to 16. Explain the procedure.
- 12-3 Sketch the waveforms of collector voltages for every transistor in a scale-of-16 counter for input pulses from 0 to 16. Briefly explain each waveform change.
- 12-4 Briefly explain how a scale-of-16 counter can be converted to a decade counter. Identify the flip-flops which must be reset in the process, and show which of 16 states of the counter are eliminated.
- 12-5 Sketch circuitry employed for resetting flip-flops when a scale-of-16 is converted to a decade counter. Briefly explain.
- 12-6 Sketch the block diagram of a decade counter. Prepare a table that shows the state of the counter after each input pulse from 0 to 10. Also show the collector waveforms for the even-numbered transistors. Explain the waveforms and the states of the counter.
- 12-7 Identify the transistors in a decade counter that should be reset to 0 before counting commences. Sketch suitable circuitry for (a) manual resetting, (b) automatic resetting, (c) resetting by pulse input. Briefly explain each circuit.

- 12-8** Refer to the logic block diagram for an MC939.MC839 integrated circuit divide-by-16 counter in Figure 12-8(a). Sketch waveforms showing the counter output voltage levels after each input pulse. Explain the operation of the counter.
- 12-9** Show how the MC939.MC839 scale-of-16 counter is modified to produce the MC938.MC838 IC decade counter. Also sketch the output waveforms of the decade counter.
- 12-10** Explain the operation of a light-emitting diode. Sketch the cross section of an LED, and identify and explain all component parts of the device.
- 12-11** Discuss the current and voltage requirements of an LED. Sketch the circuit symbol for the device, and show how it is employed in a seven-segment numerical display.
- 12-12** Three series-connected LEDs are to have 15 mA passed through them from a -9 V supply when energized. A *pnp* transistor with $h_{FE(\min)} = 75$ is to be used as a switch. The input voltage to the transistor is -9 V. Sketch an appropriate circuit and determine the resistor values required.
- 12-13** Explain the operation of a liquid crystal cell. Sketch the cross section of a liquid crystal cell and identify and explain each component part.
- 12-14** Explain *transmittive type* and *reflective type* liquid crystal cells. Discuss the voltage and current requirements for liquid crystal displays, and show how square waves are employed to drive a seven-segment liquid crystal display.
- 12-15** Explain the construction of 7-segment tungsten displays, and discuss their characteristics.
- 12-16** Using sketches, explain the construction of a digital indicator tube. Also sketch the schematic symbol for the device and explain its operation.
- 12-17** Using sketches, explain the operation of a seven-segment gas discharge display. Discuss the current and voltage requirements for the display, and explain the function of the *keep-alive cathode*. Sketch two schematic symbols in general use for seven-segment gas discharge displays.
- 12-18** Show how a diode matrix may be employed for binary to decimal conversion. Sketch the complete circuit of the diode matrix, transistor gates, and digital indicator tube.
- 12-19** For the diode matrix in the binary to decimal conversion circuitry sketched for Problem 12-18, identify the diodes that are

forward-biased and those that are reverse-biased at a decimal count of 6 and at a decimal count of 3.

- 12-20** Sketch a complete logic diagram for binary to decimal conversion. Briefly explain how the system functions.
- 12-21** Sketch a complete diode matrix for driving a seven-segment display from a digital input. Explain the operation of the circuitry, and identify the segments of the display that are energized for each decimal input.
- 12-22** Sketch a complete logic diagram for decimal to seven-segment display conversion. Briefly explain how the system functions.
- 12-23** Draw the block diagram of a scale-of-1,000 counter. Explain the operation of the system.
- 12-24** Draw the block diagram of a control system that will start and stop a counter manually and by means of input pulses. Show the waveforms of input, output, and control voltages. Explain the operation of the system.

Digital Frequency Meters and Digital Voltmeters

INTRODUCTION

If a pulse waveform is fed to the input of a digital counter for a time period of exactly one second, the counter indicates the frequency of the waveform. Suppose the counter registers 1000 at the end of a second; then the frequency of the input is 1000 PULSES PER SECOND. Essentially, a digital frequency meter is a digital counter combined with an accurate timing system. The timing system usually is such that the input frequency is sampled repeatedly. This necessitates the use of a LATCH, which keeps the display constant while the frequency remains unchanged.

A dc voltage can be converted to a frequency which is directly proportional to the voltage. Then this frequency can be measured by a digital frequency meter and the output is read as a voltage. Several methods of converting from voltage to frequency are available.

13-1 TIMING SYSTEM

A block diagram and voltage waveform of a typical timing circuit for a digital frequency meter are shown in Figure 13-1. The source of the time interval over which input pulses are counted is a very accurate crystal-controlled oscillator usually referred to as a *clock source*. The crystal usually is enclosed in a constant temperature *oven* to maintain a stable oscillation frequency.

The output frequency from the final flip-flop of a decade counter is exactly one-tenth of the input triggering frequency (see Chapter 12). This means that the time period of the output waveform is exactly ten times the time period of the input waveform. The 1 MHz output from the crystal oscillator in Figure 13-1 has a time period of $1\ \mu\text{s}$, and the output waveform from the first decade counter has a time period of $10\ \mu\text{s}$. The time period of the output from the second decade counter is $100\ \mu\text{s}$, and that from the third is 1 ms, etc. With all six decade counters, the available time periods are $1\ \mu\text{s}$, $10\ \mu\text{s}$, $100\ \mu\text{s}$, 1 ms, 10 ms, 100 ms, and 1 second.

When the counting circuits in a digital frequency meter are triggered for a period of 1 second, the display registers the input frequency directly. A count of 1000 cycles over the 1 second period represents a frequency of 1000 Hz or 1 kHz, a 5000 display indicates 5000 Hz, etc. These figures are more easily read when a decimal point is placed after the first numeral and the output is identified in kilohertz. Thus a display of 1.000 is 1 kHz, 5.000 is 5 kHz, and 5.473 is 5.473 kHz. In an LED display, the decimal point is created by use of a single suitably placed light-emitting diode. Also, a *kHz* indication usually is displayed.

Now consider the effect of using the 100 ms time period to control the counting circuits. A display of 1000 now means 1000 cycles per 100 ms. This is 10,000 cycles per second or $10\ \text{kHz}$. When the time period is switched from 1 second to 100 ms, the decimal point also is switched from the first numeral to a position after the second numeral. The 10.00 display is now read as $10.00\ \text{kHz}$, 50.00 is read as $50.00\ \text{kHz}$, etc.

When the time period is switched to 10 ms, the decimal point is moved to a new position after the third numeral on the display. A 100.0 display now becomes $100.0\ \text{kHz}$. Since this is the result of 1000 cycles of input counted over a period of 10 ms, the actual input frequency is $(1000/10\ \text{ms})$, that is, 100 kHz. With 1 ms time period, a display of 1000 indicates 1000 cycles during 1 ms, or 1 MHz. The decimal point is now moved back to its original position after the first numeral, and a *MHz* indication is displayed. Therefore, the display of 1.000 with a 1 ms time base is read as 1.000 MHz. If the $100\ \mu\text{s}$ and $10\ \mu\text{s}$ time periods are used, the decimal point is again moved so that the 1000 indication becomes 10.00 MHz and 100.0 MHz, respectively.

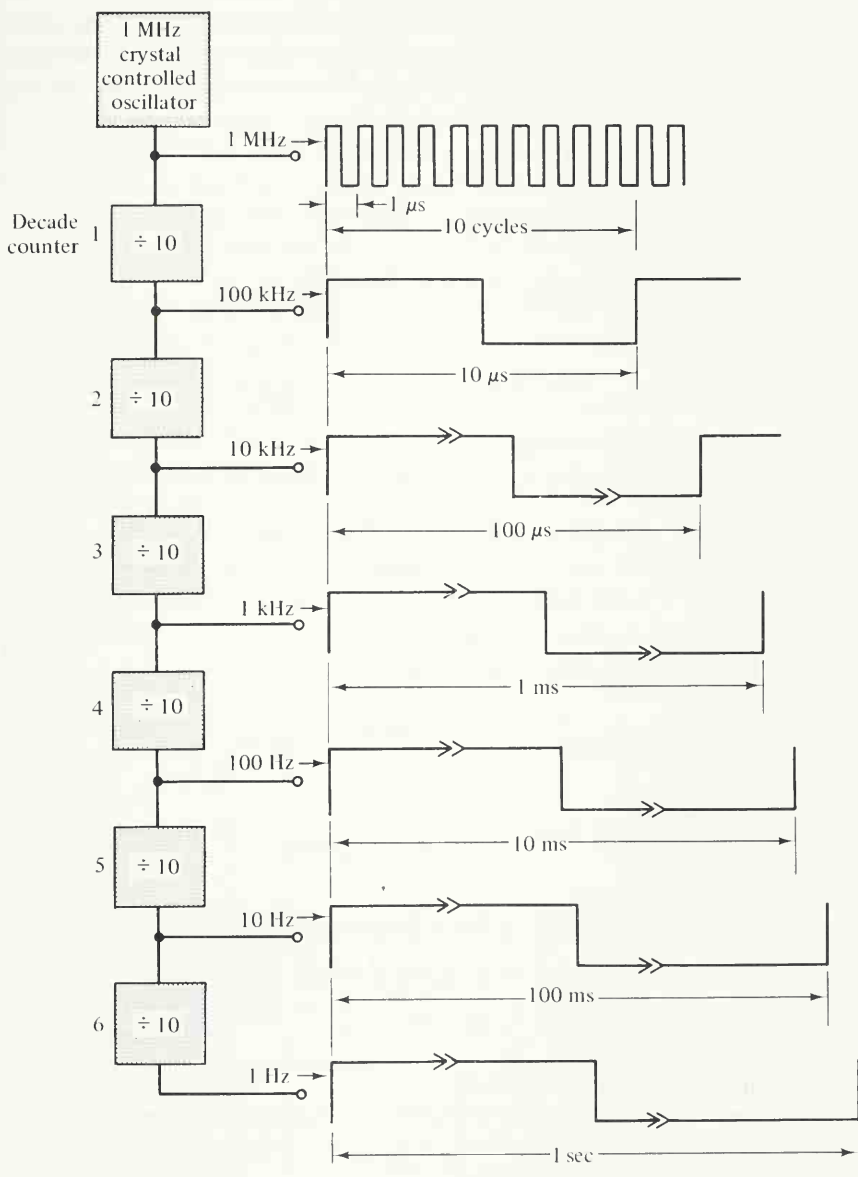


FIGURE 13-1. Time base generation for digital frequency meter.

EXAMPLE 13-1

A 3.5 kHz sine wave is applied to a digital frequency meter. The time base is derived from a 1 MHz clock generator frequency divided by decade counters. Determine the meter indication when the time base uses (a) six decade counters and (b) four decade counters.

solution

(a) When six decade counters are used:

$$\text{Time base frequency} = f_1 = \frac{1 \text{ MHz}}{10^6} = 1 \text{ Hz}$$

$$\text{Time base} = t_1 = \frac{1}{f_1} = \frac{1}{1 \text{ Hz}} = 1 \text{ sec}$$

Cycles of input

$$\text{counted during } t_1 = \text{Input frequency} \times t_1$$

$$= 3.5 \text{ kHz} \times 1 \text{ sec}$$

$$= 3,500$$

Thus, the display indication is 3500.

(b) When four decade counters are used:

$$\text{Time base frequency} = f_2 = \frac{1 \text{ MHz}}{10^4} = 100 \text{ Hz}$$

$$\text{Time base} = t_2 = \frac{1}{f_2} = \frac{1}{100 \text{ Hz}} = 10 \text{ ms}$$

Cycles of input

$$\text{counted during } t_2 = \text{Input frequency} \times t_2$$

$$= 3.5 \text{ kHz} \times 10 \text{ ms}$$

$$= 35$$

Thus, the display indication is 0035.

13-2 LATCH CIRCUITS

If the display devices in a digital frequency meter are controlled directly from the counting circuits, the display changes rapidly as the count pro-

gresses from zero. Suppose the input pulses are counted over a period of 1 second, and then the count is held constant for 1 second. The display alternates between being constant for one second and continuously changing for the next second. Therefore, the display is quite difficult to read, and the difficulty is increased when shorter time periods are employed for counting. To overcome this problem, *latch* circuits are employed.

A *latch* isolates the display devices from the counting circuits while counting is in progress. At the end of the counting time, a signal to the latch causes the display to change to the decimal equivalent of the final condition of the counting circuits. If the input frequency is constant, as is usually the case, the displayed count remains constant. The counting circuits continue to sample the input frequency, and the *latches* are repeatedly triggered to check the displays against each final state of the counting circuits.

Figure 13-2 illustrates the use of JK flip-flops as latch circuits. The input (*J* and *K*) terminals of the flip-flops are connected to the collectors of the transistors in the decade counter. The flip-flop outputs are fed to the binary-to-decimal diode matrix (Figure 12-15). The latching signal is applied to the *clock* input terminal *c* of each JK flip-flop.

The theory of the JK flip-flop is explained in Sec. 9-7 and a circuit diagram is shown in Figure 9-13. When triggered, the flip-flop outputs

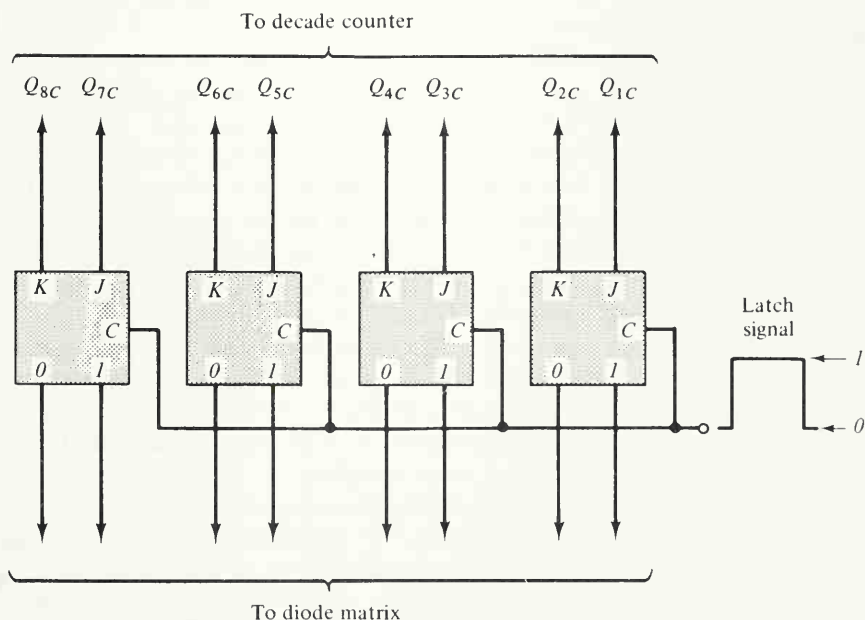


FIGURE 13-2. JK flip-flops operated as latch circuits.

assume the level of the J and K input terminals. The output then remains constant until another trigger (*i.e.*, latch) input is applied. If the input levels have changed, the output will change. If the input levels are the same as before, the flip-flop outputs remain unaltered. Thus, the latch circuits sample the output levels of the decade counter, and pass these levels to the diode matrix. Since sampling occurs only when a latch signal is applied, the inputs to the diode matrix remain constant during the time interval between latch signals. Therefore, the numerical display devices also remain in a constant state during this time, and the counting circuits can go from zero to maximum count without affecting the display.

13-3 DIGITAL FREQUENCY METER

The block diagram of a digital frequency meter is shown in Figure 13-3, and the voltage waveforms for the system are illustrated in Figure 13-4. The input signal which is to have its frequency measured is first amplified and then fed to a Schmitt trigger circuit. Amplification ensures that the signal amplitude is large enough to trigger the Schmitt circuit, and the Schmitt circuit produces a square wave output of the same frequency as the input. A square wave is required for triggering the counting circuits. Before it gets to the counting circuits, however, the square wave must pass through an *AND* gate.

The square wave passes to the counting circuits only when output 1 from the flip-flop is at logic 1 (*i.e.*, positive). The flip-flop changes state each time a negative-going output is received from the *timer*. Therefore, when $T = 1$ sec (see Figure 13-4) the flip-flop output is alternately at level 1 for one second and at level 0 for one second. Consequently the *AND* gate is alternately *on* for one second and *off* for one second. During the time that the *AND* gate is *on*, the Schmitt output triggers the counting circuits. The exact number of input pulses are counted during that time and, as already discussed, when $T = 1$ second the count is a measure of the input frequency. The timer has six (or more) available output time periods over which counting can take place. The desired time period is selected by means of a switch, as shown in Figure 13-3. A separate decimal point selector switch moves with the time base selector.

Output 2 from the flip-flop is in antiphase to output 1 (see Figure 13-4). This waveform is employed for resetting the counting circuits, and for opening and closing the latches. At the beginning of the counting time, output 2 from the flip-flop is a negative-going voltage. This triggers the reset circuitry in each decade counter. Since flip-flop output 2 is at logic 0 during the counting time, its application to the latching circuits ensures that each latch is *off*. That is, during the counting time, nothing

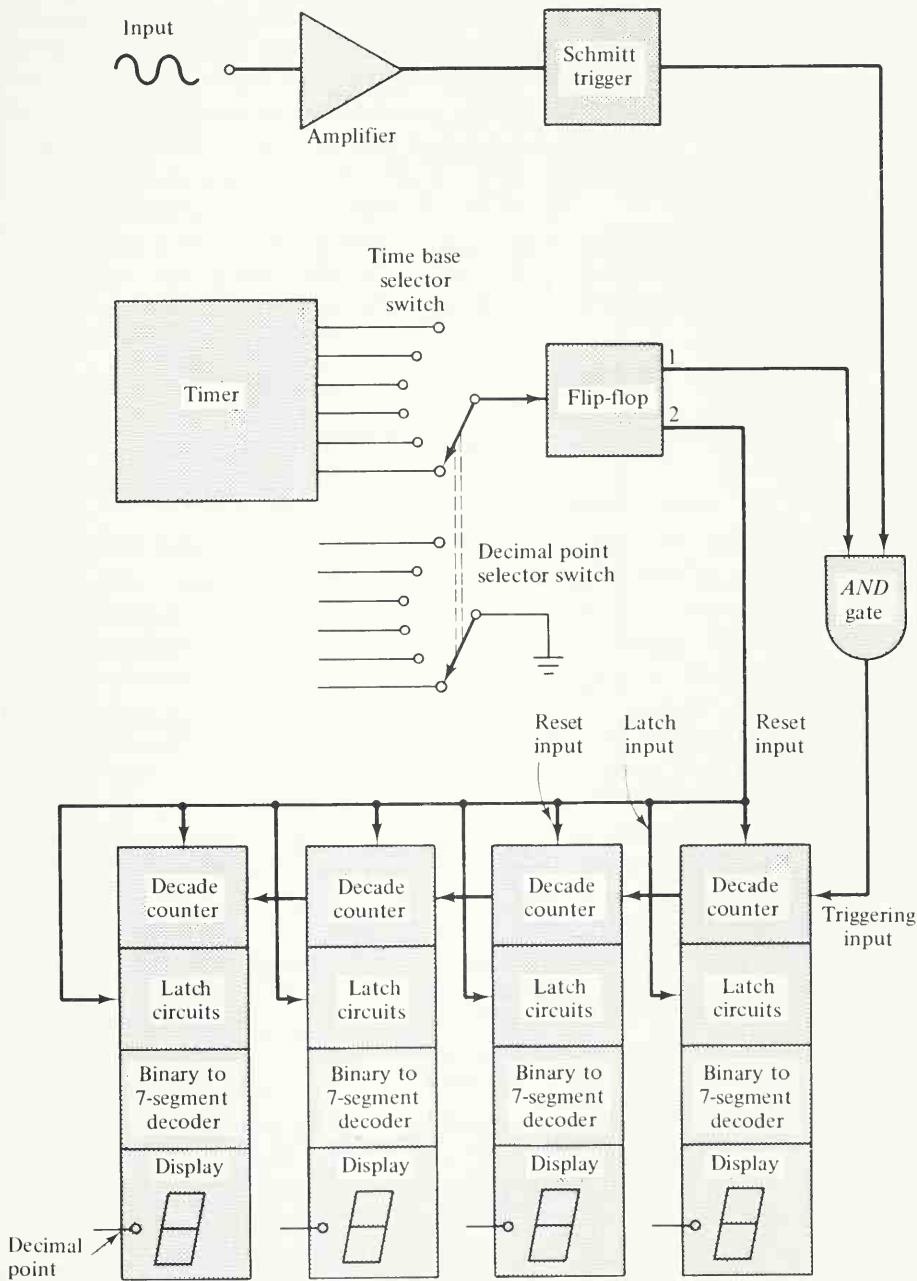


FIGURE 13-3. Block diagram of a digital frequency meter.

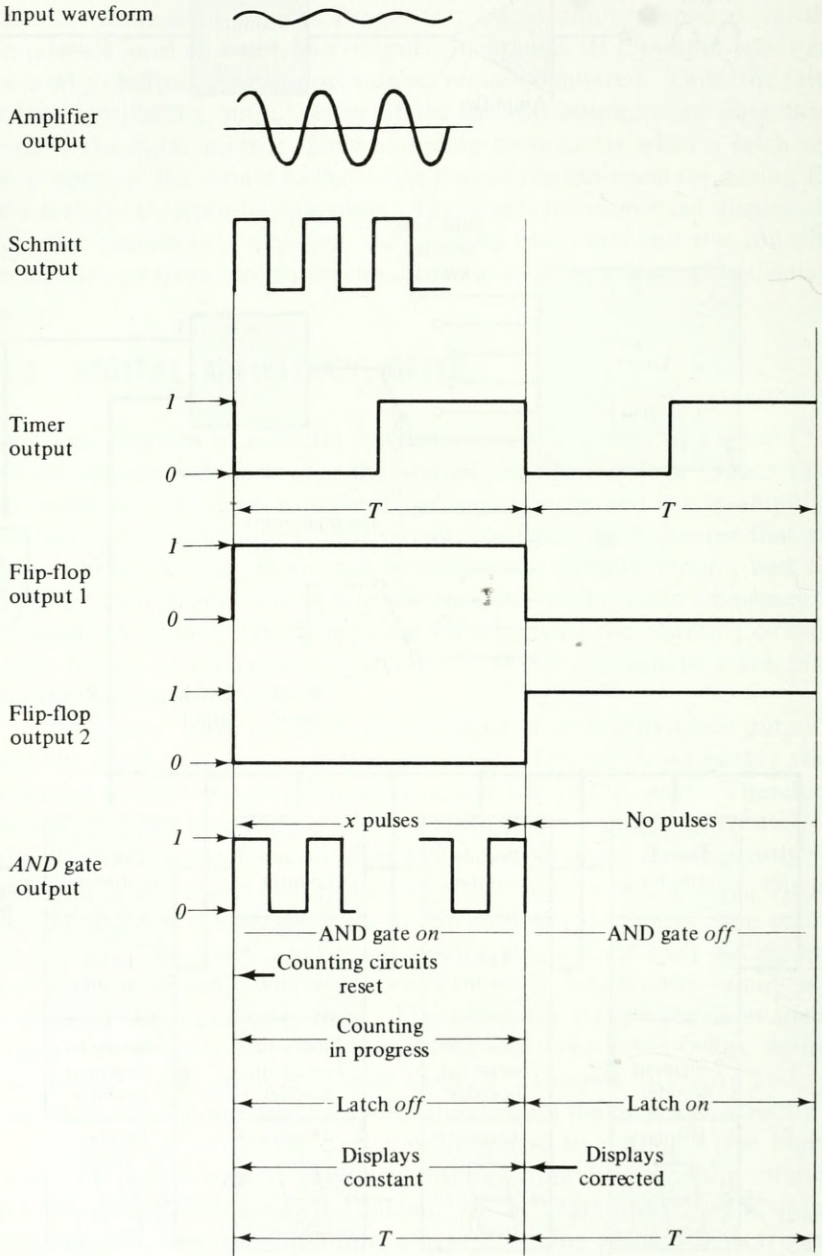


FIGURE 13-4. Waveforms for a digital frequency meter.

passes through the latching circuits. At the end of the counting time, the waveform fed to the latch inputs goes to logic 1. This triggers each latch *on* so that the conditions of the displays are corrected, if necessary, to reflect the states of the counting circuits. During the latch *on* time, the *AND* gate is *off* and no counting occurs. Therefore, once corrected, the displays remain constant. The displays remain constant also during the counting time, since the latch circuits are *off*.

The digital frequency meter can be used to measure the frequency of a signal with almost any waveform. Also, it can be employed for accurate measurement of time periods, and for determining the ratio of two frequencies.

13-4 DUAL SLOPE INTEGRATOR FOR DIGITAL VOLTMETER

In the dual slope integration type of digital voltmeter, an integrating circuit is used to generate a ramp over a timed interval. The slope of the ramp is proportional to the voltage to be measured. Consequently, the ramp amplitude is also proportional to the input voltage. The integrator then is reversed and discharged at a constant rate proportional to an accurate reference voltage. When the time for the ramp to go to zero is measured digitally, the numerical display can be read as the input voltage.

A dual slope integrating circuit is shown in Figure 13-5. The voltage V_i to be measured is applied to the input terminal of a voltage follower in order to present a high input impedance. The voltage follower output is switched via a FET (Q_1) to the input of a Miller integrator. (The voltage follower and Miller integrator are introduced in Chapter 7.) An accurate current source is also connected to the input of the Miller integrator, and the integrator output level is monitored by a *zero crossing detector*. The zero crossing detector is merely a high gain operational amplifier, which gives a large positive output when the input voltage is slightly above ground, and a large negative output when the input is slightly below ground.

The square wave (control) input to Q_1 provides the time interval over which integration occurs. This square wave is generated by using decade counters to divide the output frequency of a *clock source*. When the input to Q_1 is negative, the FET is biased *off* and V_i is isolated from the integrator. During this time, the reference current is fed into the Miller integrator circuit. The level of this reference current is

$$I_R = \frac{-V_{z1}}{R_3 + R_4 + R_5}$$

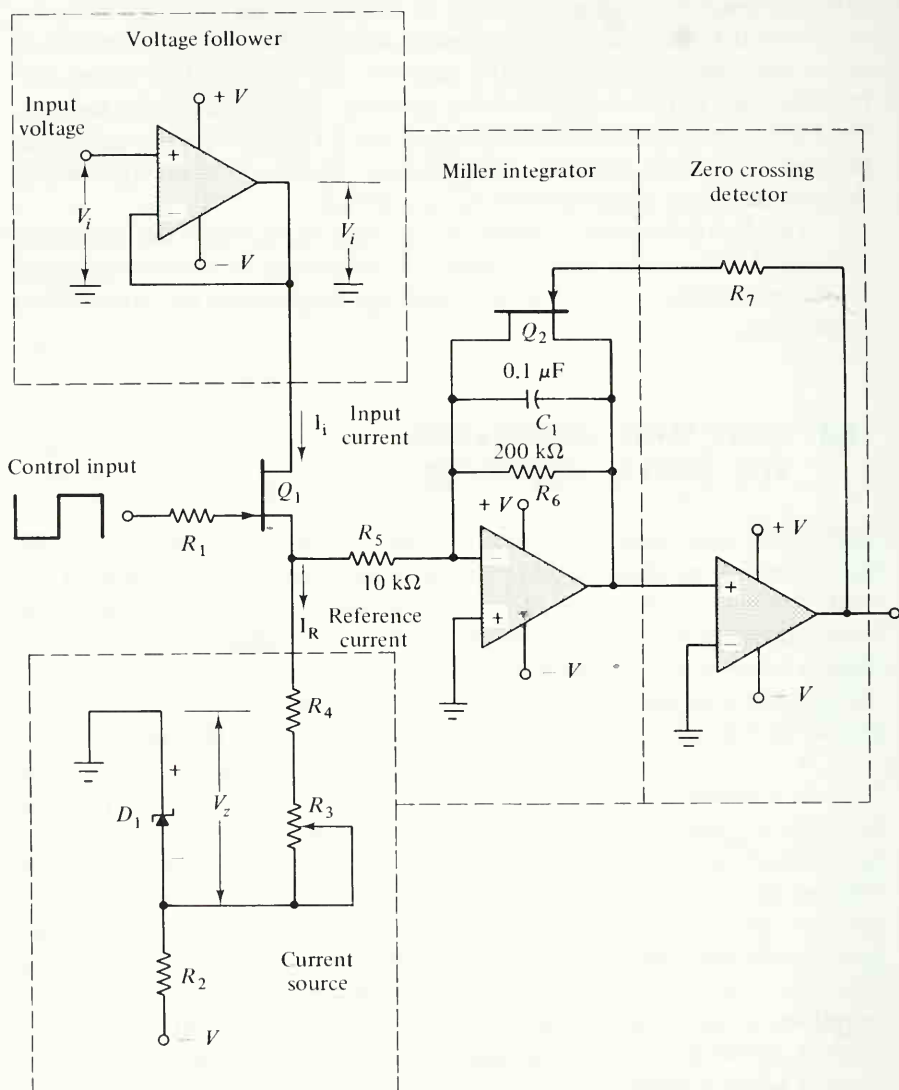


FIGURE 13-5. Dual slope integrator.

The direction of the current is such that C_1 tends to charge positively on the right-hand side, so that the output of the Miller integrator tends to be positive. However, when the output of the Miller circuit becomes slightly positive, the zero crossing detector generates a large positive output. This biases FET Q_2 on, and Q_2 short-circuits C_1 . Therefore, at the end of the negative half of the square wave input to Q_1 , capacitor C_1 is short-circuited and the Miller circuit output is held close to ground level.

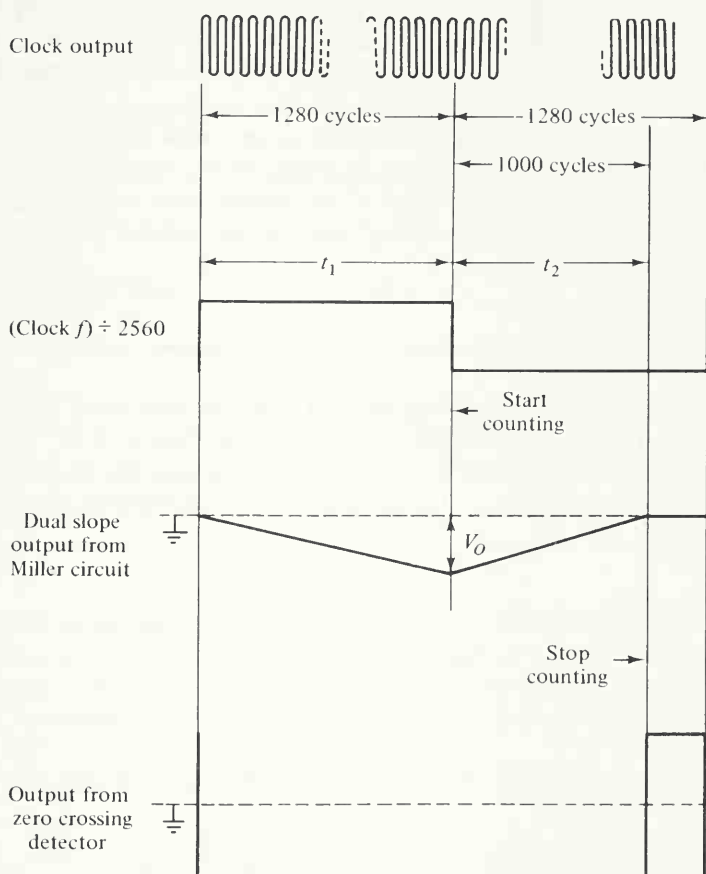


FIGURE 13-6. Waveforms for a dual slope integrator.

Transistor Q_1 switches *on* when the square wave input becomes positive. This action connects voltage V_i to resistance R_5 , and provides an input current, $I_i = V_i/R_5$, to the Miller circuit. Capacitor C_1 now charges with negative polarity on the right-hand side and this produces a negative-going output from the Miller circuit (Figure 13-6). Consequently, the zero crossing detector has a large negative output, which biases transistor Q_2 *off*; thus permitting C_1 to charge. The output from the Miller circuit is a linear negative ramp voltage, which continues during the positive portion of the square wave input to Q_1 . Since I_i is directly proportional to V_i , the slope of the ramp is also proportional to V_i . Also, the time duration t_1 of the positive input voltage is a constant. This means that the ramp amplitude V_o is directly proportional to V_i .

When the square wave input again becomes negative, Q_1 switches *off* and the reference current I_R commences to flow once more. I_R discharges

C_1 so that the Miller circuit output now becomes a positive ramp (Figure 13-6). The positive ramp continues until it arrives at ground level. Then the zero crossing detector provides an output which switches Q_2 on, discharges C_1 , and holds it in short-circuit once again.

The time t_2 for the ramp to discharge to zero now is directly proportional to the input voltage. Time t_2 is measured by starting the counting circuits at the negative-going edge of the square wave input to Q_1 , and stopping them at the positive-going edge of the output from the zero crossing detector.

EXAMPLE 13-2

The dual slope integrator in Figure 13-5 has a square wave input with each half-cycle equivalent to 1280 clock pulses (see Figure 13-6). The output frequency from the clock is 200 kHz. If 1000 pulses during time t_2 are to represent an input of $V_i = 1$ V, determine the required level of reference current.

solution

$$I_i = \frac{V_i}{R_s}$$

For $V_i = 1$ V,

$$\begin{aligned} I_i &= \frac{1 \text{ V}}{10 \text{ k}\Omega} \\ &= 100 \mu\text{A} \end{aligned}$$

$$\text{Clock frequency} = 200 \text{ kHz}$$

$$\begin{aligned} T &= \frac{1}{f} = \frac{1}{200 \text{ kHz}} \\ &= 5 \mu\text{s} \end{aligned}$$

If t_1 is the time duration of 1280 clock pulses:

$$\begin{aligned} t_1 &= 5 \mu\text{s} \times 1280 \\ &= 6.4 \text{ ms} \end{aligned}$$

I_i is applied to the integrator input for a time period t_1 . Since

$$C = \frac{It}{V}$$

$$\text{Ramp voltage } V_o = \frac{I_i t_1}{C_1} = \frac{100 \mu\text{A} \times 6.4 \text{ ms}}{0.1 \mu\text{F}} = 6.4 \text{ V}$$

If t_2 is the time duration of 1000 clock pulses,

$$\begin{aligned} t_2 &= 5 \mu\text{s} \times 1000 \\ &= 5 \text{ ms} \end{aligned}$$

and I_R must discharge C_1 in time period t_2 .

$$\begin{aligned} \therefore I_R &= \frac{C_1 V_o}{t_2} \\ &= \frac{0.1 \mu\text{F} \times 6.4 \text{ V}}{5 \text{ ms}} \\ &= 128 \mu\text{A} \end{aligned}$$

One of the most important advantages of the dual slope integration method is that small drifts in the clock frequency have little or no effect on the accuracy of measurements. Consider the following example: Let clock frequency = f ; then time period of one cycle of clock frequency = $T = 1/f$.

The time duration of 1280 clock pulses, t_1 , is $1280 \times T$.

$$\begin{aligned} V_o &= \frac{I_i t_1}{C_1} \\ &= \frac{100 \mu\text{A} \times 1280 T}{C_1} \\ t_2 &= \frac{C_1 V_o}{I_R} = \frac{C_1}{128 \mu\text{A}} \times \frac{100 \mu\text{A} \times 1280 T}{C_1} \\ &= 1000 T \end{aligned}$$

The number of clock pulses during t_2 is given by

$$\frac{t_2}{\text{Time period of clock pulses}} = \frac{1000 T}{T} = 1000$$

It is seen that when the clock frequency drifts, the digital measurement of voltage is unaffected.

13-5 DIGITAL VOLTMETER (DVM)

Figure 13-7 shows a block diagram of a DVM system employing dual slope integration. In this particular system, the clock generator has a frequency of 200 kHz. The 200 kHz is divided by a decade counter and two divide-by-16 counters as shown, giving a frequency of approximately 78 Hz. This (78 Hz) is the square wave which controls the integrator, as explained in Sec. 13-4. The 200 kHz clock signal, the 78 Hz square wave, and the integrator output are all fed to input terminals of an *AND* gate. The 200 kHz clock output acts as a triggering signal to the counting

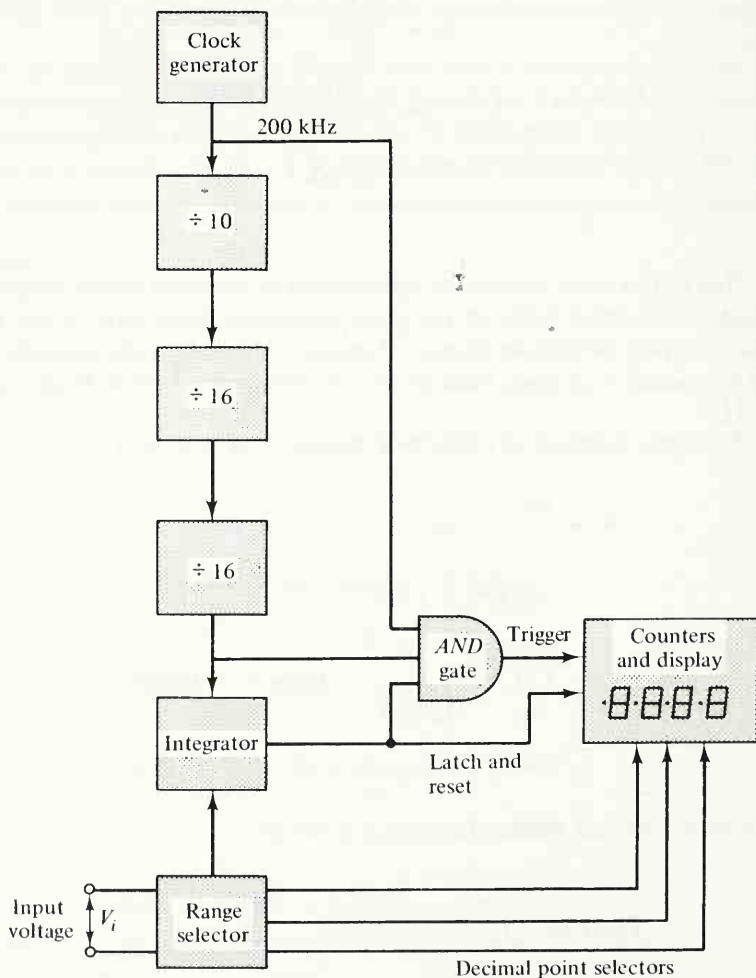


FIGURE 13-7. Digital voltmeter system.

circuitry when the other two inputs to the *AND* gate are high. This occurs during time t_2 , as illustrated in Figure 13-6. Note that the output of the zero crossing detector and the 78 Hz square wave must be inverted before being applied to the *AND* gate. The integrator output (i.e., zero crossing detector output) is also used to reset the counting circuits and to control the latch. The counting circuits are reset at the beginning of time period t_1 . Counting commences at the start of t_2 . The latch is switched *on* at the end of t_2 in order to set the displays according to the counting circuits.

The range selector is adjusted to suit the input voltage. An input of less than 1 V is applied directly to the integrator, and a decimal point is selected so that the display can indicate a maximum of 0.9999 V. An input voltage between 1 V and 10 V is first potentially divided by 10 and applied to the integrator again as a voltage less than 1 V. In this case the decimal point is selected so that the display can indicate a maximum of 9.999 V. An input voltage between 10 V and 100 V is reduced by a factor of 100 before passing to the integrator. Decimal point selection now allows the meter to indicate a maximum of 99.99 V.

REVIEW QUESTIONS AND PROBLEMS

- 13-1 Sketch the block diagram of a timing system for a digital frequency meter. Also sketch the output waveforms and carefully explain the operation of the system.
- 13-2 A crystal-controlled oscillator with an output frequency of 100 MHz is available for use in the timing circuit of a digital voltmeter. Draw a block diagram to show how time intervals of 100 μ s, 1 ms, 10 ms, and 100 ms can be obtained.
- 13-3 Discuss the numerical display obtained with a digital frequency meter when the time base is 1 second and the input frequency is 3 kHz. Explain how the time base and the display must be altered when the frequency goes to 30 kHz, 300 kHz, and 3 MHz.
- 13-4 A digital frequency meter uses a time base derived by decade counters from a 10 MHz source. Determine the display indication produced by a 1.5 kHz input when the time base uses five decade counters. Also determine the number of decade counters required for the display to read 1500.
- 13-5 Sketch a block diagram showing JK flip-flops employed as latching circuits. Carefully explain the operation of the latch, and the effect that it has on the numerical display.
- 13-6 Sketch the complete block diagram of a digital frequency meter. Also sketch the voltage waveforms that occur throughout the system. Explain the operation of the system.

- 13-7** Sketch the circuit of a *dual slope integrator*. Also sketch the circuit waveforms, and carefully explain the operation of the integrator.
- 13-8** Show that the accuracy of the dual slope integration method is not affected by small drifts in clock frequency.
- 13-9** The Miller circuit in a dual slope integrator (as in Figure 13-5) has an input resistance $R_5 = 15 \text{ k}\Omega$ and a capacitor $C_1 = 0.1 \text{ }\mu\text{F}$. The input voltage is 1 V, and each half-cycle of the square wave input is equivalent to 1500 cycles of the clock frequency. The clock frequency is 400 kHz. Determine the required reference current if the 1 V input is to be represented by a count of 1000.
- 13-10** Sketch the block diagram of a digital voltmeter using dual slope integration. Carefully explain the operation of the system.

Chapter 14

Pulse Modulation and Multiplexing

INTRODUCTION

Information can be transmitted, recorded, or otherwise processed in the form of pulses. The technique used to do this may be by PULSE AMPLITUDE MODULATION, PULSE DURATION MODULATION, PULSE POSITION MODULATION, or PULSE CODE MODULATION. Although it is the most complicated of all four methods, pulse code modulation can be the most accurate and most efficient technique. Several separate pulse-modulated signals can be transmitted or recorded on one channel by TIME DIVISION MULTIPLEXING. In this process, pulse signals are inserted in the spaces between other pulse signals. The circuits involved in pulse modulation and demodulation, and in coding and decoding time-multiplexed information are, in general, those that have been studied in previous chapters.

14-1 TYPES OF PULSE MODULATION

The instantaneous amplitude of a signal may be measured (or sampled) at regular intervals, and the measured amplitudes converted to pulses. The pulses may then be transmitted, recorded, or otherwise processed. A low-frequency alternating signal and four types of pulse modulation by which the signal may be represented are illustrated in Figure 14-1.

Pulse amplitude modulation (PAM) is the simplest type of pulse modulation. As the name implies, the amplitude of each pulse is made proportional to the instantaneous amplitude of the modulating signal [Figure 14-1(b)]. The largest pulse represents the greatest positive signal amplitude sampled, while the smallest pulse represents the largest negative sample. The time duration of each pulse may be quite short, and the time interval between pulses may be relatively long. If a radio frequency is pulse-amplitude-modulated instead of simply being amplitude-modulated, much less power is required for the transmission of information because the transmitter actually is switched *off* between pulses. This is one advantage of pulse modulation.

In *pulse duration modulation (PDM)*, also termed *pulse width modulation*, the pulses have a constant amplitude and a variable time duration. The time duration (or width) of each pulse is proportional to the instantaneous amplitude of the modulating signal [Figure 14-1(c)]. In this case, the narrowest pulse represents the most negative sample of the original signal, and the widest pulse represents the largest positive sample. When PDM is applied to radio transmission, the carrier frequency has a constant amplitude, and the transmitter *on*-time is carefully controlled. In some circumstances PDM can be more accurate than PAM. One example of this is in magnetic tape recording, where pulse widths can be recorded and reproduced with less error than pulse amplitudes.

Pulse position modulation (PPM) [Figure 14-1(d)] is more efficient than PAM or PDM for radio transmission. In PPM, all pulses have the same constant amplitude and narrow pulse width. The position in time of the pulses is made to vary in proportion to the amplitude of the modulating signal. Note that in Figure 14-1(d) each PPM pulse occurs just at the end of a PDM pulse in Figure 14-1(c). Thus, the pulses near the right-hand side of the sampling time period represent the largest positive signal sample, and those toward the left-hand side correspond to the most negative samples of the original signal. PPM uses less power than PDM and, essentially, has all the advantages of PDM. One disadvantage of PPM is that the demodulation process to recover the original signal is more difficult than with PDM.

Pulse code modulation (PCM), illustrated in Figure 14-1(e), is the most complicated type of pulse modulation. However, PCM can be the most accurate and the most efficient of the four methods. In certain

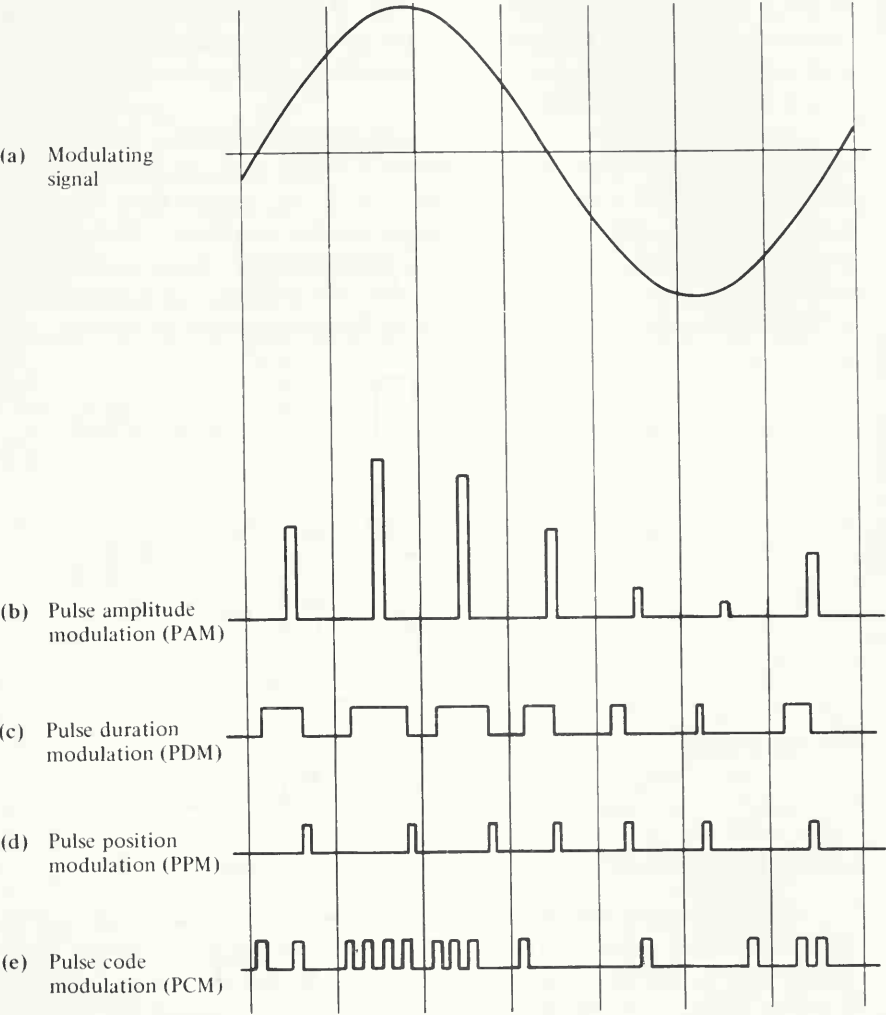


FIGURE 14-1. Types of pulse modulation.

circumstances, it may be the only type of pulse modulation that can be employed. In PCM, each amplitude sample of the original modulating signal is converted to a *binary number* (see Chapter 12). The binary number is then represented by a group of pulses, the presence of a pulse indicating 1 and the absence of a pulse indicating 0. The *four-bit* code illustrated in Figure 14-1(e) can represent only sixteen discrete levels of signal amplitude. Thus it is far from accurate. Accuracy can be improved by increasing the number of *bits* (i.e., pulses) employed. A seven-bit code, for example, can represent 128 discrete levels of signal ampli-

tude, or to an accuracy of better than 1%. The process of converting the signal to standard amplitudes which are to be represented by the binary code is termed *quantizing*, and the error introduced by this process is referred to as the *quantizing error*.

For all four pulse modulation methods the sampling frequency is determined by the highest signal frequency that must be processed. It can be shown that if samples are taken at a rate greater than twice the signal frequency, then the original signal can be recovered. However, in practice it is normal to sample at a minimum rate of about ten times the highest signal frequency. For audio, voice transmission, for example, with a “high” frequency of 3 kHz, the sampling frequency might be 30 kHz.

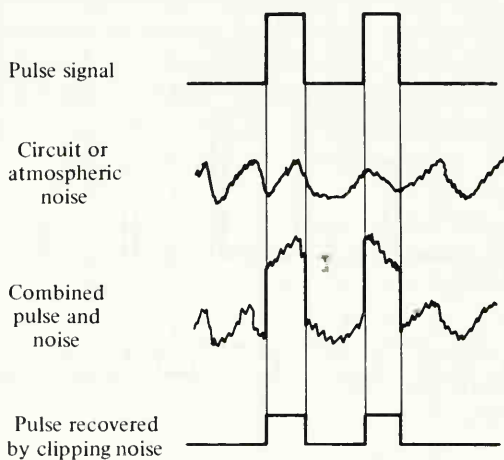


FIGURE 14-2. Effect of noise on pulse signals.

Another major advantage of pulse modulation is illustrated in Figure 14-2. When radio signals are very weak, they may be almost completely lost in circuit or atmospheric noise. If the modulation method is PDM, PPM, or PCM, the signals can be recovered simply by clipping off the noise. For this, PCM gives the best results, since it is only necessary to determine whether each pulse is present or absent.

In the following sections, modulation and demodulation methods are explained for PAM, PDM, and PPM. Before PCM techniques can be understood, *time division multiplexing* methods must be studied.

14-2 PAM MODULATION AND DEMODULATION

A process for producing a pulse amplitude modulated waveform is illustrated in Figure 14-3. The block diagram of Figure 14-3(a) shows a pulse

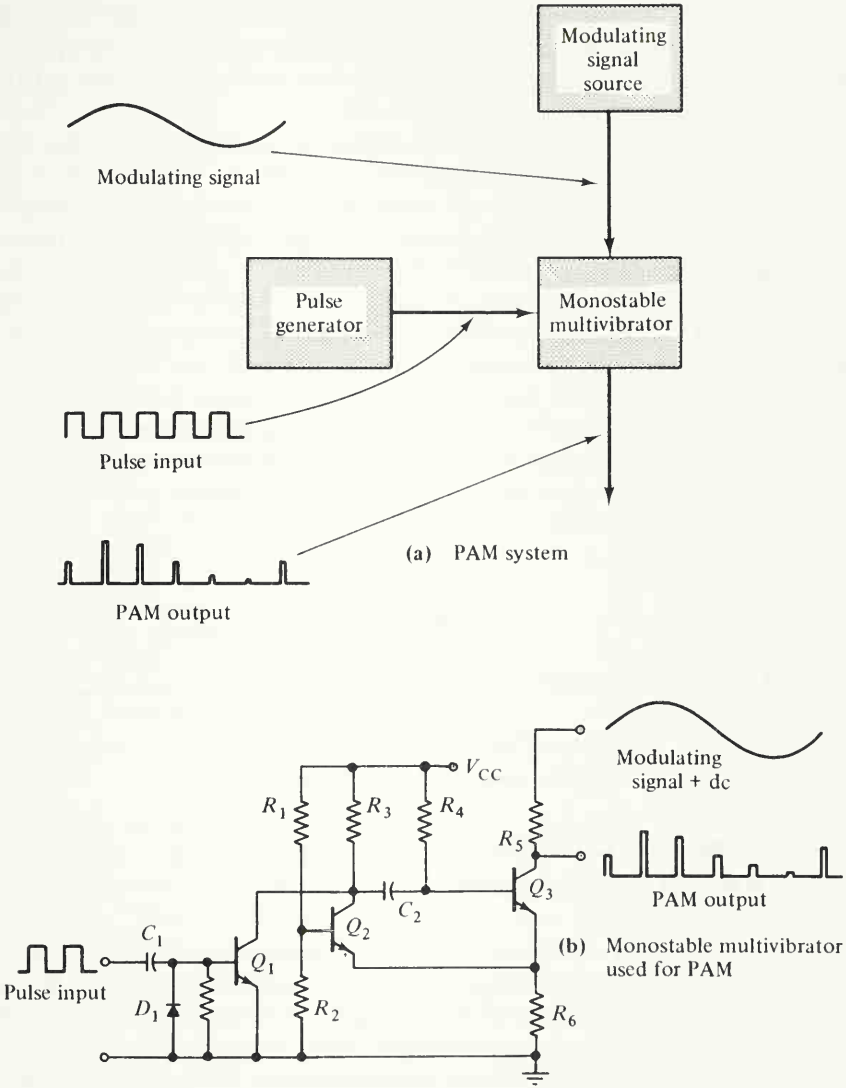


FIGURE 14-3. PAM modulating system and use of a monostable multivibrator for PAM.

generator triggering a monostable multivibrator at a sampling frequency. The output pulses from the multivibrator are made to increase and decrease in amplitude by the modulating signal. Figure 14-3(b) shows the circuit of a monostable multivibrator (Chapter 8) with its load resistance R_5 supplied from the modulating signal source. When Q_3 is *on*, the output voltage is the saturation level of Q_3 collector. When Q_3 is switched *off*

for the pulse time, the output voltage (*i.e.*, the pulse amplitude) is equal to the modulating signal level. The actual voltage applied as a supply to R_3 must have a dc component as well as the ac modulating signal. This is necessary to ensure correct operation of Q_3 .

Demodulation of PAM is accomplished simply by passing the amplitude-modulated pulses through a low-pass filter. This process is illustrated in Figure 14-4. The PAM waveform consists of the fundamental modulating frequency, and a number of high-frequency components which give the pulses their shape. The resistance R_1 and capacitance C_1 shown in Figure 14-4 form a potential divider. At low frequencies, the impedance of C_1 is very much larger than R_1 . Consequently, low-frequency signals (*i.e.*, the fundamental) are passed with very little attenuation. At high frequencies, the impedance of C_1 becomes quite small, and the signals experience severe attenuation. Thus, the filter output is the signal frequency, with perhaps a very small pulse frequency component. If necessary, more than one stage of filtering can be employed to remove the pulse frequency completely.

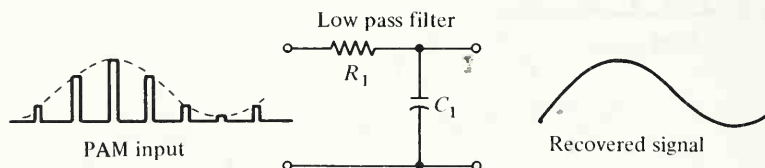


FIGURE 14-4. PAM demodulation.

14-3 PDM MODULATION AND DEMODULATION

In pulse duration modulation, the signal samples must be converted to pulses which have a time duration directly proportional to the amplitude of the samples. One method of producing PDM, shown in Figure 14-5, uses a free-running ramp generator and a *voltage comparator*.

The output voltage from a voltage comparator changes rapidly from one level to another, when the input voltage arrives at a predetermined level. In this respect, the voltage comparator is similar to a Schmitt trigger circuit. Unlike a Schmitt circuit, the voltage comparator has two input terminals. The change in output occurs at the instant that the voltages applied to the two inputs become equal. The two input voltages are *compared*, hence the name *comparator*.

Consider the voltage comparator circuit and inputs shown in Figure 14-5. Transistors Q_1 and Q_2 are emitter-coupled, and Q_1 normally is biased *on* via potential divider (R_1 and R_2). The modulating signal is

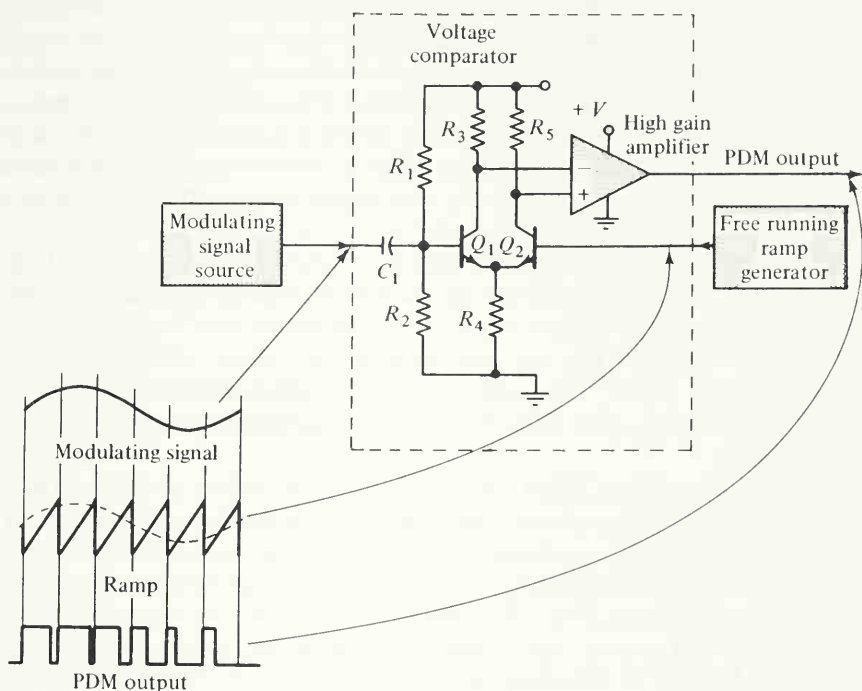


FIGURE 14-5. PDM modulating system.

capacitor-coupled via C_1 to the base of Q_1 . Thus, the voltage at the base of Q_1 is a dc level with the ac signal superimposed. The free-running ramp generator produces a ramp waveform output at the desired sampling frequency. This is directly coupled to the base of Q_2 . When the ramp waveform is at its zero level, Q_2 base is biased below Q_1 base. Thus, Q_2 is *off* and Q_1 is *on*, and the input to the amplifier inverting terminal is *low*, while that at the noninverting terminal is *high*. In this condition, the amplifier output is at its extreme positive voltage. The ramp voltage grows linearly and it eventually becomes equal to the voltage at the base of Q_1 . Now, Q_2 commences to switch *on* and, as it does so, Q_1 begins to switch *off*. This causes the voltage to rise at the inverting input terminal of the amplifier, and to fall at the noninverting terminal. Consequently, the amplifier output rapidly switches from its extreme positive level to its extreme negative level, which is ground level in the circuit shown. When the ramp waveform returns to zero, the circuit conditions revert to Q_1 *on* and Q_2 *off*, and the amplifier output returns to its extreme positive level.

It is seen that the output from the comparator is a series of positive

pulses. Each pulse commences at the instant the ramp waveform returns to zero volts, and ends when the ramp level coincides with the signal voltage. When the signal is at its highest level, the ramp takes its longest time to reach equality with Q_1 base voltage. Therefore, the output pulses at this time are of the longest duration. At the instant that the signal is at its lowest level, the ramp takes the shortest time to arrive at the same voltage as Q_2 base. Consequently, the width of the output pulses is a minimum at this instant.

An IC operational amplifier can be employed directly as a voltage comparator without the use of the additional transistors shown in Figure 14-5. IC voltage comparators are also available with built-in positive feedback to produce very fast switching of the output voltage from one extreme to the other. One such IC comparator is the $\mu A710$ manufactured by Fairchild. The data sheet for the $\mu A710$ can be found in Appendix 1-20.

Demodulation of PDM waves can be accomplished by first converting each duration-modulated pulse into an amplitude-modulated pulse. Then, filtering can be employed to recover the original modulating signal. The block diagram and waveforms for such a PDM demodulation system are shown in Figure 14-6. The PDM wave is applied to an integrator which generates a ramp-type output. The integrator output ramp always increases linearly at the same rate (*i.e.*, for constant amplitude pulses). The ramp commences at the start of each input pulse and finishes at the end of the pulse. Consequently, the ramp peak value is proportional to

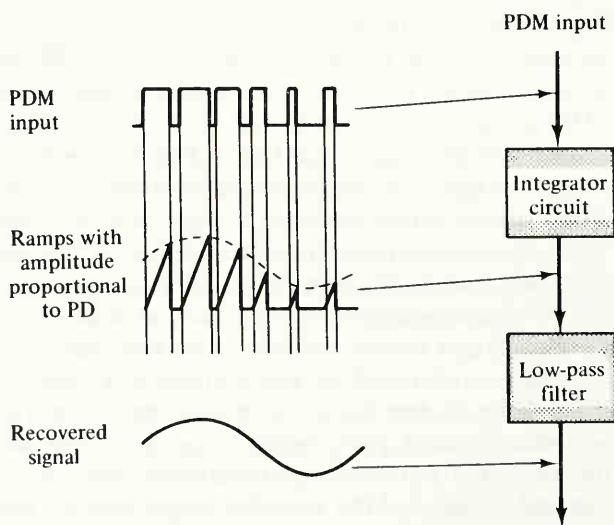


FIGURE 14-6. PDM demodulating system.

the pulse width. Since the pulse widths are made proportional to the instantaneous samples of the original signal voltage, the ramp peaks represent amplitude samples of the original signal. The integrator output waveform now is fed to the low-pass filter, which removes the high-frequency components and passes the low-frequency signal waveform.

A Miller integrator circuit (Figure 7-13) is suitable for use with the PDM demodulation system described above. The circuit, as shown, requires negative input pulses. Thus the positive PDM waveform in Figure 14-6 would first have to be passed through an inverter circuit [e.g., Figures 5-10(b) or (c)] before being applied to the integrator.

14-4 PPM MODULATION AND DEMODULATION

The simplest form of modulation process for pulse position modulation is a PDM system with the addition of a monostable multivibrator (see Figure 14-7). The monostable is arranged so that it is triggered by the trailing edges of the PDM pulses. Thus, the monostable output is a series of constant-width constant-amplitude pulses which vary in position according to the original signal amplitude.

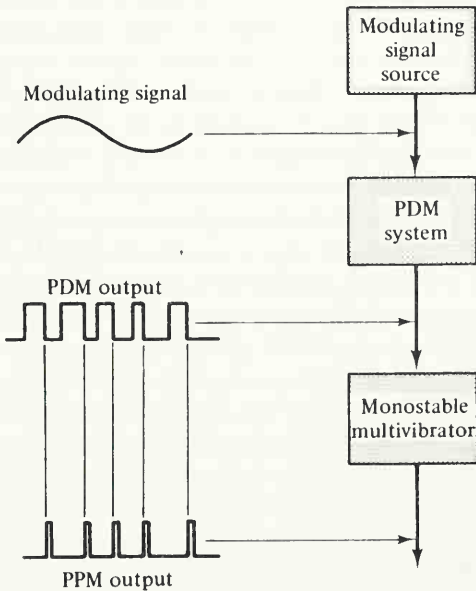


FIGURE 14-7. PPM modulating system.

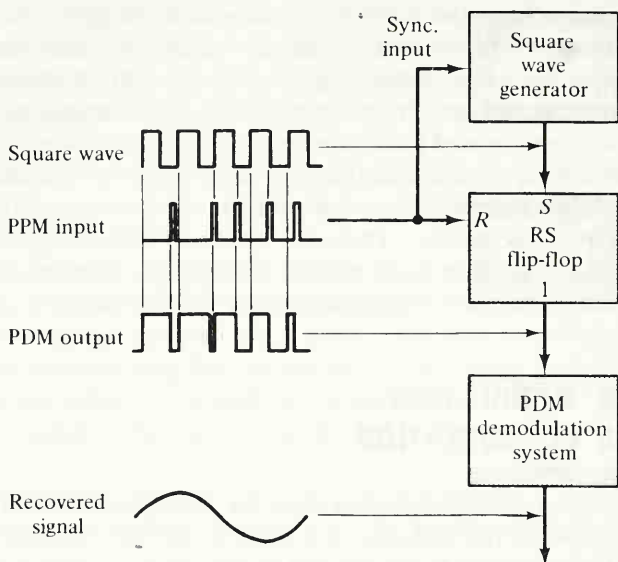


FIGURE 14-8. PPM demodulation.

For demodulation of PPM, a PDM waveform is first constructed by triggering an *RS flip-flop*, as shown in Figure 14-8. The flip-flop is triggered into its *set* condition by the leading edges of a square wave which must be synchronized with the original signal source. Synchronization is necessary so that the leading edges of the square wave coincide with the leading edges of the PDM wave that was employed to generate the PPM pulses (Figure 14-7). The flip-flop in Figure 14-8 is *reset* by the leading edge of the PPM pulses. The output of the flip-flop is now a PDM wave which may be demodulated by the process illustrated in Figure 14-6.

One of the most difficult requirements for PPM demodulation is synchronization of the square wave for triggering the flip-flop. Several alternatives are available. PPM pulses may be generated at both the leading and lagging edges of the PDM waveform in Figure 14-7. For demodulation, the leading edge pulses are applied to the *set* terminal of the RS flip-flop. In this case, a square wave generator is not required. However, some method of identifying the leading edge pulses must be employed. A more efficient system is to include periodic synchronizing pulses. For example, every fiftieth pulse might be a synchronizing pulse which corrects any frequency drift in the square wave generator. Again, some means of identifying the synchronizing pulses is essential. This could be done by making all synchronizing pulses negative while the other pulses are positive. Alternatively, the synchronizing pulses could be made larger or wider than the other PPM pulses. Perhaps the best method of

identifying a synchronizing pulse is to precede it with a longer-than-normal space. Methods for generating such a space during the modulation process and for identifying it during demodulation are similar to those employed in *time division multiplexing*, the subject of the next section.

14-5 TIME DIVISION MULTIPLEXING

14-5.1 TDM Waveforms

Suppose a 2.5 kHz signal is sampled ten times in every cycle. The samples occur at time intervals of one-tenth of the time period of the waveform, that is, at $40\mu\text{s}$ intervals. If PDM is employed, and the maximum pulse width is made less than $10\mu\text{s}$, a $30\mu\text{s}$ time interval (or space) is left between pulses. If other signals are sampled at the same rate, the additional pulse samples might be included in the $30\mu\text{s}$ space. This process, known as *time division multiplexing*, (TDM) is illustrated in Figure 14-9.

Channel 1 in Figure 14-9 is a series of PDM samples, with the first pulse shown commencing at time t_1 . Channel 2 is another series of PDM pulses with the first pulse shown commencing at t_2 , $10\mu\text{s}$ after t_1 . The second pulse in channel 2 occurs $40\mu\text{s}$ after t_2 ($10\mu\text{s}$ after t_3). For channel 3, the first pulse shown starts at t_3 , which is $20\mu\text{s}$ after t_1 and $10\mu\text{s}$ after t_2 . As in the case of the other channels, there is a $40\mu\text{s}$ time interval between commencement of each pulse in channel 3. When the pulses are time-multiplexed, as shown in Figure 14-9(d), three channels of information are contained in the waveform. This waveform now may be recorded on a single magnetic track, transmitted on a single radio frequency, or otherwise processed.

Each channel in the time-multiplexed waveform [Figure 14-9(d)] is allocated a $10\mu\text{s}$ time period. Therefore, the maximum pulse width must be less than $10\mu\text{s}$, so that the end of one pulse can be distinguished from the beginning of the next. At each sampling, the three channels occupy a total time period of $30\mu\text{s}$. This leaves a $10\mu\text{s}$ time interval, or one unoccupied channel space, between the end of the three pulses and commencement of the next three. This time period is deliberately left clear so that it may be used for synchronization in the demodulation process. Channel 1 can easily be identified (during demodulation) as the first information pulse after the *sync. space*. Channels 2 and 3 can then be identified in sequence after channel 1. The series of three (or more) information pulses together with the synchronizing space usually is termed *one frame* of the TDM waveform.

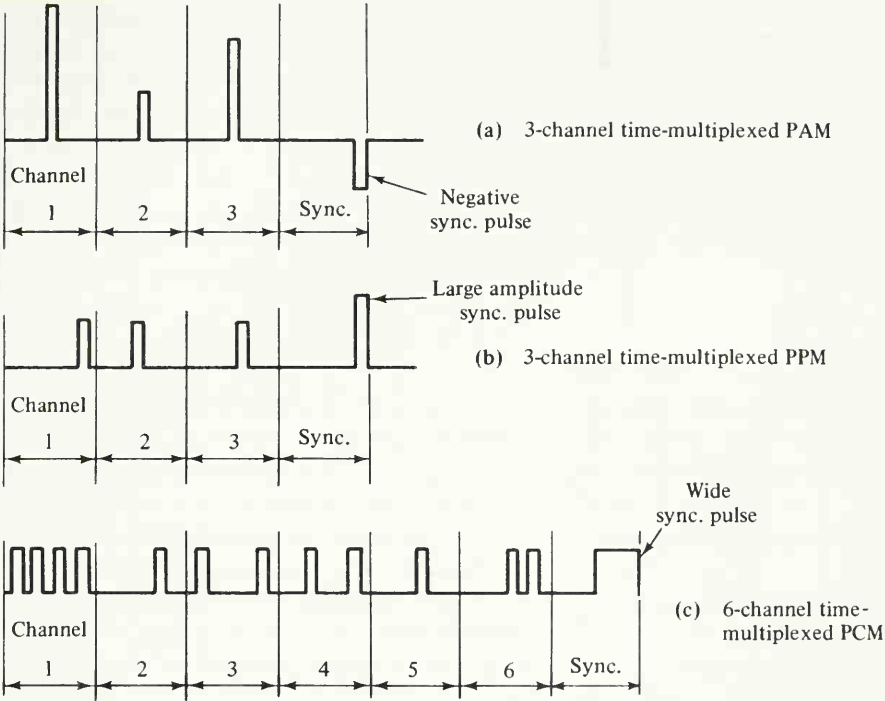


FIGURE 14-10. Time division multiplexed waveforms for PAM, PPM, and PCM.

14-5.2 Ring Counter

A *ring counter* is the circuit employed in a TDM coding system to select the signals to be sampled in the correct repetitive sequence. Triggered by input pulses, the circuit switches through a number of states equal to one more than the number of TDM channels. For a three-channel system, the ring counter must have four states, that is, three channels plus the synchronizing space. Ring counters usually are constructed of flip-flops and diode gates. The binary-to-decimal conversion system shown in Figure 12-15 could be employed as a ten-state ring counter. In this case, the outputs (to the transistor gates) would control nine signal channels and a synchronizing space.

Figure 14-11 shows a four-state ring counter made up of two flip-flops and a diode matrix. The operation of the circuit is similar to the binary-to-decimal conversion system explained in Chapter 12. In the initial condition, Q_1 and Q_3 are *off*, and the output voltage at their collectors is *high* and is represented as logic 1. Q_2 and Q_4 are *on*, so their *low*

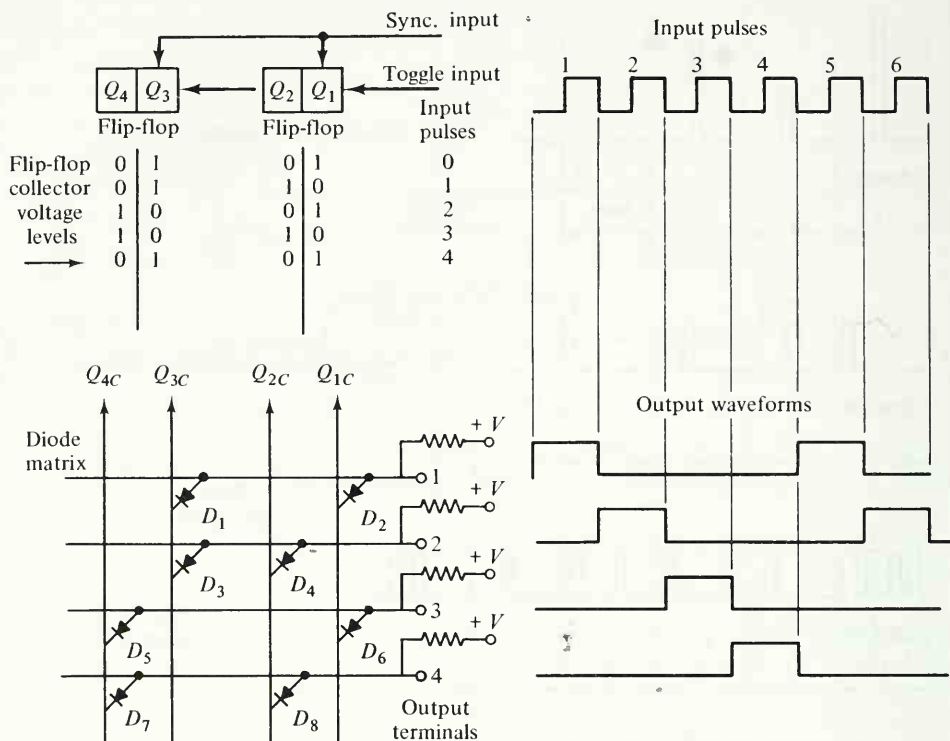


FIGURE 14-11. Flip-flop and diode matrix as four-state ring counter.

collector voltage level is represented as logic 0. This means that the voltage levels at the cathodes of D_1 and D_2 are *high*, and that the output of terminal 1 is *high*. All other output terminals have at least one diode biased *on*, holding the output voltage *low*. When the first toggle pulse is applied, the states of the flip-flops change to Q_4 *on*, Q_3 *off*, Q_2 *off*, Q_1 *on*. The cathode of D_2 has a low voltage applied so that the output of terminal 1 is *low*. Also D_3 and D_4 have *high* voltages at their cathodes, which produces a *high* output at terminal 2. While the input count remains at 1, diodes D_5 , D_6 , and D_7 have *low* cathode voltages and thus terminals 3 and 4 are *low*. Continuing through input pulse counts 2 and 3, it is seen that output terminals 3 and 4 switch *high* in turn, while all other outputs become *low*. After the count of four, the next input pulse switches the circuit back to *high* at output terminal 1. Then the sequence is repeated. The *ring counter* derives its name from the fact that it toggles in a repetitive or *ring* sequence from *state 1* to *state 4* and back through *state 1* again for the four-stage ring counter. A synchronizing input terminal also can be

provided as was explained in Chapter 12, so that a *sync. pulse* can set the circuit in its initial state.

The voltage waveforms in Figure 14-11 help to illustrate the operation of the ring counter. It is seen that in the initial state, only output terminal 1 is *high*. When the first toggle pulse is applied, output terminal 2 becomes *high*, and 1 becomes *low*. The third and fourth toggle pulses, respectively, switch outputs 3 and 4 to *high*, while all others go to *low*. On receipt of the fifth pulse, output 1 becomes *high* again, and the sequence is repeated as the input pulses continue.

14-5.3 TDM Coding System

The block diagram and waveforms for the time-multiplexing of three signals is shown in Figure 14-12. A time division multiplexing system usually is referred to as a *TDM coding system*. The system for separating the waveform into individual channels is termed a *TDM decoding system*. If pulse modulation is performed concurrently with time-multiplexing, a single modulation system can be used for all channels.

In Figure 14-12, a clock generator produces a square waveform to toggle the ring counter at the desired frequency. The ring counter outputs switch the sampling gates *on* and *off* in the correct sequence. (Sampling gates are discussed in Chapter 11.) When one output from the ring counter is *high*, all others are *low*. Thus, one sampling gate is *on*, and all others are *off*. The time periods during which a sampling gate is in the *on* and *off* states is determined by the clock generator frequency and the number of channels. For example, if the clock generator output is a 1 kHz square wave, each gate is *on* for 1 ms. For the three-channel system shown, the gates are *off* for three time periods of the clock generator (*i.e.*, for 3 ms).

Each signal to be sampled is applied to the input terminal of a sampling gate. The input of gate 0, the synchronizing gate, is grounded, so that during the *sync.* time its output is zero volts. The output of all four gates is "commoned." Thus, as each gate switches *on* in turn, amplitude samples of the signal waveforms are time-multiplexed into a single waveform. The combined output of the gates (see Figure 14-12) is in the form of a pulse-amplitude-modulated waveform with no spaces between pulses, and with a *sync.* space at the end of each set of samples.

The waveform from the gates is converted to PDM by applying it to one input of a voltage comparator. The other input terminal of the comparator has a ramp generator output applied to it, as shown in Figure 14-12. The ramp generator has a linear output and is triggered by the negative-going edges of the clock generator output, so that the ramp commences at the beginning of the output from each sampling gate. The

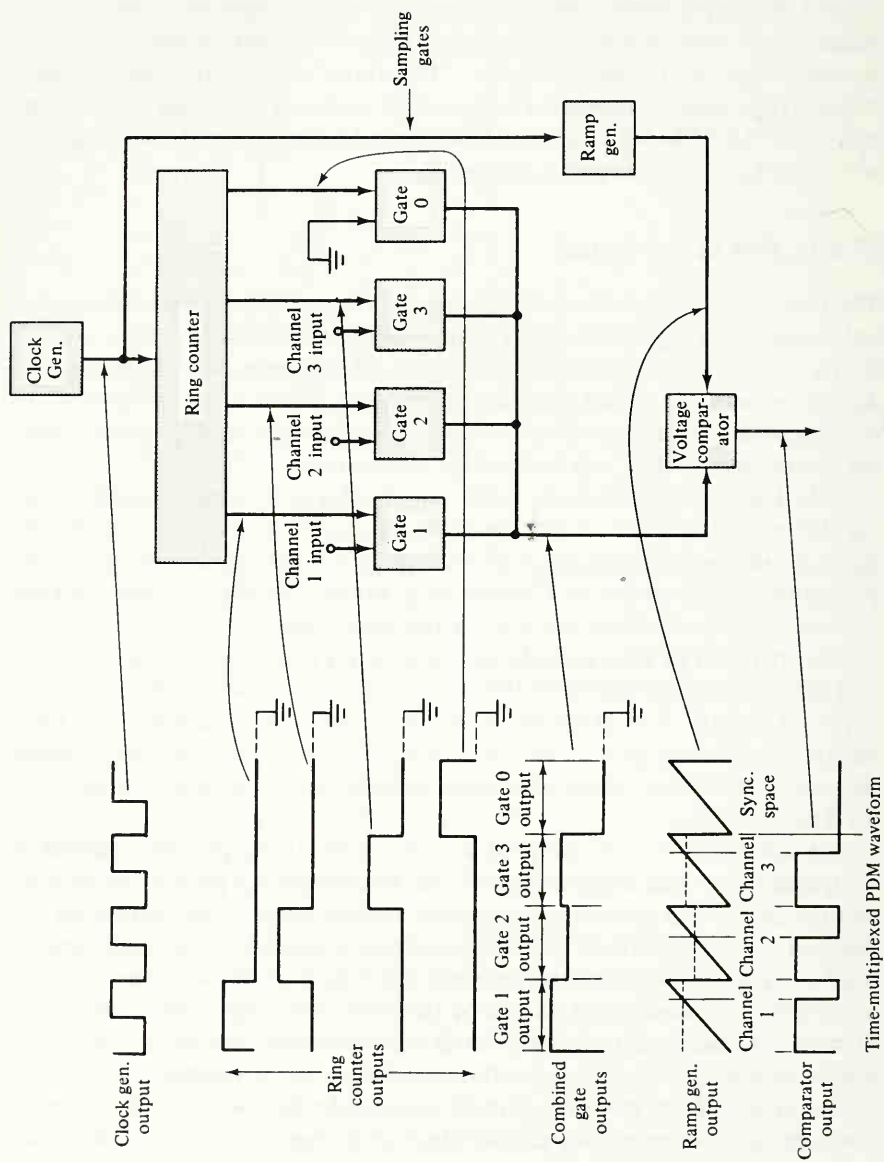


FIGURE 14-12. Three-channel time division multiplexing and pulse duration modulation system.

voltage comparator output becomes high when the ramp output becomes zero. When the ramp amplitude is equal to the amplitude of the signal being sampled, the comparator output goes to zero. (The process of converting amplitude samples to PDM was explained in Sec. 14-3.) During the sync. space, the comparator input (from the gates) remains at zero; thus the output level from the comparator does not switch positively when the ramp goes to zero. The output waveform from the system is seen to be time-multiplexed duration-modulated pulses with intervening sync. spaces.

14-5.4 TDM Decoding System

Before demodulation, time-multiplexed signals must be *decoded*, or separated into individual channels. Figure 14-13 shows the block diagram and waveforms of a system for decoding three-channel time-multiplexed PDM signals.

The waveform to be decoded is applied simultaneously to an integrator circuit, the toggle input of a ring counter, and to one input on each of three *AND* gates. The function of the integrator, and the Schmitt trigger circuit which follows it, is to detect the sync. space in the TDM waveform. A suitable integrator circuit for this situation is the ramp generator shown in Figure 7-3(b). During the time that the input pulses are applied, the ramp generator output remains at zero. When the pulses are absent the ramp output grows linearly, then rapidly returns to zero again at commencement of the next input pulse. Thus, the integrator output is a series of small ramps generated during the space time. During the synchronizing space, the integrator generates a larger-than-usual output. When this output arrives at the upper trigger point of the Schmitt circuit, the Schmitt produces an output pulse which sets the ring counter to its synchronized state. The next input pulse (*i.e.*, from channel 1) toggles the ring counter to its channel 1 state.

In the channel 1 state, the ring counter provides a positive output to *AND* gate 1, and a zero output to gates 2 and 3. At this time, channel 1 pulse is present at one input of all three *AND* gates. Only gate 1 has a positive voltage at both input terminals. Therefore, only gate 1 produces an output during the application of the pulse from channel 1. The output pulse from gate 1 commences at the beginning of channel 1, and ends at the end of the channel 1 PDM pulse. At the commencement of channel 2 (*i.e.*, on receipt of the next positive-going pulse edge) the ring counter toggles to its channel 2 state. Therefore, *AND* gate 2 now has positive voltage levels at both input terminals, while *AND* gates 1 and 3 have zero levels applied from the ring counter. Thus, gate 2 produces the channel 2

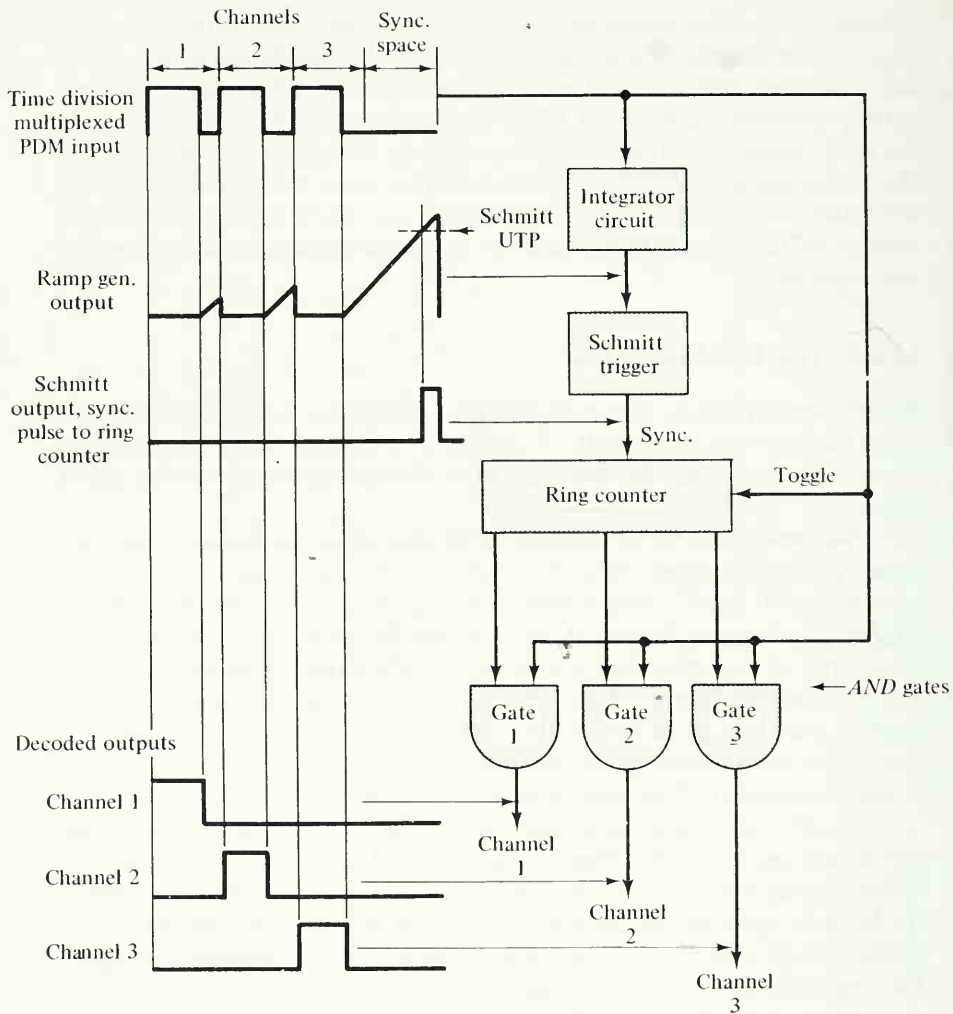


FIGURE 14-13. Decoding system for three-channel time-multiplexed PDM signals.

PDM pulse at its output terminals. Similarly, at commencement of channel 3, the ring counter toggles to its channel 3 state. *AND* gate 3 output then becomes positive for the duration of the PDM pulse in the channel 3 portion of the input waveform. It is seen that the decoding system separates the TDM wave into the individual channels. Now, each channel can be demodulated to recover the original modulating signals.

14-6 PCM MODULATION AND DEMODULATION

14-6.1 PCM Modulation System

PCM signals are essentially time division multiplexed pulses; therefore, modulation and demodulation techniques for PCM are similar to TDM methods. The block diagram of a PCM modulation system is shown in Figure 14-14, and the waveforms for the system are illustrated in Figure 14-15.

The PCM system in Figure 14-14 employs a *shift register*. This is simply a cascade of flip-flops similar to the arrangement illustrated in Figures 12-1 and 12-2. The shift register is toggled by input pulses, and counts the pulses in binary form. An output is taken from one collector of

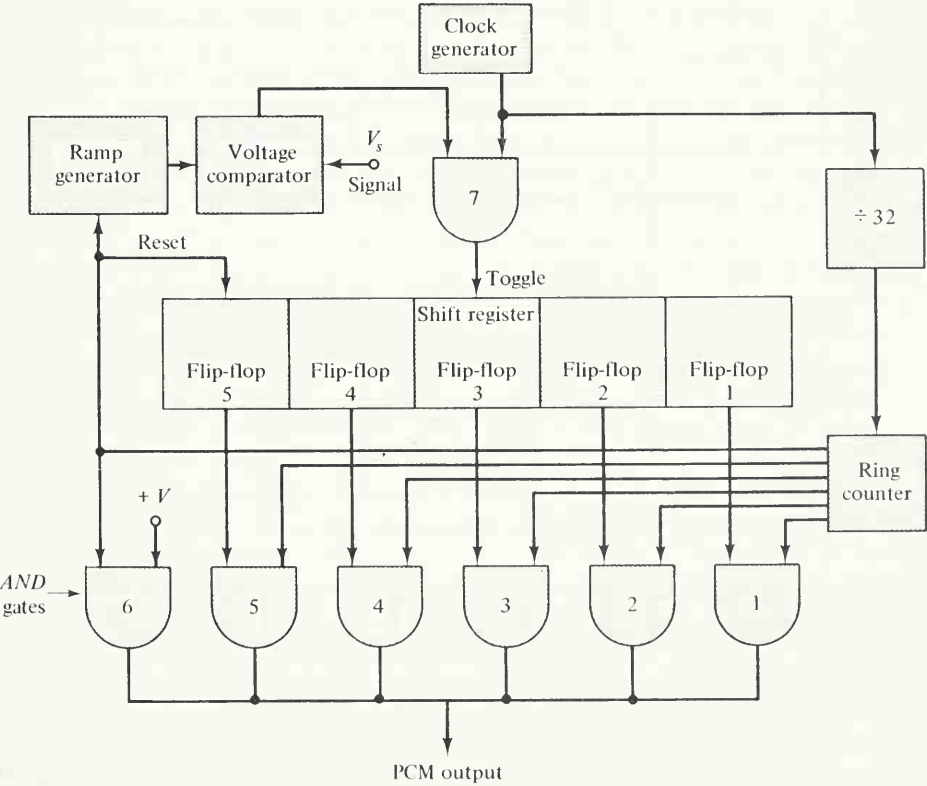


FIGURE 14-14. PCM modulating system.

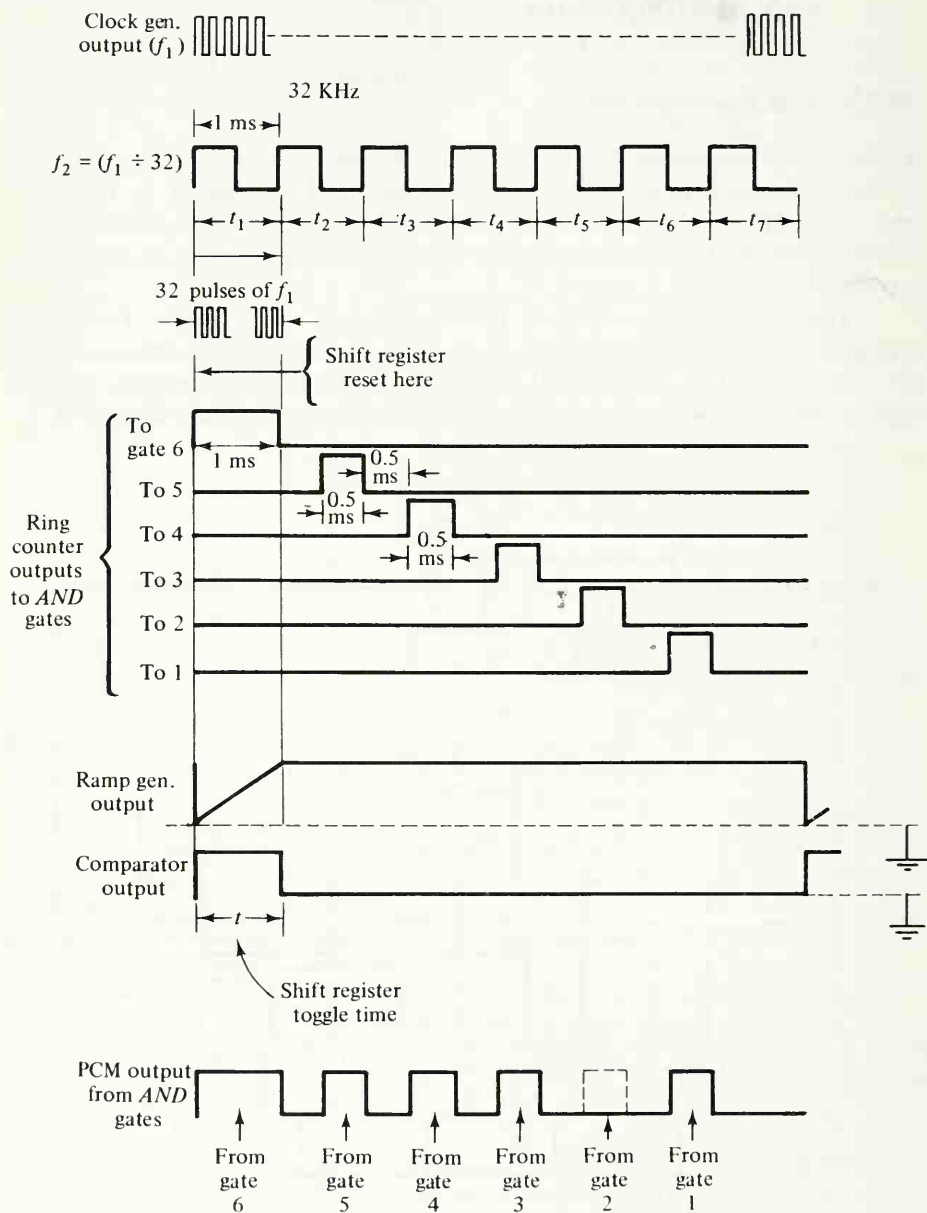


FIGURE 14-15. Waveforms for PCM modulating system.

each flip-flop. The five-stage shift register can count to binary 11111, which is equivalent to decimal 31.

The input signal voltage which is to be converted to PCM is applied to one input of a voltage comparator, and a ramp generator output is applied to the other input of the comparator. This is similar to the PDM method, in which the signal amplitude sample is converted to a time period. In Figure 14-15, the comparator output is shown as having a time duration t . To convert this time period to a five-bit binary number, the shift register is toggled by the clock generator during the time period. Once the shift register has settled at the binary equivalent of the signal sample, the ring counter is triggered to *read* the state of the shift register and produce a PCM output.

Suppose the clock generator frequency f_1 is 32 kHz. This frequency is divided by a factor of 32 to produce $f_2 = (f_1/32) = 1$ kHz (see Figure 14-15). (Frequency dividing techniques are discussed in Chapter 13.) The time period of f_2 is 1 ms, and this is used to trigger the ring counter. As shown by the waveforms in Figure 14-15, the ring counter provides a 1 ms pulse to *AND* gate 6. This pulse also goes to the ramp generator and to the *reset* input terminal of the shift register. Therefore, at commencement of time period t_1 (Figure 14-15) the shift register is set to its zero condition, and the ramp generator output is triggered from its maximum output voltage level to zero. When the ramp generator output becomes zero, it causes the output of the voltage comparator to switch from zero to its maximum voltage level. Thus, the input (from the comparator) to *AND* gate 7 is positive, and the clock generator pulses pass through to toggle the shift register.

At the commencement of time period t_1 , the ramp voltage also starts to grow linearly from the zero level. When the ramp amplitude becomes equal to the instantaneous amplitude of the signal voltage V_s , the comparator output switches to zero once again. This means that no more clock generator pulses can pass through *AND* gate 7. At this time, the state of the shift register represents the binary equivalent of the signal voltage amplitude. Since no more toggle pulses arrive, the shift register state remains constant.

The 1 ms ring counter output pulse that is applied to the ramp generator during time t_1 is also applied to *AND* gate 6. Since the other input to the gate is at $+V$, the output of gate 6 is a positive 1 ms pulse. During time period t_2 , the ring counter provides a 0.5 ms pulse to *AND* gate 5. The other input to *AND* gate 5 is derived from FF5 in the shift register. If the output of FF5 is *high*, gate 5 produces a 0.5 ms output pulse, as shown. If the flip-flop output is *low*, there is no pulse present at this point in the PCM output waveform. Through time periods t_3 , t_4 , t_5 , and t_6 , the ring counter switches *on* gates 4, 3, 2, and 1, respectively, to sample the shift register voltage levels at each flip-flop. Thus the PCM output wave-

form is produced with pulses that represent the binary equivalent of the signal sample as measured during t_1 . At the end of t_6 , a gap (t_7) is generated by the ring counter holding gates 1 to 6 *off*, then the long synchronizing pulse t_1 commences again, and the sampling and coding process is repeated.

14-6.2 PCM Decoding and Demodulation System


For decoding and demodulation, PCM signals are first processed through a TDM decoding system to separate the bits into different channels. The process, illustrated in Figure 14-16(a), shows a TDM decoding system with five output channels for a five-bit PCM system. Several techniques are available for converting the decoded PCM back to analog voltage samples. The method illustrated is termed *digital-to-analog conversion by weighted resistors*. The operational amplifier, connected as shown, is termed a *summing amplifier*.

In Figure 14-16(b) it may be seen that each pulse in a five-bit PCM code has a binary and a decimal equivalent. The decimal equivalent of bit 5 is 16 and that of bit 4 is 8, etc. The resistors R_1 to R_5 are *weighted* (or selected) to have values inversely proportional to the decimal equivalent of the bit number applied to them. Thus, if $R_1 = 16\text{ k}\Omega$ for bit 1 which has a decimal equivalent of 1, then $R_5 = 1\text{ k}\Omega$ for bit 5 with a decimal equivalent of 16. Similarly, $R_2 = 8\text{ k}\Omega$ for bit 2 (the decimal equivalent is 2), and $R_4 = 2\text{ k}\Omega$ for bit 4 (the decimal equivalent is 8). Note also that $R_6 = 1.6\text{ k}\Omega$.

Consider the effect on the summing amplifier when bit 5 is present, and all other bits are absent. Let the amplitude of all bits be $V = 1\text{ V}$. Recall, from the previous study of operational amplifiers in Chapters 5, 6, and 7, that with the noninverting terminal grounded the inverting terminal is always very close to ground potential. Therefore, with the input voltage applied at one end of R_5 and a *virtual ground* at the other end, the amplifier input current is

$$I = \frac{V_i}{R_5}$$

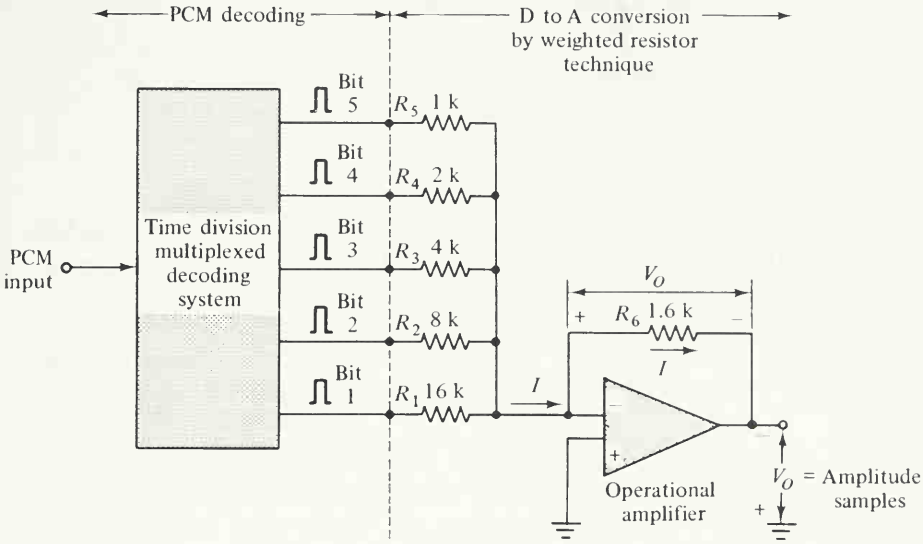Also in previous studies it was shown that the actual current flow into the amplifier terminal is near zero. Consequently, all of the input current effectively flows through R_6 . Since one end of R_6 is at the virtual ground input terminal and the other end is at the output terminal, the out-



(a) PCM decoding and demodulation

	Binary number represented by bits	Decimal equivalent
Bit 5	1 0 0 0 0	16
Bit 4	1 0 0 0	8
Bit 3	1 0 0	4
Bit 2	1 0	2
Bit 1	1	1

(b) Binary and decimal equivalents of bits in 5-bit PCM

FIGURE 14-16. PCM decoding and demodulation system.

put voltage is the voltage drop across R_6 . Thus, the output voltage is

$$\begin{aligned} V_o &= IR_6 = V_i \times (R_6/R_5) \\ &= 1 \text{ V} \times (1.6 \text{ k}\Omega/1 \text{ k}\Omega) \\ &= 1.6 \text{ V} \end{aligned}$$

Thus, bit 5 is converted to 1.6 V and since the decimal equivalent of bit 5 is 16, this seems to make sense.

When only bit 1 is present, the output becomes

$$\begin{aligned} V_o &= V_i \times (R_6/R_1) \\ &= 1 \text{ V} \times (1.6 \text{ k}\Omega/16 \text{ k}\Omega) \\ &= 0.1 \text{ V} \end{aligned}$$

This is one-sixteenth of the output produced from bit 5. Thus the two outputs are in correct proportion, since bit 5 has a decimal equivalent of 16, and bit 1 has a decimal equivalent of 1.

The combined output produced when bits 5 and 1 are present is

$$\begin{aligned} V_o &= V_i(R_6/R_5) + V_i(R_6/R_1) \\ &= V_i R_6 \times (1/R_5 + 1/R_1) \\ &= 1 \text{ V} \times 1.6 \text{ k}\Omega \times (1/1 \text{ k}\Omega + 1/16 \text{ k}\Omega) \\ &= 1.7 \text{ V} \end{aligned}$$

The decimal equivalent of 10001 (*i.e.*, bit 5 and bit 1) is 17, therefore the *summing amplifier* has summed the bits and converted the input voltages from digital form to analog form. Any combination of input bits may be considered, and the summing amplifier output calculated. It is always found that the amplifier output is directly proportional to the decimal equivalent of the binary number represented by the bits. After conversion to amplitude samples, low-pass filtering can be employed to recover the original signal. Note that the output voltage samples from the summing amplifier are negative. These can be converted to positive voltage levels by the use of another inverting amplifier.

REVIEW QUESTIONS AND PROBLEMS

- 14-1 Sketch waveforms to illustrate the various types of pulse modulation. Identify and briefly explain each type of modulation.
- 14-2 Discuss the performance of the various types of pulse modulation with respect to noise.
- 14-3 Show how a monostable multivibrator may be employed for pulse amplitude modulation. Briefly explain.
- 14-4 Sketch a block diagram for a PAM modulating system. Show the waveforms, and explain the system.
- 14-5 Sketch and explain the process for demodulating PAM signals.
- 14-6 Draw a block diagram for a PDM modulating system. Show the

circuit of the voltage comparator, and the system waveforms. Explain the modulation process.

- 14-7** Sketch a system block diagram and waveform for demodulation of PDM signals. Explain the process.
- 14-8** Using illustrations, explain the process of producing a PPM waveform.
- 14-9** Explain the process of demodulating a PPM waveform. Sketch the appropriate block diagram and voltage waveforms. Also, discuss the *synchronizing* problem which occurs with PPM and state the possible solutions.
- 14-10** Explain *time division multiplexing* and discuss its advantages. Sketch waveforms for time-multiplexed signals using PAM, PDM, PPM, and PCM.
- 14-11** Draw a block diagram and diode circuit to show how three flip-flops and a diode matrix can be employed as an eight-state ring counter. Also sketch the input and output waveforms, and explain how the ring counter functions.
- 14-12** Draw a block diagram for a four-channel TDM system which includes pulse duration modulation. Show the waveforms throughout, and explain the operation of the system.
- 14-13** Draw a block diagram for a decoding system for four-channel time-multiplexed PDM signals. Show the system waveforms and explain the operation of the system.
- 14-14** A signal having a maximum frequency of 5 kHz is to be pulse-code-modulated with not more than 2% quantizing error. Determine the number of pulses required to represent each sample, and the number of samples required per second. Explain.
- 14-15** Draw a block diagram of a PCM modulating system that would be suitable for the waveform described in problem 14-14. Sketch appropriate waveforms and explain the system process.
- 14-16** Explain the process of decoding and demodulating a 5 bit PCM signal. Sketch the appropriate circuitry and identify the level of output for each input pulse.


Appendix 1

Data Sheets

**TYPES 1N914, 1N914A, 1N914B, 1N915,
1N916, 1N916A, 1N916B and 1N917
DIFFUSED SILICON SWITCHING DIODES**

- **Extremely Stable and Reliable High-Speed Diodes**

mechanical data

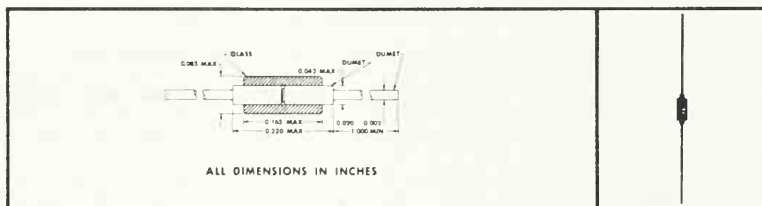

absolute maximum ratings at 25°C ambient temperature (unless otherwise noted)

[illegible]

maximum electrical characteristics at 25°C ambient temperature (unless otherwise noted)

BV_R	Min Breakdown Voltage at $100 \mu A$	100	100	100	65	100	100	100	40	v
I_R	Reverse Current at V_R	5	5	5	5	5	5	5		μA
I_R	Reverse Current at -20 v	0.025	0.025	0.025		0.025	0.025	0.025		μA
I_R	Reverse Current at -20 v at $100^\circ C$	3	3	3	5	3	3	3	25	μA
I_R	Reverse Current at -20 v at $+150^\circ C$	50	50	50		50	50	50		μA
I_R	Reverse Current at -10 v				0.025				0.05	μA
I_R	Reverse Current at -10 v at $125^\circ C$									μA
I_F	Min Fwd Current at $V_F = 1$ v	10	20	100	50	10	20	30	10	ma
V_F	at $250 \mu A$								0.64	v
V_F	at 1.5 ma								0.74	v
V_F	at 3.5 ma								0.83	v
V_F	at 5 ma			0.72	0.73			0.73		v
V_F	Min at 5 ma				0.60					v
C	Capacitance at $V_R = 0$	4	4	4	4	2	2	2	2.5	pf

operating characteristics at 25°C ambient temperature (unless otherwise noted)

[illegible]

* Trademark of Texas Instruments

* Lumatron (10 mo I_F , 10 mo I_R , recover to 1 mo)

•• EG&G (10 ma I_E , 6v V_B , recover to 1 ma)

APPENDIX 1-2*

1N4001 thru 1N4007

$I_O = 1\text{ A}$
 $V_R - \text{to } 1000\text{ V}$



Low-current, passivated silicon rectifiers in subminiature void-free, flame-proof silicone polymer case. Designed to operate under military environmental conditions.

CASE 59


MAXIMUM RATINGS (At 60 cps Sinusoidal, Input, Resistive or Inductive Load)

Rating	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage DC Blocking Voltage	$V_{RM(rep)}$ V_R	50	100	200	400	600	800	1000	Volts
RMS Reverse Voltage	V_r	35	70	140	280	420	560	700	Volts
Average Half-Wave Rectified Forward Current (75°C Ambient) (100°C Ambient)	I_O	1000 750	1000 750	1000 750	1000 750	1000 750	1000 750	1000 750	mA mA
Peak Surge Current 25°C (1/2 Cycle Surge, 60 cps)	$I_{FM(surge)}$	30	30	30	30	30	30	30	Amps
Peak Repetitive Forward Current	$I_{FM(rep)}$	10	10	10	10	10	10	10	Amps
Operating and Storage Temperature Range	T_J, T_{stg}	-65° to + 175							°C


ELECTRICAL CHARACTERISTICS

Characteristic	Symbol	Rating	Unit
Maximum Forward Voltage Drop (1 Amp Continuous DC, 25°C)	V_F	1.1	Volts
Maximum Full-Cycle Average Forward Voltage Drop (Rated Current @ 25°C)	$V_{F(AV)}$	0.8	Volts
Maximum Reverse Current @ Rated DC Voltage (25°C) (100°C)	I_R	0.01 0.05	mA
Maximum Full-Cycle Average Reverse Current (Max Rated PIV and Current, as Half-Wave Rectifier, Resistive Load, 100°C)	$I_{R(AV)}$	0.03	mA

TYPICAL FORWARD CHARACTERISTICS

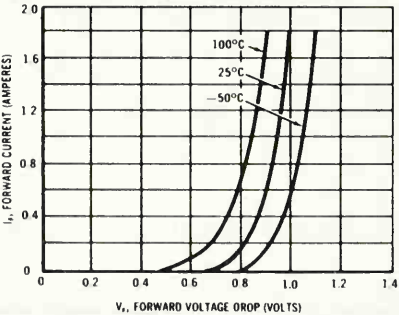

MAXIMUM DC OUTPUT

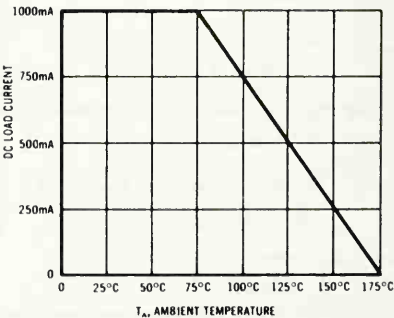

*Courtesy of Motorola, Inc.



TYPES 1N746 THRU 1N759, 1N746A THRU 1N759A
SILICON VOLTAGE REGULATOR DIODES


3.3 TO 12 VOLTS • 400 mw

GUARANTEED DYNAMIC ZENER IMPEDANCE

Available in 5% and 10% tolerances
-65 to 175°C operation & storage

mechanical data

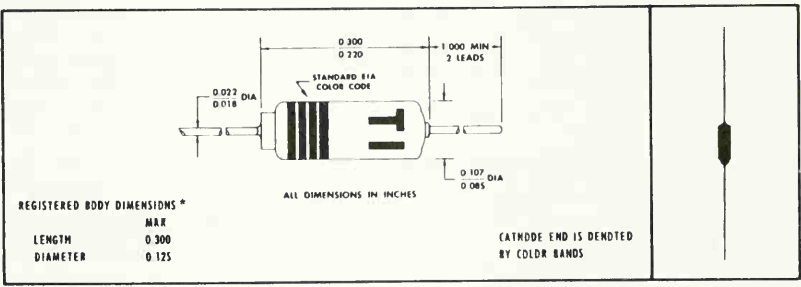The diode is encased in a hermetically sealed hard-glass package which falls within the JEDEC DO-7 outline. Unit weight is typically 0.195 gram.



*absolute maximum ratings

Average Rectified Forward Current at (or below) 25°C Free-Air Temperature	230 ma
Average Rectified Forward Current at 150°C Free-Air Temperature	85 ma
Continuous Power Dissipation at (or below) 50°C Free-Air Temperature	400 mw
Continuous Power Dissipation at 150°C Free-Air Temperature	100 mw
Operating Free-Air Temperature Range	-65°C to 175°C
Storage Temperature Range	-65°C to 175°C

*Indicates JEDEC registered data

*Courtesy of Texas Instruments, Incorporated


TYPES 1N746 THRU 1N759, 1N746A THRU 1N759A
SILICON VOLTAGE REGULATOR DIODES

*electrical characteristics at 25°C free-air temperature (unless otherwise noted)


PARAMETER	V _Z Zener Breakdown Voltage					α _Z Temperature Coefficient of Breakdown Voltage	Z _Z Small- Signal Breakdown Impedance	I _R Static Reverse Current	
TEST CONDITIONS	I _{ZT} = 20 ma					I _{ZT} = 20 ma	I _{ZT} = 20 ma, I _{Z1} = 1 ma	V _R = 1 v	V _R = 1 v, T _A = 150°C
LIMIT →	NOM	1N746-1N759 MIN MAX		1N746A-1N759A MIN MAX		TYP	MAX	MAX	MAX
UNIT →	v	v	v	v	v	%/°C	Ω	μa	μa
1N746	3.3	2.97	3.63	3.135	3.465	-0.062	28	10	30
1N747	3.6	3.24	3.96	3.420	3.780	-0.055	24	10	30
1N748	3.9	3.51	4.29	3.705	4.095	-0.049	23	10	30
1N749	4.3	3.87	4.73	4.085	4.515	-0.036	22	2	30
1N750	4.7	4.23	5.17	4.465	4.935	-0.018	19	2	30
1N751	5.1	4.59	5.61	4.845	5.355	-0.008	17	1	20
1N752	5.6	5.04	6.16	5.320	5.880	+0.006	11	1	20
1N753	6.2	5.58	6.82	5.890	6.510	+0.022	7	0.1	20
1N754	6.8	6.12	7.48	6.460	7.140	+0.035	5	0.1	20
1N755	7.5	6.75	8.25	7.125	7.875	+0.045	6	0.1	20
1N756	8.2	7.38	9.02	7.790	8.610	+0.052	8	0.1	20
1N757	9.1	8.19	10.01	8.645	9.555	+0.056	10	0.1	20
1N758	10.0	9.00	11.00	9.500	10.500	+0.050	17	0.1	20
1N759	12.0	10.80	13.20	11.400	12.600	+0.060	30	0.1	20

*Indicates JEDEC registered data


MAXIMUM POWER DISSIPATION

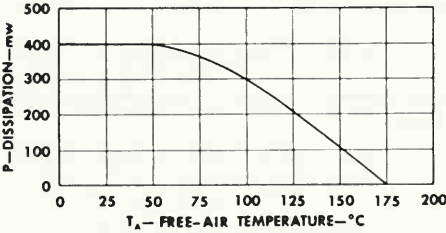

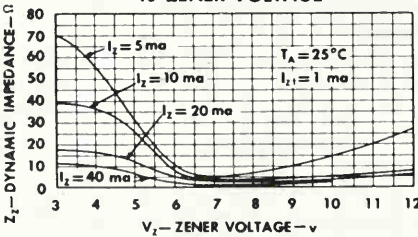TYPICAL DYNAMIC IMPEDANCE
vs ZENER VOLTAGE



TYPICAL
ZENER TEMPERATURE COEFFICIENT
vs ZENER VOLTAGE

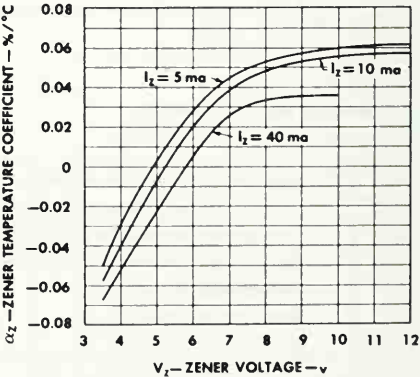


APPENDIX 1-4*

2N3903 (SILICON)
2N3904



$V_{CS} = 60\text{ V}$
 $I_C = 200\text{ mA}$
 $C_{ob} = 4.0\text{ pf (max)}$

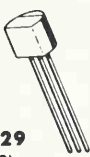

CASE 29
(TO-92)

NPN silicon annular transistors, designed for general purpose switching and amplifier applications, features one-piece, injection-molded plastic package for high reliability. The 2N3903 and 2N3904 are complementary with types 2N3905 and 2N3906, respectively.

MAXIMUM RATINGS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Rating	Unit
Collector-Base Voltage	V_{CB}	60	Vdc
Collector-Emitter Voltage	V_{CEO}	40	Vdc
Emitter-Base Voltage	V_{EB}	6	Vdc
Collector Current	I_C	200	mA dc
Total Device Dissipation @ $T_A = 60^\circ\text{C}$	P_D	210	mW
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	310 2.81	mW mW/ $^\circ\text{C}$
Thermal Resistance, Junction to Ambient	θ_{JA}	0.357	$^\circ\text{C/mW}$
Junction Operating Temperature	T_J	135	$^\circ\text{C}$
Storage Temperature Range	T_{stg}	-55 to +135	$^\circ\text{C}$

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Collector-Base Breakdown Voltage ($I_C = 10\text{ }\mu\text{A dc}$, $I_E = 0$)	BV_{CBO}	60	—	Vdc
Collector-Emitter Breakdown Voltage* ($I_C = 1\text{ mA dc}$)	BV_{CEO}^*	40	—	Vdc
Emitter-Base Breakdown Voltage ($I_E = 10\text{ }\mu\text{A dc}$, $I_C = 0$)	BV_{EBO}	6	—	Vdc
Collector Cutoff Current ($V_{CE} = 40\text{ Vdc}$, $V_{OB} = 3\text{ Vdc}$)	I_{CEX}	—	50	nA dc
Base Cutoff Current ($V_{CE} = 40\text{ Vdc}$, $V_{OB} = 3\text{ Vdc}$)	I_{BL}	—	50	nA dc

*Pulse Test: Pulse Width = 300 μsec , Duty Cycle = 2%. V_{OB} = Base Emitter Reverse Bias

*Courtesy of Motorola, Inc.

2N3903, 2N3904 (continued)

ELECTRICAL CHARACTERISTICS (continued)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS				
DC Current Gain * ($I_C = 0.1 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	h_{FE}^*	20	—	—
2N3903		40	—	—
($I_C = 1.0 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)		35	—	—
2N3903		70	—	—
2N3904		50	150	
($I_C = 10 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)		100	300	
2N3903		30	—	—
($I_C = 50 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)		60	—	—
2N3904		15	—	—
($I_C = 100 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)		30	—	—
2N3903		—	0.2	Vdc
Collector-Emitter Saturation Voltage* ($I_C = 10 \text{ mA}$, $I_B = 1 \text{ mA}$)	$V_{CE(sat)}^*$	—	0.3	
($I_C = 50 \text{ mA}$, $I_B = 5 \text{ mA}$)		—	—	
Base-Emitter Saturation Voltage* ($I_C = 10 \text{ mA}$, $I_B = 1 \text{ mA}$)	$V_{BE(sat)}^*$	0.65	0.85	Vdc
($I_C = 50 \text{ mA}$, $I_B = 5 \text{ mA}$)		—	0.95	

SMALL SIGNAL CHARACTERISTICS

High Frequency Current Gain ($I_C = 10 \text{ mA}$, $V_{CE} = 20 \text{ V}$, $f = 100 \text{ mc}$)	2N3903 2N3904	$ h_{fe} $	2.5 3.0	— —	— —
Current-Gain-Bandwidth Product ($I_C = 10 \text{ mA}$, $V_{CE} = 20 \text{ V}$, $f = 100 \text{ mc}$)	2N3903 2N3904	f_T	250 300	— —	mc
Output Capacitance ($V_{CB} = 5 \text{ Vdc}$, $I_E = 0$, $f = 100 \text{ kc}$)		C_{ob}	—	4	pf
Input Capacitance ($V_{OB} = 0.5 \text{ Vdc}$, $I_C = 0$, $f = 100 \text{ kc}$)		C_{ib}	—	8	pf
Small Signal Current Gain ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3903 2N3904	h_{fe}	50 100	200 400	—
Voltage Feedback Ratio ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3903 2N3904	h_{re}	0.1 0.5	5.0 8.0	$\times 10^{-4}$
Input Impedance ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3903 2N3904	h_{ie}	0.5 1.0	8 10	Kohms
Output Admittance ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	Both Types	h_{oe}	1.0	40	μmhos
Noise Figure ($I_C = 100 \mu\text{A}$, $V_{CE} = 5 \text{ V}$, $R_g = 1 \text{ Kohms}$, Noise Bandwidth = 10 cps to 15.7 kc)	2N3903 2N3904	NF	— —	8 5	db

SWITCHING CHARACTERISTICS

Delay Time	$V_{CC} = 3 \text{ Vdc}$, $V_{OB} = 0.5 \text{ Vdc}$, $I_C = 10 \text{ mA}$, $I_{B1} = 1 \text{ mA}$	t_d	—	35	nsec
Rise Time		t_r	—	35	nsec
Storage Time	$V_{CC} = 3 \text{ Vdc}$, $I_C = 10 \text{ mA}$, $I_{B1} = I_{B2} = 1 \text{ mA}$	t_s	—	175 200	nsec
Fall Time		t_f	—	50	nsec

*Pulse Test: Pulse Width = 300 μsec , Duty Cycle = 2%

V_{OB} = Base Emitter Reverse Bias

APPENDIX 1-5 *

2N3905 (SILICON)
2N3906



$V_{CB} = 40\text{ V}$
 $I_C = 200\text{ mA}$
 $C_{ob} = 4.5\text{ pf (max)}$



PNP silicon annular transistor, designed for general purpose switching and amplifier applications, features one-piece, injection-molded plastic package for high reliability. The 2N3905 and 2N3906 are complementary with types 2N3903 and 2N3904, respectively.

MAXIMUM RATINGS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Rating	Unit
Collector-Base Voltage	V_{CB}	40	Vdc
Collector-Emitter Voltage	V_{CEO}	40	Vdc
Emitter-Base Voltage	V_{EB}	5	Vdc
Collector Current	I_C	200	mA dc
Total Device Dissipation @ $T_A = 60^\circ\text{C}$	P_D	210	mW
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	310 2.81	mW mW/ $^\circ\text{C}$
Thermal Resistance, Junction to Ambient	θ_{JA}	0.357	$^\circ\text{C}/\text{mW}$
Junction Operating Temperature	T_J	135	$^\circ\text{C}$
Storage Temperature Range	T_{stg}	-55 to +135	$^\circ\text{C}$

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

OFF CHARACTERISTICS

Collector-Base Breakdown Voltage ($I_C = 10\text{ }\mu\text{A dc}$, $I_E = 0$)	BV_{CBO}	40	—	Vdc
Collector-Emitter Breakdown Voltage* ($I_C = 1\text{ mA dc}$)	BV_{CEO}^*	40	—	Vdc
Emitter-Base Breakdown Voltage ($I_E = 10\text{ }\mu\text{A dc}$, $I_C = 0$)	BV_{EBO}	5	—	Vdc
Collector Cutoff Current ($V_{CE} = 40\text{ Vdc}$, $V_{OB} = 3\text{ Vdc}$)	I_{CEX}	—	50	nA dc
Base Cutoff Current ($V_{CE} = 40\text{ Vdc}$, $V_{OB} = 3\text{ Vdc}$)	I_{BL}	—	50	nA dc

*Pulse Test: Pulse Width = 300 μsec , Duty Cycle = 2%

V_{OB} = Base Emitter Reverse Bias

*Courtesy of Motorola, Inc.

2N3905, 2N3906 (continued)

ELECTRICAL CHARACTERISTICS (continued)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS				
DC Current Gain* ($I_C = 0.1 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	2N3905 2N3906	h_{FE}^*	30 60	—
($I_C = 1.0 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	2N3905 2N3906		40 60	—
($I_C = 10 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	2N3905 2N3906		50 100	150 300
($I_C = 50 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	2N3905 2N3906		30 60	—
($I_C = 100 \text{ mA}$, $V_{CE} = 1 \text{ Vdc}$)	2N3905 2N3906		15 30	—
Collector-Emitter Saturation Voltage* ($I_C = 10 \text{ mA}$, $I_B = 1 \text{ mA}$) ($I_C = 50 \text{ mA}$, $I_B = 5 \text{ mA}$)		$V_{CE(sat)}^*$	— —	0.25 0.4 Vdc
Base-Emitter Saturation Voltage* ($I_C = 10 \text{ mA}$, $I_B = 1 \text{ mA}$) ($I_C = 50 \text{ mA}$, $I_B = 5 \text{ mA}$)		$V_{BE(sat)}^*$	0.65 —	0.85 0.95 Vdc

SMALL SIGNAL CHARACTERISTICS

High-Frequency Current Gain ($I_C = 10 \text{ mA}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ mc}$)	2N3905 2N3906	$ h_{fe} $	2.0 2.5	— —	—
Current-Gain-Bandwidth Product ($I_C = 10 \text{ mA}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ mc}$)	2N3905 2N3906	f_T	200 250	— —	mc
Output Capacitance ($V_{CB} = 5 \text{ Vdc}$, $I_E = 0$, $f = 100 \text{ kc}$)		C_{ob}	—	4.5	pf
Input Capacitance ($V_{OB} = 0.5 \text{ Vdc}$, $I_C = 0$, $f = 100 \text{ kc}$)		C_{ib}	—	10	pf
Small Signal Current Gain ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3905 2N3906	h_{fe}	50 100	200 400	—
Voltage Feedback Ratio ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3905 2N3906	h_{re}	0.1 1.0	5 10	$\times 10^{-4}$
Input Impedance ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3905 2N3906	h_{ie}	0.5 2.0	8 12	Kohms
Output Admittance ($I_C = 1.0 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $f = 1 \text{ kc}$)	2N3905 2N3906	h_{oe}	1.0 3.0	40 60	μmhos
Noise Figure ($I_C = 100 \mu\text{A}$, $V_{CE} = 5 \text{ V}$, $R_g = 1 \text{ Kohms}$, Noise Bandwidth = 10 cps to 15.7 kc)	2N3905 2N3906	NF	— —	5.0 4.0	db

SWITCHING CHARACTERISTICS

Delay Time	$V_{CC} = 3 \text{ Vdc}$, $V_{OB} = 0.5 \text{ Vdc}$, $I_C = 10 \text{ mA}$, $I_{B1} = 1 \text{ mA}$	t_d	—	35	nsec
Rise Time		t_r	—	35	nsec
Storage Time	$V_{CC} = 3 \text{ Vdc}$, $I_C = 10 \text{ mA}$, $I_{B1} = I_{B2} = 1 \text{ mA}$	2N3905 2N3906	t_s	— —	200 225 nsec
Fall Time		2N3905 2N3906	t_f	— —	80 75 nsec

*Pulse Test: PW = 300 μsec , Duty Cycle = 2%

V_{OB} = Base-Emitter Reverse Bias

TYPES 2N929, 2N930
N-P-N PLANAR SILICON TRANSISTORS

FOR EXTREMELY LOW-LEVEL, LOW-NOISE, HIGH-GAIN,
SMALL-SIGNAL AMPLIFIER APPLICATIONS

- Guaranteed h_{fe} at 10 μ a, $T_A = -55^{\circ}\text{C}$ and 25°C
- Guaranteed Low-Noise Characteristics at 10 μ a
- Usable at Collector Currents as Low as 1 μ a
- Very High Reliability
- 2N929 and 2N930 Also Are Available to MIL-S-19500/253 (Sig C)

*mechanical data



*absolute maximum ratings at 25°C free-air temperature (unless otherwise nated)

Collector-Base Voltage	45 v
Collector-Emitter Voltage (See Note 1)	45 v
Emitter-Base Voltage	5 v
Collector Current	30 ma
Total Device Dissipation at (or below) 25°C Free-Air Temperature (See Note 2)	300 mw
Total Device Dissipation at (or below) 25°C Case Temperature (See Note 3)	600 mw
Operating Collector Junction Temperature	175°C
Storage Temperature Range	-65°C to +200°C

NOTES 1 This value applies when the base emitter diode is open-circuited
2 Operate linearly to 175°C free air temperature at the rate of 2.0 mw/°C
3 Operate linearly to 175°C case temperature at the rate of 4.0 mw/°C

*Indicates JEDEC registered data

*Courtesy of Texas Instruments, Incorporated

TYPES 2N929, 2N930

N-P-N PLANAR SILICON TRANSISTOR

*electrical characteristics at 25°C free-air temperature (unless otherwise noted)

PARAMETER	TEST CONDITIONS	2N929		2N930		UNIT
		MIN	MAX	MIN	MAX	
BV_{CEO} Collector-Emitter Breakdown Voltage	$I_C = 10 \text{ ma}$, $I_B = 0$, (See Note 4)	45		45		v
BV_{EBO} Emitter-Base Breakdown Voltage	$I_E = 10 \text{ ma}$, $I_C = 0$	5		5		v
I_{CBO} Collector Cutoff Current	$V_{CB} = 45 \text{ v}$, $I_E = 0$		10		10	na
I_{CES} Collector Cutoff Current (See Note 5)	$V_{CE} = 45 \text{ v}$, $V_{BE} = 0$		10		10	na
	$V_{CE} = 45 \text{ v}$, $V_{BE} = 0$, $T_A = 170^\circ\text{C}$		10		10	μa
I_{CEO} Collector Cutoff Current	$V_{CE} = 5 \text{ v}$, $I_B = 0$		2		2	na
I_{EBO} Emitter Cutoff Current	$V_{EB} = 5 \text{ v}$, $I_C = 0$		10		10	na
h_{FE} Static Forward Current Transfer Ratio	$V_{CE} = 5 \text{ v}$, $I_C = 10 \mu\text{a}$	40	120	100	300	
	$V_{CE} = 5 \text{ v}$, $I_C = 10 \mu\text{a}$, $T_A = -55^\circ\text{C}$	10		20		
	$V_{CE} = 5 \text{ v}$, $I_C = 500 \mu\text{a}$	60		150		
	$V_{CE} = 5 \text{ v}$, $I_C = 10 \text{ ma}$, (See Note 4)		350		600	
V_{BE} Base-Emitter Voltage	$I_B = 0.5 \text{ ma}$, $I_C = 10 \text{ ma}$, (See Note 4)	0.6	1.0	0.6	1.0	v
$V_{CE(sat)}$ Collector-Emitter Saturation Voltage	$I_B = 0.5 \text{ ma}$, $I_C = 10 \text{ ma}$, (See Note 4)		1.0		1.0	v
h_{ib} Small-Signal Common-Base Input Impedance	$V_{CB} = 5 \text{ v}$, $I_E = -1 \text{ ma}$, $f = 1 \text{ kc}$	25	32	25	32	ohm
h_{rb} Small-Signal Common-Base Reverse Voltage Transfer Ratio	$V_{CB} = 5 \text{ v}$, $I_E = -1 \text{ ma}$, $f = 1 \text{ kc}$	0	6.0×10^{-4}	0	6.0×10^{-4}	
h_{ob} Small-Signal Common-Base Output Admittance	$V_{CB} = 5 \text{ v}$, $I_E = -1 \text{ ma}$, $f = 1 \text{ kc}$	0	1.0	0	1.0	μmho
h_{fe} Small-Signal Common-Emitter Forward Current Transfer Ratio	$V_{CE} = 5 \text{ v}$, $I_C = 1 \text{ ma}$, $f = 1 \text{ kc}$	60	350	150	600	
$ h_{fe} $ Small-Signal Common-Emitter Forward Current Transfer Ratio	$V_{CE} = 5 \text{ v}$, $I_C = 500 \mu\text{a}$, $f = 30 \text{ mc}$	1.0		1.0		
C_{ob} Common-Base Open-Circuit Output Capacitance	$V_{CB} = 5 \text{ v}$, $I_E = 0$, $f = 1 \text{ mc}$		8		8	pf

*operating characteristics at 25°C free-air temperature

PARAMETER	TEST CONDITIONS	2N929	2N930	UNIT
		MAX	MAX	
NF Average Noise Figure	$V_{CE} = 5 \text{ v}$, $I_C = 10 \mu\text{a}$, $R_G = 10 \text{ k}\Omega$ Noise Bandwidth 10 cps to 15.7 kc	4	3	db

NOTES: 4. These parameters must be measured using pulse techniques. PW = 300 μsec , Duty Cycle $\leq 2\%$.

5. I_{CES} may be used in place of I_{CBO} for circuit stability calculations.

*Indicates JEDEC registered data


TYPES 2N4418 AND 2N4419 N-P-N EPITAXIAL PLANAR SILICON TRANSISTORS

SELECT† TRANSISTORS FOR HIGH-SPEED SWITCHING APPLICATIONS

- 2N4418 Electrically Similar to the 2N2369
- Rugged, One-Piece Construction with Standard TO-18 100-mil Pin Circle

mechanical data

These transistors are encapsulated in a plastic compound specifically designed for this purpose, using a highly mechanized process‡ developed by Texas Instruments. The case will withstand soldering temperatures without deformation. These devices exhibit stable characteristics under high-humidity conditions and are capable of meeting MIL-STD-202C method 106B. The transistors are insensitive to light.

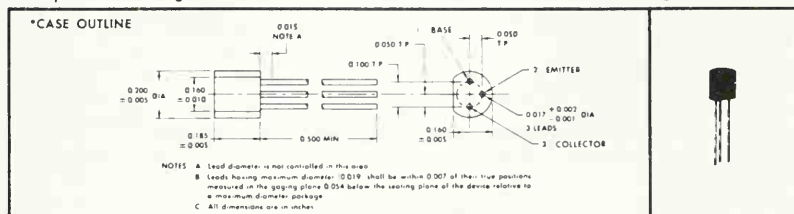

absolute maximum ratings at 25°C free-air temperature (unless otherwise noted)

	2N4418	2N4419
Collector-Base Voltage	40 V	30 V
Collector-Emitter Voltage (See Note 1)	40 V	30 V
Collector-Emmitter Voltage (See Note 2)	15 V	12 V
Emitter-Base Voltage	4.5 V	4.5 V
Continuous Collector Current	← 200 mA →	
Peak Collector Current (See Note 3)	← 500 mA →	
Continuous Device Dissipation at (or below) 25°C Free-Air Temperature (See Note 4)	← 360 mW →	
Continuous Device Dissipation at (or below) 25°C Lead Temperature (See Note 5)	← 500 mW →	
Storage Temperature Range	−65°C to 150°C	
Lead Temperature 1/16 Inch from Case for 10 Seconds	← 260°C →	

electrical characteristics at 25°C free-air temperature (unless otherwise noted)

PARAMETER		TEST CONDITIONS	2N4418		2N4419		UNIT
			MIN	MAX	MIN	MAX	
$V_{BR(CBO)}$	Collector-Base Breakdown Voltage	$I_C = 10 \mu A, I_E = 0$	40		30		V
$V_{BR(CEO)}$	Collector-Emitter Breakdown Voltage	$I_C = 10 \text{ mA}, I_B = 0$, See Note 6	15		12		V
$V_{BR(CES)}$	Collector-Emitter Breakdown Voltage	$I_C = 10 \mu A, V_{BE} = 0$	40		30		V
$V_{BR(EBO)}$	Emitter-Base Breakdown Voltage	$I_E = 10 \mu A, I_C = 0$	4.5		4.5		V
I_{CBO}	Collector Cutoff Current	$V_{CB} = 20 \text{ V}, I_E = 0$		0.4		0.4	μA
		$V_{CB} = 20 \text{ V}, I_E = 0, T_A = 70^\circ C$		3		3	μA
I_{EBO}	Emitter Cutoff Current	$V_{EB} = 3 \text{ V}, I_C = 0$		20		25	nA
h_{FE}	Static Forward Current Transfer Ratio	$V_{CE} = 1 \text{ V}, I_C = 10 \text{ mA}$, See Note 6	40	120	30		
		$V_{CE} = 2 \text{ V}, I_C = 100 \text{ mA}$, See Note 6	20				
V_{BE}	Base-Emitter Voltage	$I_B = 1 \text{ mA}, I_C = 10 \text{ mA}$	0.72	0.87	0.72	0.87	V
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_B = 1 \text{ mA}, I_C = 10 \text{ mA}$		0.25		0.25	V
$ h_{fe} $	Small-Signal Common-Emitter Forward Current Transfer Ratio	$V_{CE} = 10 \text{ V}, I_C = 10 \text{ mA}, f = 100 \text{ MHz}$	5		4		
C_{cb}	Collector-Base Capacitance	$V_{CB} = 5 \text{ V}, I_E = 0, f = 1 \text{ MHz}$, See Note 7		4		4	pF

NOTES: 1. This value applies when the base-emitter diode is short-circuited.

2. These values apply between 0 and 200 mA collector current when the base-emitter diode is open-circuited. Maximum rated voltage and 200 mA collector current may be simultaneously applied provided the time of application is 10 μs or less and the duty cycle is 2% or less.

3. This value applies for $t_p \leq 10 \mu s$ and duty cycle $\leq 2\%$.

4. Derate linearly to 150°C free-air temperature at the rate of 2.88 mW/deg.

5. Derate linearly to 150°C lead temperature at the rate of 4 mW/deg. Lead temperature is measured on the collector lead 1/16 inch from the case.

6. These parameters must be measured using pulse techniques. $t_p = 300 \mu s$, duty cycle $\leq 2\%$.

7. C_{cb} is measured using three-terminal measurement techniques with the emitter guarded.

*Indicates JEDEC registered data

†Trademark of Texas Instruments

‡Patent Pending

*Courtesy of Texas Instruments, Incorporated

TYPES 2N4418 AND 2N4419
N-P-N EPITAXIAL PLANAR SILICON TRANSISTORS

*switching characteristics at 25°C free-air temperature

PARAMETER	TEST CONDITIONS†	2N4418	2N4419	UNIT
		MAX	MAX	
t_d Delay Time	$I_C = 10\text{ mA}$, $I_{B(1)} = 1\text{ mA}$, $V_{BE(off)} = 0$, $R_L = 280\ \Omega$, See Figure 1	10	10	ns
t_r Rise Time		12	14	ns
t_{on} Turn-on Time		20	22	ns
t_s Storage Time	$I_C = 10\text{ mA}$, $I_{B(1)} = 1\text{ mA}$, $I_{B(2)} = -1\text{ mA}$, $R_L = 280\ \Omega$, See Figure 2	12	14	ns
t_f Fall Time		14	16	ns
t_{off} Turn-off Time		22	28	ns
t_x Storage Time	$I_C = 10\text{ mA}$, $I_{B(1)} = 10\text{ mA}$, $I_{B(2)} = -10\text{ mA}$, See Figure 3	18	20	ns

†Voltage and current values shown are nominal; exact values vary slightly with transistor parameters.

*PARAMETER MEASUREMENT INFORMATION

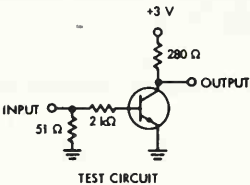


FIGURE 1

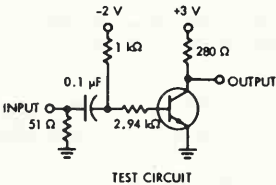
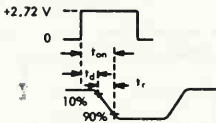


FIGURE 2


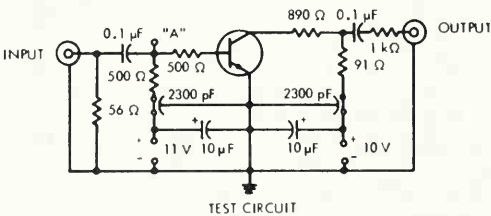
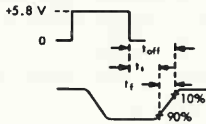


FIGURE 3

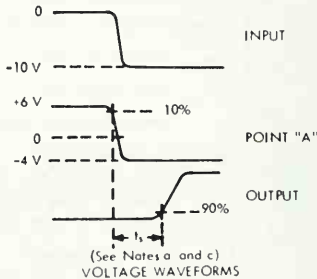

NOTES: a. The input waveforms are supplied by a generator with the following characteristics: $Z_{out} = 50\ \Omega$, $t_r \leq 1\text{ ns}$, $t_p \geq 200\text{ ns}$, duty cycle $\leq 2\%$.
b. Waveforms of figures 1 and 2 are monitored on an oscilloscope with the following characteristics: $t_r \leq 1\text{ ns}$, $R_{in} \geq 100\text{ k}\Omega$, $C_{in} \leq 10\text{ pF}$.
c. Output waveform of figure 3 is monitored on an oscilloscope with the following characteristics: $t_r \leq 1\text{ ns}$, $Z_{in} = 50\ \Omega$.

*Indicates JEDEC registered data


APPENDIX 1-8*

TYPES 2N4856, 2N4857, 2N4858, 2N4859, 2N4860, 2N4861
N-CHANNEL EPITAXIAL PLANAR SILICON FIELD-EFFECT TRANSISTORS

SYMMETRICAL N-CHANNEL FIELD-EFFECT TRANSISTORS
FOR HIGH-SPEED COMMUTATOR AND CHOPPER APPLICATIONS
2N4859 Formerly T1XS41

- Low $r_{ds(on)}$: 25 Ω Max (2N4856, 2N4859)
- Low $I_{D(off)}$: 0.25 nA Max

*mechanical data

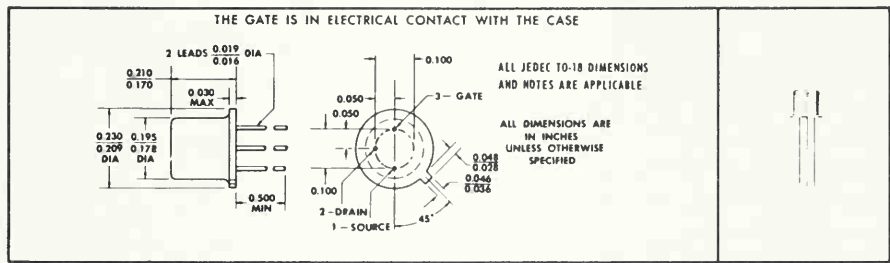

*absolute maximum ratings at 25°C free-air temperature (unless otherwise noted)

	2N4856	2N4859
	2N4857	2N4860
	2N4858	2N4861
Drain-Gate Voltage	40 V	30 V
Drain-Source Voltage	40 V	30 V
Reverse Gate-Source Voltage	-40 V	-30 V
Forward Gate Current	← 50 mA →	
Continuous Device Dissipation at (or below) 25°C Free-Air Temperature (See Note 1)	← 360 mW →	
Storage Temperature Range	-65°C to 200°C	
Lead Temperature 1/8 Inch from Case for 10 Seconds	← 300°C →	

NOTE 1: Derate linearly to 175°C free air temperature at the rate of 2.4 mW/deg.
*Indicates JEDEC registered data

*Courtesy of Texas Instruments, Incorporated

TYPES 2N4856 THRU 2N4861

N-CHANNEL EPITAXIAL PLANAR SILICON FIELD-EFFECT TRANSISTORS

*electrical characteristics at 25°C free-air temperature (unless otherwise noted)

PARAMETER	TEST CONDITIONS	2N4856		2N4857		2N4858		2N4859		2N4860		2N4861		UNIT
		MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
V_{BRIGSS} Gate-Source Breakdown Voltage	$I_G = -1 \mu A, V_{DS} = 0$	-40		-40		-40		-30		-30		-30		V
I_{GSS} Gate Reverse Current	$V_{GS} = -20 V, V_{DS} = 0$		-0.25		-0.25		-0.25							nA
	$V_{GS} = -20 V, V_{DS} = 0, T_A = 150^\circ C$		-0.5		-0.5		-0.5							μA
	$V_{GS} = -15 V, V_{DS} = 0$							-0.25		-0.25		-0.25		nA
	$V_{GS} = -15 V, V_{DS} = 0, T_A = 150^\circ C$							-0.5		-0.5		-0.5		μA
$I_{D(off)}$ Drain Cutoff Current	$V_{DS} = 15 V, V_{GS} = -10 V$	0.25		0.25		0.25		0.25		0.25		0.25		nA
	$V_{DS} = 15 V, V_{GS} = -10 V, T_A = 150^\circ C$	0.5		0.5		0.5		0.5		0.5		0.5		μA
$V_{GS(off)}$ Gate-Source Cutoff Voltage	$V_{DS} = 15 V, I_D = 0.5 mA$	-4	-10	-2	-6	-0.8	-4	-4	-10	-2	-6	-0.8	-4	V
I_{DSS} Zero-Gate-Voltage Drain Current	$V_{DS} = 15 V, V_{GS} = 0, \text{ See Note 2}$	50		20	100	8	80	50		20	100	8	80	mA
$V_{DS(on)}$ Drain-Source On-State Voltage	$I_D = 20 mA, V_{GS} = 0$	0.75						0.75						V
	$I_D = 10 mA, V_{GS} = 0$			0.50						0.50				V
	$I_D = 5 mA, V_{GS} = 0$					0.50						0.50		V
$r_{ds(on)}$ Small-Signal Drain-Source On-State Resistance	$V_{GS} = 0, I_D = 0, f = 1 kHz$	25		40		60		25		40		60		Ω
C_{iss} Common-Source Short-Circuit Input Capacitance	$V_{GS} = -10 V, V_{DS} = 0, f = 1 MHz$	18		18		18		18		18		18		pF
C_{rss} Common-Source Short-Circuit Reverse Transfer Capacitance	$V_{GS} = -10 V, V_{DS} = 0, f = 1 MHz$	8		8		8		8		8		8		pF

*switching characteristics at 25°C free-air temperature

PARAMETER	TEST CONDITIONS	2N4856 2N4859	2N4857 2N4860	2N4858 2N4861	UNIT
		MAX	MAX	MAX	
$t_{d(on)}$ Turn-On Delay Time	$V_{DD} = 10 V, I_{D(on)}^\dagger = \begin{cases} 20 mA (2N4856, 2N4859) \\ 10 mA (2N4857, 2N4860) \\ 5 mA (2N4858, 2N4861) \end{cases}$	6	6	10	ns
t_r Rise Time	$V_{GS(on)} = 0, V_{GS(off)} = \begin{cases} -10 V (2N4856, 2N4859) \\ -6 V (2N4857, 2N4860) \\ -4 V (2N4858, 2N4861) \end{cases}$	3	4	10	ns
t_{off} Turn-Off Time	See Figure 1	25	50	100	ns

NOTE 2: This parameter must be measured using pulse techniques. $t_p \approx 100 ms$, duty cycle $\leq 10\%$.

*Indicates JEDEC registered data

†These are nominal values; exact values vary slightly with transistor parameters.

APPENDIX 1-9*

2N5457 (SILICON)

2N5458

2N5459

Silicon N-channel junction field-effect transistors depletion mode (Type A) designed for general-purpose audio and switching applications.



CASE 29 (5)
(TO-92)

Drain and source may be
interchanged.

MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Drain-Source Voltage	V_{DS}	25	Vdc
Drain-Gate Voltage	V_{DG}	25	Vdc
Reverse Gate-Source Voltage	$V_{GS(r)}$	25	Vdc
Gate Current	I_G	10	mAdc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	$P_D^{(2)}$	310 2.82	mW mW/ $^\circ\text{C}$
Operating Junction Temperature	$T_J^{(2)}$	135	$^\circ\text{C}$
Storage Temperature Range	$T_{stg}^{(2)}$	-65 to +150	$^\circ\text{C}$

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Typ	Max	Unit
----------------	--------	-----	-----	-----	------

OFF CHARACTERISTICS

Gate-Source Breakdown Voltage ($I_G = -10\mu\text{Adc}$, $V_{DS} = 0$)		BV_{GSS}	25	—	—	Vdc
Gate Reverse Current ($V_{GS} = -15\text{ Vdc}$, $V_{DS} = 0$) ($V_{GS} = -15\text{ Vdc}$, $V_{DS} = 0$, $T_A = 100^\circ\text{C}$)		I_{GSS}	— —	— —	1.0 200	nAdc
Gate-Source Cutoff Voltage ($V_{DS} = 15\text{ Vdc}$, $I_D = 10\text{ nAdc}$)	2N5457 2N5458 2N5459	$V_{GS(off)}$	0.5 1.0 2.0	— — —	6.0 7.0 8.0	Vdc
Gate-Source Voltage ($V_{DS} = 15\text{ Vdc}$, $I_D = 100\mu\text{Adc}$) ($V_{DS} = 15\text{ Vdc}$, $I_D = 200\mu\text{Adc}$) ($V_{DS} = 15\text{ Vdc}$, $I_D = 400\mu\text{Adc}$)	2N5457 2N5458 2N5459	V_{GS}	— — —	2.5 3.5 4.5	— — —	Vdc

ON CHARACTERISTICS

Zero-Gate-Voltage Drain Current ⁽¹⁾ ($V_{DS} = 15\text{ Vdc}$, $V_{GS} = 0$)	I_{DSS}	2N5457 2N5458 2N5459	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mAdc
---	-----------	----------------------------	-------------------	-------------------	------------------	------

DYNAMIC CHARACTERISTICS

Forward Transfer Admittance ⁽¹⁾ ($V_{DS} = 15\text{ Vdc}$, $V_{GS} = 0$, $f = 1\text{ kHz}$)	$ y_{fs} $	2N5457 2N5458 2N5459	1000 1500 2000	3000 4000 4500	5000 5500 6000	$\mu\text{ mhos}$
Output Admittance ⁽¹⁾ ($V_{DS} = 15\text{ Vdc}$, $V_{GS} = 0$, $f = 1\text{ kHz}$)	$ y_{os} $		—	10	50	$\mu\text{ mhos}$
Input Capacitance ($V_{DS} = 15\text{ Vdc}$, $V_{GS} = 0$, $f = 1\text{ MHz}$)	C_{iss}		—	4.5	7.0	pF
Reverse Transfer Capacitance ($V_{DS} = 15\text{ Vdc}$, $V_{GS} = 0$, $f = 1\text{ MHz}$)	C_{rss}		—	1.5	3.0	pF

⁽¹⁾ Pulse Test: Pulse Width $\leq 630\text{ ms}$, Duty Cycle $\leq 10\%$

⁽²⁾ Continuous package improvements have enhanced these guaranteed Maximum Ratings as follows: $P_D = 1.0\text{ W}$ @ $T_C = 25^\circ\text{C}$.
Derate above $25^\circ\text{C} = 8.0\text{ mW}/^\circ\text{C}$, $T_J = -65\text{ to }+150^\circ\text{C}$, $\theta_{JA} = 125^\circ\text{C}/\text{W}$

*Courtesy of Motorola, Inc.

APPENDIX 1-10*

2N4391 (SILICON)

2N4392



2N4393

SILICON N-CHANNEL
JUNCTION FIELD-EFFECT TRANSISTORS

Depletion Mode (Type A) Junction Field-Effect Transistors designed for chopper and high-speed switching applications.

- Low Drain-Source "On" Resistance –
 $r_{ds(on)} = 30 \text{ Ohms (Max) @ } f = 1.0 \text{ kHz (2N4391)}$
- Low Gate Reverse Current –
 $I_{GSS} = 0.1 \text{ nAdc (Max) @ } V_{GS} = 20 \text{ Vdc}$
- Guaranteed Switching Characteristics

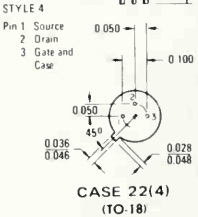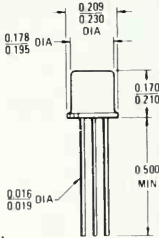
N-CHANNEL
JUNCTION FIELD-EFFECT
TRANSISTORS
(Type A)



MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Drain-Source Voltage	V_{DS}	40	Vdc
Drain-Gate Voltage	V_{DG}	40	Vdc
Gate-Source Voltage	V_{GS}	40	Vdc
Forward Gate Current	$I_{G(I)}$	50	mAdc
Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.8 10	Watts mW/ $^\circ\text{C}$
Operating Junction Temperature Range	T_J	-65 to +175	$^\circ\text{C}$
Storage Temperature Range	T_{stg}	-65 to +200	$^\circ\text{C}$

FIGURE 1 SWITCHING TIMES TEST CIRCUIT

 

*Courtesy of Motorola, Inc.

2N4391, 2N4392, 2N4393 (continued)

ELECTRICAL CHARACTERISTICS (T_A = 25°C unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Gate-Source Breakdown Voltage (I _G = 1.0 μAdc, V _{DS} = 0)	V _{(BR)GSS}	40	-	Vdc
Gate-Source Forward Voltage (I _G = 1.0 nAdc, V _{DS} = 0)	V _{GS(I)}	-	1.0	Vdc
Gate-Source Voltage (V _{DS} = 20 Vdc, I _D = 1.0 nAdc)	V _{GS}	4.0 2.0 0.5	10 5.0 3.0	Vdc
Gate Reverse Current (V _{GS} = 20 Vdc, V _{DS} = 0)	I _{GSS}	-	0.1	nAdc
(V _{GS} = 20 Vdc, V _{DS} = 0, T _A = 150°C)		-	0.2	μAdc
Drain-Cutoff Current (V _{DS} = 20 Vdc, V _{GS} = 12 Vdc)	I _{D(off)}	-	0.1	nAdc
(V _{DS} = 20 Vdc, V _{GS} = 7.0 Vdc)		-	0.1	
(V _{DS} = 20 Vdc, V _{GS} = 5.0 Vdc)		-	0.1	
(V _{DS} = 20 Vdc, V _{GS} = 12 Vdc, T _A = 150°C)		-	0.2	μAdc
(V _{DS} = 20 Vdc, V _{GS} = 7.0 Vdc, T _A = 150°C)		-	0.2	
(V _{DS} = 20 Vdc, V _{GS} = 5.0 Vdc, T _A = 150°C)		-	0.2	
ON CHARACTERISTICS				
Zero-Gate Voltage Drain Current (1) (V _{DS} = 20 Vdc, V _{GS} = 0)	I _{DSS}	50 25 5.0	150 75 30	mAdc
Drain-Source "ON" Voltage (I _D = 12 mAdc, V _{GS} = 0)	V _{DS(on)}	-	0.4	Vdc
(I _D = 6.0 mAdc, V _{GS} = 0)		-	0.4	
(I _D = 3.0 mAdc, V _{GS} = 0)		-	0.4	
Static Drain-Source "ON" Resistance (I _D = 1.0 mAdc, V _{GS} = 0)	r _{DS(on)}	-	30 60 100	Ohms
SMALL-SIGNAL CHARACTERISTICS				
Drain-Source "ON" Resistance (V _{GS} = 0, I _D = 0, f = 1.0 kHz)	r _{ds(on)}	-	30 60 100	Ohms
Input Capacitance (V _{DS} = 20 Vdc, V _{GS} = 0, f = 1.0 MHz)	C _{iss}	-	14	pF
Reverse Transfer Capacitance (V _{DS} = 0, V _{GS} = 12 Vdc, f = 1.0 MHz)	C _{rss}	-	3.5	pF
(V _{DS} = 0, V _{GS} = 7.0 Vdc, f = 1.0 MHz)		-	3.5	
(V _{DS} = 0, V _{GS} = 5.0 Vdc, f = 1.0 MHz)		-	3.5	
SWITCHING CHARACTERISTICS				
Turn-On Time (See Figure 1) (I _{D(on)} = 12 mAdc)	t _{on}	-	15	ns
(I _{D(on)} = 6.0 mAdc)		-	15	
(I _{D(on)} = 3.0 mAdc)		-	15	
Rise Time (See Figure 1) (I _{D(on)} = 12 mAdc)	t _r	-	5.0	ns
(I _{D(on)} = 6.0 mAdc)		-	5.0	
(I _{D(on)} = 3.0 mAdc)		-	5.0	
Turn-Off Time (See Figure 1) (V _{GS(off)} = 12 Vdc)	t _{off}	-	20	ns
(V _{GS(off)} = 7.0 Vdc)		-	35	
(V _{GS(off)} = 5.0 Vdc)		-	50	
Fall Time (See Figure 1) (V _{GS(off)} = 12 Vdc)	t _f	-	15	ns
(V _{GS(off)} = 7.0 Vdc)		-	20	
(V _{GS(off)} = 5.0 Vdc)		-	30	

(1) Pulse Test: Pulse Width < 100 μs, Duty Cycle < 1.0%.

μ A741 FREQUENCY-COMPENSATED OPERATIONAL AMPLIFIER FAIRCHILD LINEAR INTEGRATED CIRCUITS


GENERAL DESCRIPTION — The μ A741 is a high performance monolithic Operational Amplifier constructed using the Fairchild Planar* epitaxial process. It is intended for a wide range of analog applications. High common mode voltage range and absence of "latch-up" tendencies make the μ A741 ideal for use as a voltage follower. The high gain and wide range of operating voltage provides superior performance in integrator, summing amplifier, and general feedback applications.

- NO FREQUENCY COMPENSATION REQUIRED
- SHORT CIRCUIT PROTECTION
- OFFSET VOLTAGE NULL CAPABILITY
- LARGE COMMON-MODE AND DIFFERENTIAL VOLTAGE RANGES
- LOW POWER CONSUMPTION
- NO LATCH UP

ABSOLUTE MAXIMUM RATINGS

Supply Voltage	
Military (741)	± 22 V
Commercial (741C)	± 18 V
Internal Power Dissipation (Note 1)	
Metal Can	500 mW
DIP	670 mW
Mini DIP	310 mW
Flatpak	570 mW
Differential Input Voltage	± 30 V
Input Voltage (Note 2)	± 15 V
Storage Temperature Range	
Metal Can, DIP, and Flatpak	-65°C to $+150^{\circ}\text{C}$
Mini DIP	-55°C to $+125^{\circ}\text{C}$
Operating Temperature Range	
Military (741)	-55°C to $+125^{\circ}\text{C}$
Commercial (741C)	0°C to $+70^{\circ}\text{C}$
Lead Temperature (Soldering)	
Metal Can, DIP, and Flatpak (60 seconds)	300°C
Mini DIP (10 seconds)	260°C
Output Short Circuit Duration (Note 3)	Indefinite

EQUIVALENT CIRCUIT

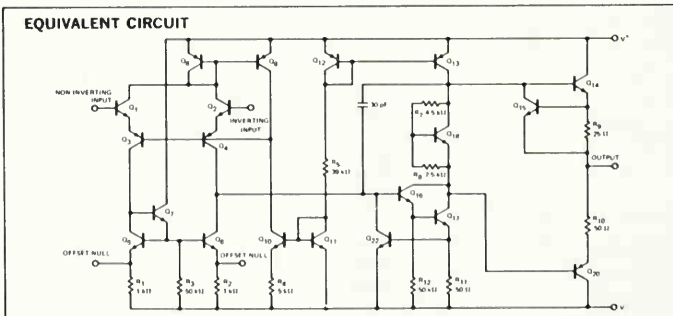

Notes on following pages.

CONNECTION DIAGRAMS

8-LEAD METAL CAN (TOP VIEW) PACKAGE OUTLINE 5B




Note: Pin 4 connected to case

ORDER INFORMATION

TYPE	PART NO.
741	741HM
741C	741HC

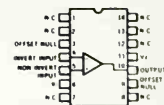
14-LEAD DIP (TOP VIEW) PACKAGE OUTLINE 6A



ORDER INFORMATION

TYPE	PART NO.
741	741DM
741C	741DC

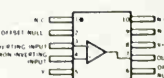10-LEAD FLATPAK (TOP VIEW) PACKAGE OUTLINE 3F



ORDER INFORMATION

TYPE	PART NO.
741	741FM

8-LEAD MINIDIP (TOP VIEW) PACKAGE OUTLINE 9T



ORDER INFORMATION

TYPE	PART NO.
741C	741TC

*Planar is a patented Fairchild process

*Courtesy of Fairchild Semiconductors

ELECTRICAL CHARACTERISTICS ($V_S = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ unless otherwise specified)


PARAMETERS (see definitions)		CONDITIONS	MIN.	TYP.	MAX.	UNITS
Input Offset Voltage		$R_S < 10\text{ k}\Omega$		1.0	5.0	mV
Input Offset Current				20	200	nA
Input Bias Current				80	500	nA
Input Resistance			0.3	2.0		M Ω
Input Capacitance				1.4		pF
Offset Voltage Adjustment Range				± 15		mV
Large Signal Voltage Gain		$R_L > 2\text{ k}\Omega$, $V_{OUT} = \pm 10\text{ V}$	50,000	200,000		
Output Resistance				75		Ω
Output Short Circuit Current				25		mA
Supply Current				1.7	2.8	mA
Power Consumption				50	85	mW
Transient Response (Unity Gain)	Risetime	$V_{IN} = 20\text{ mV}$, $R_L = 2\text{ k}\Omega$, $C_L < 100\text{ pF}$		0.3		μs
	Overshoot			5.0		%
Slew Rate		$R_L > 2\text{ k}\Omega$		0.5		V/ μs

The following specifications apply for $-55^\circ\text{C} < T_A < +125^\circ\text{C}$:


Input Offset Voltage	$R_S < 10\text{ k}\Omega$		1.0	6.0	mV
	$T_A = +125^\circ\text{C}$		7.0	200	nA
Input Offset Current	$T_A = -55^\circ\text{C}$		85	500	nA
	$T_A = +125^\circ\text{C}$		0.03	0.5	μA
Input Bias Current	$T_A = -55^\circ\text{C}$		0.3	1.5	μA
Input Voltage Range		± 12	± 13		V
Common Mode Rejection Ratio	$R_S < 10\text{ k}\Omega$	70	90		dB
Supply Voltage Rejection Ratio	$R_S < 10\text{ k}\Omega$		30	150	$\mu\text{V/V}$
Large Signal Voltage Gain	$R_L > 2\text{ k}\Omega$, $V_{OUT} = \pm 10\text{ V}$	25,000			
Output Voltage Swing	$R_L > 10\text{ k}\Omega$	± 12	± 14		V
	$R_L > 2\text{ k}\Omega$	± 10	± 13		V
Supply Current	$T_A = +125^\circ\text{C}$		1.5	2.5	mA
	$T_A = -55^\circ\text{C}$		2.0	3.3	mA
Power Consumption	$T_A = +125^\circ\text{C}$		45	75	mW
	$T_A = -55^\circ\text{C}$		60	100	mW

TYPICAL PERFORMANCE CURVES FOR 741

 
**OPEN LOOP VOLTAGE GAIN
AS A FUNCTION OF
SUPPLY VOLTAGE**



 **OUTPUT VOLTAGE SWING
AS A FUNCTION OF
SUPPLY VOLTAGE**



 **INPUT COMMON MODE
VOLTAGE RANGE AS A
FUNCTION OF SUPPLY VOLTAGE**



741C

ELECTRICAL CHARACTERISTICS ($V_S = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$ unless otherwise specified)


PARAMETERS (see definitions)		CONDITIONS	MIN.	TYP.	MAX.	UNITS
Input Offset Voltage		$R_S \leq 10\text{ k}\Omega$		2.0	6.0	mV
Input Offset Current				20	200	nA
Input Bias Current				80	500	nA
Input Resistance			0.3	2.0		M Ω
Input Capacitance				1.4		pF
Offset Voltage Adjustment Range				± 15		mV
Input Voltage Range			± 12	± 13		V
Common Mode Rejection Ratio		$R_S \leq 10\text{ k}\Omega$	70	90		dB
Supply Voltage Rejection Ratio		$R_S \leq 10\text{ k}\Omega$		30	150	$\mu\text{V/V}$
Large Signal Voltage Gain		$R_L \geq 2\text{ k}\Omega$, $V_{OUT} = \pm 10\text{ V}$	20,000	200,000		
Output Voltage Swing		$R_L \geq 10\text{ k}\Omega$	± 12	± 14		V
		$R_L \geq 2\text{ k}\Omega$	± 10	± 13		V
Output Resistance				75		Ω
Output Short Circuit Current				25		mA
Supply Current				1.7	2.8	mA
Power Consumption				50	85	mW
Transient Response (Unity Gain)	Risetime	$V_{IN} = 20\text{ mV}$, $R_L = 2\text{ k}\Omega$, $C_L \leq 100\text{ pF}$		0.3		μs
	Overshoot			5.0		%
Slew Rate		$R_L \geq 2\text{ k}\Omega$		0.5		V/ μs

The following specifications apply for $0^\circ\text{C} \leq T_A \leq +70^\circ\text{C}$:


Input Offset Voltage					7.5	mV
Input Offset Current					300	nA
Input Bias Current					800	nA
Large Signal Voltage Gain		$R_L \geq 2\text{ k}\Omega$, $V_{OUT} = \pm 10\text{ V}$	15,000			
Output Voltage Swing		$R_L \geq 2\text{ k}\Omega$	± 10	± 13		V

TYPICAL PERFORMANCE CURVES FOR 741C

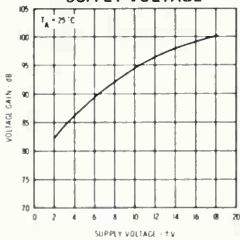
OPEN LOOP VOLTAGE GAIN
AS A FUNCTION OF
SUPPLY VOLTAGE



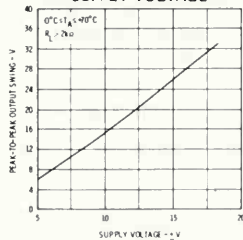OUTPUT VOLTAGE SWING
AS A FUNCTION OF
SUPPLY VOLTAGE



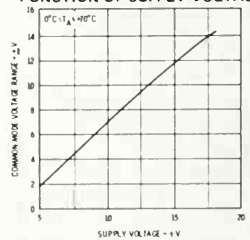INPUT COMMON MODE
VOLTAGE RANGE AS A
FUNCTION OF SUPPLY VOLTAGE



NOTES:

- Rating applies to ambient temperatures up to 70°C . Above 70°C ambient derate linearly at $6.3\text{ mW}/^\circ\text{C}$ for the Metal Can, $8.3\text{ mW}/^\circ\text{C}$ for the DIP, $5.6\text{ mW}/^\circ\text{C}$ for the Mini DIP and $7.1\text{ mW}/^\circ\text{C}$ for the Flatpak.
- For supply voltages less than $\pm 15\text{ V}$, the absolute maximum input voltage is equal to the supply voltage.
- Short circuit may be to ground or either supply. Rating applies to $+125^\circ\text{C}$ case temperature or 75°C ambient temperature.

APPENDIX 1-12*

TYPES 2N3980, 2N4947 THRU 2N4949
P-N PLANAR UNIJUNCTION SILICON TRANSISTORS

**PLANAR UNIJUNCTION TRANSISTORS SPECIFICALLY CHARACTERIZED
FOR A WIDE RANGE OF MILITARY, SPACE, AND INDUSTRIAL APPLICATIONS:**

2N3980 for General-Purpose UJT Applications

2N4947 for High-Frequency Relaxation-Oscillator Circuits


2N4948 for Thyristor (SCR) Trigger Circuits

2N4949 for Long-Time-Delay Circuits

- **Planar Process Ensures Extremely Low Leakage, High Performance for Low Driving Currents, and Greatly Improved Reliability**

*mechanical dota

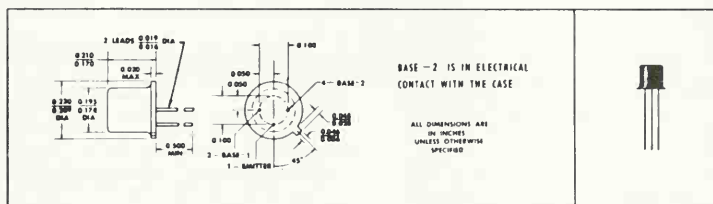Package outline is same as JEDEC TO-18 except for lead position. All TO-18 registration notes also apply to this outline.



* absolute maximum ratings at 25°C free-air temperature (unless otherwise noted)

Emitter - Base Two Reverse Voltage	-30 V
Interbase Voltage	See Note 1
Continuous Emitter Current	50 mA
Peak Emitter Current (See Note 2)	1 A
Continuous Device Dissipation at (or below) 25°C Free-Air Temperature (See Note 3)	360 mW
Storage Temperature Range	-65°C to 200°C
Lead Temperature 1/8 Inch from Case for 10 Seconds	260°C

NOTES: 1. Interbase voltage is limited solely by power dissipation, $V_{B2-B1} \leq \sqrt{P_{B2-B1} \cdot R_{\theta JA}}$

2 This value applies for a capacitive discharge through the emitter-base one diode. Current must fall to 0.37 A within 3 ms and pulse repetition rate must not exceed 10 pps.

3. Derate linearly to 175°C free air temperature at the rate of 2.4 mW/deg

*Indicates JEOEC registered data

*Courtesy of Texas Instruments, Incorporated

TYPES 2N3980, 2N4947 THRU 2N4949 **P-N PLANAR UNIJUNCTION SILICON TRANSISTORS**

*electrical characteristics at 25°C free-air temperature (unless otherwise noted)

PARAMETER	TEST CONDITIONS	2N3980		2N4947		2N4948		2N4949		UNIT
		MIN	MAX	MIN	MAX	MIN	MAX	MIN	MAX	
r_{BB} Static Interbase Resistance	$V_{B2, B1} = 3 \text{ V}, I_E = 0$	4	8	4	9.1	4	12	4	12	k Ω
$r_{E, BB}$ Interbase Resistance	$V_{B2, B1} = 3 \text{ V}, I_E = 0, T_A = -45^\circ\text{C to } 100^\circ\text{C}$	See Note 4								
α_T Intrinsic Standoff Ratio	$V_{B2, B1} = 10 \text{ V}$, See Figure 1	0.4	0.9	0.1	0.9	0.1	0.9	0.1	0.9	%/deg
$I_{B2(mod)}$ Modulated Interbase Current	$V_{B2, B1} = 10 \text{ V}, I_E = 50 \text{ mA}$, See Note 5	12		12		12		12		mA
I_{EB2O} Emitter Reverse Current	$V_{B2, B1} = -30 \text{ V}, I_{B1} = 0$	-10		-10		-10		-10		μA
	$V_{B2, B1} = -30 \text{ V}, I_{B1} = 0, T_A = 125^\circ\text{C}$	-1		-1		-1		-1		μA
I_P Peak Point Emitter Current	$V_{B2, B1} = 25 \text{ V}$	2		2		2		1		μA
$V_{EB1(sat)}$ Emitter-Base-One Saturation Voltage	$V_{B2, B1} = 10 \text{ V}, I_E = 50 \text{ mA}$, See Note 5	.3		.3		.3		.3		V
I_V Valley Point Emitter Current	$V_{B2, B1} = 20 \text{ V}$	1	10	4		2		2		mA
V_{CB1} Base-One Peak Pulse Voltage	See Figure 2	6		3		6		3		V

NOTES: 4. Temperature coefficient α_T is determined by the following formula:

$$\alpha_T = \left[\frac{(r_{BB} @ 100^\circ\text{C}) - (r_{BB} @ -45^\circ\text{C})}{r_{BB} @ 25^\circ\text{C}} \right] \frac{100\%}{165 \text{ deg}}$$

To obtain r_{BB} for a given temperature $T_{A(2)}$, use the following formula:

$$r_{BB(2)} = [r_{BB} @ 25^\circ\text{C}] [1 + (\alpha_T/100\%)(T_{A(2)} - 25^\circ\text{C})]$$

5. These parameters are measured using pulse techniques. $I_P = 300 \mu\text{A}$, duty cycle $\leq 2\%$.

***PARAMETER MEASUREMENT INFORMATION**

 


FIGURE 1 — TEST CIRCUIT FOR INTRINSIC STANDOFF RATIO (η)

η — Intrinsic Standoff Ratio — This parameter is defined in terms of the peak point voltage, V_P , by means of the equation: $V_P = \eta V_{B2, B1} + V_B$, where V_B is about 0.56 volt at 25°C and decreases with temperature at about 3 millivolts/deg.

The circuit used to measure η is shown in the figure. In this circuit, R_1 , C_1 and the unijunction transistor form a relaxation oscillator, and the remainder of the circuit serves as a peak voltage detector with the diode D_1 automatically subtracting the voltage V_B . To use the circuit, the "cal" button is pushed, and R_2 is adjusted to make the current meter M_1 read full scale. The "cal" button then is released and the value of η is read directly from the meter, with $\eta = 1$ corresponding to full scale deflection of 100 μA .

D_1 : 1N437, or equivalent, with the following characteristics:

$V_F = 0.565 \text{ V}$ at $I_F = 50 \mu\text{A}$,

$I_R \leq 2 \mu\text{A}$ at $V_R = 20 \text{ V}$

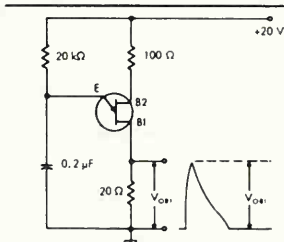


FIGURE 2 — V_{CB1} TEST CIRCUIT

*Indicates JEDEC registered data

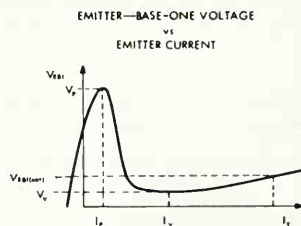


FIGURE 3 — GENERAL STATIC EMITTER CHARACTERISTIC CURVE

APPENDIX 1-13*



SILICON PROGRAMMABLE
UNIUNCTION TRANSISTORS

designed to enable the engineer to "program" unijunction characteristics such as R_{BB} , η , I_V , and I_P by merely selecting two resistor values. Application includes thyristor trigger, oscillator, pulse and timing circuits. These devices may also be used in special thyristor applications due to the availability of an anode gate. Supplied in an inexpensive TO 92 plastic package for high volume requirements, this package is readily adaptable for use in automatic insertion equipment.

- Programmable – R_{BB} , η , I_V and I_P
- Low On-State Voltage – 1.5 Volts Maximum @ $I_F = 50\text{ mA}$
- Low Gate to Anode Leakage Current – 10 nA Maximum
- High Peak Output Voltage – 11 Volts Typical
- Low Offset Voltage – 0.35 Volt Typical ($R_G = 10\text{ k ohms}$)

SILICON
PROGRAMMABLE UNIUNCTION
TRANSISTORS


40 VOLTS
375 mW



MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Power Dissipation (1) Derate Above 25°C	P_F $1/\theta_{JA}$	375 5.0	mW mW/°C
DC Forward Anode Current (2) Derate Above 25°C	I_T	200 2.67	mA mA/°C
*DC Gate Current	I_G	±50	mA
Repetitive Peak Forward Current 100 μ s Pulse Width, 1.0% Duty Cycle *20 μ s Pulse Width, 1.0% Duty Cycle	I_{TRM}	1.0 2.0	Amp Amp
Non-Repetitive Peak Forward Current 10 μ s Pulse Width	I_{TSM}	5.0	Amp
*Gate to Cathode Forward Voltage	V_{GKF}	40	Volt
*Gate to Cathode Reverse Voltage	V_{GKR}	-5.0	Volt
*Gate to Anode Reverse Voltage	V_{GAR}	40	Volt
*Anode to Cathode Voltage	V_{AK}	±40	Volt
Operating Junction Temperature Range	T_J	-50 to +100	°C
*Storage Temperature Range	T_{stg}	-55 to +150	°C

*Indicates JEDEC Registered Data
(1) JEDEC Registered Data is 300 mW, derating at 4.0 mW/°C.
(2) JEDEC Registered Data is 150 mA

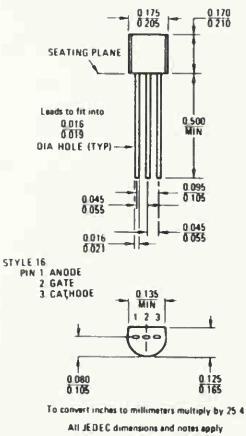

CASE 29-02
TO 92
PLASTIC

*Courtesy of Motorola, Inc.

2N6027, 2N6028 (continued)

ELECTRICAL CHARACTERISTICS (T_A = 25°C unless otherwise noted)

Characteristic	Figure	Symbol	Min	Typ	Max	Unit
•Peak Current (V _S = 10 Vdc, R _G = 1.0 MΩ) (V _S = 10 Vdc, R _G = 10 k ohms)	2,9,11 2N6027 2N6028 2N6027 2N6028	I _p	— — — —	1.25 0.08 4.0 0.70	2.0 0.15 5.0 1.0	μA
•Offset Voltage (V _S = 10 Vdc, R _G = 1.0 MΩ) (V _S = 10 Vdc, R _G = 10 k ohms)	1 2N6027 2N6028 (Both Types)	V _T	0.2 0.2 0.2	0.70 0.50 0.35	1.6 0.6 0.6	Volts
•Valley Current (V _S = 10 Vdc, R _G = 1.0 MΩ) (V _S = 10 Vdc, R _G = 10 k ohms) (V _S = 10 Vdc, R _G = 200 Ohms)	1,4,5 2N6027 2N6028 2N6027 2N6028 2N6027 2N6028	I _V	— — 70 25 1.5 1.0	18 18 270 270 — —	50 25 — — — —	μA mA
•Gate to Anode Leakage Current (V _S = 40 Vdc, T _A = 25°C, Cathode Open) (V _S = 40 Vdc, T _A = 75°C, Cathode Open)	— —	I _{G AO}	— —	1.0 3.0	10 —	nAdc
•Gate to Cathode Leakage Current (V _S = 40 Vdc, Anode to Cathode Shorted)	—	I _{G KS}	—	5.0	50	nAdc
•Forward Voltage (I _F = 50 mA Peak)	1,6	V _F	—	0.8	1.5	Volts
•Peak Output Voltage (V _B = 20 Vdc, C _C = 0.2 μF)	3,7	V _O	6.0	11	—	Volts
•Pulse Voltage Rise Time (V _B = 20 Vdc, C _C = 0.2 μF)	3	t _r	—	40	80	ns

* Indicates JEDEC Registered Data

FIGURE 1 – ELECTRICAL CHARACTERIZATION

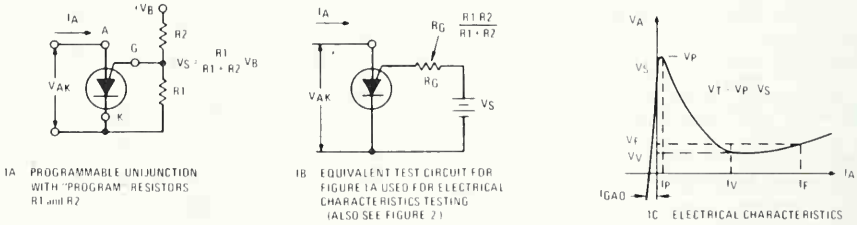


FIGURE 2 – PEAK CURRENT (I_p) TEST CIRCUIT


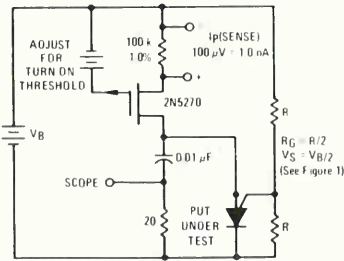


FIGURE 3 – V_O AND t_r TEST CIRCUIT

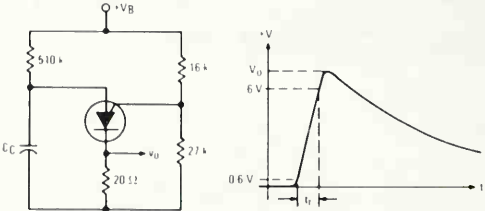


DUAL J-K FLIP-FLOP

MHTL MC660 series

MC663P

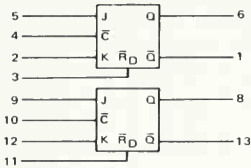Two J-K flip-flops in a single package. Each flip-flop has a direct reset input in addition to the clocked inputs.




TRUTH TABLE

t_n		t_{n+1}	
J	K	Q	\bar{Q}
0	0	Q_n	\bar{Q}_n
1	0	1	0
0	1	0	1
1	1	\bar{Q}_n	Q_n

Input Loading Factor
 \bar{R}_D Input = 2
 \bar{C} Input = 1.5
Other Inputs = 1
Output Loading Factor = 9
Loading factors are valid from -30°C to $+75^\circ\text{C}$
with $V_{CC} = 15 \pm 1 \text{ Vdc}$
 $t_{Tog} = 3.0 \text{ MHz typ}$
Total Power Dissipation = 200 mW typ

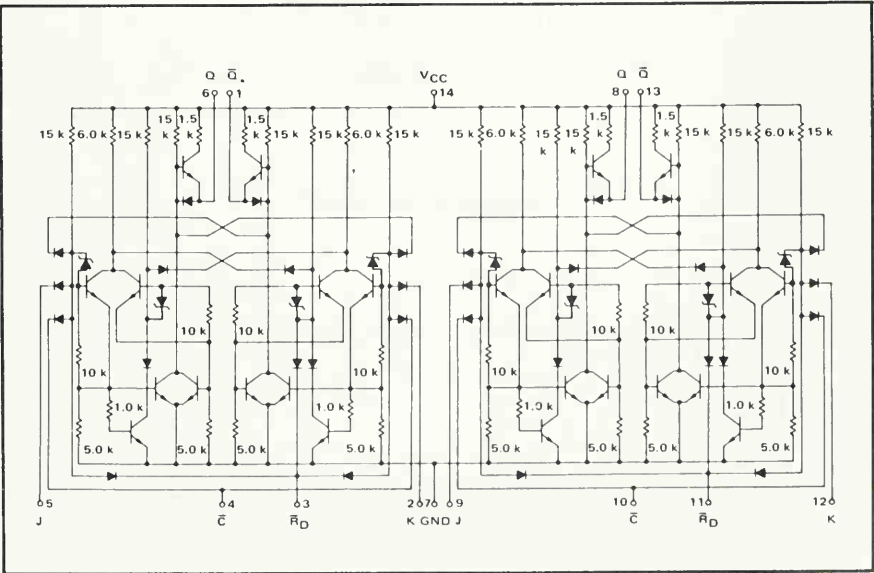Direct Input (\bar{R}_D) must be high.
0 = low state
1 = high state
 t_n = time period prior to negative transition of clock pulse
 t_{n+1} = time period subsequent to negative transition of clock pulse
 Q_n = state of Q output in time period t_n
NOTE: A low state "0" at the direct reset \bar{R}_D causes a low state "0" at the Q output and the complement at the \bar{Q} output.




MC663P (continued)

ELECTRICAL CHARACTERISTICS



Unless otherwise noted, tests are shown for only one flip-flop. The other flip-flop is tested in the same manner.

Unless otherwise noted, tests are shown for only one flip-flop. The other flip-flop is tested in the same manner.										TEST CURRENT / VOLTAGE VALUES (All Temperatures)								CP _A	CP _B	Ground
				mA				Volts												
		I _{OL}	I _{OH}	V _{IL}	V _{IH}	V _I	V _S	V _{CECL}	V _{CECH}											
		10, 8	-0.027	6.50	8.50	1.5	16.0	14.0	16.0											
										TEST CURRENT / VOLTAGE APPLIED TO PINS LISTED BELOW										
Characteristic	Symbol	Pin Under Test	TEST LIMITS						Unit	I _{OL}	I _{OH}	V _{IL}	V _{IH}	V _I	V _S	V _{CECL}	V _{CECH}			
			-30°C		+25°C		+75°C													
			Min	Max	Min	Max	Min	Max												
Output Voltage	V _{OL} V _{OH}	1	-	1.5	-	1.5	-	1.5	V _{dc}	1	-	2	3, 5	-	-	14	-	4	-	7
		6	-	1.5	-	1.5	-	1.5	6	-	5	2, 3	-	-	14	-	4	-	7	
		1	-	-	12.5	-	12.5	-	-	-	1	2, 3	5	-	-	14	-	4	-	7
		1	-	-	12.5	-	12.5	-	-	-	1	5	2, 3	-	-	14	-	4	-	7
		6	-	-	12.5	-	12.5	-	-	-	6	2	3, 5	-	-	14	-	4	-	7
Short-Circuit Current	I _{SC}	1	-	-	-6.5	-15	-6.5	-15	mAdc	-	-	3, 4	-	-	-	14	-	-	1, 7	
Reverse Current	I _R 3 _R 2 _R 1 _R	2	-	-	-	2.0	-	2.0	μAdc	-	-	-	-	-	2	14	-	-	3, 4, 5, 7	
		3	-	-	-	6.0	-	6.0	-	-	-	-	-	3	2, 4, 5, 14	-	-	7		
		4	-	-	-	4.0	-	4.0	-	-	-	-	-	4	14	-	-	2, 3, 5, 7		
		5	-	-	-	2.0	-	2.0	-	-	-	-	-	5	14	-	-	2, 3, 4, 7		
Forward Current	I _F	2	-	-	-	-1.20	-	-1.20	mAdc	-	-	-	2	-	-	14	-	4	7	
		3	-	-	-	-1.20	-	-1.20	-	-	-	-	3	-	-	14	-	2, 4, 5, 7		
		4	-	-	-	-1.20	-	-1.20	-	-	-	-	4	-	-	2, 5, 14	-	7		
		5	-	-	-	-1.20	-	-1.20	-	-	-	-	5	-	-	14	-	4	7	
Power Drain Current (Both Flip-Flops)	I _{CCL} I _{CCH}	14	-	-	-	16.7	-	-	mAdc	-	-	-	-	-	-	14	-	-	2, 3, 4, 5, 7, 9, 10, 11, 12	
		14	-	-	-	16.7	-	-	mAdc	-	-	-	-	-	-	14	-	-	7	

Pins not listed are left open.

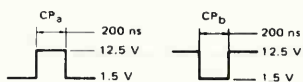 $t_r \leq 1.0 \mu s$ (10% to 90%) $t_f \leq 1.0 \mu s$ (90% to 10%)

TOGGLE MODE TEST CIRCUIT

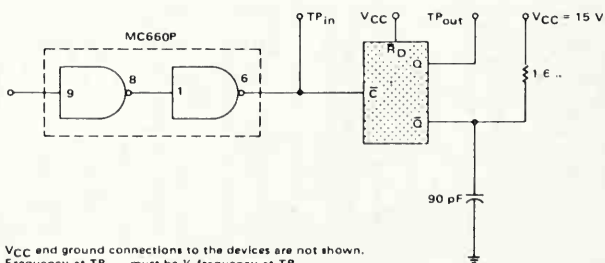
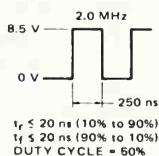


V_{CC} and ground connections to the devices are not shown. Frequency at TP_{OUT} must be 1/2 frequency at TP_{IN}.

EXPANDABLE DUAL 4-INPUT GATES
MC930F · MC830F, P
MC961F · MC861F, P


EXPANDABLE DUAL 3-2 INPUT GATES
MC930G · MC830G
MC961G · MC861G

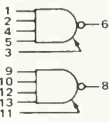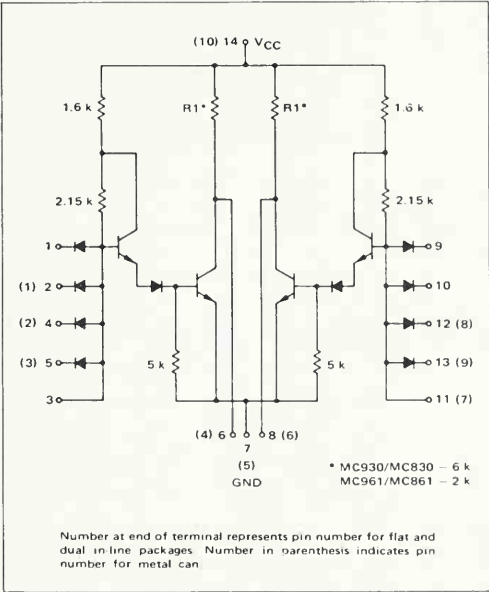This gate element, in the 14-pin flat and dual in-line packages, consists of two expandable 4-input NAND gate circuits. Since the metal can (G suffix) has only 10 pins, that circuit consists of one 3-input and one 2-input expandable gate. The elements may be cross-coupled to form a bistable multivibrator, or the outputs may be connected in parallel to perform the logic "OR" function.



MC930F/MC830F, P
MC961F/MC861F, P

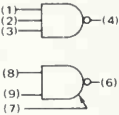Positive Logic: $6 = 1 \cdot 2 \cdot 4 \cdot 5 \cdot [3]$
Negative Logic: $6 = 1 + 2 + 4 + 5 + [3]$




MC930G/MC830G
MC961G/MC861G

Positive Logic: $4 = 1 \cdot 2 \cdot 3$
Negative Logic: $4 = 1 + 2 + 3$

Input Loading Factor = 1
Output Loading Factor
MC930/MC830 = 8
MC961/MC861 = 7
Total Power Dissipation
MC930/MC830 = 22 mW typ/pkg
MC961/MC861 = 33 mW typ/pkg
Propagation Delay Time
MC930/MC830 = 30 ns typ
MC961/MC861 = 25 ns typ

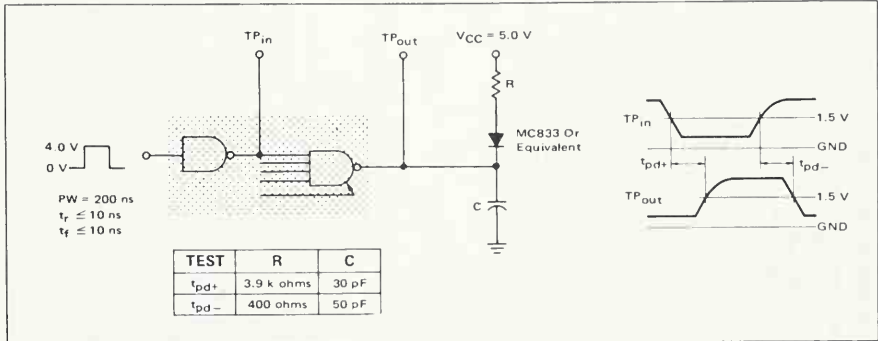SWITCHING TIME TEST CIRCUIT AND WAVEFORMS



*Courtesy of Motorola, Inc.

MC930F/MC830F, P, MC961F/MC861F, P (continued)
MC930G/MC830G, MC961G/MC861G (continued)

ELECTRICAL CHARACTERISTICS

Test procedures are shown for only one gate. The other gate is tested in the same manner.

NOTE: Although the test conditions and test limits are the same for devices in ALL available packages, the table shows pin connections for testing only the flat and dual in-line packaged devices. To test devices in the metal can, substitute pin numbers shown in the conversion table below.



PACKAGE	PIN NUMBER													
Flat/Dual In-Line	1	2	3	4	5	6	7	8	9	10	11	12	13	14
Metal Can	—	1	—	2	3	4	5	6	—	—	7	8	9	10

Characteristic	Symbol	Pin Under Test	MC930, MC961 TEST LIMITS						MC830, MC861 TEST LIMITS								
			-55°C			+25°C			0°C			+25°C			+75°C		
			Min	Max	Unit	Min	Max	Unit	Min	Max	Unit	Min	Max	Unit	Min	Max	Unit
Output Voltage	V _{OL}	6	-	0.40	-	0.40	-	0.45	V _{dc}	-	0.45	-	0.45	-	0.50	V _{dc}	
	V _{OH}	6	2.50	-	2.60	-	2.50	-		2.60	-	2.60	-	2.50	-		
		8	-	-	-	-	-	-		-	-	-	-	-	-	-	
		↑	-	-	-	-	-	-		-	-	-	-	-	-	-	
Short-Circuit Current																	
I _{SC}		6	-	-1.34	-	-1.34	-	-1.30	mA _{dc}	-	-1.30	-	-1.30	-	-1.25	mA _{dc}	
		8	-	-4.00	-	-4.00	-	-3.90	mA _{dc}	-	-3.90	-	-3.90	-	-3.75	mA _{dc}	
Reverse Current	I _R	1	2.0	-	2.0	-	5.0	μA _{dc}		5.0	-	5.0	-	10	μA _{dc}		
		2	-	-	-	-	-	-		-	-	-	-	-	-		
		5	-	-	-	-	-	-		-	-	-	-	-	-		
Output Leakage Current	I _{CEX}	6	-	-	-	50	-	μA _{dc}		-	-	100	-	-	μA _{dc}		
Forward Current	I _F	1	-	-1.60	-	-1.60	-	-1.50	mA _{dc}	-	-1.40	-	-1.40	-	-1.33	mA _{dc}	
		2	-	-	-	-	-	-		-	-	-	-	-	-		
		4	-	-	-	-	-	-		-	-	-	-	-	-		
		5	-	-	-	-	-	-		-	-	-	-	-	-		
Power Drain Current (Total Device)	I _{PDH}	14	-	-	-	6.5	-	mA _{dc}		-	-	8.0	-	-	mA _{dc}		
MC930, MC961	I _{PDH}	14	-	-	-	10.7	-	-		-	-	13.1	-	-	-		
MC930, MC961	I _{max}	14	-	-	-	5.5	-	-		-	-	8.0	-	-	-		
All Types																	
Switching Times																	
MC930, MC830	t _{pd+}	1, 6	-	-	25	80	-	ns		-	25	80	-	-	ns		
	t _{pd-}	1, 8	-	-	10	30	-	-		-	10	30	-	-	-		
MC961, MC861	t _{pd+}	1, 6	-	-	15	80	-	-		-	15	60	-	-	-		
	t _{pd-}	1, 6	-	-	10	30	-	-		-	10	25	-	-	-		

[illegible]


Pins not listed are left open.

3-INPUT GATES


MECL MC300 series

MC306 • MC307

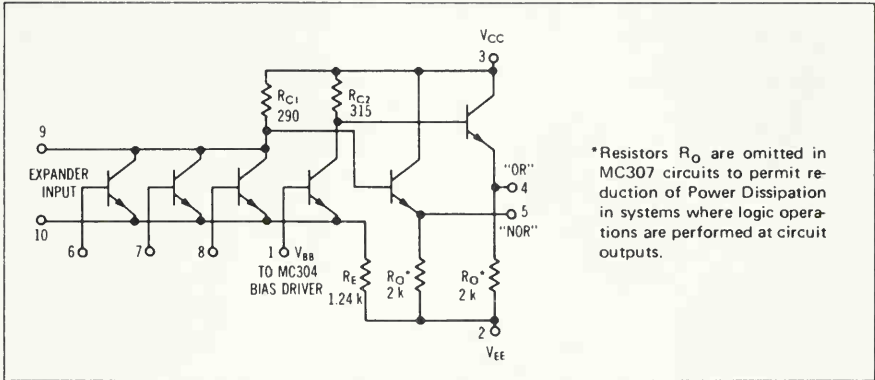
Expandable 3-input gates that provide the positive logic "NOR" function and its complement simultaneously. MC307 omits output pull-down resistors, permitting reduction of power dissipation.




SWITCHING TIME TEST CIRCUIT

 

PROPAGATION DELAY

 

RISE AND FALL TIME

 

Fan-in obtained with MC305 input expanders; all but driven input connected to -5.2 V.


*Courtesy of Motorola, Inc.

ELECTRICAL CHARACTERISTICS

Characteristic		Test Conditions V _{dc} ± 1%										Test Limits						Unit	
		-55°C		+25°C		+125°C		-55°C		+25°C		+125°C							
		Min	Max	Min	Max	Min	Max	Min	Max	Min	Max	Min	Max						
Power Supply	MC306	—	—	—	2.6.7.8	1	—	—	3	I _h (2)	—	8.85	—	8.85	—	8.15	mAdc		
Grain Current	MC307	—	—	—	2.6.7.8	1	—	—	3	I _h (2)	—	3.6	—	3.6	—	3.3	mAdc		
Input Current	6	—	—	—	2.7.8	1	—	—	3	I _h (6)	—	—	—	100	—	—	μAdc		
	7	—	—	—	2.6.8	1	—	—	3	I _h (7)	—	—	—	↓	—	—	↓		
	8	—	—	—	2.6.7	1	—	—	3	I _h (8)	—	—	—	—	—	—	↓		
"NOR" Logical "1" Output Voltage	—	—	6	—	2.7.8	1	—	—	3	V _h (5)	-0.825	-0.945	-0.690	-0.795	-0.525	-0.655	V _{dc}		
	—	—	7	—	2.6.8	1	—	—	3	V _h (5)	—	—	—	—	—	—	↓		
	—	—	8	—	2.6.7	1	—	—	3	V _h (5)	—	—	—	—	—	—	↓		
"NOR" Logical "0" Output Voltage	—	6	—	—	2.7.8	1	—	—	3	V _h (5)	-1.560	-1.450	-1.465	-1.750	-1.340	-1.675	V _{dc}		
	—	7	—	—	2.6.8	1	—	—	3	V _h (5)	—	—	—	—	—	—	↓		
	—	8	—	—	2.6.7	1	—	—	3	V _h (5)	—	—	—	—	—	—	↓		
"OR" Logical "1" Output Voltage	—	6	—	—	2.7.8	1	—	—	3	V _h (4)	-0.825	-0.945	-0.690	-0.795	-0.525	-0.655	V _{dc}		
	—	7	—	—	2.6.8	1	—	—	3	V _h (4)	—	—	—	—	—	—	↓		
	—	8	—	—	2.6.7	1	—	—	3	V _h (4)	—	—	—	—	—	—	↓		
"OR" Logical "0" Output Voltage	—	6	—	—	2.7.8	1	—	—	3	V _h (4)	-1.560	-1.450	-1.465	-1.750	-1.340	-1.675	V _{dc}		
	—	7	—	—	2.6.8	1	—	—	3	V _h (4)	—	—	—	—	—	—	↓		
	—	8	—	—	2.6.7	1	—	—	3	V _h (4)	—	—	—	—	—	—	↓		
"NOR" Output Voltage Change (No load to full load)	—	—	6	—	2.7.8	1	—	5 ①	3	ΔV _h (5)	—	-0.055	—	-0.055	—	-0.060	Volts		
	—	—	7	—	2.6.8	1	—	4 ②	3	ΔV _h (4)	—	-0.055	—	-0.055	—	-0.060	Volts		
"OR" Output Voltage Change (No load to full load)	—	—	6	—	2.7.8	1	—	4 ③	3	ΔV _h (4)	—	-0.055	—	-0.055	—	-0.060	Volts		
	—	—	7	—	2.6.8	1	—	—	3	ΔV _h (4)	—	—	—	—	—	—	↓		
"NOR" Saturation Breakpoint Voltage	—	—	—	—	2.7.8	1	6 ④	—	3	V _h (5)	—	-0.40	—	-0.55	—	-0.68	V _{dc}		
	—	—	—	—	2.6.8	1	7 ④	—	3	V _h (5)	—	—	—	—	—	—	↓		
—	—	—	—	—	2.6.7	1	8 ④	—	3	V _h (5)	—	—	—	—	—	—	↓		
Switching Times	Pulse In	Pulse Out									Typ		Max		Typ		Max		ns
Propagation Delay Time	6	4	—	—	2.7.8	1	—	—	3	t _{eh} (4)	7.0	11.0	7.0	11.5	9.5	14.5			
	6	5	—	—	2.7.6	1	—	—	3	t _{eh} (5)	5.5	10.0	5.5	10.5	7.0	12.5			
	6	4	—	—	2.7.8	1	—	—	3	t _{eh} (4)	5.5	10.0	5.5	11.0	7.0	12.5			
	6	5	—	—	2.7.6	1	—	—	3	t _{eh} (5)	7.0	10.5	7.0	11.0	9.5	14.5			
Rise Time	6	4	—	—	2.7.8	1	—	—	3	t _r (4)	6.0	8.5	6.0	10.0	8.0	13.0			
	6	5	—	—	2.7.6	1	—	—	3	t _r (5)	7.5	11.5	7.5	12.5	9.5	15.0			
Fall Time	6	4	—	—	2.7.8	1	—	—	3	t _f (4)	6.5	10.5	6.5	12.0	9.0	15.0			
	6	5	—	—	2.7.6	1	—	—	3	t _f (5)	6.5	12.0	6.5	12.5	9.0	15.0			

Pins not listed are left open ① Input voltage is adjusted to obtain dV_{ih} "NOR" / dV_{ih} = 0 ② Current test conditions: no load = 0, full load = -2.5mAdc ± 5%

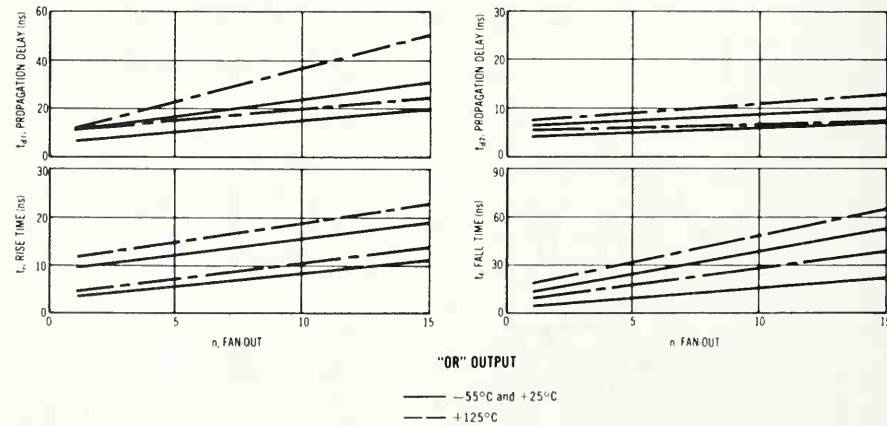SWITCHING CHARACTERISTICS (10% to 90% distribution)






0.3" SOLID STATE
SEVEN SEGMENT
INDICATOR

5082-7740

TENTATIVE DATA AUGUST 1973

Features

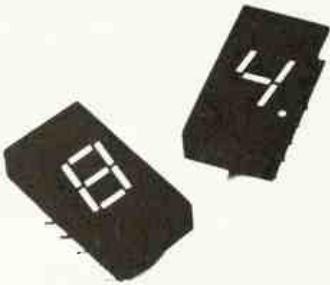- COMMON CATHODE
- RIGHT HAND DP
- EXCELLENT CHARACTER APPEARANCE
 - Continuous Uniform Segments
 - Wide Viewing Angle
 - High Contrast
- IC COMPATIBLE
 - 1.7V per Segment
- STANDARD 0.3" DIP LEAD CONFIGURATION
 - PC Board or Standard Socket Mountable
- CATEGORIZED FOR LUMINOUS INTENSITY
 - Assures Uniformity of Light Output from Unit to Unit within a Single Category




Description

The HP 5082-7740 is a common cathode LED numeric display with a right hand decimal point. The large 0.3" high character size generates a bright, continuously uniform 7 segment display. Designed for viewing distances of up to 10 feet, this single digit display has been human engineered to provide a high contrast ratio and wide viewing angle.

The 5082-7740 utilizes a standard 0.3" dual-in-line package configuration that allows for quick mounting on PC boards or in standard IC sockets. Requiring a forward voltage of only 1.7V, the display is inherently IC compatible allowing for easy integration into electronic calculators, credit card verifiers, TVs, radios, and digital clocks.

Package Dimensions

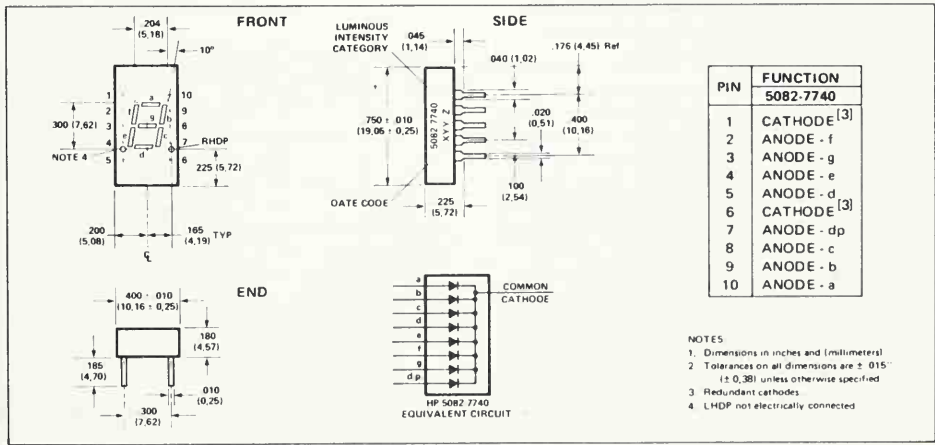

*Courtesy of Hewlett Packard, Inc.

Absolute Maximum Ratings

Power Dissipation $T_A = 25^{\circ}\text{C}$	400mW
Operating Temperature Range	-20°C to $+85^{\circ}\text{C}$
Storage Temperature Range	-20°C to $+85^{\circ}\text{C}$
Average Forward Current/Segment or Decimal Pt. $T_A = 25^{\circ}\text{C}$ [1]	25 mA
Peak Forward Current/Segment or Decimal Pt. $T_A = 25^{\circ}\text{C}$ (Pulse Duration $\leq 500\mu\text{s}$)	150mA
Reverse Voltage/Segment or Decimal Pt.	6V
Max. Solder Temperature 1/16" Below Seating Plane ($t \leq 5 \text{ sec.}$) [2]	230°C

NOTES: 1. Derate from 25°C at .25mA/ $^{\circ}\text{C}$ per segment or D.P. 2. Clean only in Freon TF, Isopropanol, or water.

Electrical/Optical Characteristics at $T_A=25^{\circ}\text{C}$

Description	Symbol	Test Condition	Min.	Typ.	Max.	Units
Luminous Intensity/Segment [1]	$I_{\nu \text{ AVE}}$	$I_{\text{PEAK}} = 100\text{mA}$ 10% Duty Cycle	50	150		μcd
		$I_F = 20\text{mA DC}$		250		
Peak Wavelength	λ_{PEAK}			655		nm
Forward Voltage/Segment or D.P.	V_F	$I_F = 100\text{mA}$		1.6	2.3	V
Reverse Current/Segment or D.P.	I_R	$V_R = 6\text{V}$			100	μA
Rise and Fall Time [2]	t_r, t_f			10		ns
Temperature Coefficient of Forward Voltage	$\Delta V_F / ^{\circ}\text{C}$			-2.0		mV/ $^{\circ}\text{C}$
Temperature Coefficient of Luminous Intensity	$\Delta I_{\nu} / ^{\circ}\text{C}$			-1.0		%/ $^{\circ}\text{C}$

NOTES: 1. The digits are categorized for luminous intensity such that the variation from digit to digit within a category is not discernible to the eye. Intensity categories are designated by a letter located on the right hand side of the package.
2. Time for a 10%-90% change of light intensity for step change in current.

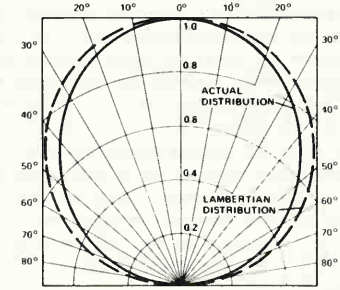


Figure 1. Normalized Angular Distribution of Luminous Intensity.

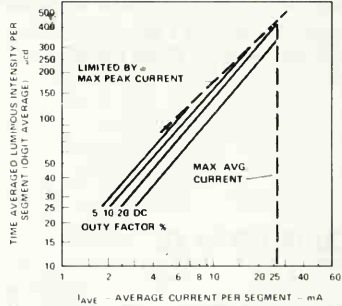


Figure 2. Typical Time Averaged Luminous Intensity per Segment versus Average Current.

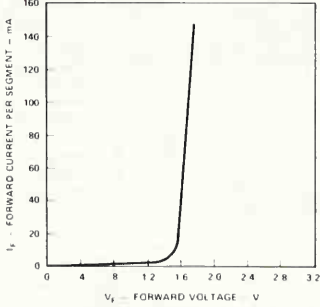


Figure 3. Forward Current versus Forward Voltage.

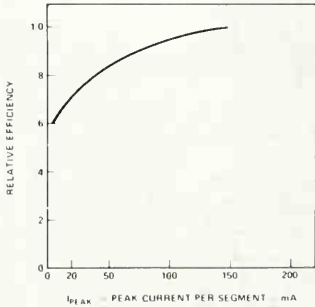


Figure 4. Relative Efficiency (Luminous Intensity per Unit Current) versus Peak Current per Segment.

For more information, call your local HP Sales Office or East (201) 265-5000-Midwest (312) 677-0400-South (404) 436-6181-West (213) 877-1282. Or, write: Hewlett-Packard, 1501 Page Mill Road, Palo Alto, California 94304. In Europe, Post Office Box 85, CH-1217 Meyrin 2, Geneva, Switzerland. In Japan, YHP, 1-59-1, Yoyogi, Shibuya-Ku, Tokyo, 151.

Printed in U.S.A.

BULLETIN LC 1003
MARCH, 1973



**SERIES 1603-02
REFLECTIVE**

LIQUID CRYSTAL DISPLAYS

- **Optimum Readability**
- **Single Plane Viewing**
- **MOS Compatibility**
- **No Back Lighting Required**

- **Low Profile**
- **Microwatt Power Consumption**
- **Low Cost**
- **Ideal for High Ambient Light Environment**

The IEE Series 1603-02 is a $3\frac{1}{2}$ decade Liquid Crystal Display with four floating decimals and an overflow plus or minus one (\pm). A colon is incorporated in the display for additional application-advantages such as clocks, etc.


The IEE Series 1603-02 reflective Liquid Crystal Display consists of a layer of micron-thin liquid crystal material confined between two sheets of glass, one sheet having a clear conductive electrode and the other a reflective coating etched in a segmented pattern to create a digital display. The organic material requires extremely low power in order to be an effective display. Upon generation of an electric field, the liquid layer becomes turbulent and scatters light. This scattering effect (caused by a continuous change in the index of refraction) appears as an optically dense area; by selectively

energizing appropriate segments, a digital format is obtained. When the applied field is removed, the liquid crystal material returns to its original quiescent, transparent condition.

Reflective displays eliminate the need for back-lighting, which makes them excellent displays for use in portable equipment or in equipment where low power consumption is a definite consideration.

For optimum life, liquid crystals are operated on A.C. (40-100 Hz) which, coupled with a 15-30 volt range, make them directly compatible with MOS logic. Numerous companies are engaged in the manufacture of standard MOS circuits for use with Liquid Crystal Displays and this list may be obtained from Industrial Electronic Engineers, Inc. (IEE) upon request.

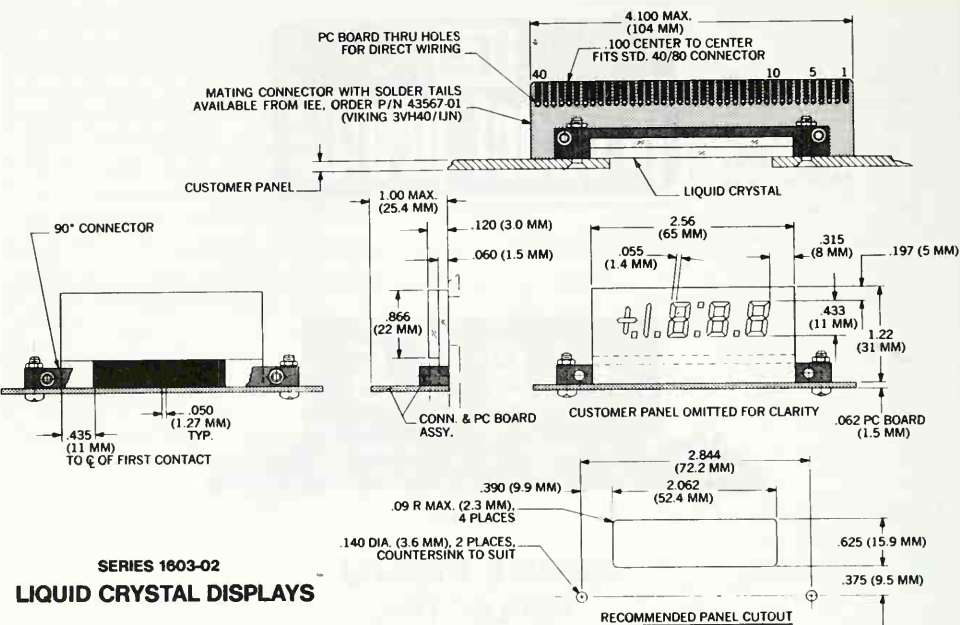*Courtesy of Industrial Electronic Engineers, Inc.



ELECTRICAL SPECIFICATIONS

Operating Voltage: A.C. 40-100 Hz. Typical 24 Volt (Peak to Peak). Maximum 40 Volt. Minimum 10 Volt.

Power Consumption: 20 microwatts per segment (maximum).

Rise Time: 50 milliseconds.

Decay Time: 150 milliseconds.

Contrast Ratio: 15:1 minimum.

Life: 10,000 hrs. minimum at 24 V.A.C.

Operating Temperature: 5°C to 55°C.

Storage Temperature: -10°C to 70°C.

Relative Humidity: 0 to 100%.

MECHANICAL SPECIFICATIONS

Package Size: See diagram.

Character Size: .433" (11 MM).

Character Width: .260" (7.6 MM).

Segment Width: .055" (1.4 MM).

Decimal Point Width: .06" (1.5 MM).

Decimal Point Height: .08" (2 MM).

Contacts:

The conductive electrodes on the Series 1603-02 Liquid Crystal Displays are terminated in an edge board configuration having .050" (1.3 MM) spacing, which allows the use of an edge connector or a spring contact right angle connector to be used in conjunction with printed circuit board patterns.

ORDERING INFORMATION

	Part No.
Liquid Crystal	1603-02
Right Angle Connector	22076-01
Mounting Kit (PC Board with right angle connector attached)	22077-01

AVAILABILITY:

Series 1603-02 displays and optional hardware (connector, PC boards) are available for customer evaluation from shelf stock. For large quantity requirements and/or special designs, consult IEE for information.



Industrial Electronic Engineers, Inc.

7720 Lemona Avenue, Van Nuys, California 91405

Phone: (213) 787-0311 TWX (910) 495-1707

Our European Office: 6707 Schifferstadt, Eichendorff-Allee 19, Germany, Phone: 06235-662.

ALCO[®] INCANDESCENT READOUTS

MS-5030E SERIES 7-SEGMENT READOUTS

Presenting a series that combines several of the most sought features — large, well-styled characters; bright, wide angle display; low voltage operation; compatibility with available TTL integrated circuit decoder drivers; and low cost. These 5 volt plug-in display units produce 0.79" high characters, plus a decimal point. Each unit consists of a molded phenolic lamp housing with eight T-1 lamps, a filter screen and a polycarbonate filter lens, and pin terminations for use with sockets or decoder driver modules. Unit is supplied less socket (order separately, see below).

SPECIFY FILTER COLOR: Red or Clear.

SPECIFICATIONS:

Temperature Rise:
20°C.

Vibration:
3.0G @ 1,600 Hz., 1 min.
each of three planes.

Weight:
0.7 oz. (Max.), less socket

Materials:
Case: Black phenolic resin
Lens: Polycarbonate resin
Pins: Nickel plated brass

Lamps:
T-1 5V @ 30mA


Current Drain:
60mA (Min.), 240mA (Max.)

Power Consumption:
300mW (Min.), 1.2W Max.)

Character Height:
0.79 inches

Lamp M.S.C.P.:
0.028 candlepower

Lamp Life:
20,000 hours (average)

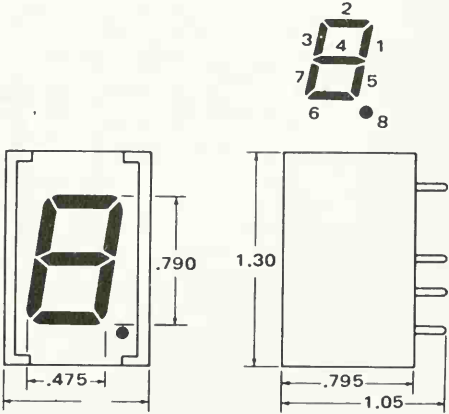

*Courtesy of Alco Electronics Inc.





μ A710 HIGH-SPEED DIFFERENTIAL COMPARATOR FAIRCHILD LINEAR INTEGRATED CIRCUITS

- IMPROVED SPECIFICATIONS
- 2 mV MAXIMUM OFFSET VOLTAGE
- 3 μ A MAXIMUM OFFSET CURRENT
- 1250 MINIMUM VOLTAGE GAIN
- 10 μ V/ $^{\circ}$ C MAXIMUM OFFSET VOLTAGE DRIFT

GENERAL DESCRIPTION — The μ A710 is a differential voltage comparator intended for applications requiring high accuracy and fast response times. It is constructed on a single silicon chip using the Fairchild Planar* epitaxial process. The device is useful as a variable threshold Schmidt trigger, a pulse height discriminator, a voltage comparator in high-speed A-D converters, a memory sense amplifier or a high-noise immunity line receiver. The output of the comparator is compatible with all integrated logic forms.

ABSOLUTE MAXIMUM RATINGS

Positive Supply Voltage	+14.0 V
Negative Supply Voltage	-7.0 V
Peak Output Current	10 mA
Differential Input Voltage	± 5.0 V
Input Voltage	± 7.0 V
Internal Power Dissipation	
TO-99 [Note 1]	300 mW
Flat Package [Note 2]	200 mW
Operating Temperature Range	-55 $^{\circ}$ C to +125 $^{\circ}$ C
Storage Temperature Range	-65 $^{\circ}$ C to +150 $^{\circ}$ C
Lead Temperature (Soldering, 60 sec.)	300 $^{\circ}$ C

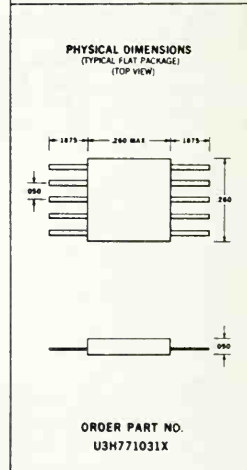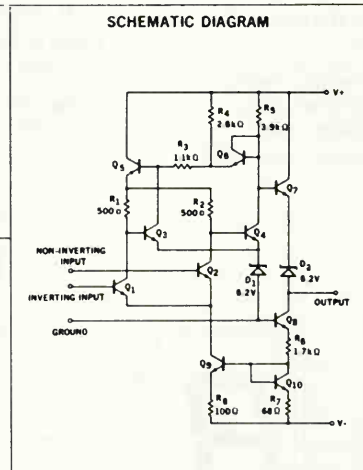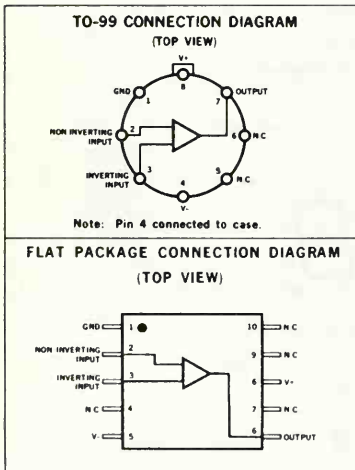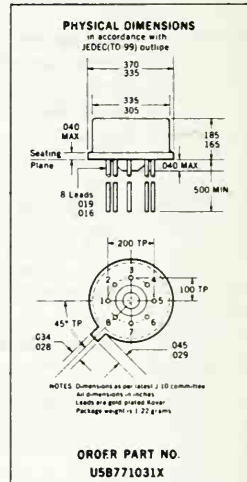

Notes on page 2

* Planar is a patented Fairchild process

313 FAIRCHILD DRIVE, MOUNTAIN VIEW, CALIFORNIA, (415) 962-5011, TWX: 910-379-6435

*Courtesy of Fairchild Semiconductors

FAIRCHILD
SEMICONDUCTOR
A DIVISION OF FAIRCHILD CAMERA AND INSTRUMENT CORPORATION

FAIRCHILD LINEAR INTEGRATED CIRCUITS $\mu A710$

ELECTRICAL CHARACTERISTICS ($T_A = +25^\circ\text{C}$, $V^+ = 12.0\text{V}$, $V^- = -6.0\text{V}$ unless otherwise specified)

PARAMETER (see definitions)	CONDITIONS (Note 4)	MIN.	TYP.	MAX.	UNITS
Input Offset Voltage	$R_i \leq 200\Omega$		0.6	2.0	mV
Input Offset Current			0.75	3.0	μA
Input Bias Current			13	20	μA
Voltage Gain		1250	1700		
Output Resistance			200		Ω
Output Sink Current	$\Delta V_{in} \geq 5\text{ mV}$, $V_{out} = 0$	2.0	2.5		mA
Response Time [Note 3]			40		ns

The following specifications apply for $-55^\circ\text{C} \leq T_A \leq +125^\circ\text{C}$:

Input Offset Voltage	$R_i \leq 200\Omega$			3.0	mV
Average Temperature Coefficient of Input Offset Voltage	$R_i = 50\Omega$, $T_A = 25^\circ\text{C}$ to $T_A = +125^\circ\text{C}$ $R_i = 50\Omega$, $T_A = 25^\circ\text{C}$ to $T_A = -55^\circ\text{C}$		3.5 2.7	10 10	$\mu\text{V}/^\circ\text{C}$ $\mu\text{V}/^\circ\text{C}$
Input Offset Current	$T_A = +125^\circ\text{C}$ $T_A = -55^\circ\text{C}$		0.25 1.8	3.0 7.0	μA μA
Average Temperature Coefficient of Input Offset Current	$T_A = 25^\circ\text{C}$ to $T_A = +125^\circ\text{C}$ $T_A = 25^\circ\text{C}$ to $T_A = -55^\circ\text{C}$		5.0 15	25 75	nA/ $^\circ\text{C}$ nA/ $^\circ\text{C}$
Input Bias Current	$T_A = -55^\circ\text{C}$		27	45	μA
Input Voltage Range	$V^- = -7.0\text{V}$	± 5.0			V
Common Mode Rejection Ratio	$R_i \leq 200\Omega$	80	100		dB
Differential Input Voltage Range		± 5.0			V
Voltage Gain		1000			
Positive Output Level	$\Delta V_{in} \geq 5\text{ mV}$, $0 \leq I_{out} \leq 5.0\text{ mA}$	2.5	3.2	4.0	V
Negative Output Level	$\Delta V_{in} \geq 5\text{ mV}$	-1.0	-0.5	0	V
Output Sink Current	$T_A = +125^\circ\text{C}$, $\Delta V_{in} \geq 5\text{ mV}$, $V_{out} = 0$ $T_A = -55^\circ\text{C}$, $\Delta V_{in} \geq 5\text{ mV}$, $V_{out} = 0$	0.5 1.0	1.7 2.3		mA mA
Positive Supply Current	$V_{out} \leq 0$		5.2	9.0	mA
Negative Supply Current			4.6	7.0	mA
Power Consumption			90	150	mW

NOTES:

- (1) Rating applies for case temperatures to $+125^\circ\text{C}$; derate linearly at $5.6\text{ mW}/^\circ\text{C}$ for ambient temperatures above $+105^\circ\text{C}$.
- (2) Derate linearly at $4.4\text{ mW}/^\circ\text{C}$ for case temperatures above $+115^\circ\text{C}$; derate linearly at $3.3\text{ mW}/^\circ\text{C}$ for ambient temperatures above $+100^\circ\text{C}$.
- (3) The response time specified (see definitions) is for a 100-mV input step with 5-mV overdrive.
- (4) The input offset voltage and input offset current (see definitions) are specified for a logic threshold voltage of 1.8V at -55°C , 1.4V at $+25^\circ\text{C}$ and 1.0V at $+125^\circ\text{C}$.

Appendix 2

Resistor and Capacitor Values

APPENDIX 2-1

TYPICAL STANDARD RESISTOR VALUES

Ω	Ω	Ω	$k\Omega$	$k\Omega$	$k\Omega$	$M\Omega$	$M\Omega$
—	10	100	1	10	100	1	10
—	12	120	1.2	12	120	1.2	—
—	15	150	1.5	15	150	1.5	15
—	18	180	1.8	18	180	1.8	—
—	22	220	2.2	22	220	2.2	22
2.7	27	270	2.7	27	270	2.7	—
3.3	33	330	3.3	33	330	3.3	—
3.9	39	390	3.9	39	390	3.9	—
4.7	47	470	4.7	47	470	4.7	—
5.6	56	560	5.6	56	560	5.6	—
6.8	68	680	6.8	68	680	6.8	—
—	82	820	8.2	82	820	—	—

APPENDIX 2-2

TYPICAL STANDARD CAPACITOR VALUES

pF	pF	pF	pF	μF	μF	μF	μF	μF	μF	μF
5	50	500	5000		0.05	0.5	5	50	500	5000
—	51	510	5100		—	—	—	—	—	—
—	56	560	5600		0.056	0.56	5.6	56	—	5600
—	—	—	6000		0.06	—	6	—	—	6000
—	62	620	6200		—	—	—	—	—	—
—	68	680	6800		0.068	0.68	6.8	—	—	—
—	75	750	7500		—	—	—	75	—	—
—	—	—	8000		—	—	8	80	—	—
—	82	820	8200		0.082	0.82	8.2	82	—	—
—	91	910	9100		—	—	—	—	—	—
10	100	1000		0.01	0.1	1	10	100	1000	10000
—	110	1100		—	—	—	—	—	—	—
12	120	1200		0.012	0.12	1.2	—	—	—	—
—	130	1300		—	—	—	—	—	—	—
15	150	1500		0.015	0.15	1.5	15	150	1500	—
—	160	1600		—	—	—	—	—	—	—
18	180	1800		0.018	0.18	1.8	18	180	—	—
20	200	2000		0.02	0.2	2	20	200	2000	—
22	220	2200		—	0.22	2.2	22	—	—	—
24	240	2400		—	—	—	—	240	—	—
—	250	2500		—	0.25	—	25	250	2500	—
27	270	2700		0.027	0.27	2.7	27	270	—	—
30	300	3000		0.03	0.3	3	30	300	3000	—
33	330	3300		0.033	0.33	3.3	33	330	3300	—
36	360	3600		—	—	—	—	—	—	—
39	390	3900		0.039	0.39	3.9	39	—	—	—
—	—	4000		0.04	—	4	—	400	—	—
43	430	4300		—	—	—	—	—	—	—
47	470	4700		0.047	0.47	4.7	47	—	—	—

APPENDIX 2-2 TYPICAL STANDARD CAPACITOR VALUES

40	41	42	1518	15
----	----	----	----	-----	-----	-----	-----	------	------	------	------	----

INDEX

A

Action region	88
Active output pull-up	272
AND gate	258, 259
Aperiodic waveform	3
Astable multivibrator	214, 217
collector coupled	214
design	218
emitter coupled	220, 221
frequency control	219, 220
synchronization	220
waveforms	217
Asymmetrical base triggering	243, 244
Asymmetrical collector triggering	237, 238

Avalanche diode	61
Average pulse amplitude	10, 13, 14

B

Back plane	322
Base triggering	243, 244
Biased clamping circuits	76, 77
Biased shunt clipper	69
Binary to decimal conversion	326, 327, 329
Bistable multivibrator	223
asymmetrical base triggering	243, 244
asymmetrical collector triggering	238
collector coupled	223, 224
collector steered base triggering	245
emitter coupled	230
emitter triggering	247
IC bistable	250
symmetrical base triggering	244
symmetrical collector triggering	239
Bootstrap ramp generator	170, 171
IC circuit	175, 176
waveforms	171
Bootstrapping capacitor	170
Breakdown diode	61

C

Capacitor charging	33, 34
Capacitor coupled inverter	117
Cascaded flip-flops	305
Cathode ray oscilloscope	3
Clamping circuits	72
biased clamping circuit	76
negative voltage clamper	72
positive voltage clamper	73
Zener diode clamper	78
Clipping circuits	62
biased shunt clipper	69
noise clipper	64

Clipping circuits (<i>Contd.</i>)	
series clipper	62
shunt clipper	67
Clock pulse	314
Clock source	340
CMOS logic gates	282
CMOS NAND gate	283
CMS NOR gate	284
CMOS switch	105
Cold cathode tube	323
Collector coupled astable multivibrator	214
Collector coupled bistable multivibrator	223
Collector coupled monostable multivibrator	193
Collector cut-off current	88
Collector triggering	238, 239
Commutating capacitors	225
Comparator	360
Complementary MOS	105
Constant current circuit	158
Constant current ramp generator	159
Counting circuits	305
decade counter	310, 317
divide-by-16	315
IC counters	314
scale-of-10	310
scale-of-16	308, 315
scale-of-10,000	383
Coupling capacitors	117
CR circuit	28
capacitor charging current	33, 34
capacitor charging time	33, 34
capacitor voltage	30, 33, 34
response to pulse	40
settled waveform	40
time constant	35
CR ramp generator	155
CRT	3
CRT time base	189
Current gain	87
Current-mode logic	278
Current sink	267
Current switch	294
Cut-off region	88, 89, 90

D

DC restorer	72
Dead zone	65
Decade counter	310, 317
Decay time	94
Decimal-to-7 segment	331
Delay time	93
Differentiated waveforms	50, 51, 53, 54
Differentiating circuits	49
Digital counting	305
Digital displays	318
Digital frequency meter	339
Digital indicator tube	323
Digital readouts	318
Digital to analog conversion	376
Digital voltmeter	352
Diode:	
AND gate	258
characteristics	58
clamper circuit	72
clipper circuit	62
forward current	58
forward volt drop	59
logic	263
matrix	326, 330
noise clipper	64
OR gate	260
protection	112
reverse current	59
reverse recovery time	60
reverse voltage	58
sampling gate	288
switch	58
Zener diode	61
Diode transistor logic (DTL)	263
Divide-by-16 counter	314
Drain current	102
Drain-gate leakage current	104
Drain-source <i>on</i> resistance	103
Drain-source voltage	103
Dual slope integration	347

Duty cycle	9
Dynamic scattering	320

E

Emitter-base reverse voltage	68
Emitter coupled astable multivibrator	220
Emitter coupled bistable multivibrator	230
Emitter coupled logic (ECL)	278
Emitter coupled monostable multivibrator	204
Emitter follower	172
Emitter triggering	247
Enhancement MOSFET	105
Expandable gate	267
Exponential change	6
Exponential constant	6
Exponential waveform	6

F

Fall time (t_f)	10, 94
Fan-in	267
Fan-out	267
FET inverter	124
FET sampling gate	297, 300
FET switch	101
Flip-flops	223
IC	250
in cascade	305
JK	252
reset-set (RS)	251
reset-set-toggle (RST)	252
set-clear (SC)	251
set-clear-toggle (SCT)	252
toggle (T)	250
Fourier analysis	18
Fractional tilt	22
Frequency division	309, 340
Frequency meter	339
Frequency response	21
Frequency synthesis	18
Fundamental frequency	18

G

Gas discharge display	324
Gates:	
logic (<i>see also</i> Logic gates)	257
sampling (<i>see also</i> Sampling gates)	288

H

Harmonic	15
Harmonic analysis	18
h_{FE}	87
High frequency distortion	20
High threshold logic (HTL)	270
Hysteresis	144

I

IC:	
comparator	360
counters	314
flip-flops (<i>see</i> Flip-flops)	
logic gates (<i>see</i> Logic gates)	
monostable multivibrator	214
IC operational amplifier	126
input bias current	126
input impedance	126
input off-set current	126
input off-set voltage	126
integrator	180
inverter	127
inverting amplifier	180
inverting input	126
monostable multivibrator	210
non-inverting input	126
ramp generator	175
Schmitt trigger	146
slew rate	127
virtual ground	182
voltage follower	175
Ideal pulse	7
Ideal transistor switch	85

Incandescent read-out	322
Integrated waveforms	44, 46, 48
Integrating circuits	43, 180
Intrinsic stand-off ratio	163
Inverter circuits	110
capacitor coupled	117
diode protection	112
direct coupled	110
FET	124
IC	126
speed-up capacitor	114

J

JFET inverter	124
JFET series gate	297
JFET shunt gate	300
JFET switch	101
JK flip flop	252, 343

K

Keep-alive cathode	325
--------------------------	-----

L

Lagging edge	7
Latch	342
Leading edge	7
Leakage current	88, 104
Light emitting diodes (LED)	318
Limiter circuit	62
Linear ramp generator	170
Liquid crystal displays	320
Logic gates:	
active output pull-up	272
AND gate	258
CMOS	282
comparison of logic types	285
current mode logic	278
current sink	267

Logic gates (*Contd.*)

diode gates	258
diode transistor logic (DTL)	263
emitter coupled logic (ECL)	278
expandable gate	267
fan-in	267
fan-out	267
high threshold logic (HTL)	270
loading factor	269
modified DTL	267
NAND gate	263
negative logic	262
noise immunity	271
NOR gate	266
NOT gate	263
OR gate	260
positive logic	262
propagation delay time	266
resistor transistor logic (RTL)	272
transistor transistor logic (TTL)	275
Lower cut-off frequency	22
Lower trigger point	134

M

Mark length	9
Mark-to-space ratio	9
Matrix (diode)	326, 330
Memory capacitors	225
Miller effect	180
Miller integrator	181
Modified DTL	267
Monostable multivibrator	192
collector coupled	193
design	196, 205
emitter coupled	204
IC	214
IC operational amplifier	210
PW control	204
triggering	202
MOSFET sampling gates	303
MOSFET switch	105

Multivibrator:	
astable (<i>see also</i> Astable multivibrator)	214
bistable (<i>see also</i> Bistable multivibrator)	223
monostable	
(<i>see also</i> Monostable multivibrator)	192

N

NAND gate	263
Negative clipper circuits	62, 67
Negative logic	262
Negative voltage clamper	72
Noise clipper	64
Non-repetitive waveforms	3
Non-saturated switch	92
NOR gate	266
NOT gate	263
Numerical displays	318
digital indicator tube	323
gas discharge display	324
incandescent	322
light emitting diode	318
liquid crystal cell	320
three-and-a-half digit	322
tungsten	322

O

One-shot multivibrator	193
Operational amplifier (<i>see</i> IC operational amplifier)	
OR gate	260
Oscilloscope	3
Overdriven transistor	92
Overshoots	20

P

Peak point current	163
Periodic waveforms	2
Positive clamping circuits	73
Positive clipping circuits	62

Positive logic	262
Practical transistor switch	88
Programmable UJT (PUT)	167
Propagation delay time	266
Pulse repetition frequency (PRF)	7
Pulse repetition rate (PRR)	7
Pulse modulation:	
pulse amplitude modulation (PAM)	356
pulse code modulation (PCM)	356
pulse duration modulation (PDM)	356
pulse position modulation (PPM)	356
pulse width modulation (PWM)	356
Pulse multiplexing	365
Pulse waveform:	
amplitude	10
duration	9
duty cycle	9
fall time (t_f)	10
ideal pulse	7
lagging edge	7
mark-to-space ratio	9
repetition frequency (PRF)	7
repetition rate (PRR)	7
rise time (t_r)	10
tilt	10
trailing edge	7
width	9

Q

Quantizing	358
------------------	-----

R

Ramp generators	153
bootstrap	170, 175
constant current	157
CR	153
free running	178
IC operational amplifier	175
Miller integrator	180
PUT	167
UJT	162

Recovery time	100
Rectangular waveform	5
Reflective type cell	320
Regeneration	134
Relaxation oscillator	162
Resistor transistor logic (RTL)	272
Resolving time	100
Reverse breakdown	61
Reverse breakdown region	61
Reverse recovery time	60
Reverse saturation current	88
Ring counter	367
(Rise time (t_r))	10

S

Sampling gates	288
bipolar series	290
bipolar shunt	294
diode	288
JFET series	297
JFET shunt	300
MOSFET	303
Saturated transistor	90
Saturation region	88
Saturation voltage	90
Sawtooth wave	6
Scale-of-10 counter	310, 317
Scale-of-16 counter	308, 314
Scale-of-10,000 counter	333
Schmitt trigger circuit	132
analysis	138
design	135, 141
hysteresis	144
IC operational amplifier	146
lower trigger point (LTP)	134
output/input characteristics	143
regeneration	134
speed-up-capacitor	142
upper trigger point (UTP)	134
waveforms	135
Series clipper	62

Series gate	290, 297
Series noise clipper	64
Set-clear (SC) flip-flop	251
Settled waveform	40
Settling time	100
Seven segment displays (<i>see</i> Numerical displays)	
Shift register	373
Shunt clipper	67
Shunt gate	294, 300
Sine wave	5
Slew rate	127
Slope	10
Space width	9
Speed-up capacitor	97
Spike waveform	6
Square wave	5
Square wave generator	214
Steering resistance	243
Step change	5
Storage time	94
Strip-chart recorder	3
Summing amplifier	376
Switch:	
CMOS	105
diode	57
JFET	101
MOSFET	105
transistor	85
Switching times:	
decay time	94
delay time	93
fall time	94
reverse recovery time	60
rise time	94
storage time	94
turn-off time	94
turn-on time	94
Symmetrical base triggering	243
Symmetrical collector triggering	237
Synchronizing	164, 180, 186
Synchronizing gate	369
Synchronizing space	365

T

Tilt	10
Time base	188
Time base generation	341
Time constant	35
Time division multiplexing (TDM)	365
Time period	7
Timing system	340
Toggle (T) flip-flop	250
Trailing edge	7
Transients	3
Transistor:	
characteristics	89
current levels	88
reverse base-emitter voltage	68
switching	85
switching times	94
Transistor transistor logic (TTL)	275
Triangular waveform	5
Triangular waveform generator	186
Triggering	243
Truth table	306
Tungsten display	322
Turn-off time	94
Turn-on time	94

U

Unijunction transistor (UJT)	162
equivalent circuit '	162
intrinsic stand-off ratio	163
programmable UJT (PUT)	167
relaxation oscillator	164
Upper cut-off frequency	38
Upper trigger point	134

V

Valley point current	163
$V_{CE(sat)}$	90
Virtual ground	182

Voltage comparator	360
Voltage follower	175
Voltage level detector	135
Voltage reference source	61
Voltage switch	294

W

Waveform distortion	20
Waveforms:	
exponential	6
pulse	5
ramp	5
rectangular	5
sine	5
spike	6
square	5
triangular	5

Z

Zener diode	61
characteristics	61
clamping circuits	78
clipping circuits	70
noise clipper	66
Zero crossing detector	347

